



CHAPTER 6



Single-Stage Integrated-Circuit Amplifiers

Outline



- Comparison between the MOS and the BJT
- From **discrete** circuit to **integrated** circuit
 - Philosophy, Biasing, ...etc.
- Frequency response
- The **Common-Source** and **Common-Emitter** amplifier with active loads
- The **Common-Gate** and **Common-Base** amplifier with active load
- The **Source** and **Emitter Follower**
- The CS and CE amplifier with **source degeneration**
- Current mirrors with improved performance
- **Cascode** amplifier and **transistor pairings**



6-1 Comparison between the MOS and the BJT

DC characteristics

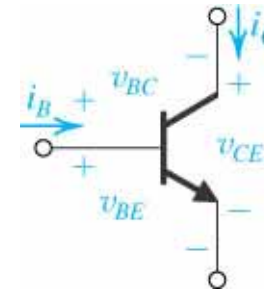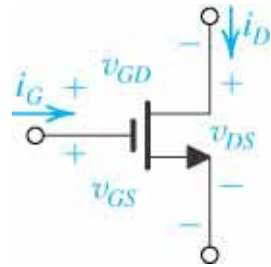


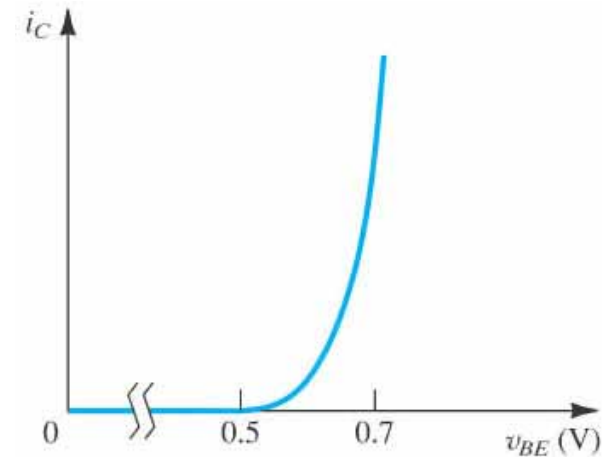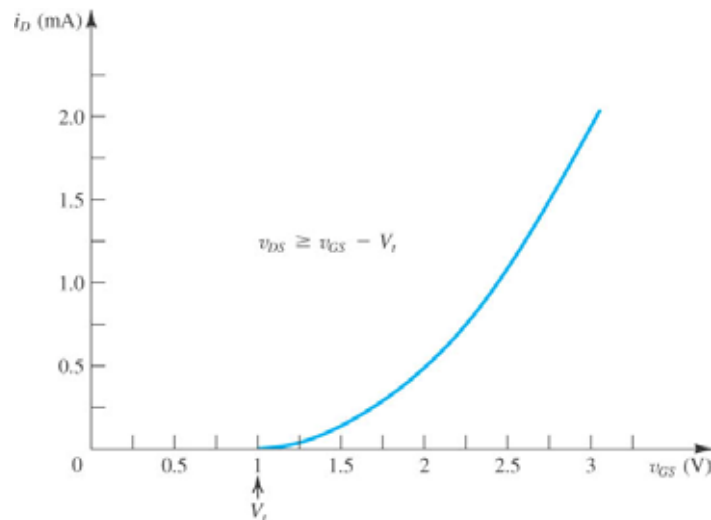- Transconductor ($i_D - v_{GS}$ v.s. $i_C - v_{BE}$)




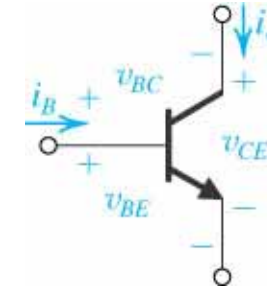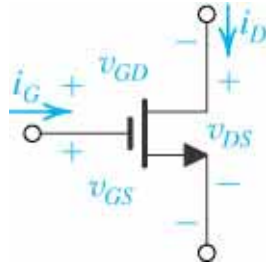

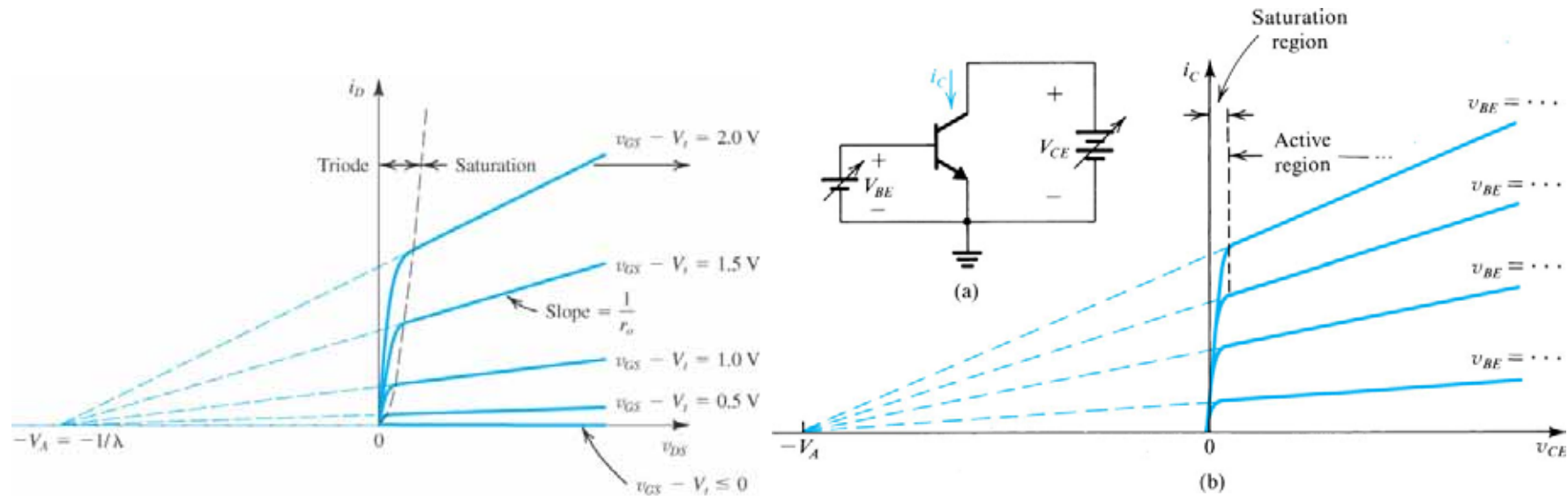• Channel-length modulation ($i_D - v_{DS}$) v.s. Early effect ($i_C - v_{CE}$)



Low-frequency operation

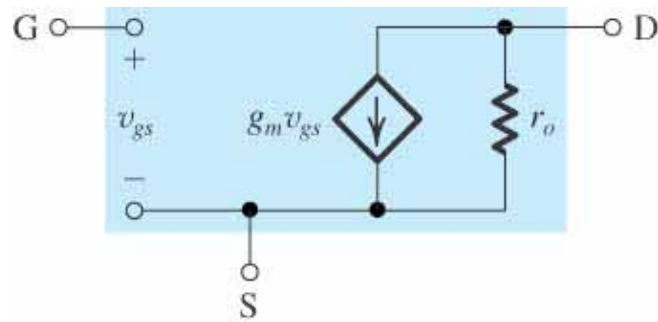


- Input resistance

- Transconductance

$$g_m = \sqrt{2(\mu_n C_{ox}) \left(\frac{W}{L}\right) I_D}$$



- Output resistance

- Intrinsic gain

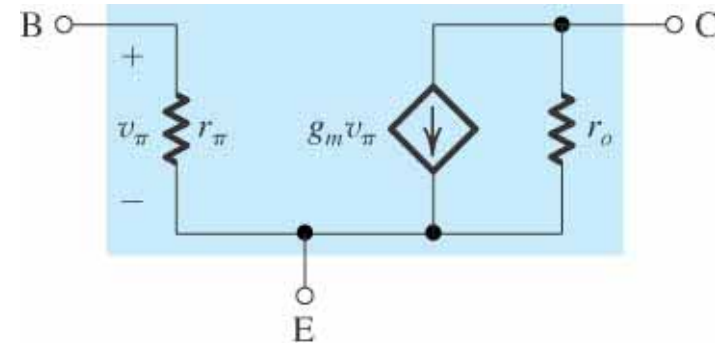


$$g_m = \frac{I_C}{V_T}$$

High-frequency operation

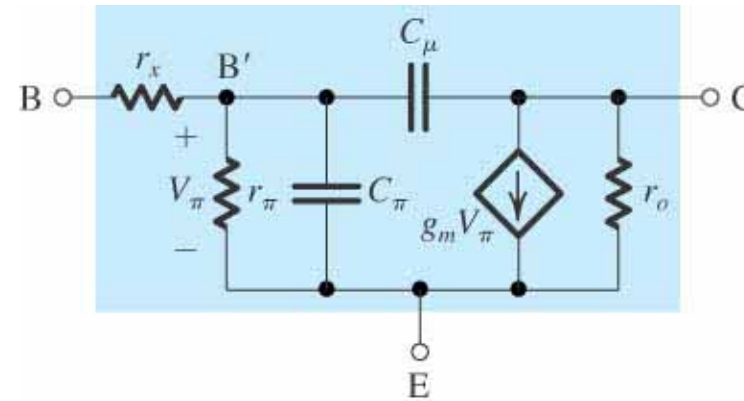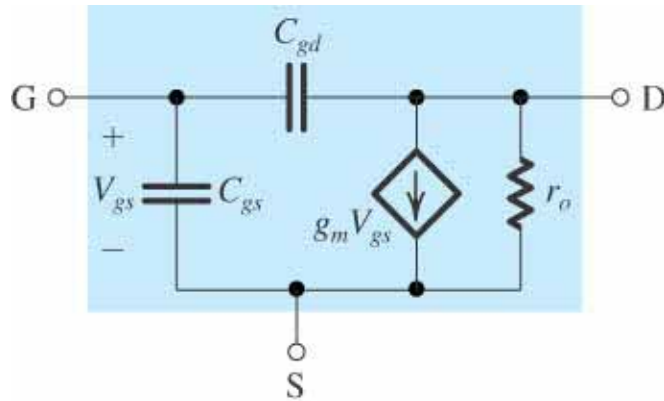

• Cutoff frequency

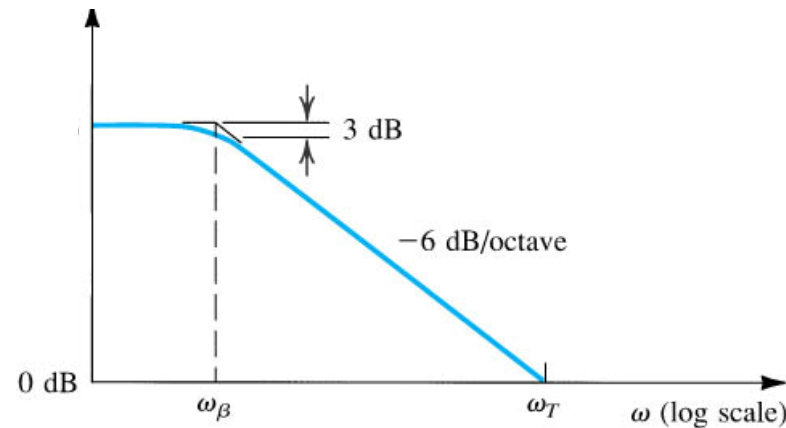

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

For $C_{gs} \gg C_{gd}$ and $C_{gs} \cong \frac{2}{3}WLC_{ox}$

$$f_T \cong \frac{1.5\mu V_{OV}}{2\pi L^2}$$


$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})}$$

For $C_{\pi} \gg C_{\mu}$ and $C_{\pi} \cong C_{de}$

$$f_T \cong \frac{2\mu V_T}{2\pi W^2}$$

Trends in IC technology

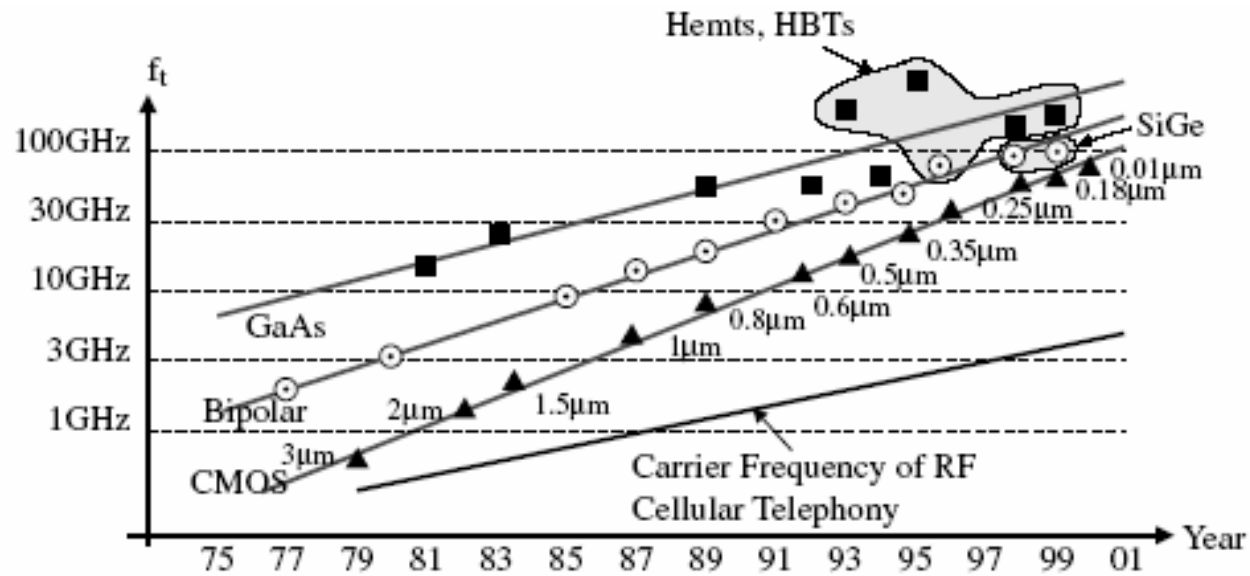- Technology speed figure of merit v.s. Time:



- Estimated frequency performance based on scaling

Technology	f_t	f_{max}
0.35 micron	25GHz	40GHz
0.25 micron	40GHz	≈60-70GHz
0.18 micron	60GHz	≈90-100GHz




Comparison

From analogue or digital point of view?

	BJT	MOS
DC range of operation	>5 decades of $I_C \propto e^{V_{BE}}$	2-3 decades of $I_D \propto (V_{GS} - V_T)^2$
Small-signal output resistance (r_o)	Slightly larger	Smaller for short channel
Cutoff frequency (f_T)	100GHz	50GHz
Switch implementation	Poor	Good
Noise (thermal about the same)	Less 1/f	More 1/f
Capacitor implementation	Voltage dependent	Reasonably good




6-2 From Discrete- to Integrated- circuit

Components

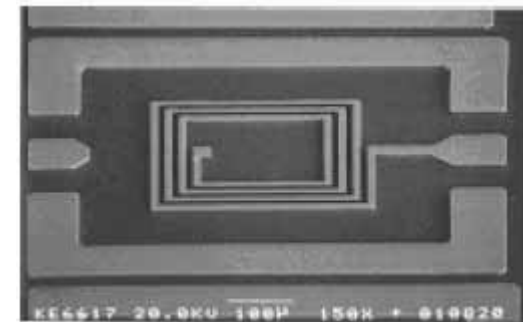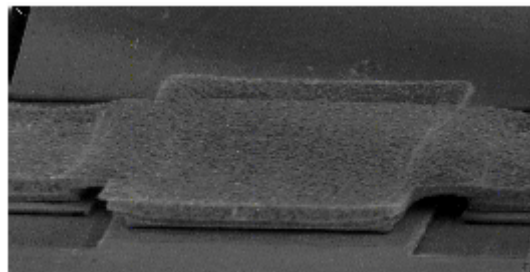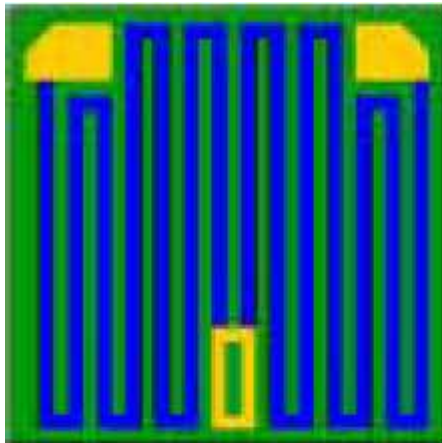


(The pictures are copied from http://140.114.23.141/htdocs/course/922_EE226002/Introduction.pdf , S.H. Hsu)

Hardware products

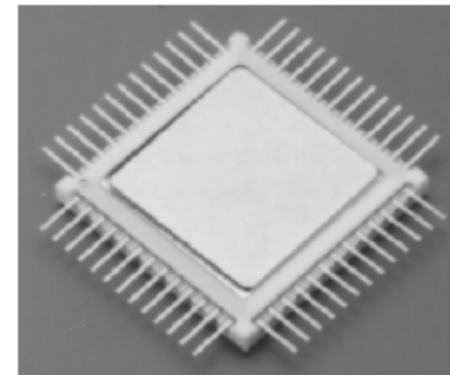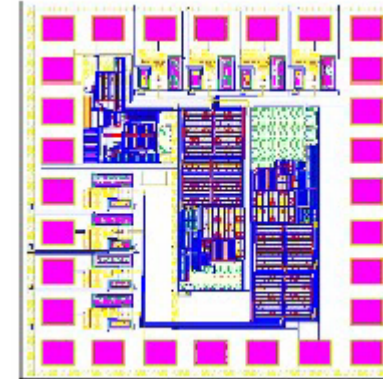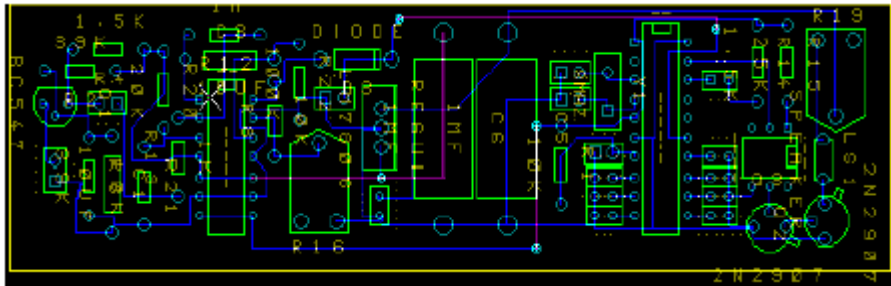

(The pictures are copied from http://140.114.23.141/htdocs/course/922_EE226002/Introduction.pdf , S.H. Hsu)

Design topologies

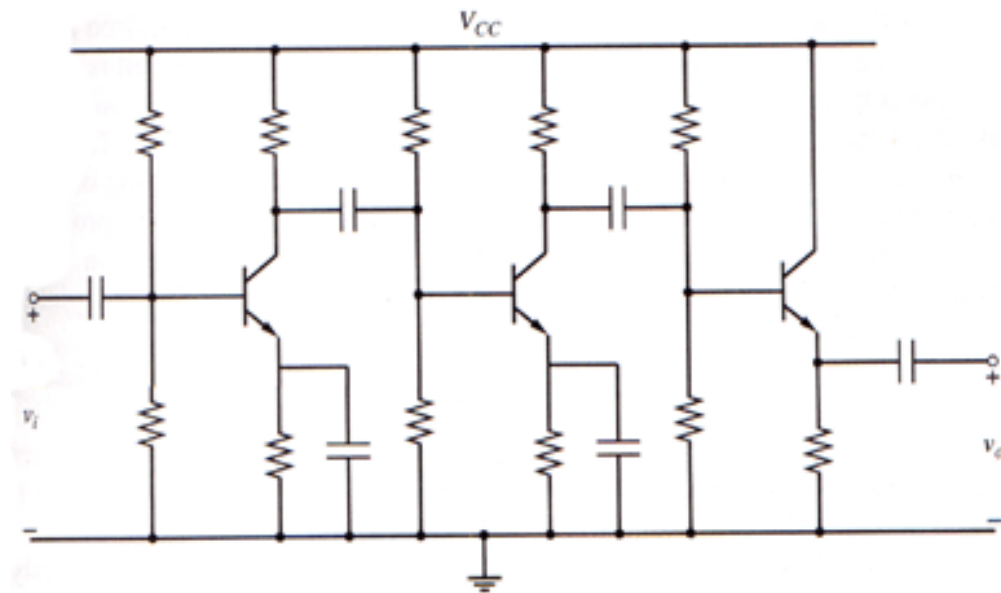


- Active load to replace R




R=?

- Current biasing
- Direct-coupled

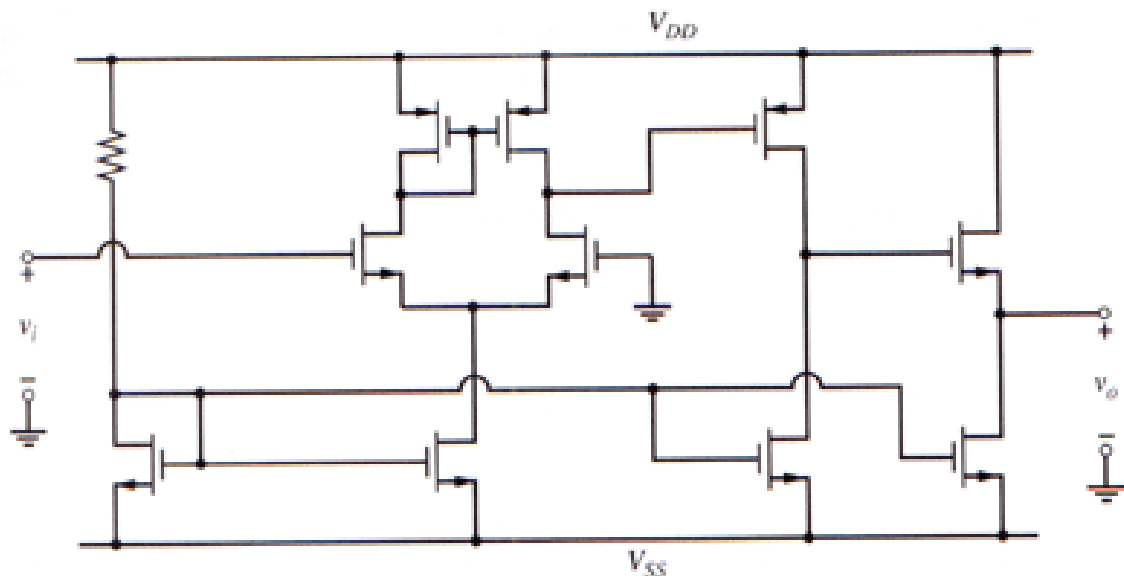→ Differential architecture to decouple DC signals (Ch7)




IC Biasing – current mirror (amplifier)

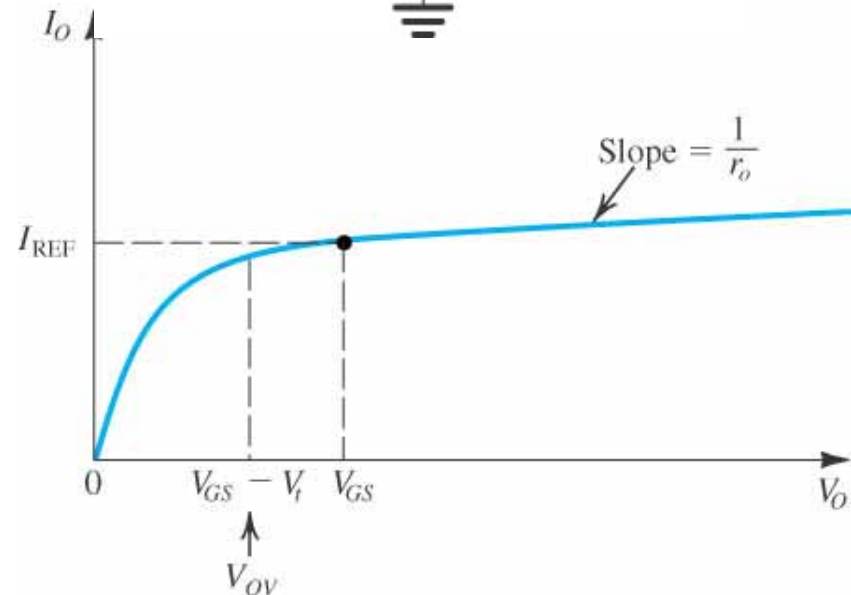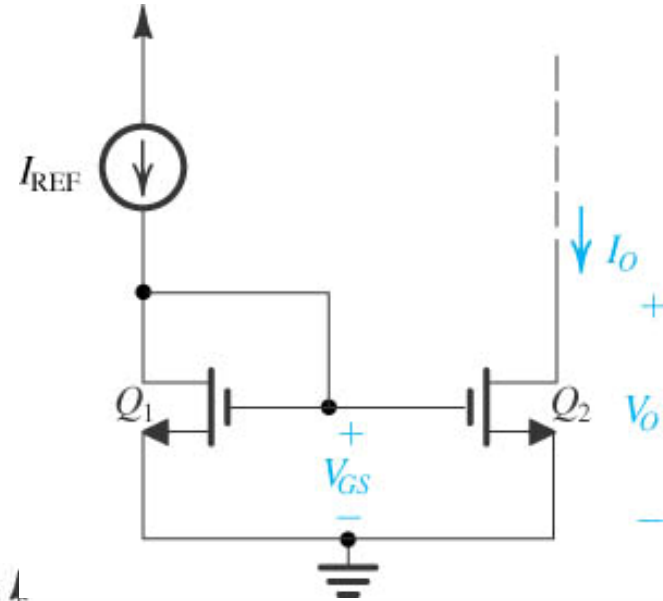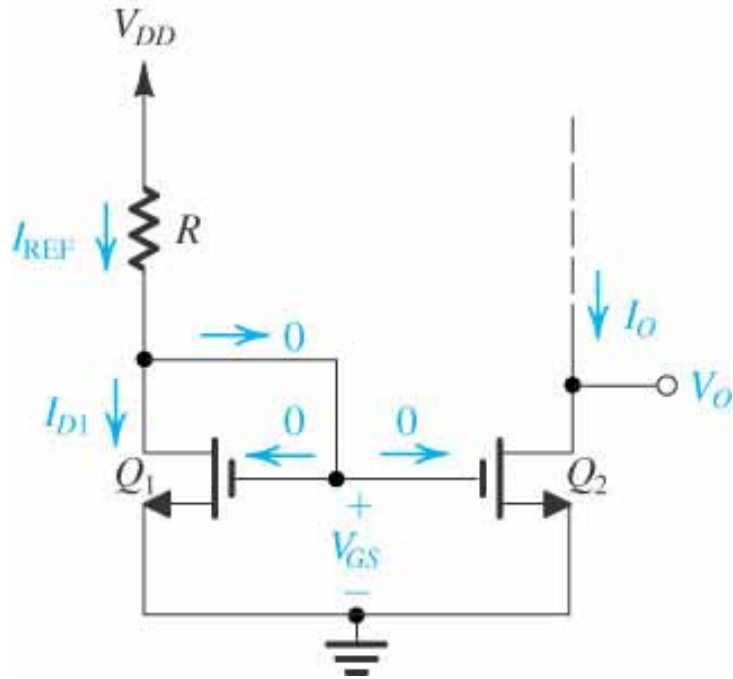


- $I_O / I_{REF} =$
- Minimum $V_O =$
- Effect of $r_o :$

Current steering

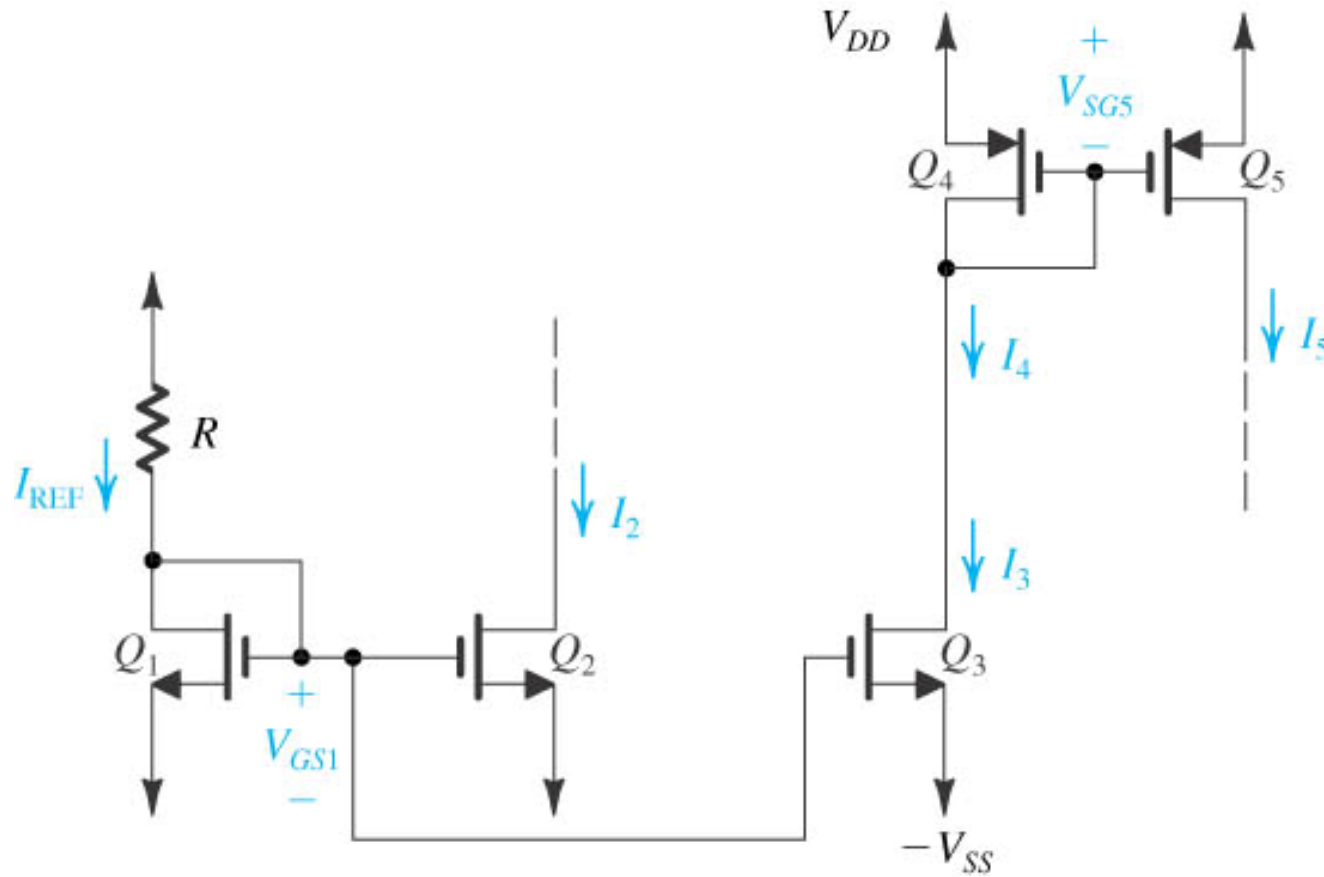

BJT current mirror

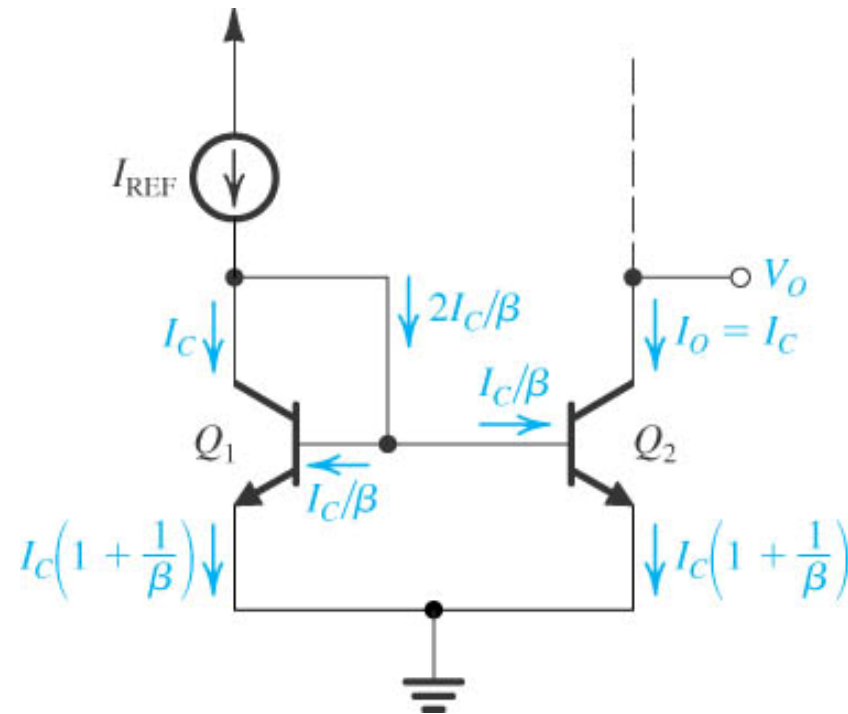

- $I_o / I_{REF} =$

- Minimum $V_o =$


- Effect of r_o :

$$\frac{I_o}{I_{REF}} = \frac{m}{1 + \frac{m+1}{\beta}}$$

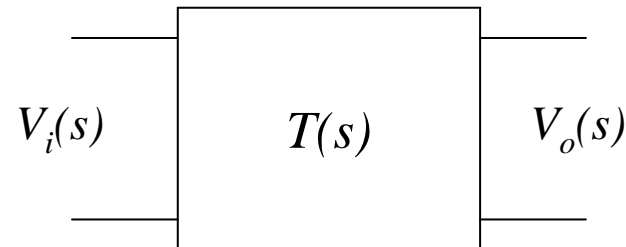6-3 Frequency response

- In analysing the frequency response of circuits,
capacitors $\rightarrow 1/sC$
inductors $\rightarrow sL$

$$T(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{s^n + b_{n-1} s^{n-1} + \dots + b_0}$$



Substituting $s=j\omega$ into $T(s) \rightarrow$ The gain and phase response v.s. ω

$$T(s) = a_m \frac{(s - Z_1)(s - Z_2) \cdots (s - Z_m)}{(s - P_1)(s - P_2) \cdots (s - P_n)}$$

Zeros :

Poles :

Bode plot $|T(s)|$ $\angle T(s)$


a pole $T(s) = \frac{1}{s + p_0}$

a zero $T(s) = s + z_0$

How about positive-valued poles/zeros?

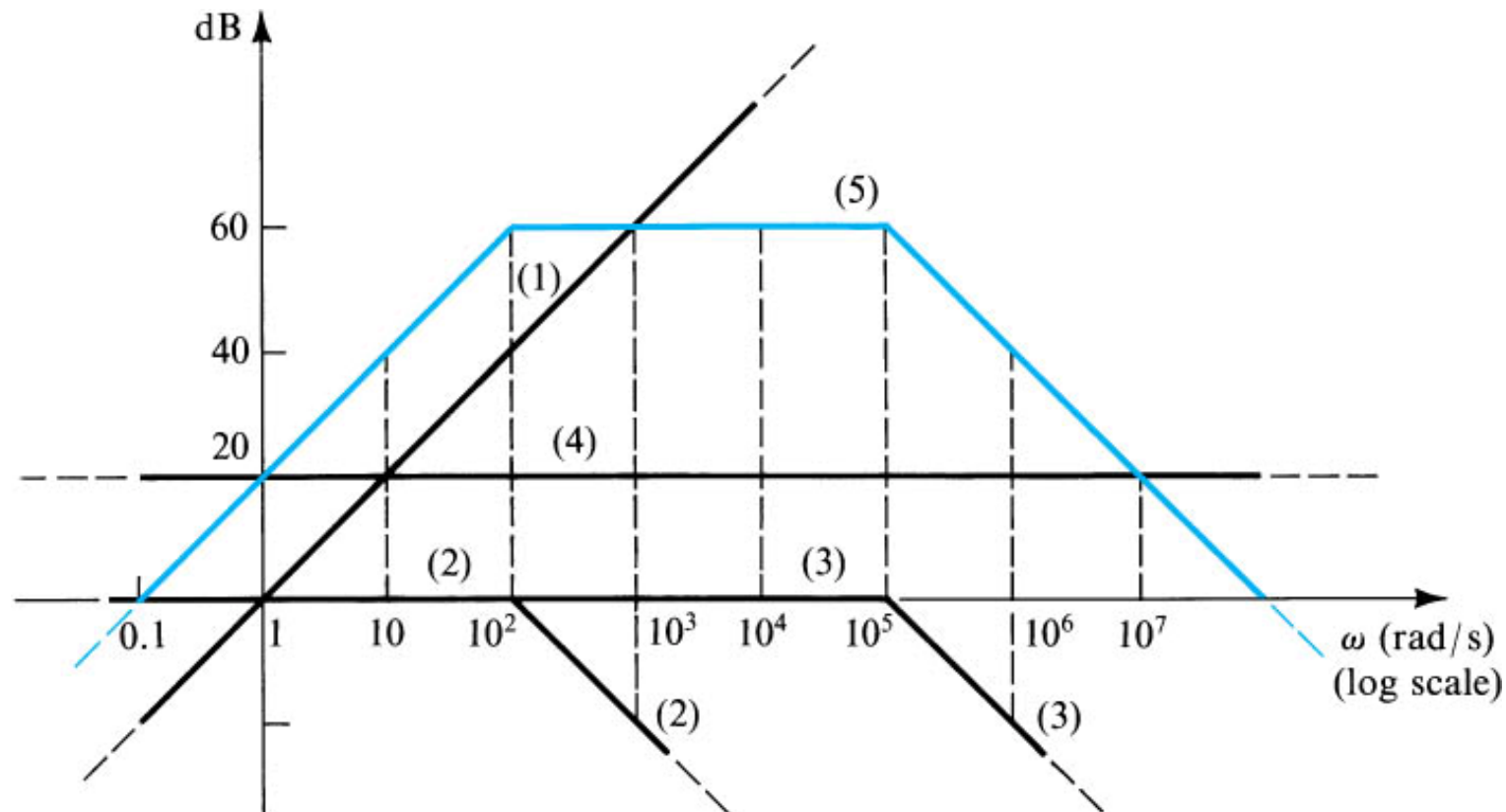
Example

$$T(s) = \frac{10s}{(1 + s/10^2)(1 + s/10^5)}$$



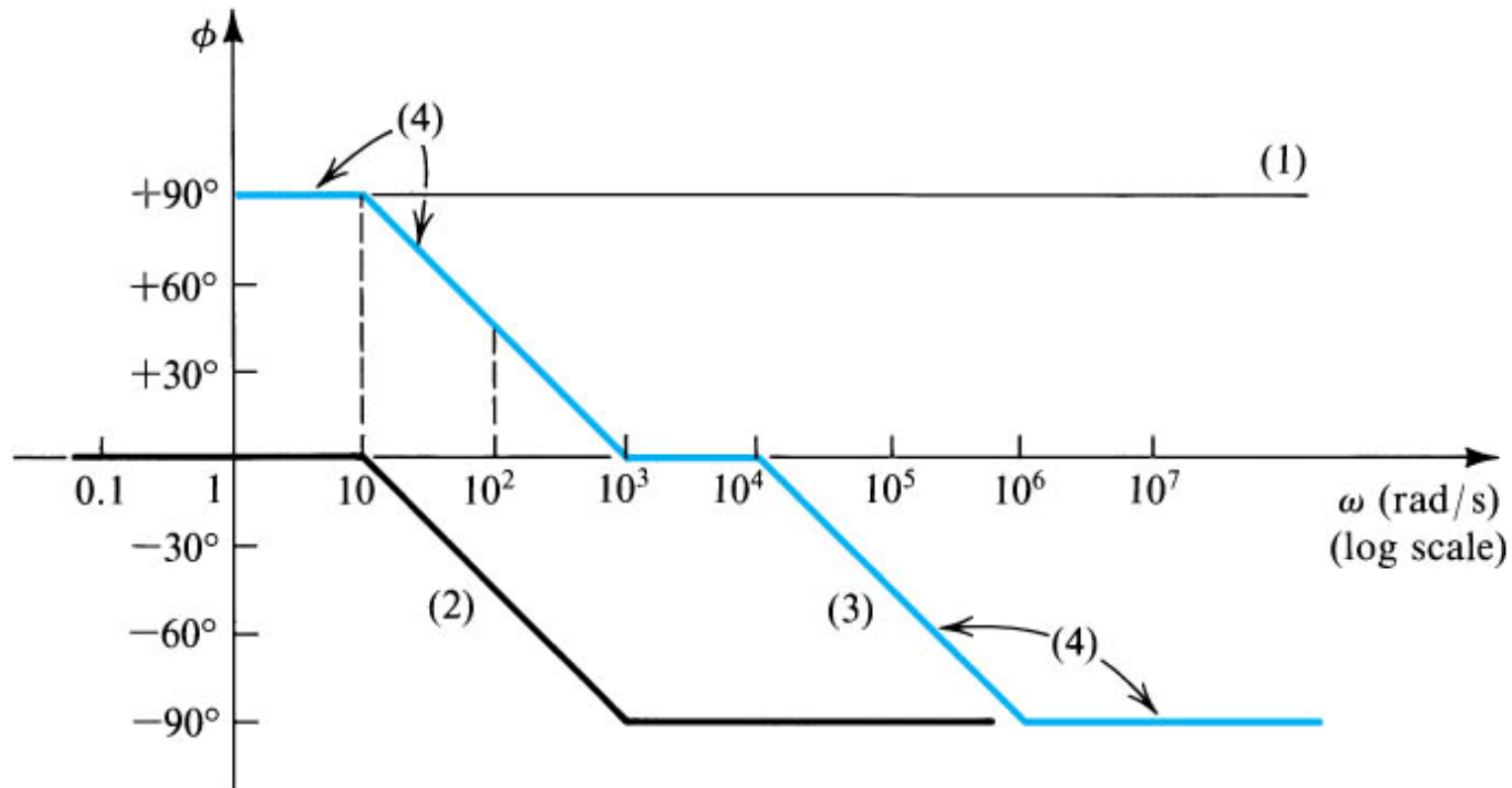Example- continued


$$T(s) = \frac{10s}{(1 + s/10^2)(1 + s/10^5)}$$



High-frequency response

- Frequency response of a direct-coupled amplifier
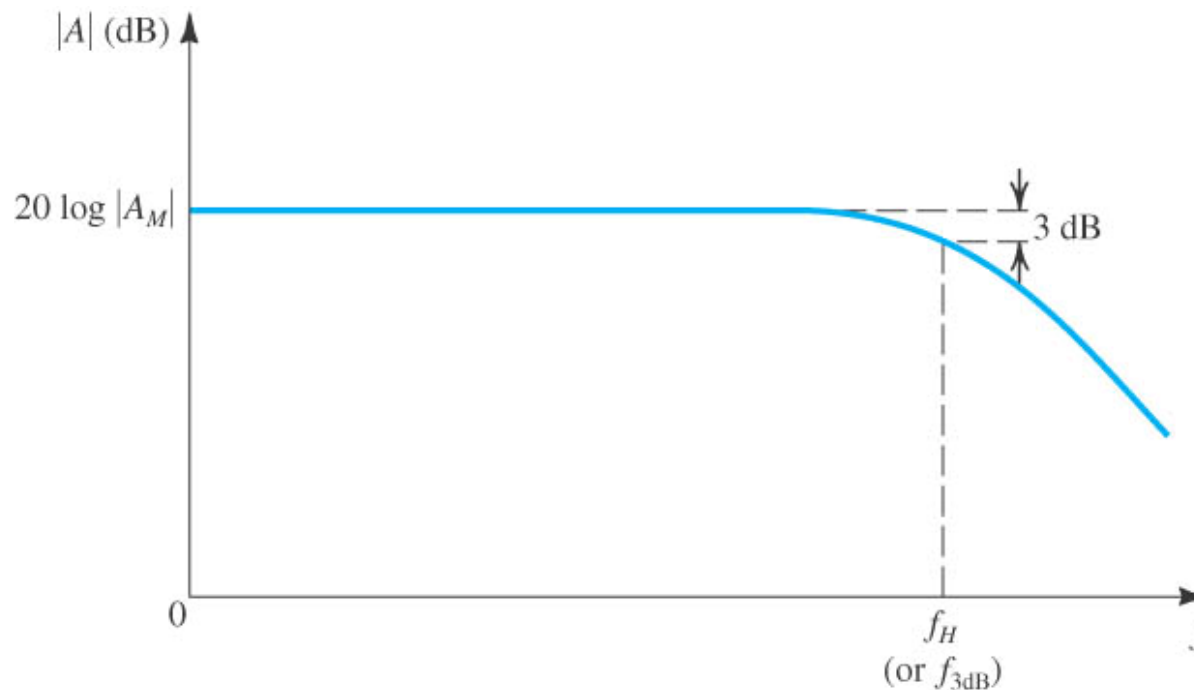
$$F_H(s) = \frac{(1 + s/z_1)(1 + s/z_2) \cdots (1 + s/z_n)}{(1 + s/p_1)(1 + s/p_2) \cdots (1 + s/p_n)}$$



We are mostly interested in **3-dB frequency, f_H (or f_{3dB})**

Methods to derive f_H

- If a dominant pole exists $F_H(s) \cong \frac{1}{1 + s/w_{P1}}$

- If not, use the cond. $|F(w_H)| = 1/2$ to derive


$$w_H \cong 1 / \sqrt{\left(\frac{1}{w_{P1}^2} + \frac{1}{w_{P2}^2} + \dots + \frac{1}{w_{Pn}^2} \right) - \left(\frac{1}{w_{Z1}^2} + \frac{1}{w_{Z2}^2} + \dots + \frac{1}{w_{Zn}^2} \right)}$$

- Open-circuit time constants


$$w_H \cong \frac{1}{\sum_i C_i R_{io}}$$

R_{io} : resistance seen by C_i when all other Cs are open-circuit
and all sources equal zeros



Example 6.6

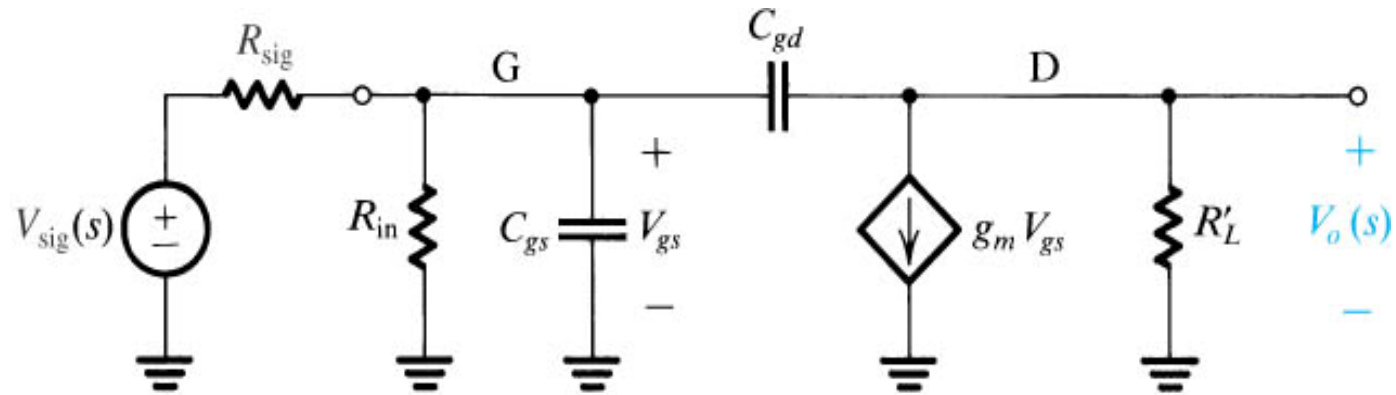


(a)

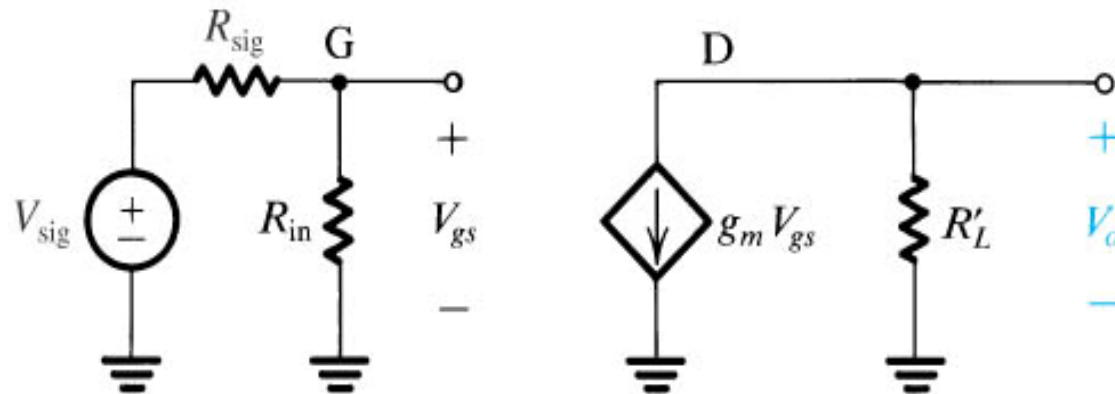


(b)

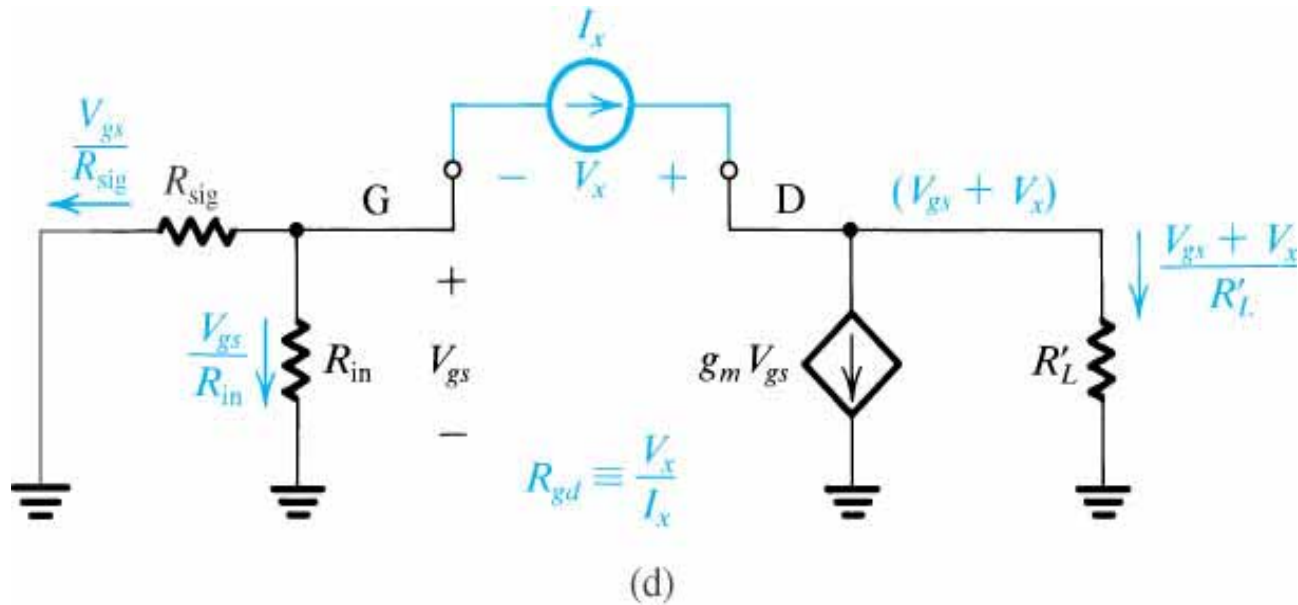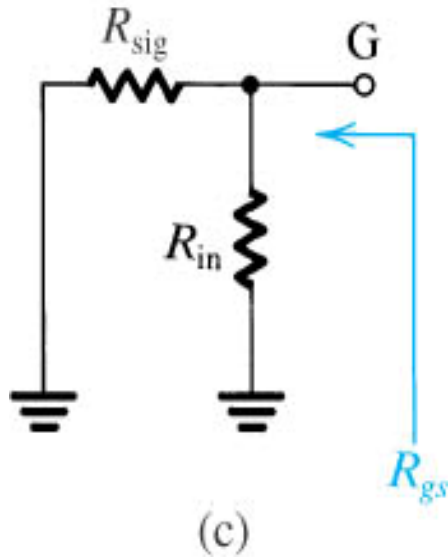

Miller's theorem – one useful technique for analysing freq response

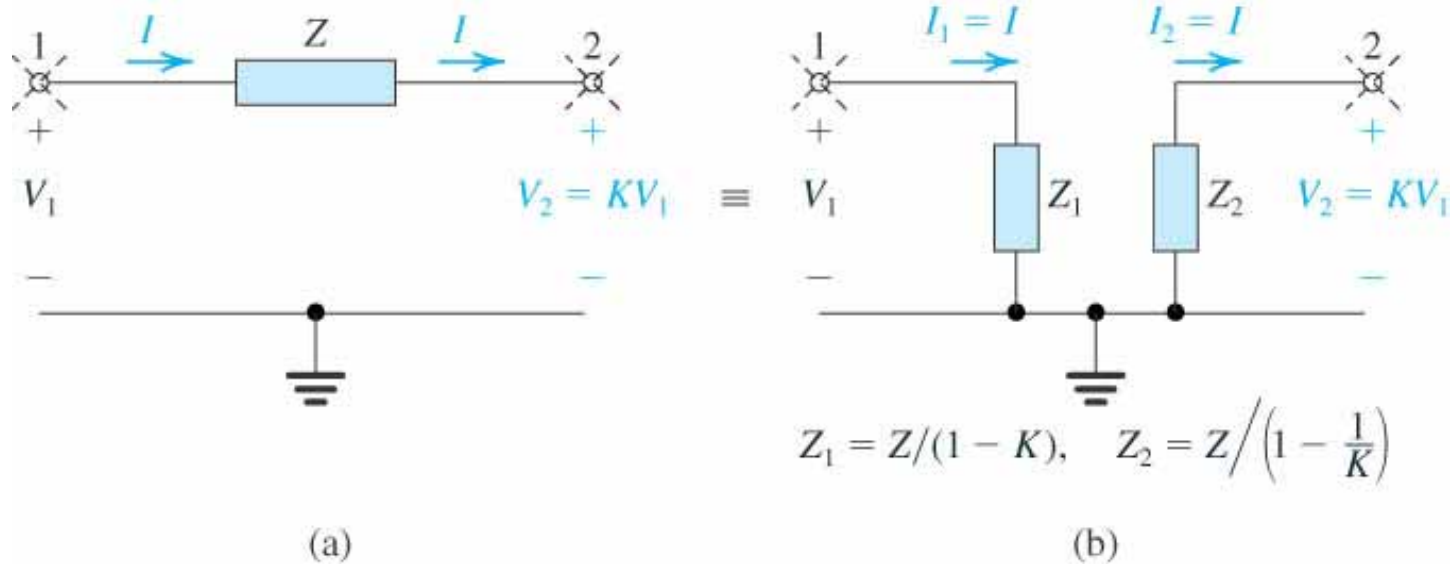


Example 6.7

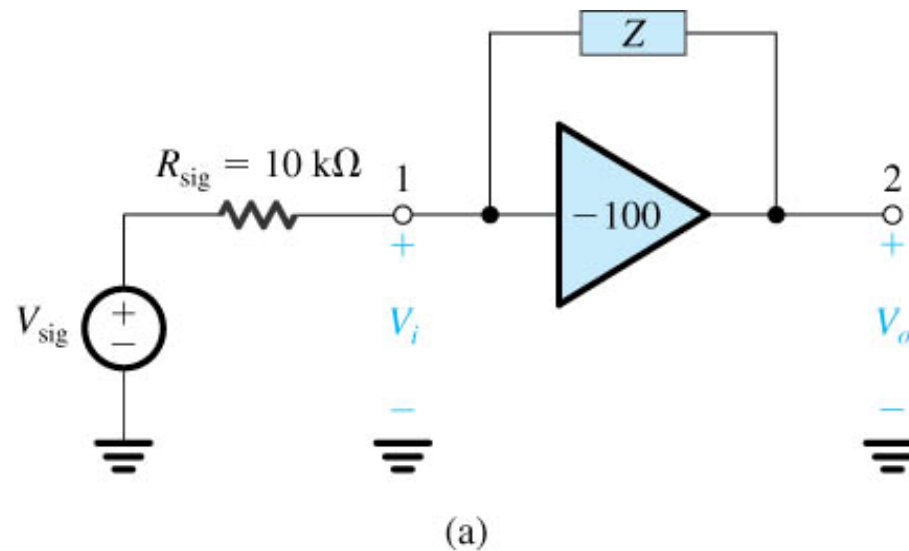

6-4 Common-Source and Common-Emitter amplifiers with active loads

Common-source amplifier

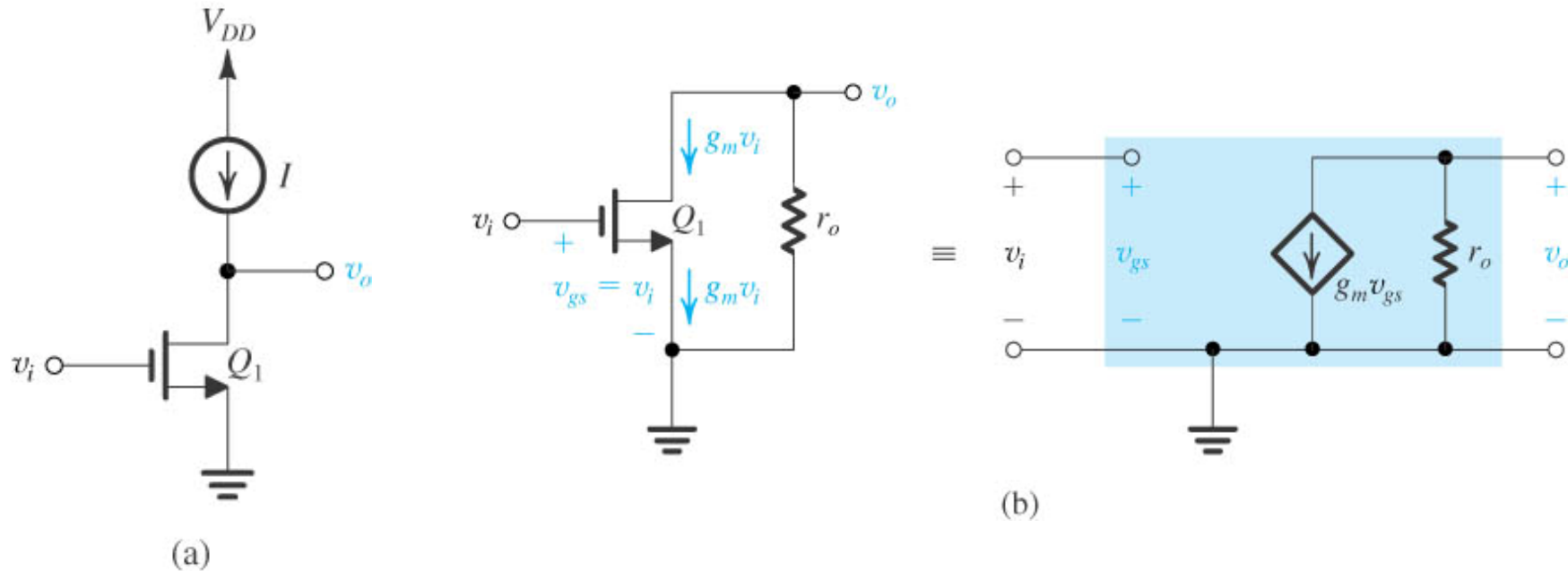


$$R_i =$$



$$A_{vo} =$$

$$R_o =$$

Common-source amplifier with active load

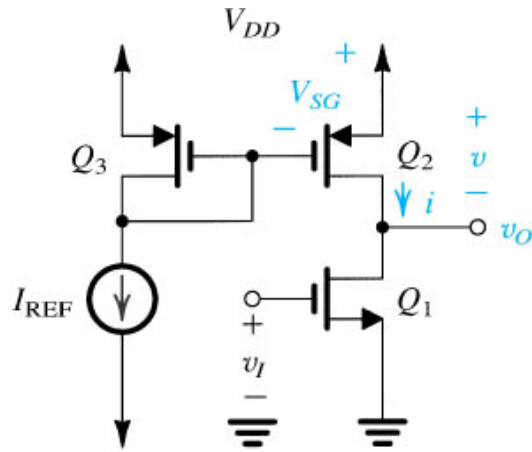


(a)

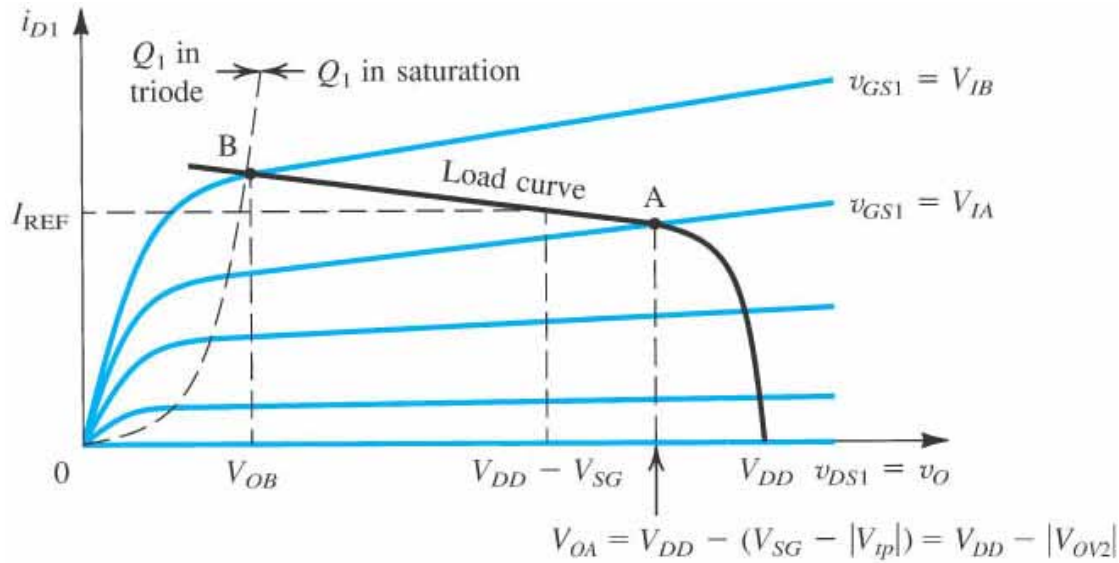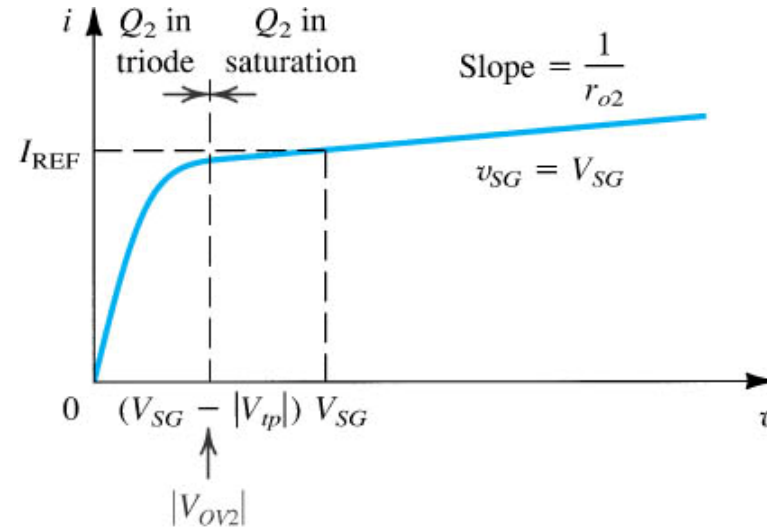

(c)

• **Large-signal characteristics**

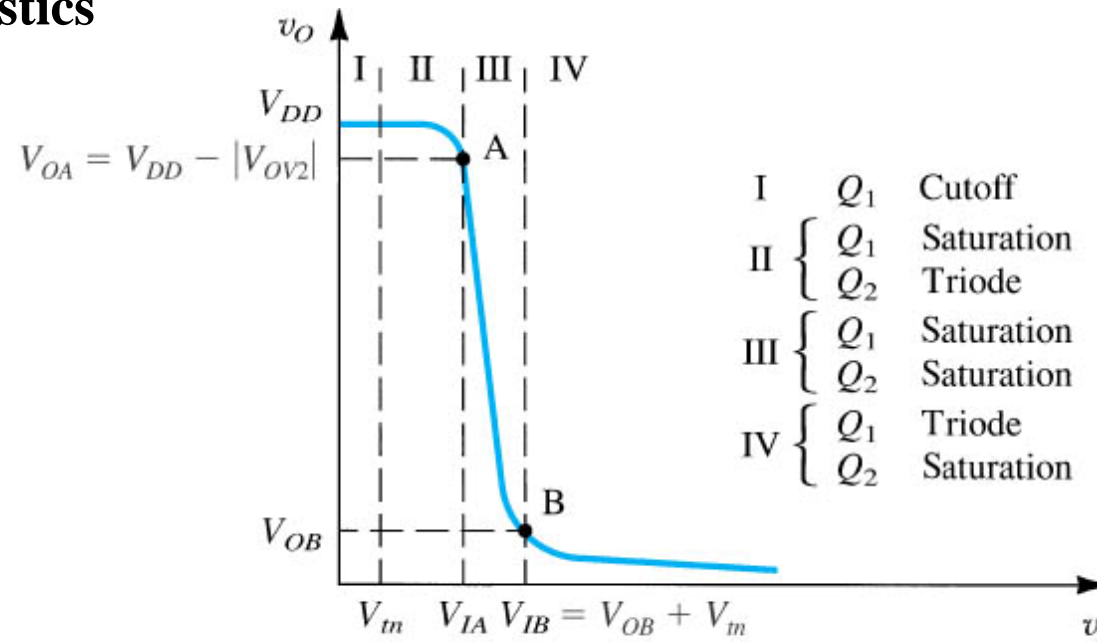


(d)

• **Small-signal characteristics (in region III)**

$R_{in} =$


$A_v =$

$R_{out} =$

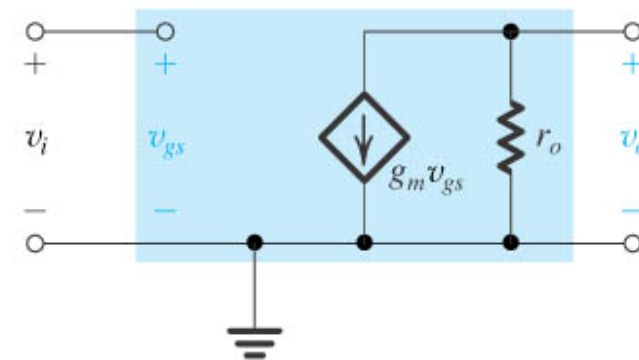


(b)


• **High-frequency response**

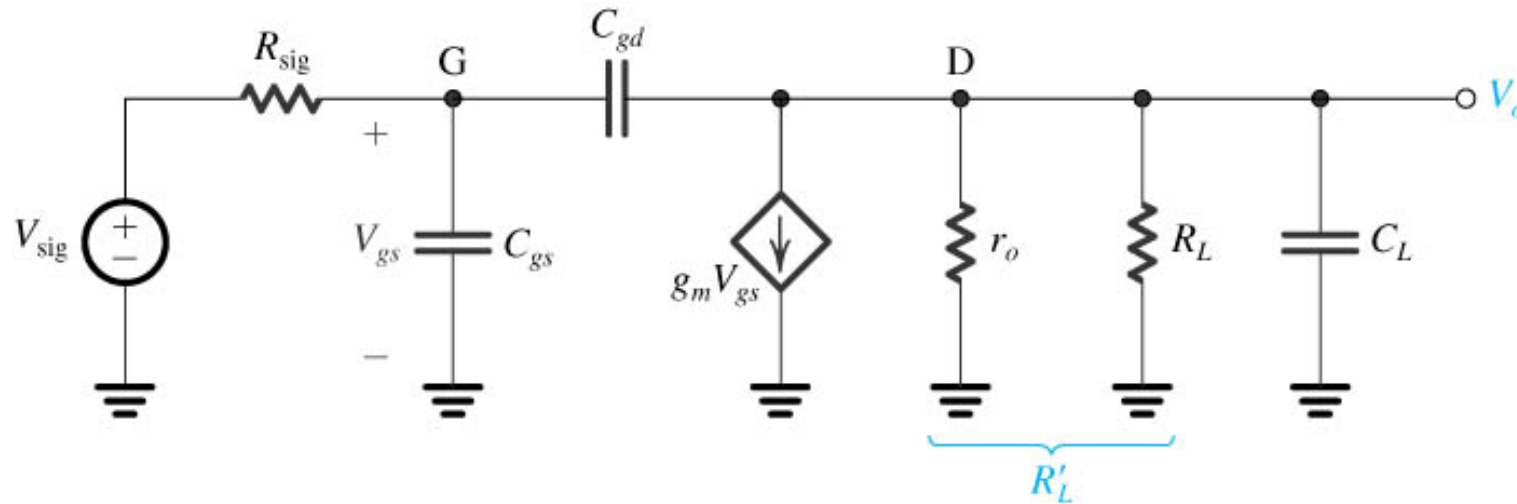


(i) Analysis by **Miller's Theorem**

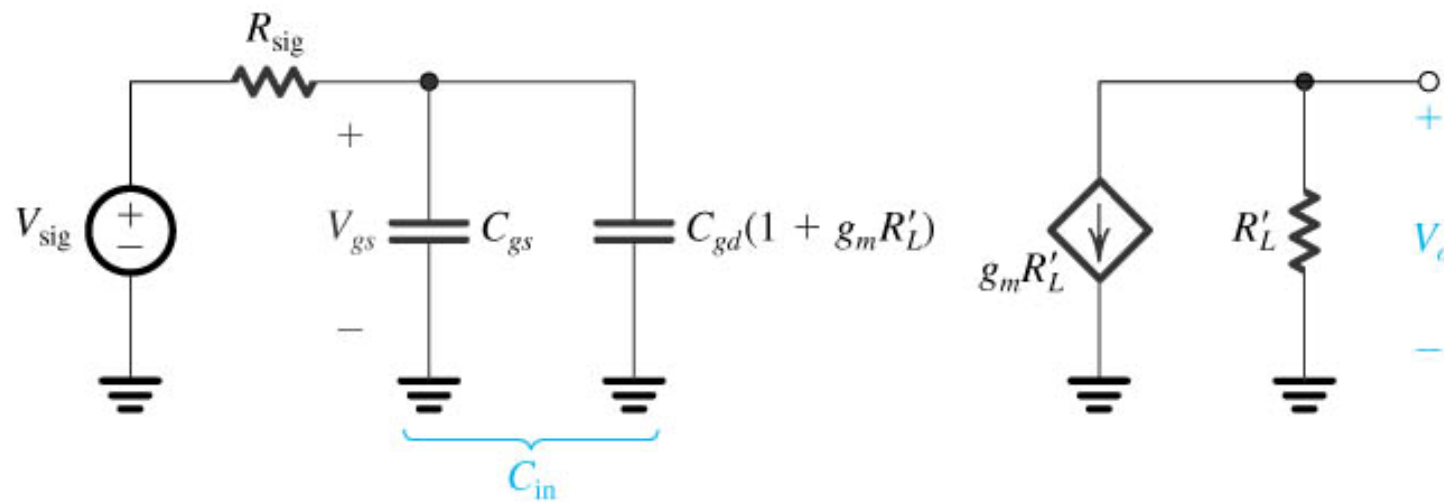

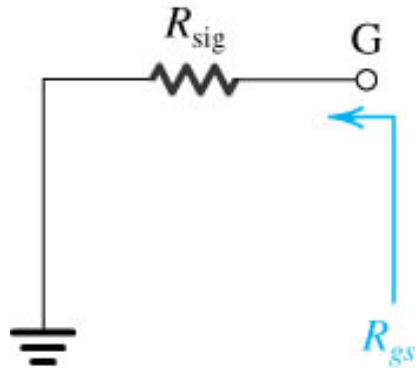(ii) Analysis by **Open-circuit time constants**




(a)

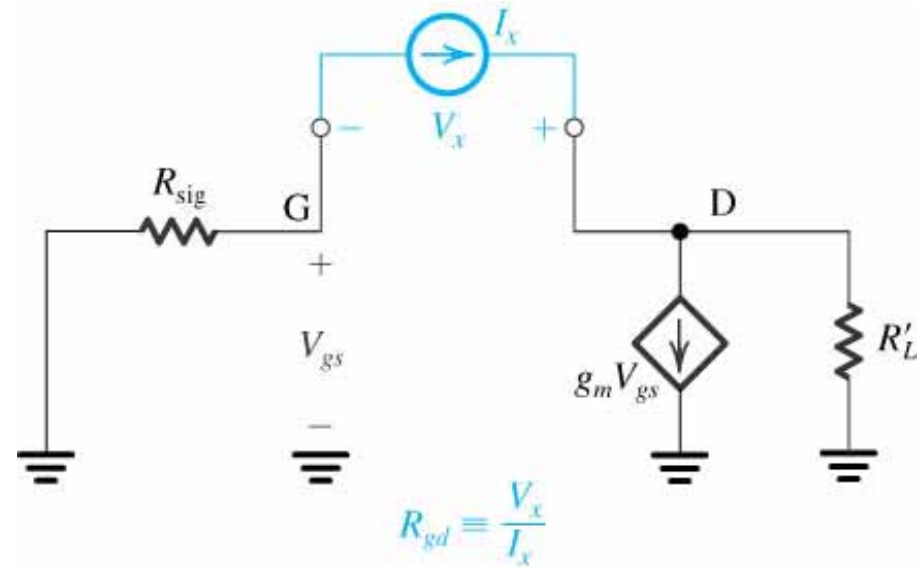


$$R_{gd} \equiv \frac{V_x}{I_x}$$

(b)

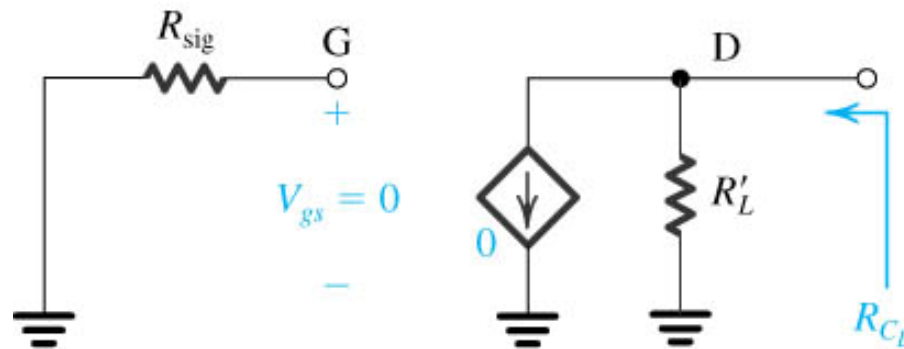


(c)


(iii) Exact analysis

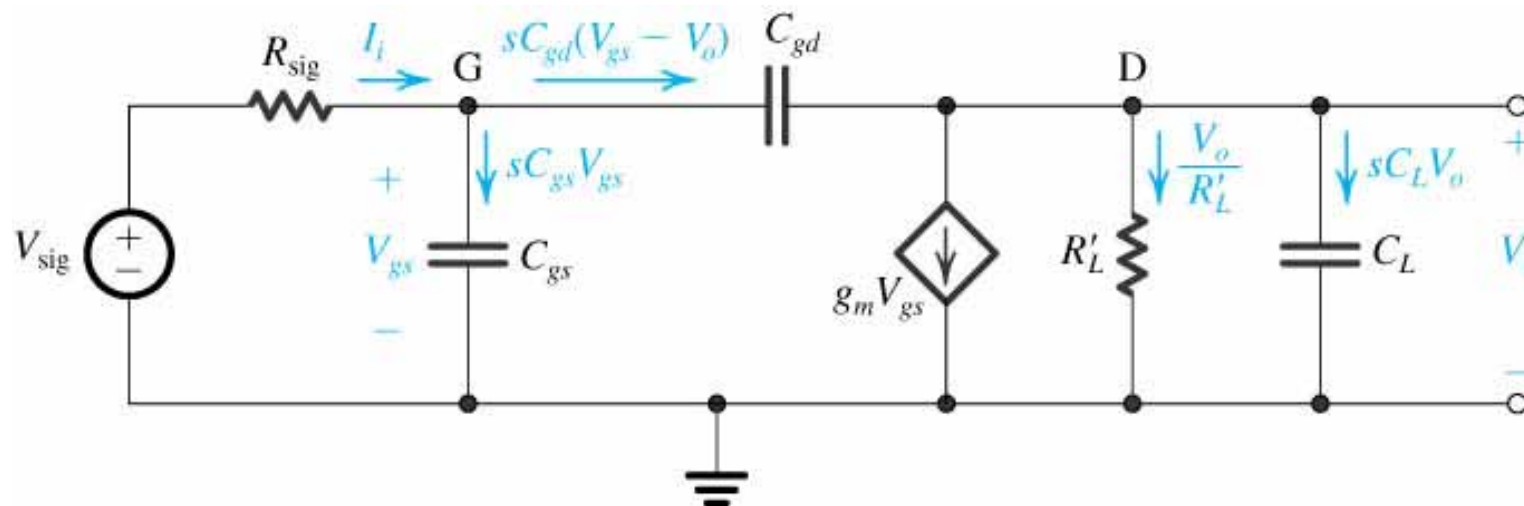

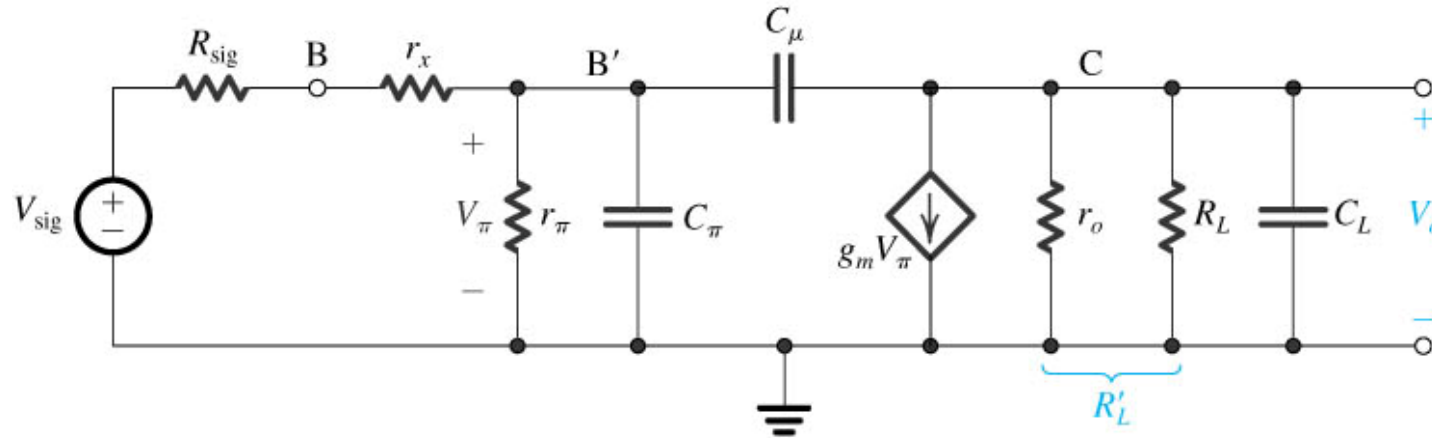Formulas for Common-Emitter amplifier with active load



(a)

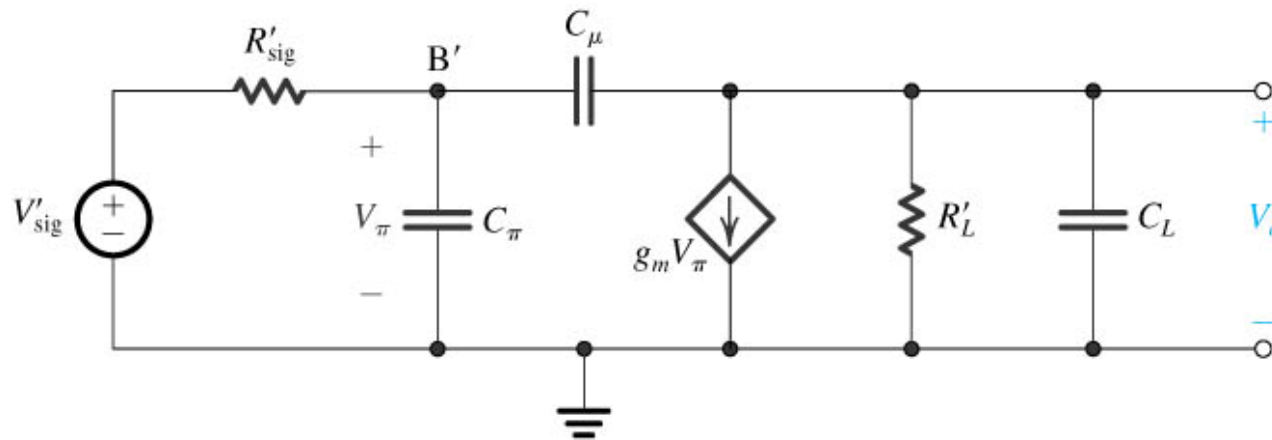

(b)