

Chapter 11

Balanced Three-Phase Circuits

11.1-2 Three-Phase Systems

11.3 Analysis of the Y-Y Circuit


11.4 Analysis of the Y- Δ Circuit

11.5 Power Calculations in Balanced Three-Phase Circuits

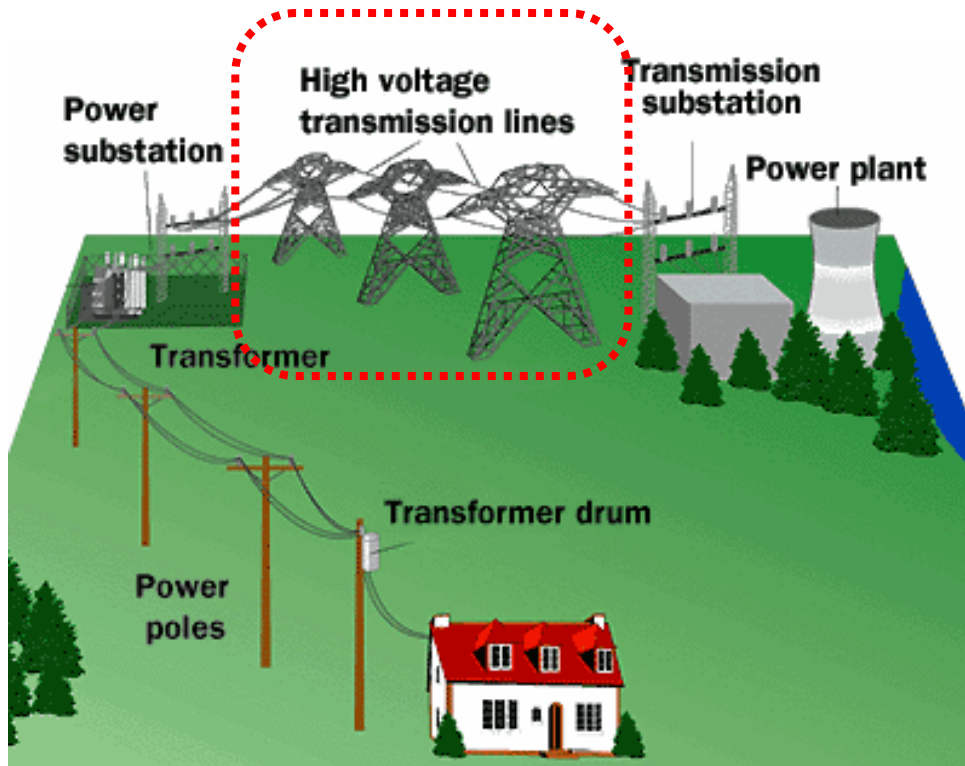11.6 Measuring Average Power in Three-Phase Circuits

Overview

- An electric power distribution system looks like:



where the power transmission uses “balanced three-phase” configuration.

Why three-phase?

- Three-phase generators can be driven by **constant** force or torque (to be discussed).
- Industrial applications, such as high-power motors, welding equipments, have **constant** power output if they are three-phase systems (to be discussed).

Key points

- What is a three-phase circuit (source, line, load)?
- Why a balanced three-phase circuit can be analyzed by an **equivalent one-phase circuit**?
- How to get all the unknowns (e.g. line voltage of the load) by the result of one-phase circuit analysis?
- Why the **total instantaneous power** of a balanced three-phase circuit is a **constant**?




Section 11.1, 11.2

Three-Phase Systems

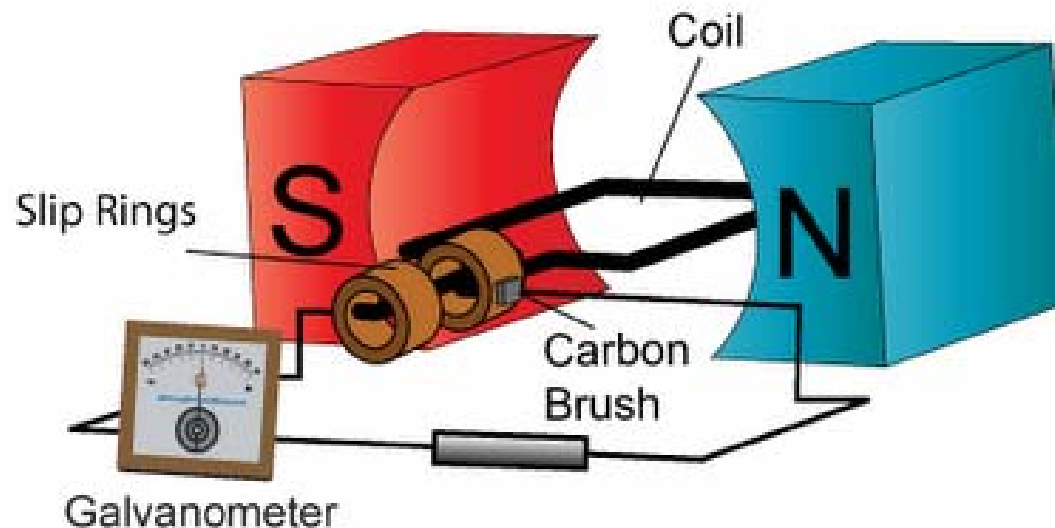1. Three-phase sources
2. Three-phase systems

One-phase voltage sources


- One-phase ac generator: static magnets, one rotating coil, single output voltage $v(t) = V_m \cos \omega t$.





(www.ac-motors.us)

Three-phase voltage sources

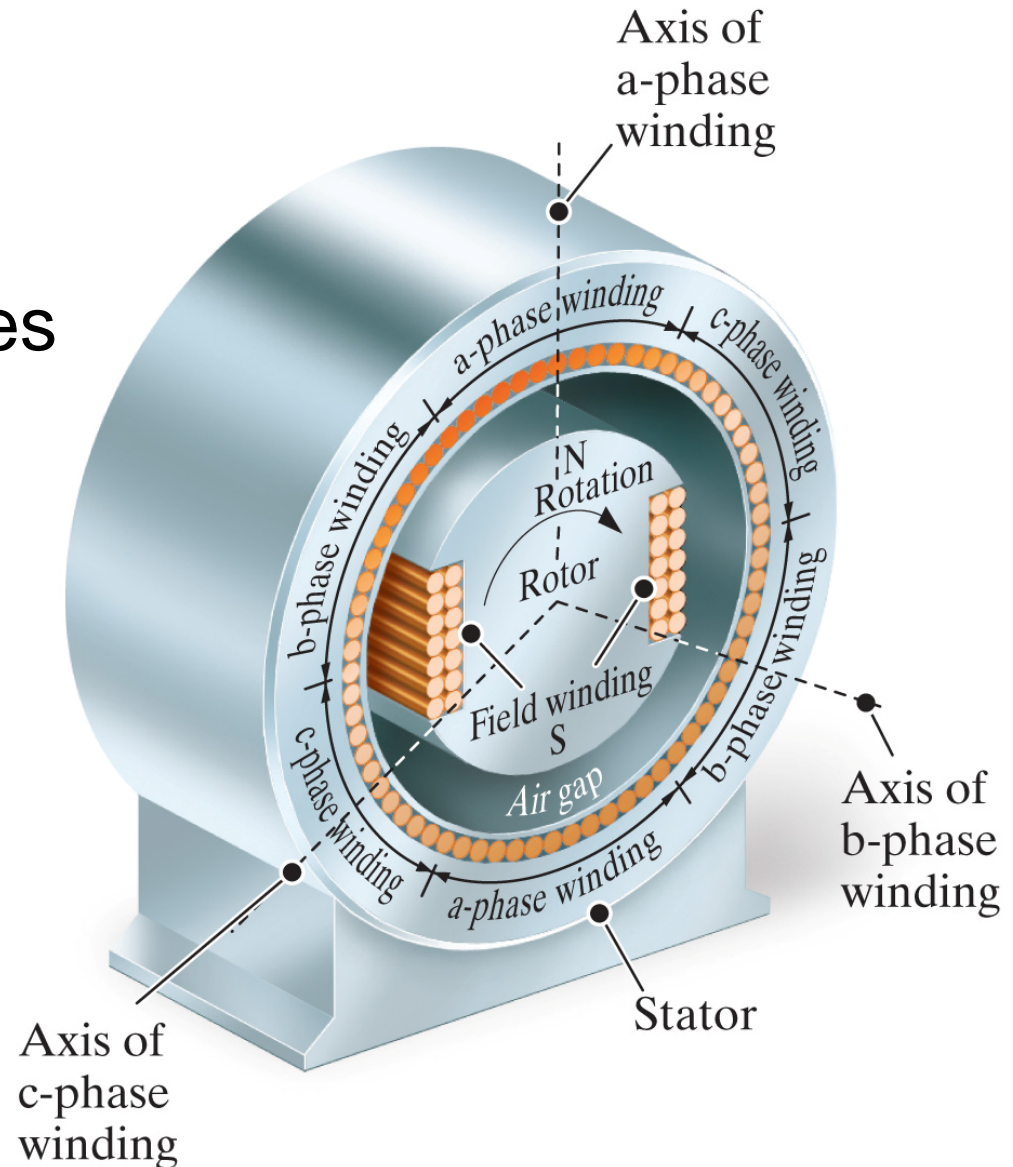- Three static coils, rotating magnets, three output voltages $v_a(t)$, $v_b(t)$, $v_c(t)$.





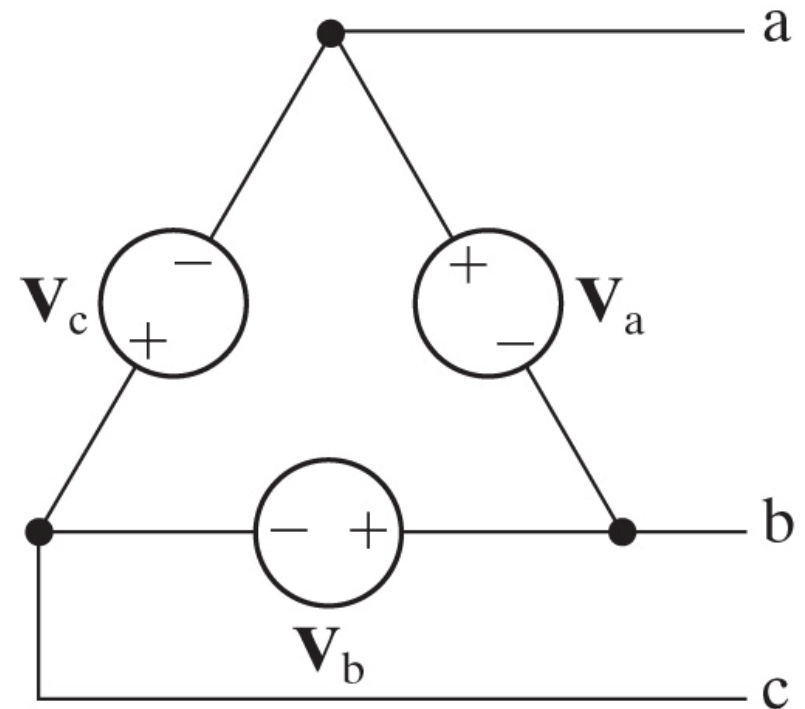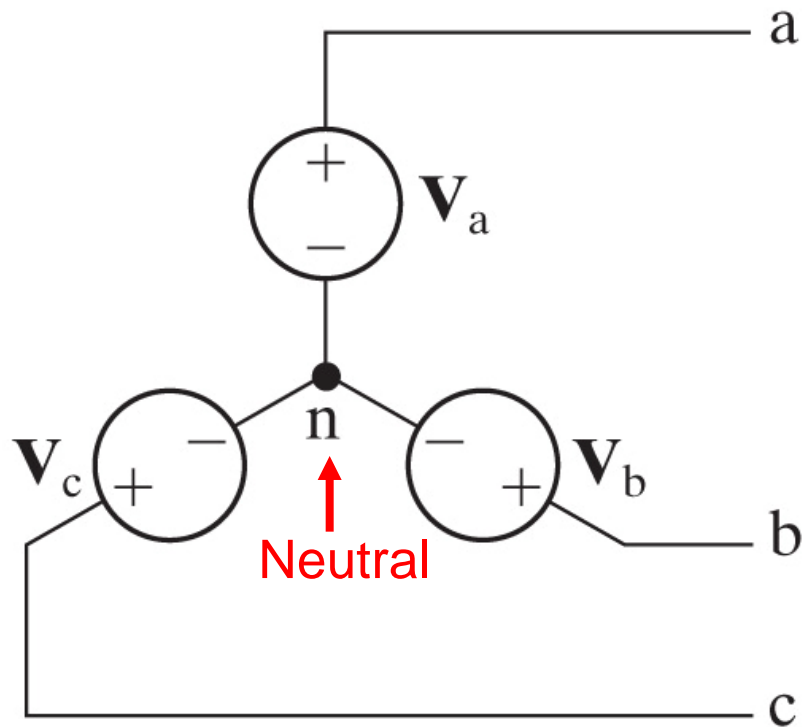Ideal Y- and Δ -connected voltage sources



Real Y- and Δ -connected voltage sources

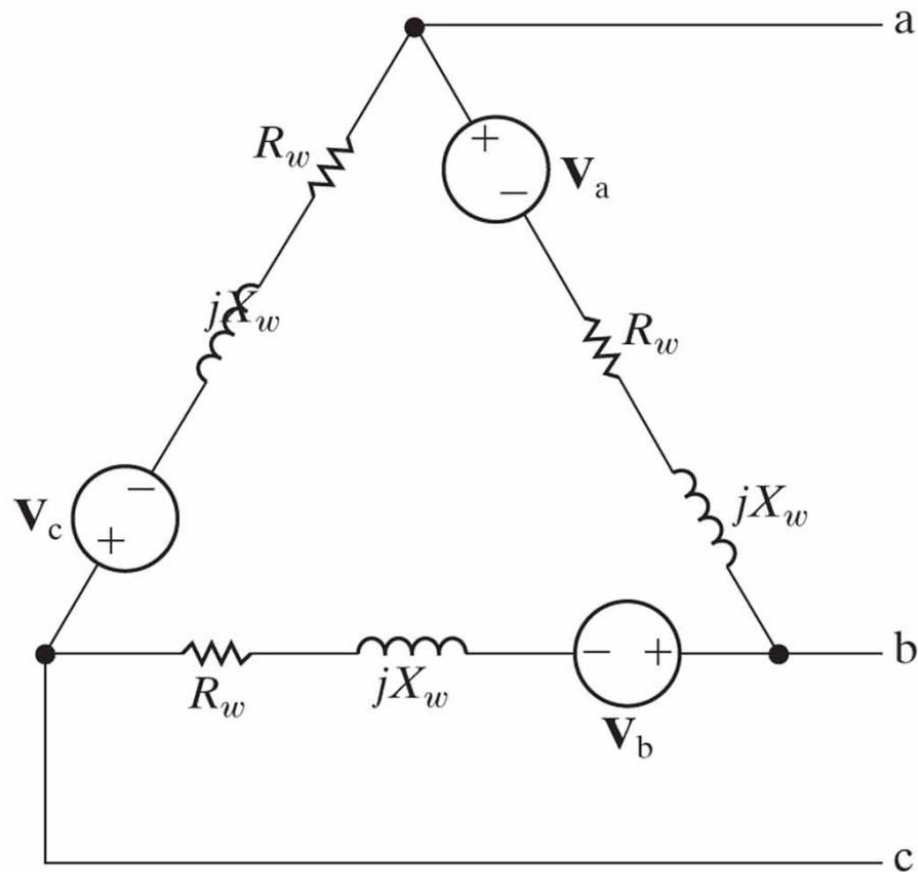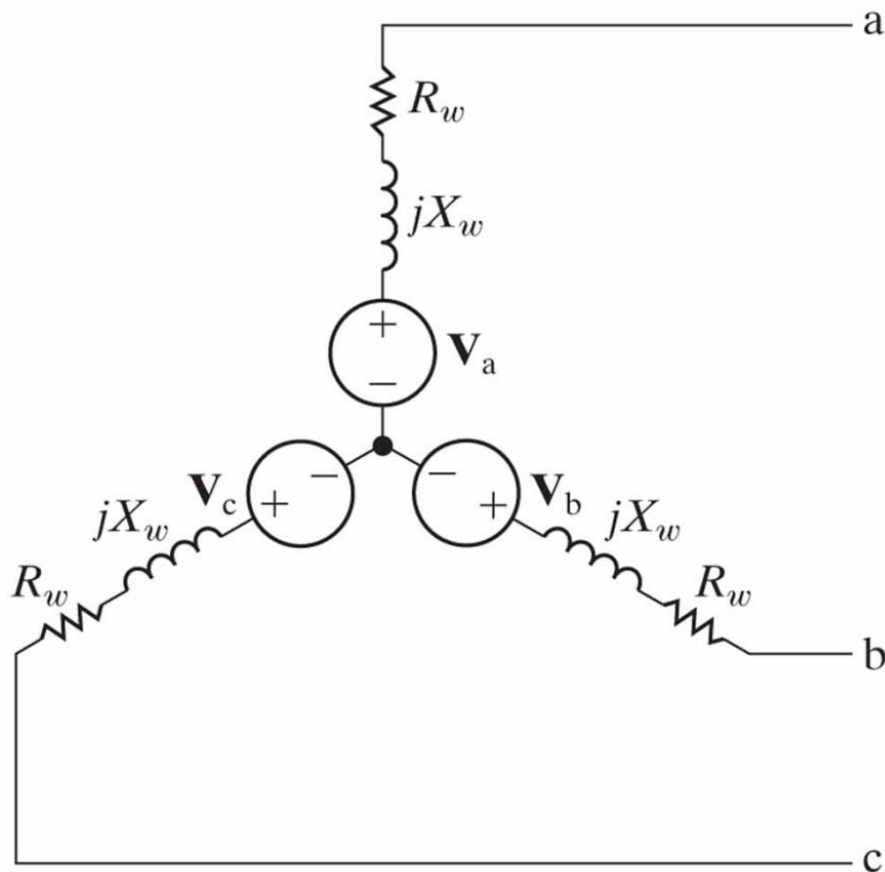- Internal impedance of a generator is usually **inductive** (due to the use of coils).





Balanced three-phase voltages


- Three sinusoidal voltages of the same amplitude, frequency, but differing by 120° phase difference with one another.
- There are two possible sequences:
 1. abc (positive) sequence: $v_b(t)$ lags $v_a(t)$ by 120° .
 2. acb (negative) sequence: $v_b(t)$ leads $v_a(t)$ by 120° .

abc sequence

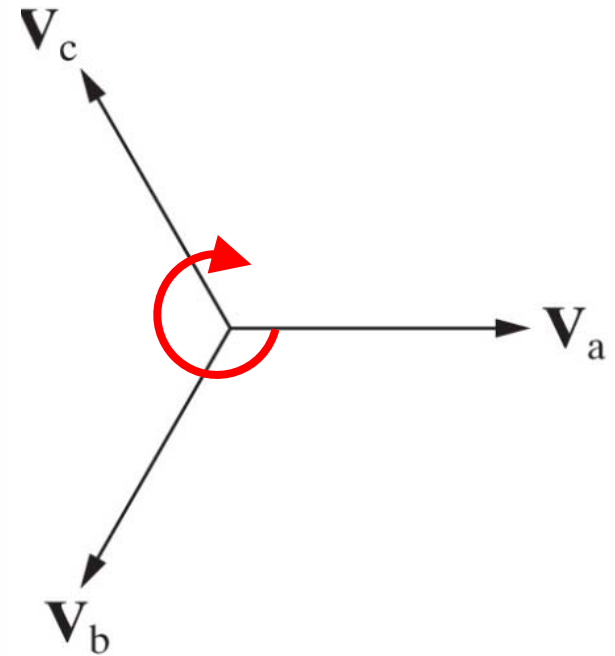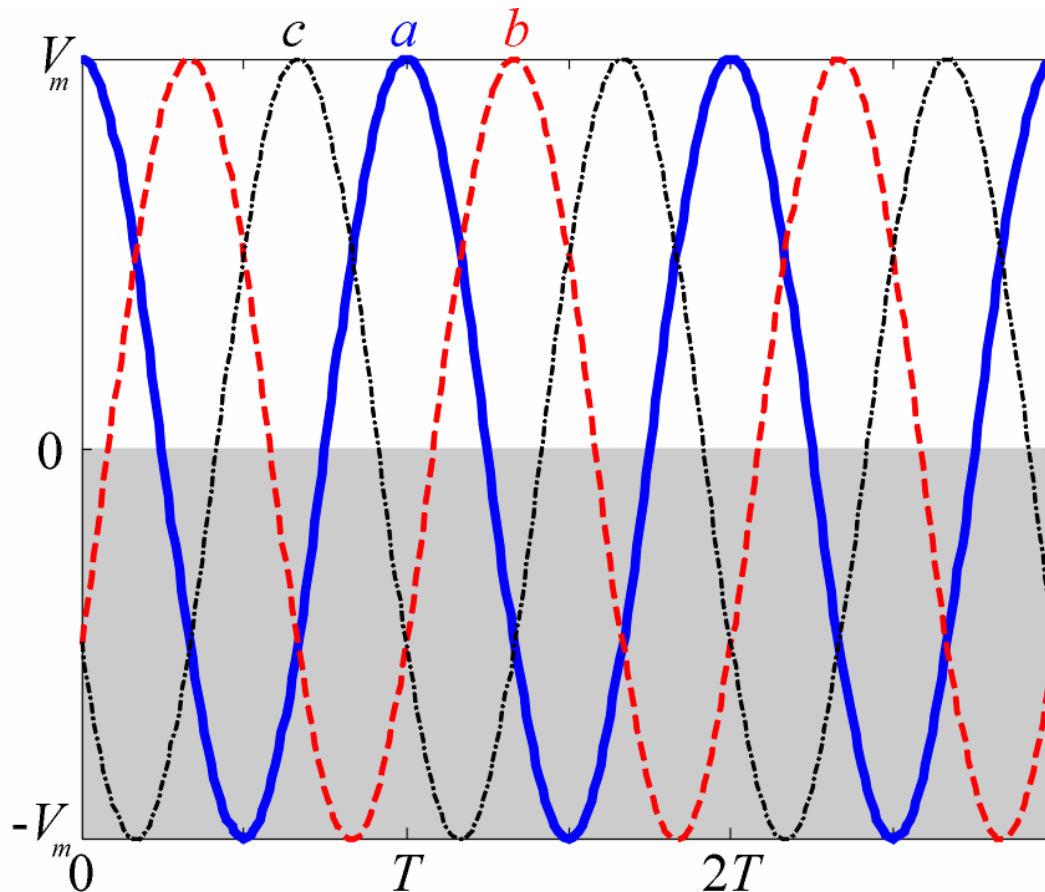
- $v_b(t)$ lags $v_a(t)$ by 120° or $T/3$.
- $\mathbf{V}_a = V_m \angle 0^\circ$, $\mathbf{V}_b = V_m \angle -120^\circ$, $\mathbf{V}_c = V_m \angle +120^\circ$.



Three-phase systems

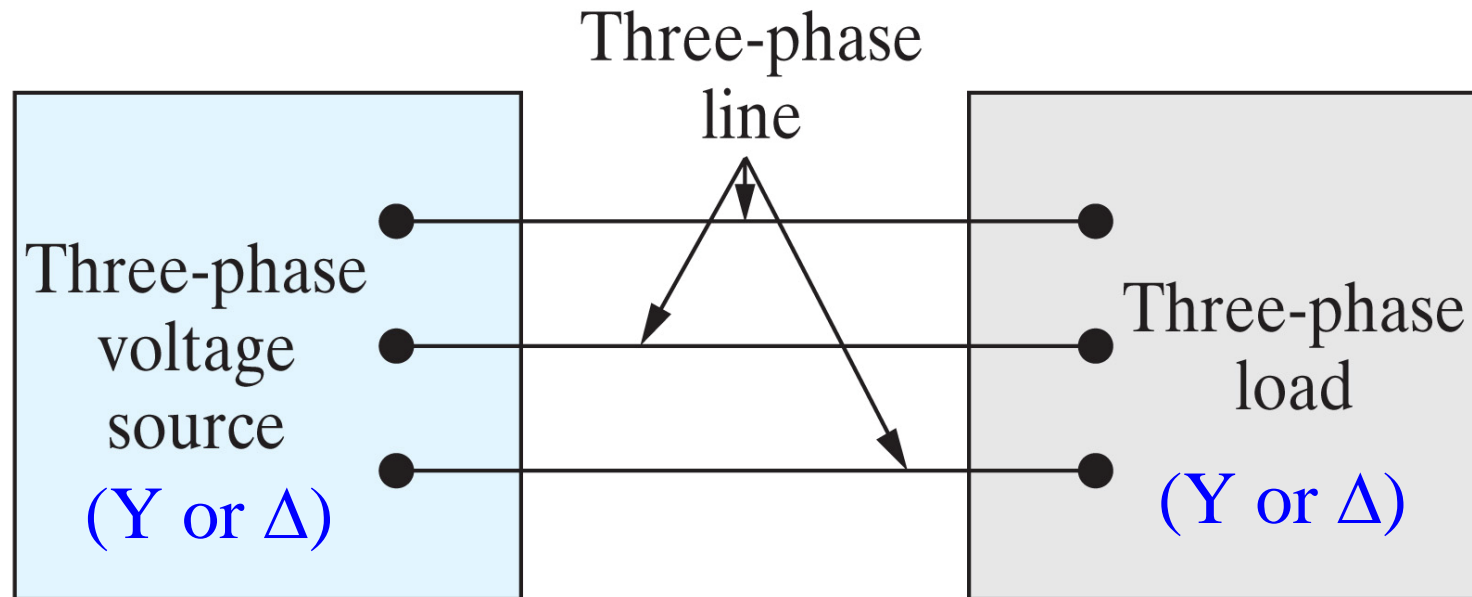

- Source-load can be connected in four configurations: Y-Y, Y-Δ, Δ-Y, Δ-Δ.
- It's sufficient to analyze Y-Y, while the others can be treated by Δ-Y and Y-Δ transformations.

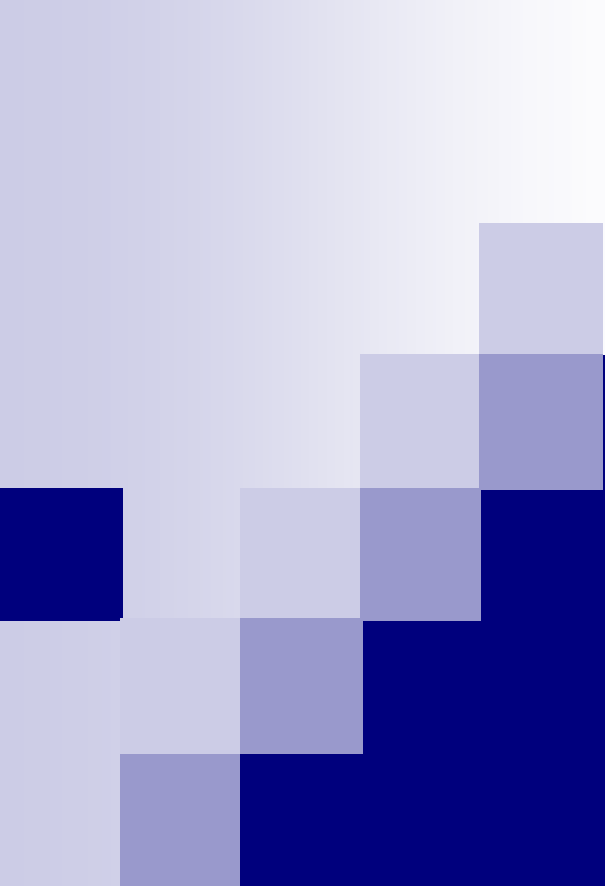


Section 11.3

Analysis of the Y-Y Circuit


1. Equivalent one-phase circuit for balanced Y-Y circuit
2. Line currents, phase and line voltages

General Y-Y circuit model

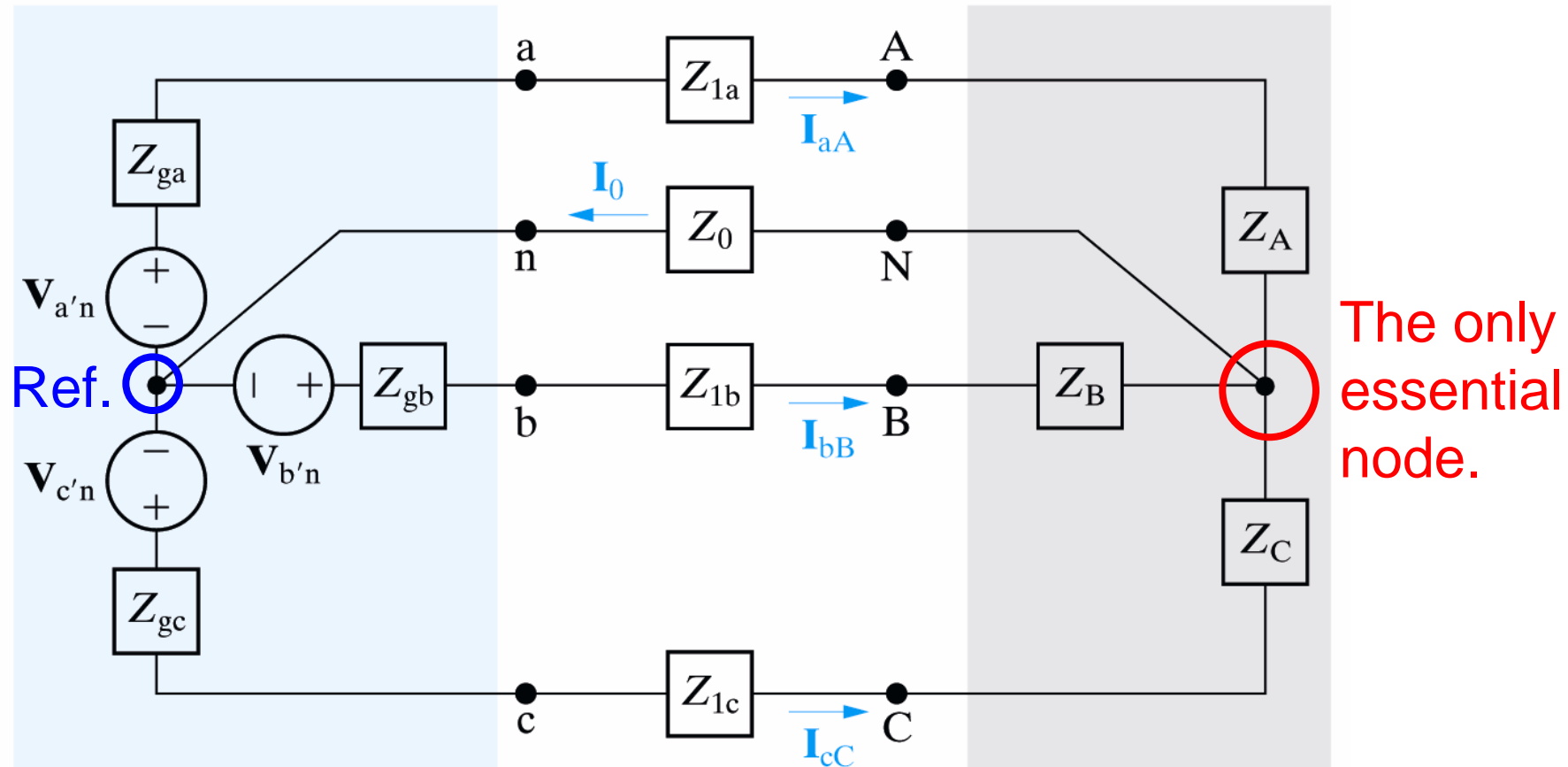

Unknowns to be solved

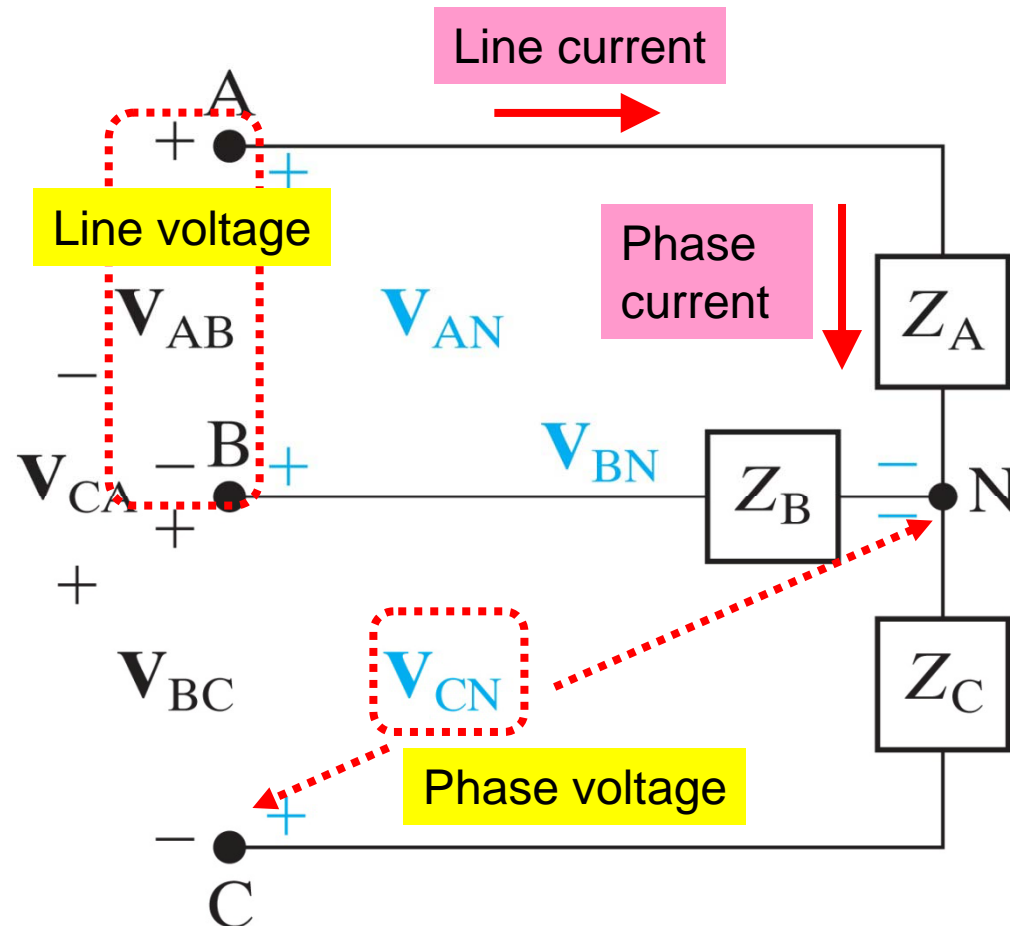- Line (line-to-line) voltage: voltage across any pair of lines.
- Phase (line-to-neutral) voltage: voltage across a single phase.
- For Y-connected load, line current equals phase current.



Solution to general three-phase circuit

- No matter it's **balanced or imbalanced** three-phase circuit, KCL leads to one equation:

$$\mathbf{I}_0 = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC}, \Rightarrow$$

$$\frac{\mathbf{V}_N}{Z_0} = \frac{\mathbf{V}_{a'n} - \mathbf{V}_N}{Z_{ga} + Z_{1a} + Z_A} + \frac{\mathbf{V}_{b'n} - \mathbf{V}_N}{Z_{gb} + Z_{1b} + Z_B} + \frac{\mathbf{V}_{c'n} - \mathbf{V}_N}{Z_{gc} + Z_{1c} + Z_C} \dots (1),$$

↓	↓	↓	↓
Impedance of neutral line.	Total impedance along line aA.	Total impedance along line bB.	Total impedance along line cC.

which is sufficient to solve \mathbf{V}_N (thus the entire circuit).

Solution to “balanced” three-phase circuit

■ For balanced three-phase circuits,

1. $\{\mathbf{V}_{a'n}, \mathbf{V}_{b'n}, \mathbf{V}_{c'n}\}$ have equal magnitude and 120° relative phases;

2. $\{Z_{ga} = Z_{gb} = Z_{gc}\}, \{Z_{1a} = Z_{1b} = Z_{1c}\}, \{Z_A = Z_B = Z_C\}$;
 \Rightarrow total impedance along any line is the same


$$Z_{ga} + Z_{1a} + Z_A = \dots = \mathbf{Z}_\phi.$$

■ Eq. (1) becomes:
$$\frac{\mathbf{V}_N}{Z_0} = \frac{\mathbf{V}_{a'n} - \mathbf{V}_N}{Z_\phi} + \frac{\mathbf{V}_{b'n} - \mathbf{V}_N}{Z_\phi} + \frac{\mathbf{V}_{c'n} - \mathbf{V}_N}{Z_\phi},$$


$$\Rightarrow \mathbf{V}_N \left(\frac{1}{Z_0} + \frac{3}{Z_\phi} \right) = \frac{\mathbf{V}_{a'n} + \mathbf{V}_{b'n} + \mathbf{V}_{c'n}}{Z_\phi} = 0, \quad \mathbf{V}_N = 0.$$

Meaning of the solution

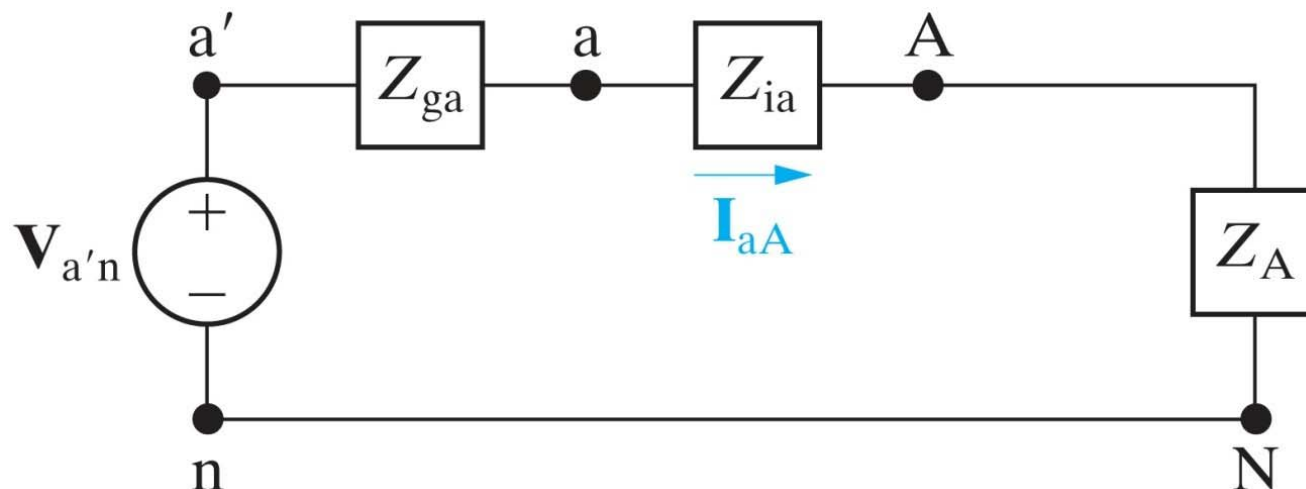- $V_N = 0$ means no voltage difference between nodes n and N in the presence of Z_0 . \Rightarrow Neutral line is **both short** ($v = 0$) **and open** ($i = 0$).
- The three-phase circuit can be separated into 3 one-phase circuits (open), while each of them has a short between nodes n and N .



Equivalent one-phase circuit

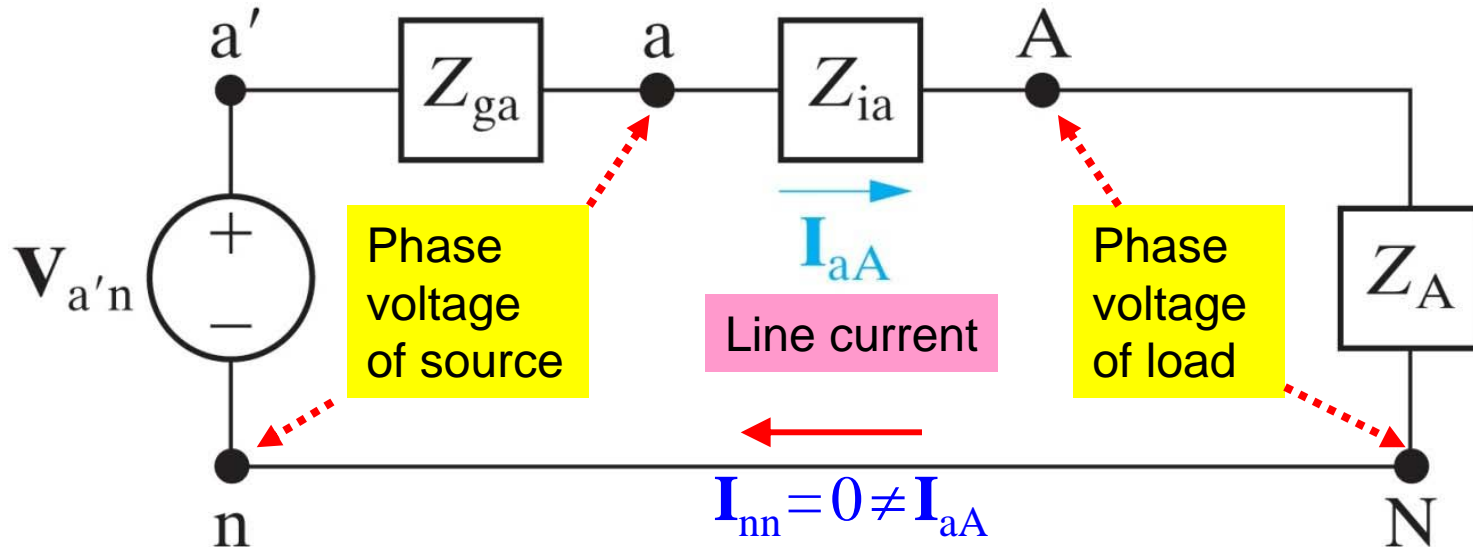

- Directly giving the line current & phase voltages:


$$I_{aA} = \frac{V_{a'n} - \cancel{V_N}}{(Z_{ga} + Z_{1a} + Z_A) = Z_\phi}, \quad V_{AN} = I_{aA} Z_A, \quad V_{an} = I_{aA} (Z_{1a} + Z_A).$$

- Unknowns of phases b, c can be determined by the fixed (abc or acb) **sequence relation**.


The 3 line and phase currents in abc sequence

- Given $\mathbf{I}_{aA} = \mathbf{V}_{a'n} / Z_\phi$, the other 2 line currents are:
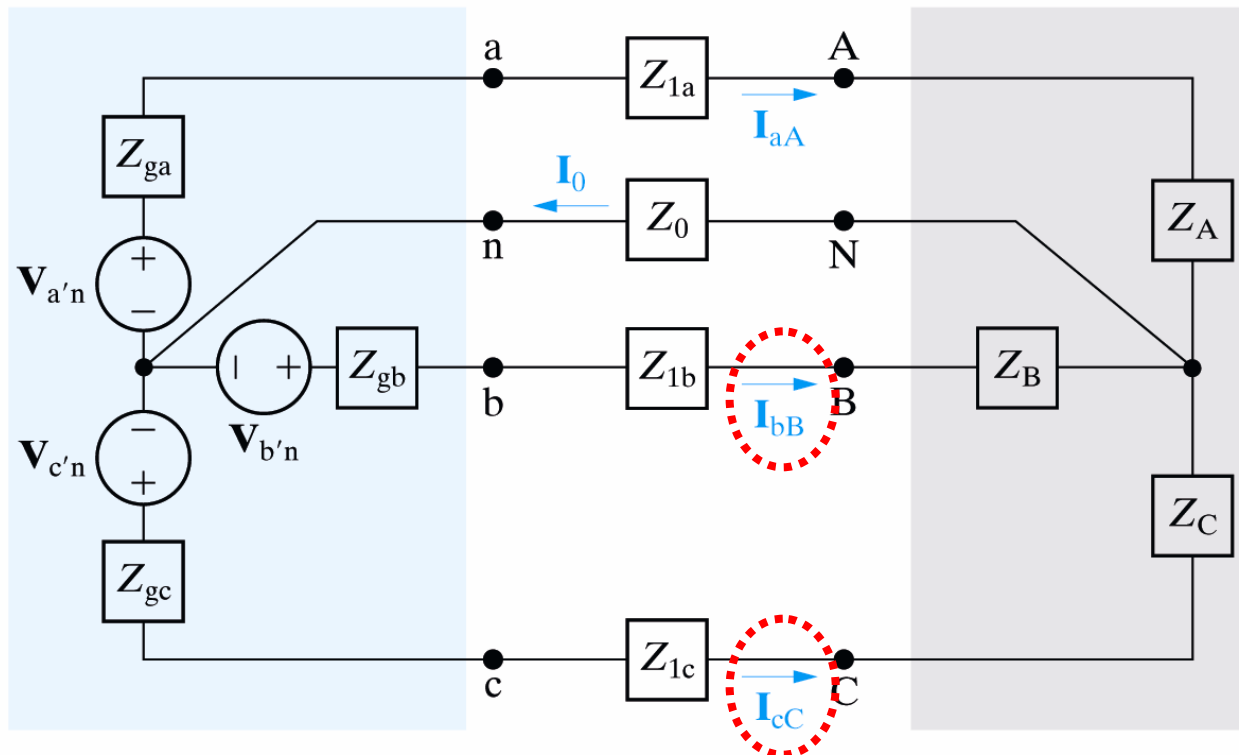
$$\mathbf{I}_{bB} = \frac{\mathbf{V}_{b'n}}{Z_\phi} = \mathbf{I}_{aA} \angle -120^\circ, \quad \mathbf{I}_{cC} = \frac{\mathbf{V}_{c'n}}{Z_\phi} = \mathbf{I}_{aA} \angle 120^\circ,$$



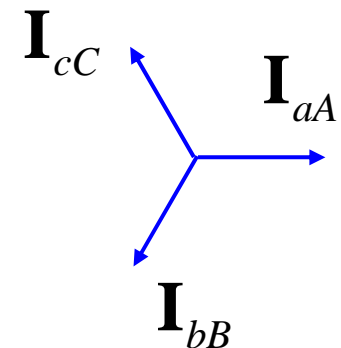which still follow the abc sequence relation.




The phase & line voltages of the load in abc seq.

$$\mathbf{V}_{AN} = \mathbf{V}_{a'n} \frac{Z_A}{Z_\phi}, \mathbf{V}_{BN} = \mathbf{V}_{b'n} \frac{Z_B}{Z_\phi} = \mathbf{V}_{AN} \angle -120^\circ, \mathbf{V}_{CN} = \mathbf{V}_{AN} \angle 120^\circ.$$

$$\begin{aligned} \mathbf{V}_{AB} &= \mathbf{V}_{AN} - \mathbf{V}_{BN} \\ &= \mathbf{V}_{AN} - (\mathbf{V}_{AN} \angle -120^\circ) \\ &= \sqrt{3} \mathbf{V}_{AN} \angle +30^\circ, \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{BC} &= (\mathbf{V}_{AN} \angle -120^\circ) - (\mathbf{V}_{AN} \angle +120^\circ) \\ &= \sqrt{3} \mathbf{V}_{AN} \angle -90^\circ, \end{aligned}$$
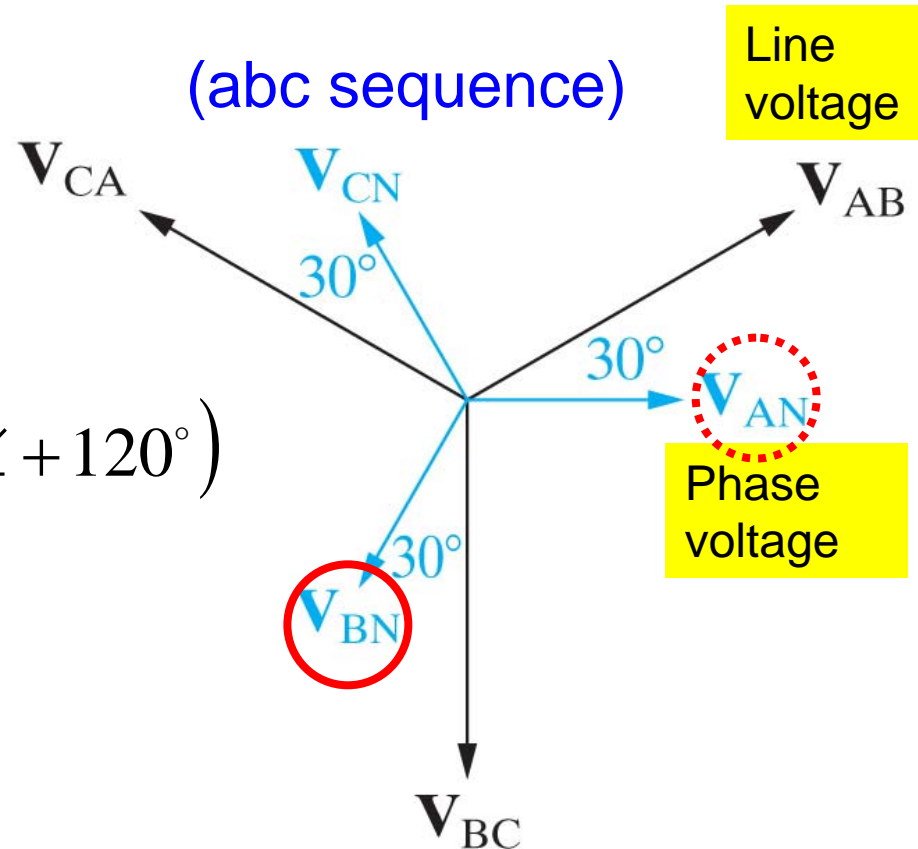
$$\begin{aligned} \mathbf{V}_{CA} &= (\mathbf{V}_{AN} \angle +120^\circ) - \mathbf{V}_{AN} \\ &= \sqrt{3} \mathbf{V}_{AN} \angle +150^\circ. \end{aligned}$$




The phase & line voltages of the load in acb seq.

$$\begin{aligned}\mathbf{V}_{AB} &= \mathbf{V}_{AN} - \mathbf{V}_{BN} \\ &= \mathbf{V}_{AN} - (\mathbf{V}_{AN} \angle +120^\circ) \\ &= \sqrt{3} \mathbf{V}_{AN} \angle -30^\circ,\end{aligned}$$

$$\begin{aligned}\mathbf{V}_{BC} &= (\mathbf{V}_{AN} \angle +120^\circ) - (\mathbf{V}_{AN} \angle -120^\circ) \\ &= \sqrt{3} \mathbf{V}_{AN} \angle +90^\circ,\end{aligned}$$

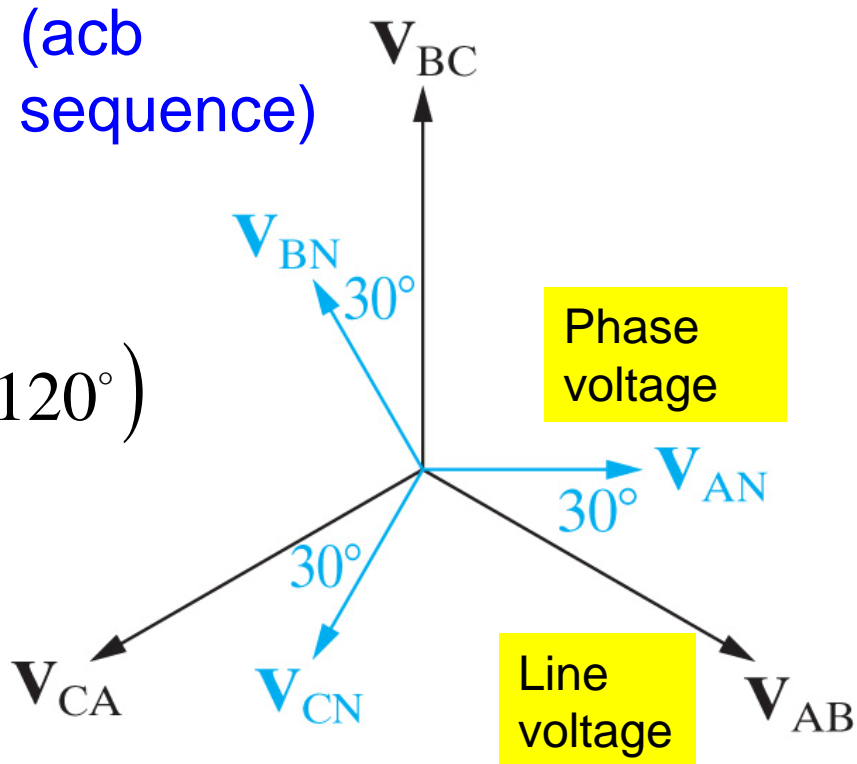
$$\begin{aligned}\mathbf{V}_{CA} &= (\mathbf{V}_{AN} \angle -120^\circ) - \mathbf{V}_{AN} \\ &= \sqrt{3} \mathbf{V}_{AN} \angle -150^\circ.\end{aligned}$$



- Line voltages are $\sqrt{3}$ times bigger, leading (abc) or lagging (acb) the phase voltages by 30° .

Example 11.1 (1)

- Q: What are the line currents, phase and line voltages of the load and source, respectively?

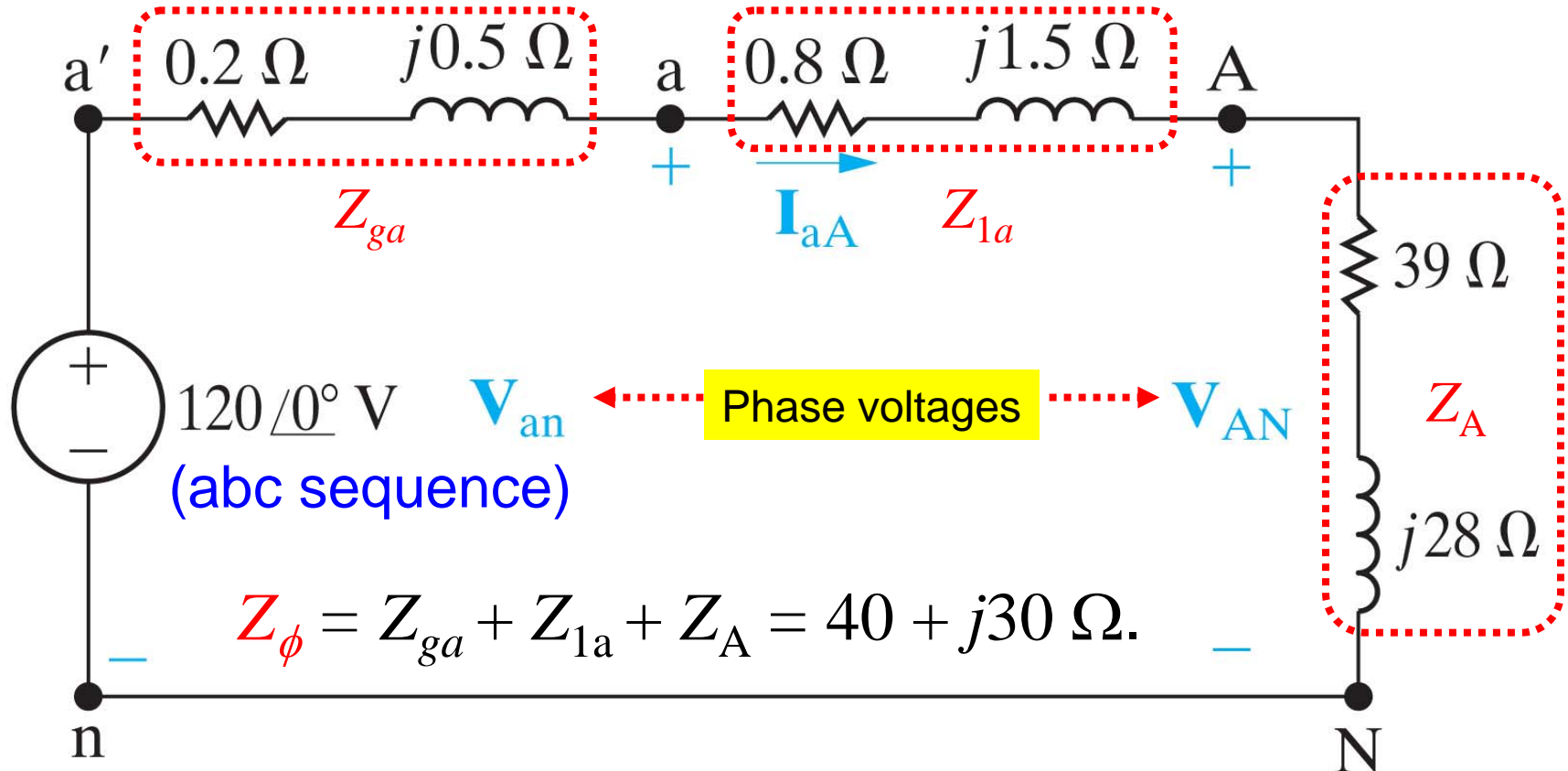

Example 11.1 (2)

- The 3 **line currents** (of both load & source) are:

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{a'n}}{Z_{ga} + Z_{1a} + Z_A} = \frac{120\angle 0^\circ}{40 + j30} = (2.4\angle -36.87^\circ) \text{ A},$$

$$\mathbf{I}_{bB} = \mathbf{I}_{aA}\angle -120^\circ = (2.4\angle -156.87^\circ) \text{ A},$$

$$\mathbf{I}_{cC} = \mathbf{I}_{aA}\angle +120^\circ = (2.4\angle +83.13^\circ) \text{ A}.$$

- The 3 **phase voltages** of the **load** are:

$$\mathbf{V}_{AN} = \mathbf{I}_{aA}Z_A = (2.4\angle -36.87^\circ)(39 + j28) = (115.22\angle -1.19^\circ) \text{ V}.$$

$$\mathbf{V}_{BN} = \mathbf{V}_{AN}\angle -120^\circ = (115.22\angle -121.19^\circ) \text{ V},$$

$$\mathbf{V}_{CN} = \mathbf{V}_{AN}\angle +120^\circ = (115.22\angle +118.81^\circ) \text{ V}.$$

Example 11.1 (3)

- The 3 **line voltages** of the **load** are:

$$\mathbf{V}_{AB} = (\sqrt{3} \angle 30^\circ) \mathbf{V}_{AN}$$

$$= (\sqrt{3} \angle 30^\circ) (115.22 \angle -1.19^\circ)$$


$$= (199.58 \angle +28.81^\circ) \text{ V},$$

$$\mathbf{V}_{BC} = \mathbf{V}_{AB} \angle -120^\circ$$

$$= (199.58 \angle -91.19^\circ) \text{ V},$$

$$\mathbf{V}_{CA} = \mathbf{V}_{AB} \angle +120^\circ$$

$$= (199.58 \angle +148.81^\circ) \text{ V}.$$

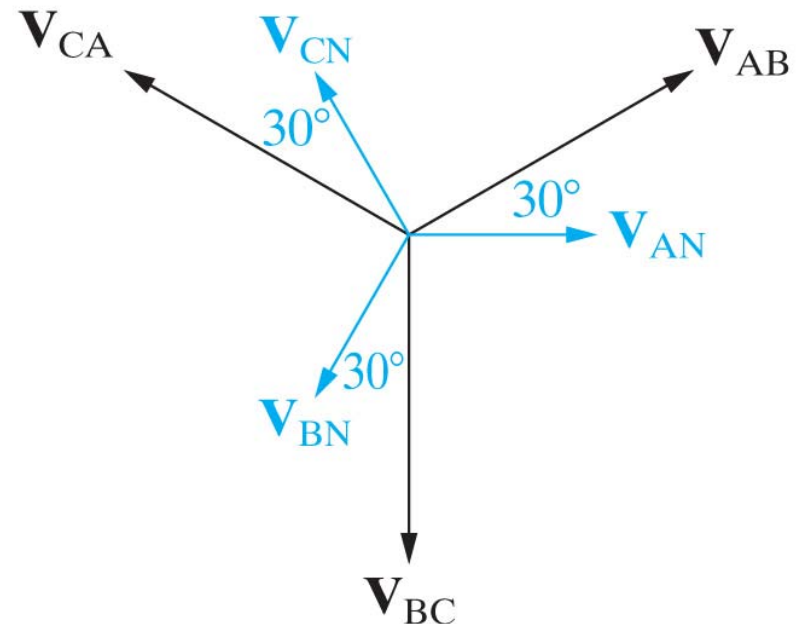

Example 11.1 (4)

- The 3 **phase voltages** of the **source** are:

$$\begin{aligned}\mathbf{V}_{an} &= \mathbf{V}_{a'n} - \mathbf{I}_{aA}Z_{ga} = 120 - (2.4 \angle -36.87^\circ)(0.2 + j0.5) \\ &= (118.9 \angle -0.32^\circ) \text{ V},\end{aligned}$$

$$\mathbf{V}_{bn} = \mathbf{V}_{an} \angle -120^\circ = (118.9 \angle -120.32^\circ) \text{ V},$$


$$\mathbf{V}_{cn} = \mathbf{V}_{an} \angle +120^\circ = (118.9 \angle +119.68^\circ) \text{ V}.$$

- The three **line voltages** of the **source** are:

$$\begin{aligned}\mathbf{V}_{ab} &= (\sqrt{3} \angle 30^\circ) \mathbf{V}_{an} = (\sqrt{3} \angle 30^\circ)(118.9 \angle -0.32^\circ) \\ &= (205.94 \angle +29.68^\circ) \text{ V},\end{aligned}$$

$$\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ = (205.94 \angle -90.32^\circ) \text{ V},$$


$$\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ = (205.94 \angle +149.68^\circ) \text{ V}.$$

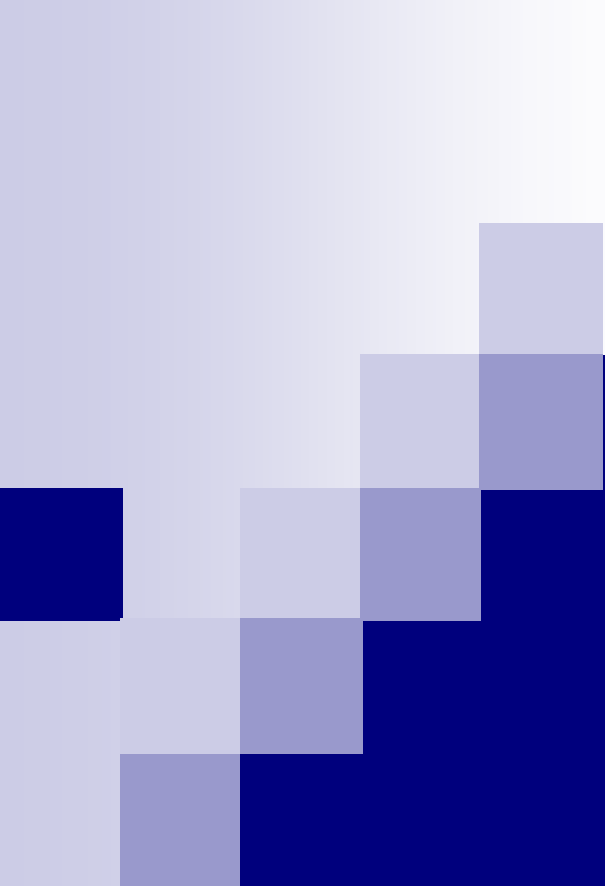

Section 11.4


Analysis of the Y- Δ Circuit

Load in Δ configuration

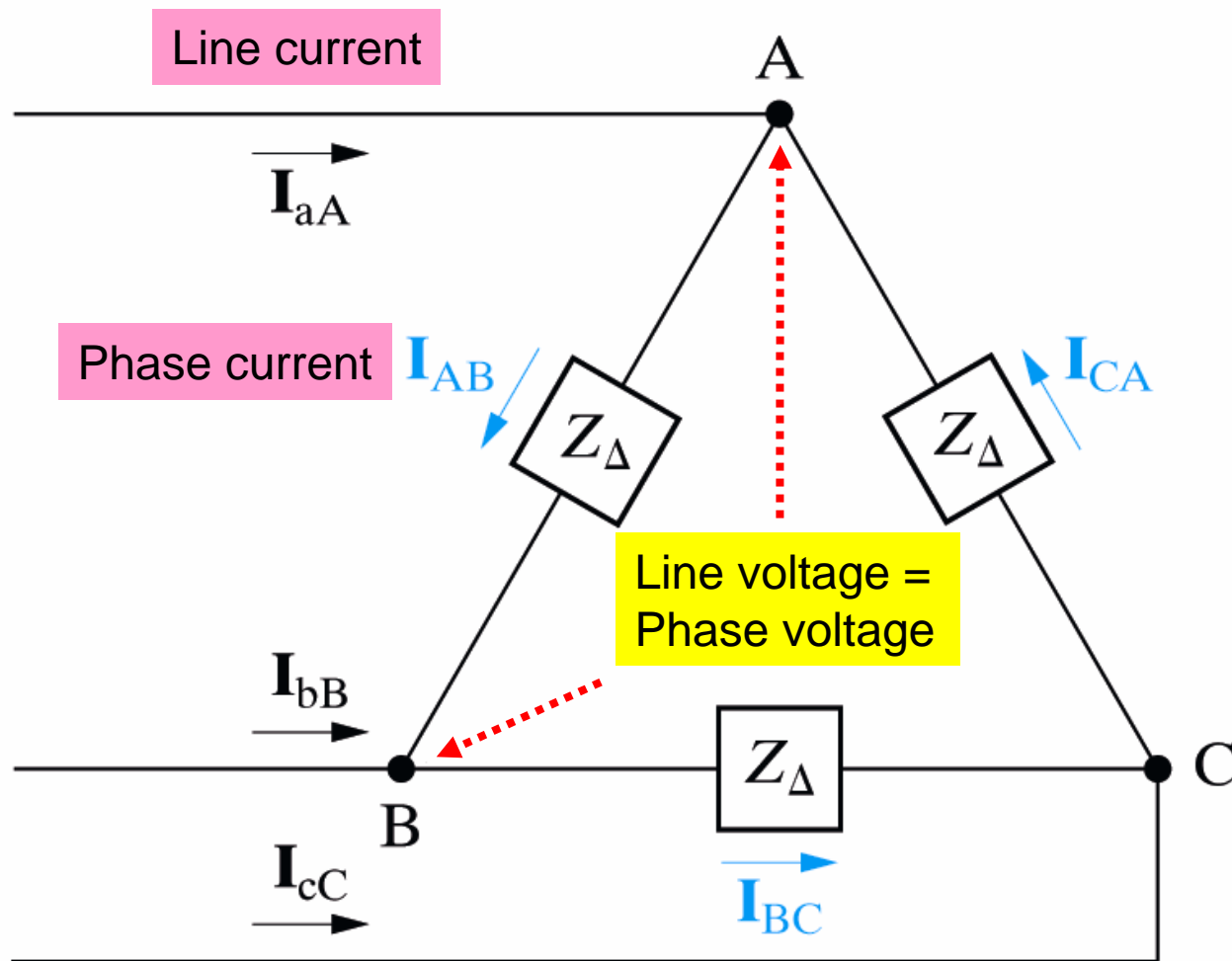

Δ -Y transformation for balanced 3-phase load

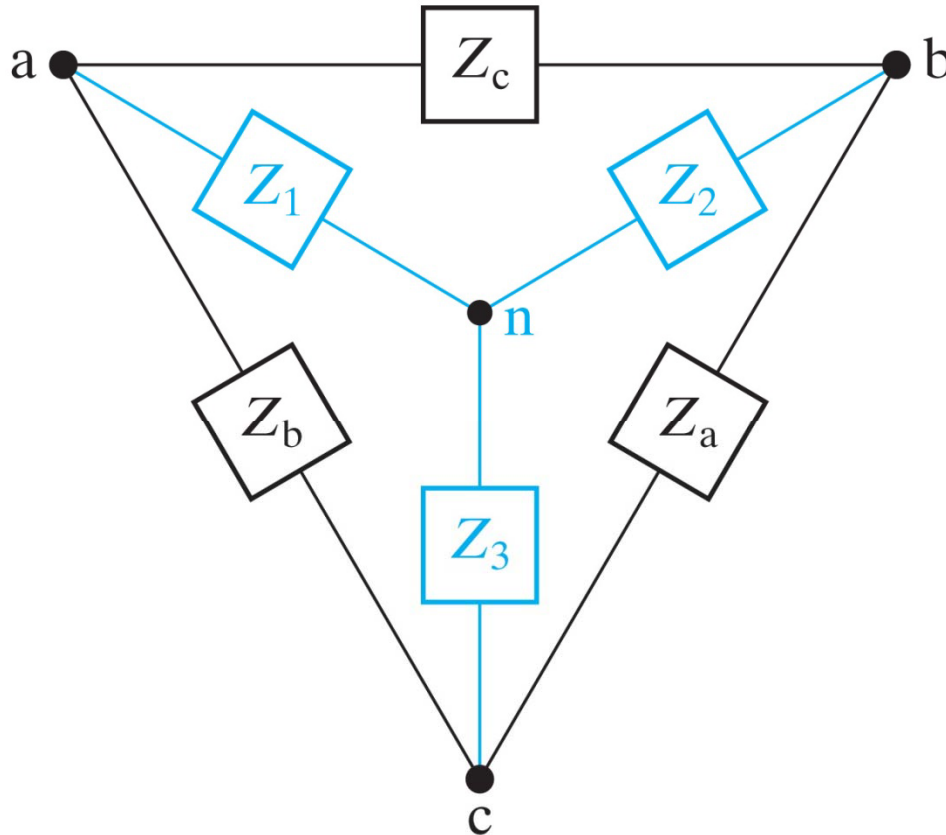- The impedance of each leg in Y-configuration (Z_Y) is one-third of that in Δ -configuration (Z_Δ):



$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c},$$


$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c},$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}.$$

$$\Rightarrow Z_Y = \frac{Z_\Delta Z_\Delta}{3Z_\Delta} = \frac{Z_\Delta}{3}.$$

Equivalent one-phase circuit

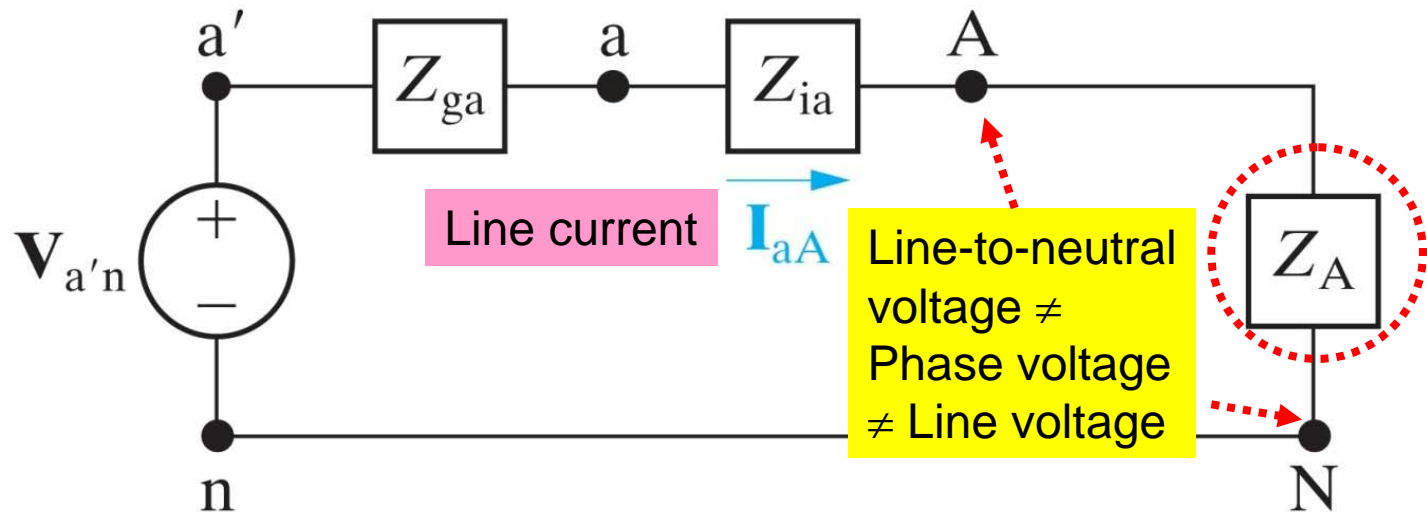- The 1-phase equivalent circuit in **Y-Y** config. continues to work if Z_A is replaced by $Z_\Delta/3$:




directly giving the line current:
$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{a'n}}{Z_{ga} + Z_{ia} + Z_A},$$


and line-to-neutral voltage:
$$\mathbf{V}_{AN} = \mathbf{I}_{aA} Z_A.$$

The 3 phase currents of the load in abc seq.

- Can be solved by 3 node equations once the 3 line currents \mathbf{I}_{aA} , \mathbf{I}_{bB} , \mathbf{I}_{cC} are known:

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_{bB} = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_{cC} = \mathbf{I}_{CA} - \mathbf{I}_{BC}.$$

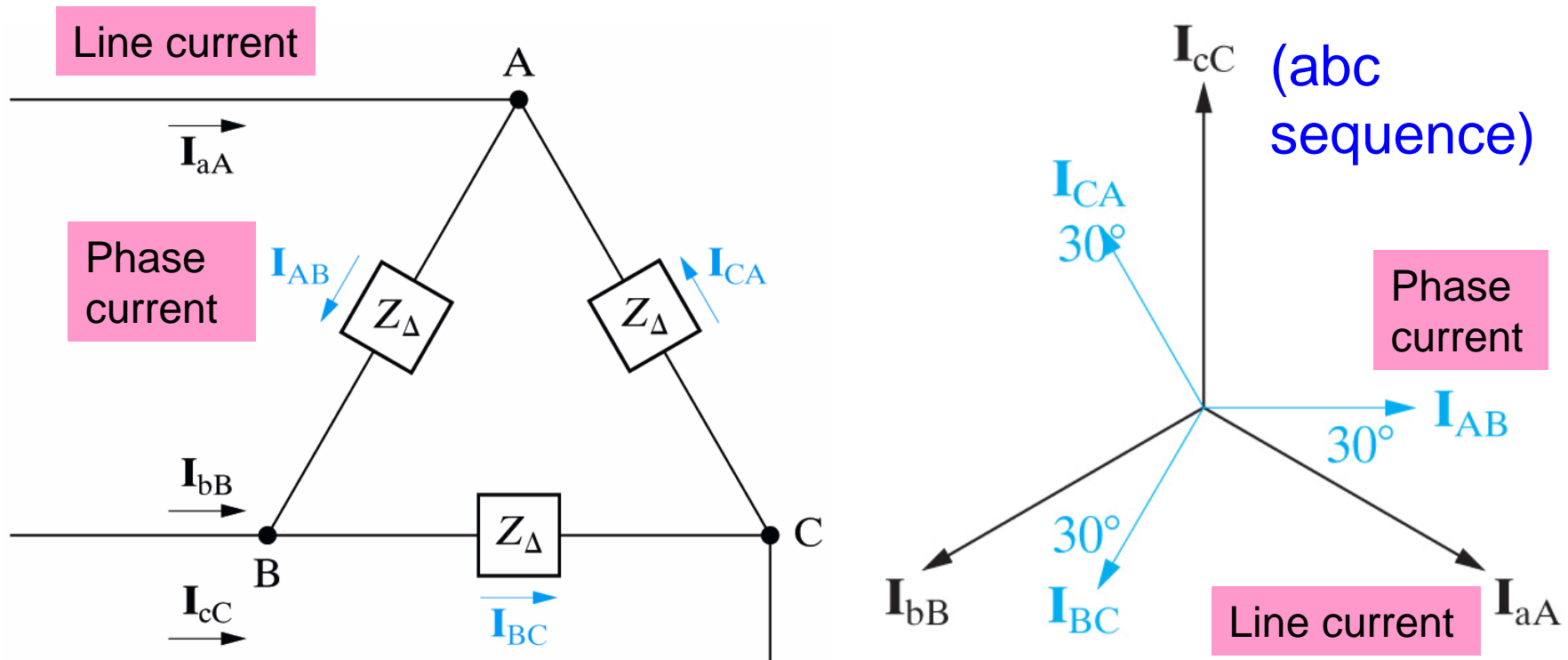

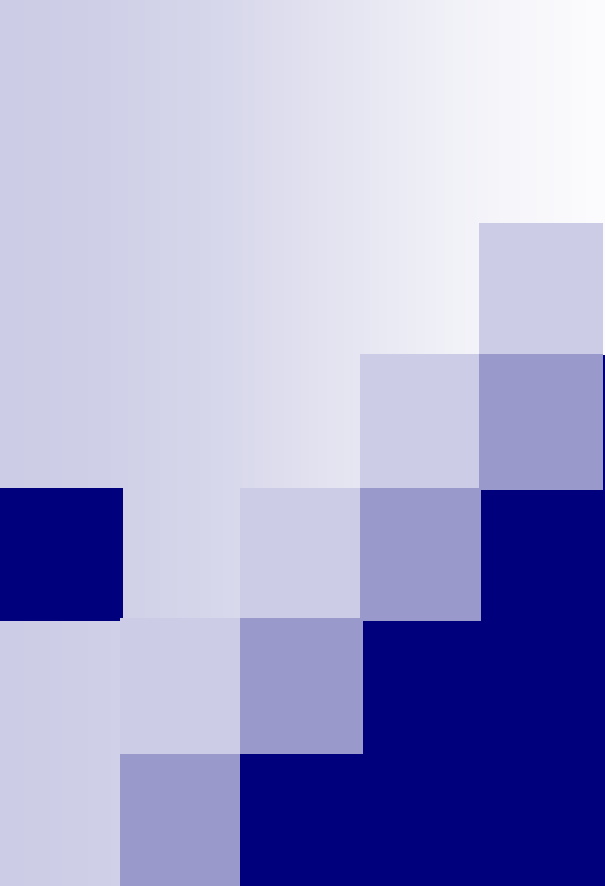

Section 11.5

Power Calculations in Balanced Three-Phase Circuits


1. Complex powers of one-phase and the entire Y-Load
2. The total instantaneous power

Average power of balanced Y-Load

- The average power delivered to Z_A is:

$$P_A = V_\phi I_\phi \cos \theta_\phi,$$

$$\begin{cases} V_\phi \equiv |\mathbf{V}_{AN}| = V_L / \sqrt{3}, \\ I_\phi \equiv |\mathbf{I}_{aA}| = I_L, \quad (\text{rms value}) \\ \theta_\phi \equiv \angle V_\phi - \angle I_\phi = \angle Z_A. \end{cases}$$

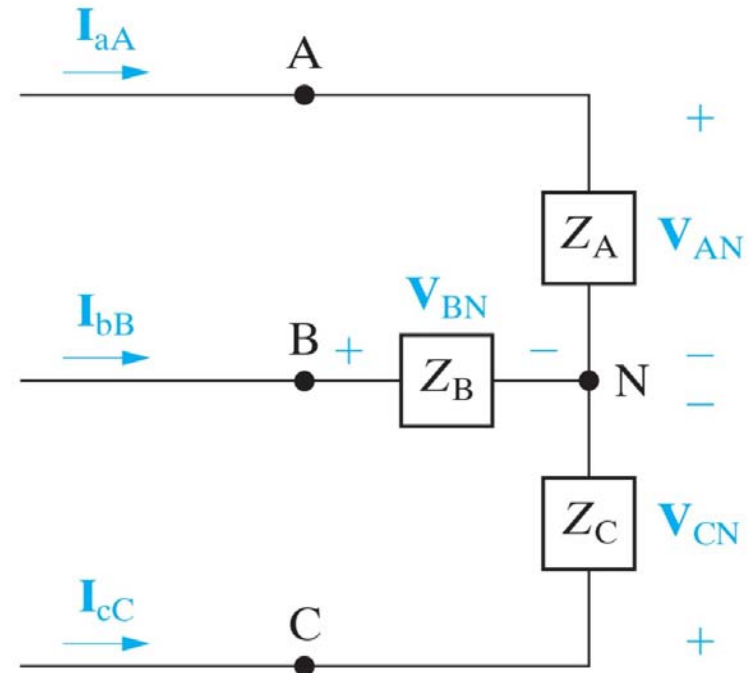

- The total power delivered to the Y-Load is:

$$P_{tot} = 3P_A = 3V_\phi I_\phi \cos \theta_\phi = \sqrt{3}V_L I_L \cos \theta_\phi.$$

Complex power of a balanced Y-Load

- The **reactive** powers of one phase and the entire Y-Load are:

$$\begin{cases} Q_{\phi} = V_{\phi} I_{\phi} \sin \theta_{\phi}, \\ Q_{tot} = 3V_{\phi} I_{\phi} \sin \theta_{\phi} = \sqrt{3} V_L I_L \sin \theta_{\phi}. \end{cases}$$


- The **complex** powers of one phase and the entire Y-Load are:

$$\begin{cases} S_{\phi} = P_{\phi} + jQ_{\phi} = V_{\phi} I_{\phi} e^{j\theta_{\phi}} = \mathbf{V}_{\phi} \mathbf{I}_{\phi}^*; \\ S_{tot} = 3S_{\phi} = 3V_{\phi} I_{\phi} e^{j\theta_{\phi}} = \sqrt{3} V_L I_L e^{j\theta_{\phi}}. \end{cases}$$

One-phase instantaneous powers

- The instantaneous power of load Z_A is:
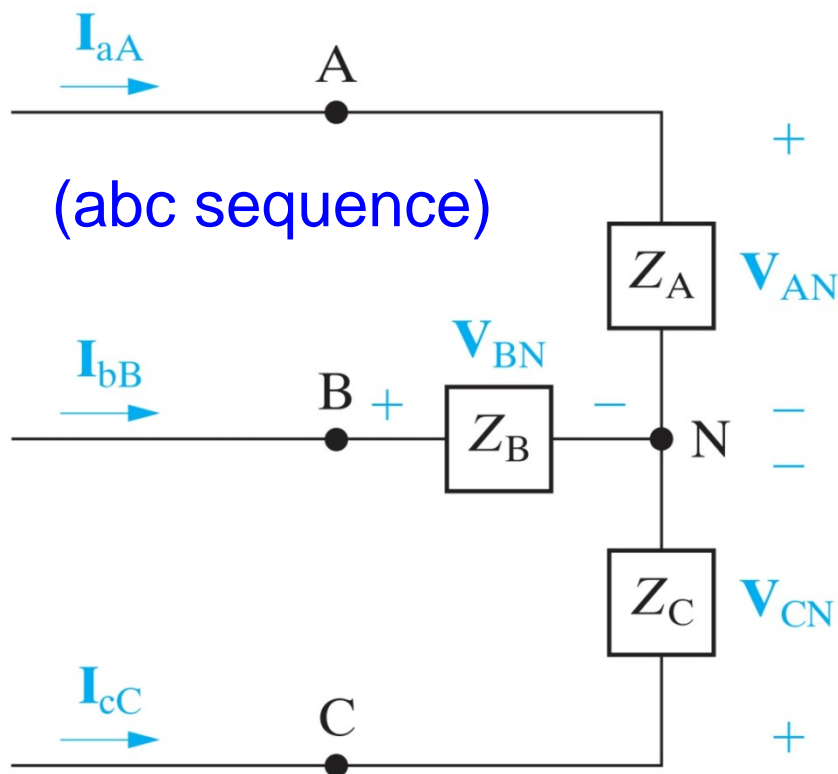
$$p_A(t) = v_{AN}(t)i_{aA}(t) = V_m I_m \cos \omega t \cos(\omega t - \theta_\phi).$$



- The instantaneous powers of Z_A , Z_C are:

$$\begin{aligned} p_B(t) &= v_{BN}(t)i_{bB}(t) \\ &= V_m I_m \cos(\omega t - 120^\circ) \\ &\quad \cos(\omega t - \theta_\phi - 120^\circ), \\ p_C(t) &= V_m I_m \cos(\omega t + 120^\circ) \\ &\quad \cos(\omega t - \theta_\phi + 120^\circ). \end{aligned}$$

Total instantaneous power


- The instantaneous power of the entire Y-Load is a constant **independent of time!**

$$\begin{aligned} p_{tot}(t) &= p_A(t) + p_B(t) + p_C(t) = 1.5V_m I_m \cos \theta_\phi \\ &= 1.5(\sqrt{2}V_\phi)(\sqrt{2}I_\phi) \cos \theta_\phi = 3V_\phi I_\phi \cos \theta_\phi. \end{aligned}$$

- The **torque** developed at the shaft of a 3-phase motor is **constant**, \Rightarrow less vibration in machinery powered by 3-phase motors.
- The torque required to empower a 3-phase generator is constant, \Rightarrow need steady input.

Example 11.5 (1)

- Q: What are the complex powers provided by the source and dissipated by the line of a-phase?
- The equivalent one-phase circuit in Y-Y configuration is:

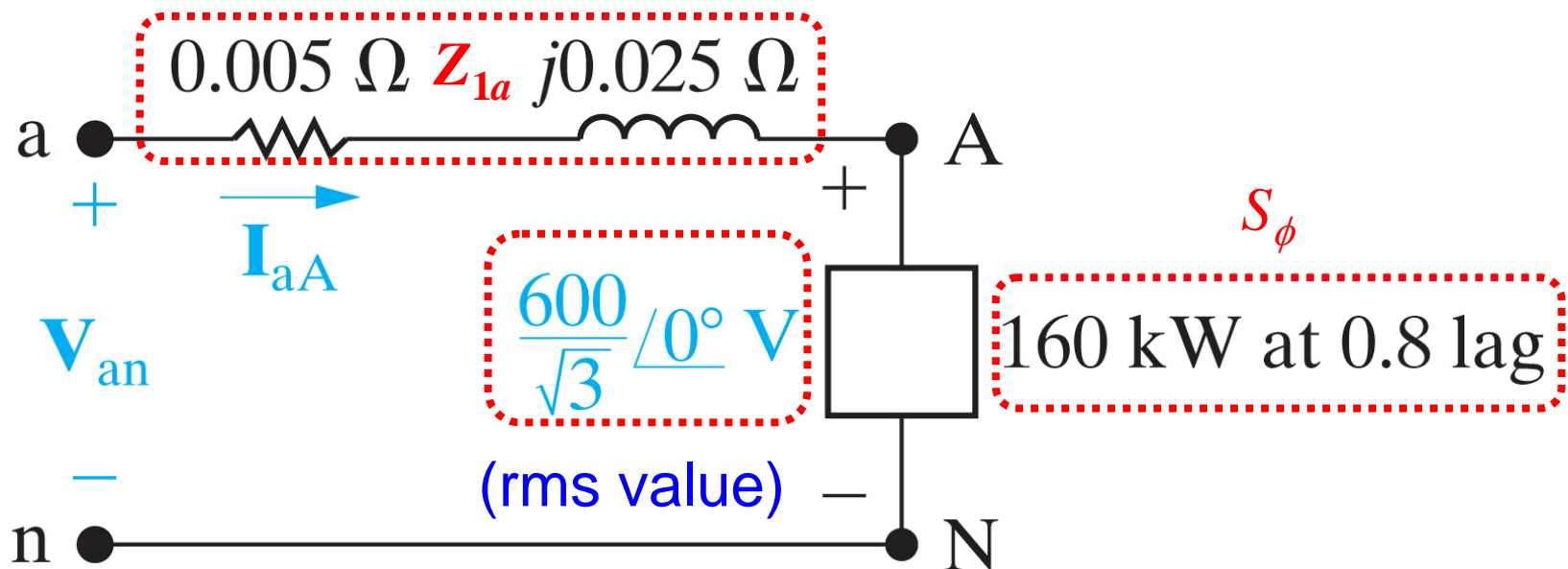

Example 11.5 (2)

- The line current of a-phase can be calculated by the complex power is:

$$S_{\phi} = \mathbf{V}_{\phi} \mathbf{I}_{\phi}^*, (160 + j120)10^3 = \frac{600}{\sqrt{3}} \mathbf{I}_{aA}^*,$$
$$\Rightarrow \mathbf{I}_{aA} = (577.35 \angle -36.87^{\circ}) \text{ A}.$$

- The a-phase voltage of the source is:

$$\begin{aligned} \mathbf{V}_{an} &= \mathbf{V}_{AN} + \mathbf{I}_{aA} \mathbf{Z}_{1a} \\ &= 600/\sqrt{3} + (577.35 \angle -36.87^{\circ})(0.005 + j0.025) \\ &= (357.51 \angle 1.57^{\circ}) \text{ V}. \end{aligned}$$

Example 11.5 (3)

- The complex power provided by the **source** of a-phase is:

$$\begin{aligned} S_{an} &= \mathbf{V}_{an} \mathbf{I}_{aA}^* = (357.51 \angle 1.57^\circ)(577.35 \angle 36.87^\circ) \\ &= (206.41 \angle 38.44^\circ) \text{ kVA}. \end{aligned}$$

- The complex power dissipated by the **line** of a-phase is:

$$\begin{aligned} S_{aA} &= |\mathbf{I}_{aA}|^2 Z_{1a} = (577.35)^2 (0.005 + j0.025) \\ &= (8.50 \angle 78.66^\circ) \text{ kVA}. \end{aligned}$$

Key points

- What is a three-phase circuit (source, line, load)?
- Why a balanced three-phase circuit can be analyzed by an **equivalent one-phase circuit**?
- How to get all the unknowns (e.g. line voltage of the load) by the result of one-phase circuit analysis?
- Why the **total instantaneous power** of a balanced three-phase circuit is a **constant**?