

# Chapter 13


## The Laplace Transform in Circuit Analysis

---

- 13.1      Circuit Elements in the  $s$  Domain
- 13.2-3    Circuit Analysis in the  $s$  Domain
- 13.4-5    The Transfer Function and Natural Response
- 13.6      The Transfer Function and the Convolution Integral
- 13.7      The Transfer Function and the Steady-State Sinusoidal Response
- 13.8      The Impulse Function in Circuit Analysis
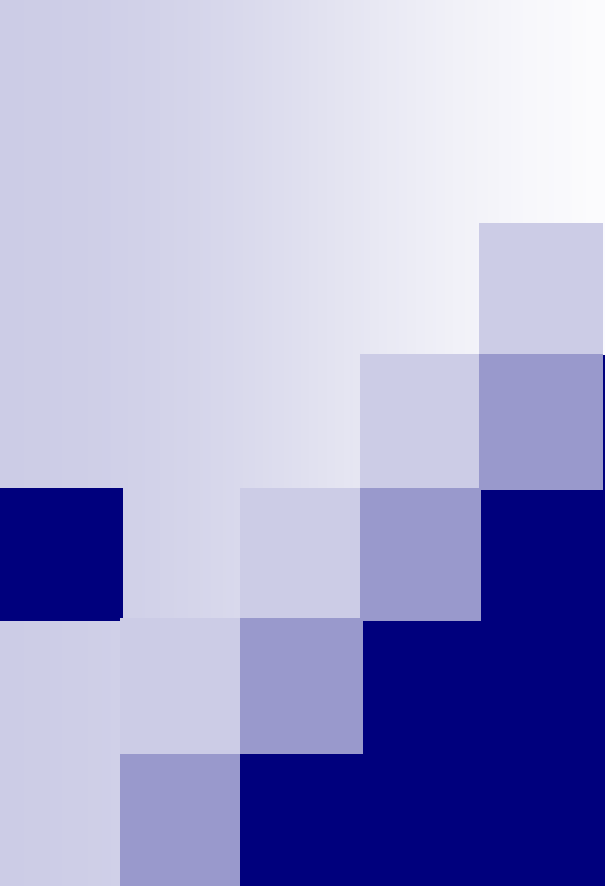
## Key points

- How to represent the **initial energy** of L, C in the s-domain?
- Why the **functional forms** of natural and steady-state responses are determined by the **poles** of transfer function  $H(s)$  and excitation source  $X(s)$ , respectively?
- Why the output of an LTI circuit is the **convolution** of the input and impulse response?  
How to interpret the **memory** of a circuit by convolution?



# Section 13.1

## Circuit Elements in the $s$ Domain

1. Equivalent elements of R, L, C

## A resistor in the s domain

- $iv$ -relation in the time domain

$$v(t) = R \cdot i(t).$$

- By operational Laplace transform:

$$\begin{aligned} L\{v(t)\} &= L\{R \cdot i(t)\} = R \cdot L\{i(t)\} , \\ \Rightarrow V(s) &= R \cdot I(s). \end{aligned}$$

- Physical units:  $V(s)$  in volt-seconds,  $I(s)$  in ampere-seconds.

## An inductor in the s domain

- $iv$ -relation in the time domain

$$v(t) = L \cdot \frac{d}{dt} i(t).$$

- By operational Laplace transform:


$$L\{v(t)\} = L\{L \cdot i'(t)\} = L \cdot L\{i'(t)\},$$

$$\Rightarrow V(s) = L \cdot [sI(s) - I_0] = sL \cdot I(s) - LI_0.$$

initial current


# Equivalent circuit of an inductor

■ Series equivalent:

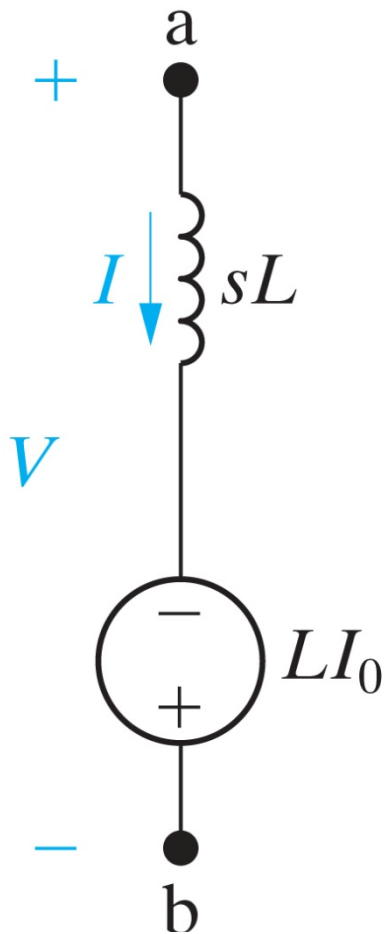

■ Parallel equivalent:

Thévenin →  
Norton

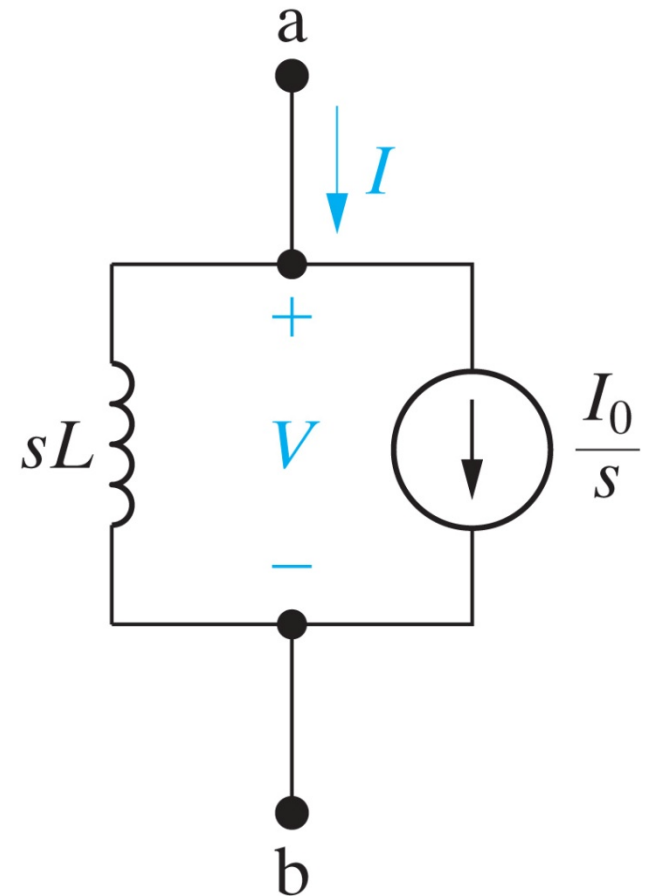

## A capacitor in the s domain

- $iv$ -relation in the time domain

$$i(t) = C \cdot \frac{d}{dt} v(t).$$

- By operational Laplace transform:


$$L\{i(t)\} = L\{C \cdot v'(t)\} = C \cdot L\{v'(t)\},$$

$$\Rightarrow I(s) = C \cdot [sV(s) - \overset{\circ}{V_0}] = sC \cdot V(s) - CV_0.$$

initial voltage

# Equivalent circuit of a capacitor


## ■ Parallel equivalent:

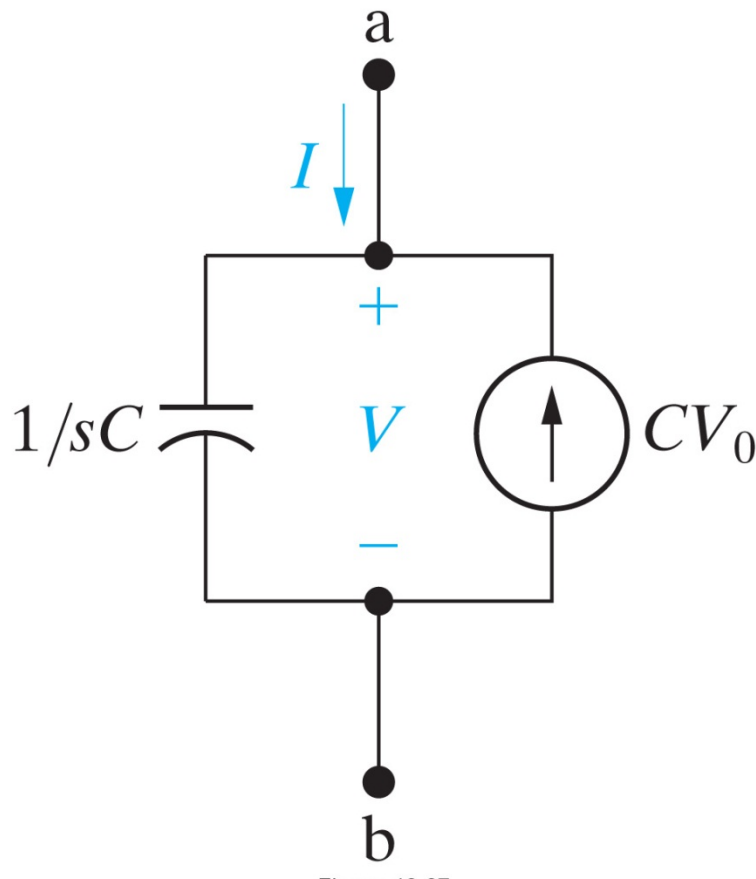


Norton  $\rightarrow$   
Thévenin



## ■ Series equivalent:

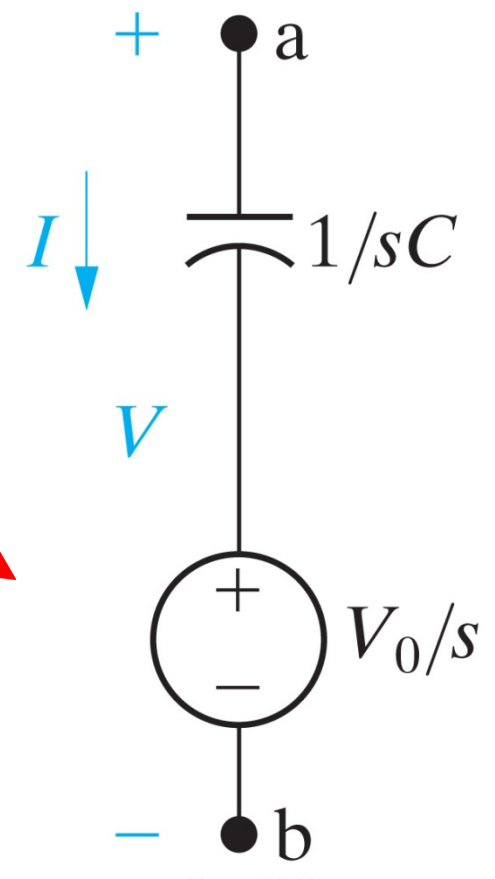



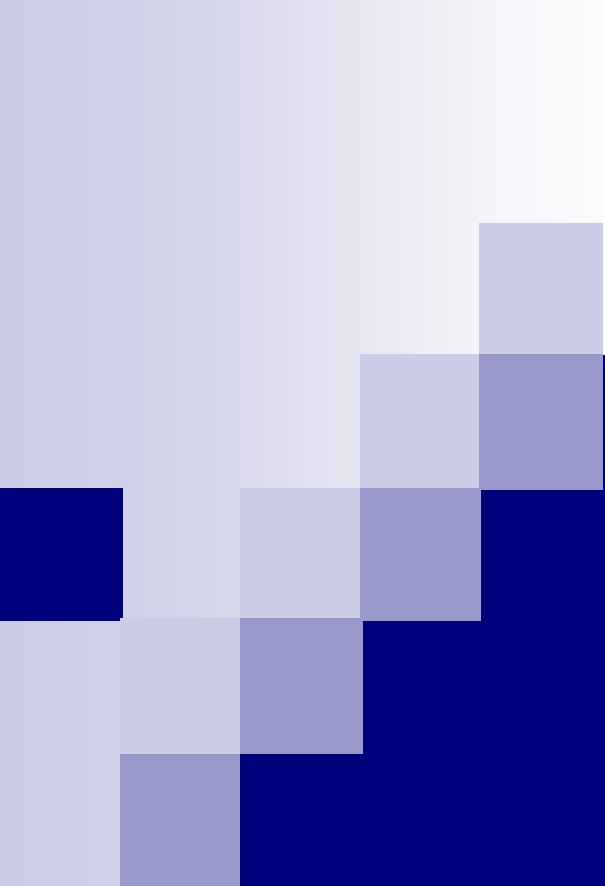

# Section 13.2, 13.3

## Circuit Analysis in the $s$ Domain

1. Procedures
2. Nature response of RC circuit
3. Step response of RLC circuit
4. Sinusoidal source
5. MCM
6. Superposition

## How to analyze a circuit in the s-domain?


1. Replacing each circuit element with its **s-domain equivalent**. The **initial energy** in L or C is taken into account by adding **independent source** in series or parallel with the element impedance.
2. Writing & solving **algebraic equations** by the same circuit analysis techniques developed for resistive networks.
3. Obtaining the t-domain solutions by **inverse Laplace transform**.

## Why to operate in the s-domain?

- It is convenient in solving **transient responses** of linear, lumped parameter circuits, for the initial conditions have been incorporated into the equivalent circuit.
- It is also useful for circuits with **multiple essential nodes and meshes**, for the simultaneous ODEs have been reduced to simultaneous algebraic equations.
- It can correctly predict the **impulsive response**, which is more difficult in the t-domain (Sec. 13.8).

# Nature response of an RC circuit (1)

- Q:  $i(t)$ ,  $v(t) = ?$

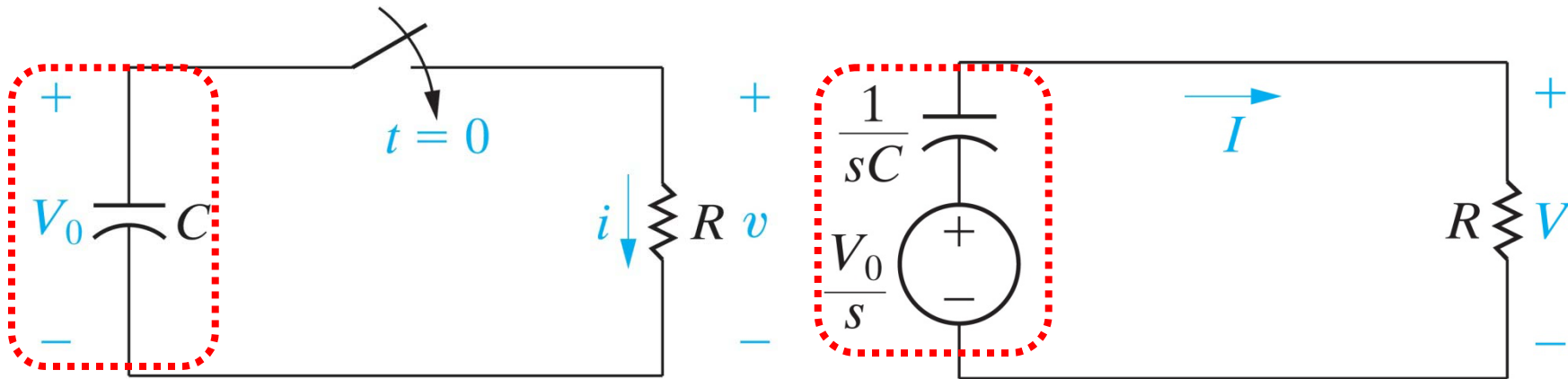

- Replacing the charged capacitor by a **Thévenin** equivalent circuit in the s-domain.
- KVL,  $\Rightarrow$  algebraic equation & solution of  $I(s)$ :

$$\frac{V_0}{s} = \frac{I}{sC} + IR, \Rightarrow I(s) = \frac{CV_0}{1 + RCs} = \frac{V_0/R}{s + (RC)^{-1}}.$$

## Nature response of an RC circuit (2)


- The t-domain solution is obtained by inverse Laplace transform:

$$\begin{aligned} i(t) &= L^{-1} \left\{ \frac{V_0/R}{s + (RC)^{-1}} \right\} = \frac{V_0}{R} e^{-t/(RC)} L^{-1} \left\{ \frac{1}{s} \right\} \\ &= \frac{V_0}{R} e^{-t/(RC)} u(t). \end{aligned}$$

- $i(0^+) = V_0/R$ , which is true for  $v_C(0^+) = v_C(0^-) = V_0$ .
- $i(\infty) = 0$ , which is true for capacitor becomes open (no loop current) in steady state.
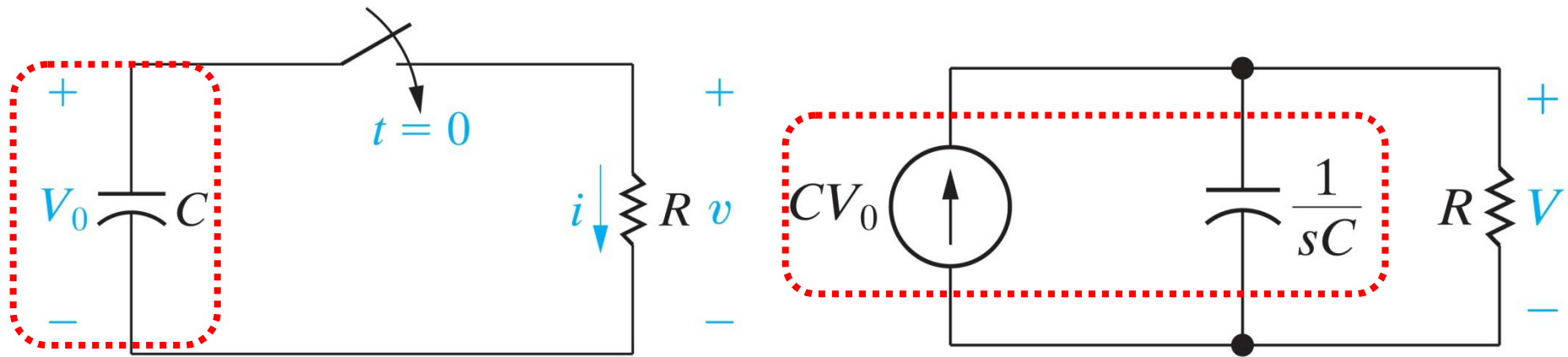
## Nature response of an RC circuit (3)

- To directly solve  $v(t)$ , replacing the charged capacitor by a **Norton** equivalent in the s-domain.





- Solve  $V(s)$ , perform inverse Laplace transform:

$$CV_0 = sCV + \frac{V}{R}, \Rightarrow V(s) = \frac{V_0}{s + (RC)^{-1}}.$$

$$\Rightarrow v(t) = L^{-1}\left\{V_0 / \left[s + (RC)^{-1}\right]\right\} = V_0 e^{-t/(RC)} u(t) = Ri(t).$$

# Step response of a parallel RLC (1)

- Q:  $i_L(t) = ?$

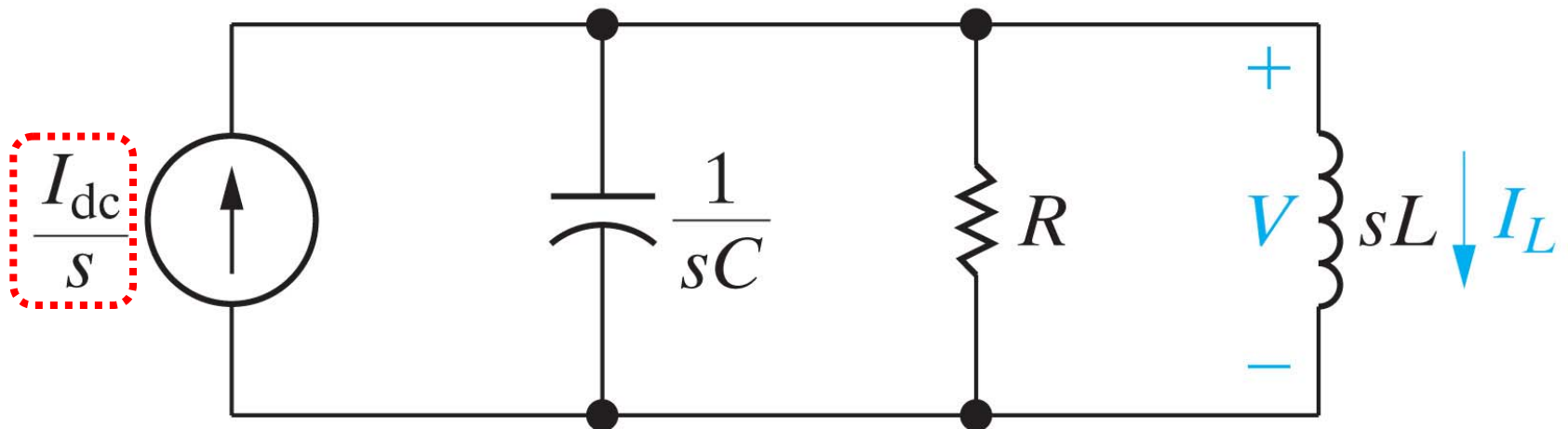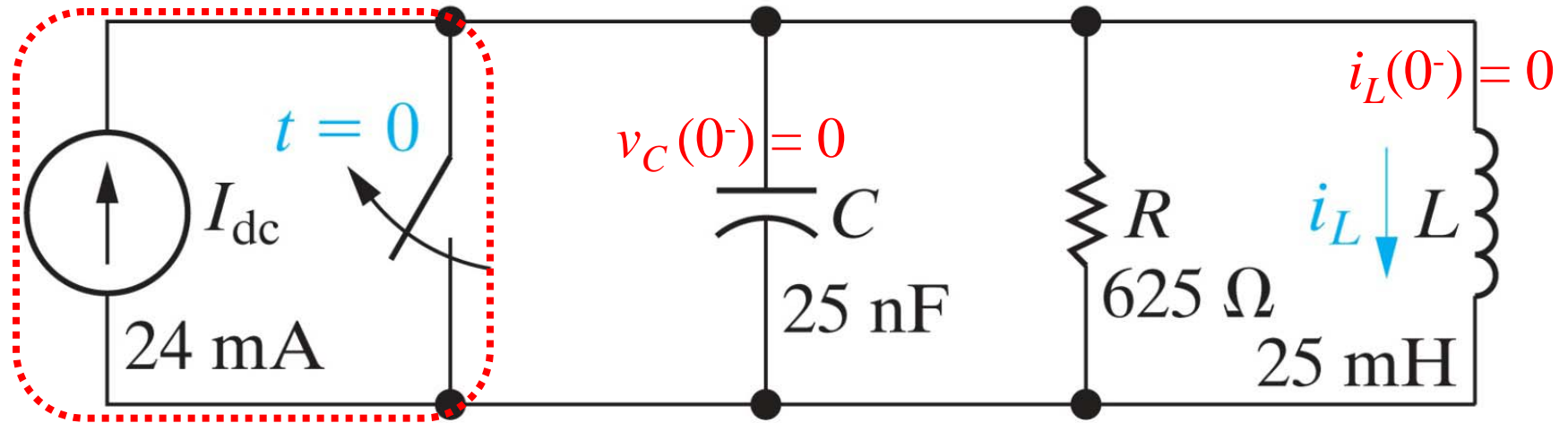

## Step response of a parallel RLC (2)

- KCL,  $\Rightarrow$  algebraic equation & solution of  $V(s)$ :

$$\frac{I_{dc}}{s} = sCV + \frac{V}{R} + \frac{V}{sL}, \Rightarrow V(s) = \frac{I_{dc}/C}{s^2 + (RC)^{-1}s + (LC)^{-1}}.$$

- Solve  $I_L(s)$ :

$$\begin{aligned} I_L(s) &= \frac{V(s)}{sL} = \frac{I_{dc}(LC)^{-1}}{s[s^2 + (RC)^{-1}s + (LC)^{-1}]} \\ &= \frac{3.84 \times 10^7}{s[s^2 + (6.4 \times 10^4)s + (1.6 \times 10^9)]}. \end{aligned}$$



## Step response of a parallel RLC (3)

- Perform partial fraction expansion and inverse Laplace transform:

$$I_L(s) = \frac{24}{s} + \frac{20\angle 127^\circ}{s - (-32k + j24k)} + \frac{20\angle -127^\circ}{s - (-32k - j24k)} \text{ (mA} \cdot \text{s)}.$$

$$\begin{aligned} i_L(t) &= 24u(t) + \left[ 20e^{j127^\circ} e^{-(32k)t} e^{j(24k)t} u(t) + c.c. \right] \\ &= \left\{ 24 + 40e^{-(32k)t} \cos[(24k)t + 127^\circ] \right\} u(t) \text{ (mA)} \\ &= \left\{ 24 - e^{-(32k)t} [24\cos(24k)t - 32\sin(24k)t] \right\} u(t) \text{ (mA)}. \end{aligned}$$

## Transient response due to a sinusoidal source (1)

- For a parallel RLC circuit, replace the current source by a sinusoidal one:  $i_g(t) = I_m \cos \omega t \cdot u(t)$ .

The algebraic equation changes:

$$sCV + \frac{V}{R} + \frac{V}{sL} = I_g = \frac{sI_m}{s^2 + \omega^2},$$

$$\Rightarrow V(s) = \frac{(I_m/C)s^2}{(s^2 + \omega^2)[s^2 + (RC)^{-1}s + (LC)^{-1}]},$$

$$\Rightarrow I_L(s) = \frac{V}{sL} = \frac{I_m(LC)^{-1}s}{(s^2 + \omega^2)[s^2 + (RC)^{-1}s + (LC)^{-1}]}.$$

## Transient response due to a sinusoidal source (2)

- Perform partial fraction expansion and inverse Laplace transform:

$$I_L(s) = \frac{K_1}{s - j\omega} + \frac{K_1^*}{s + j\omega} + \frac{K_2}{s - (-\alpha + j\beta)} + \frac{K_2^*}{s - (-\alpha - j\beta)}.$$



DrivingNeperDamped  
frequencyfrequencyfrequency

$$i_L(t) = \left\{ \underline{2|K_1|\cos(\omega t + \angle K_1)} + \underline{2|K_2|e^{-\alpha t}\cos(\beta t + \angle K_2)} \right\} u(t).$$

Steady-stateNatural response (RLC  
response (source)parameters)

## Step response of a 2-mesh circuit (1)

- Q:  $i_1(t), i_2(t) = ?$

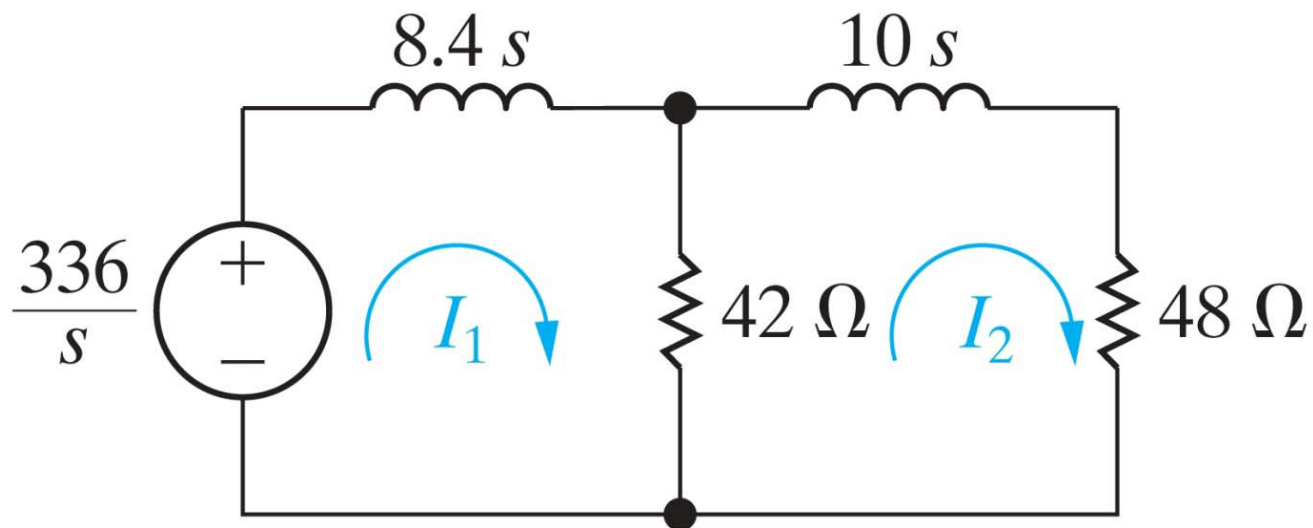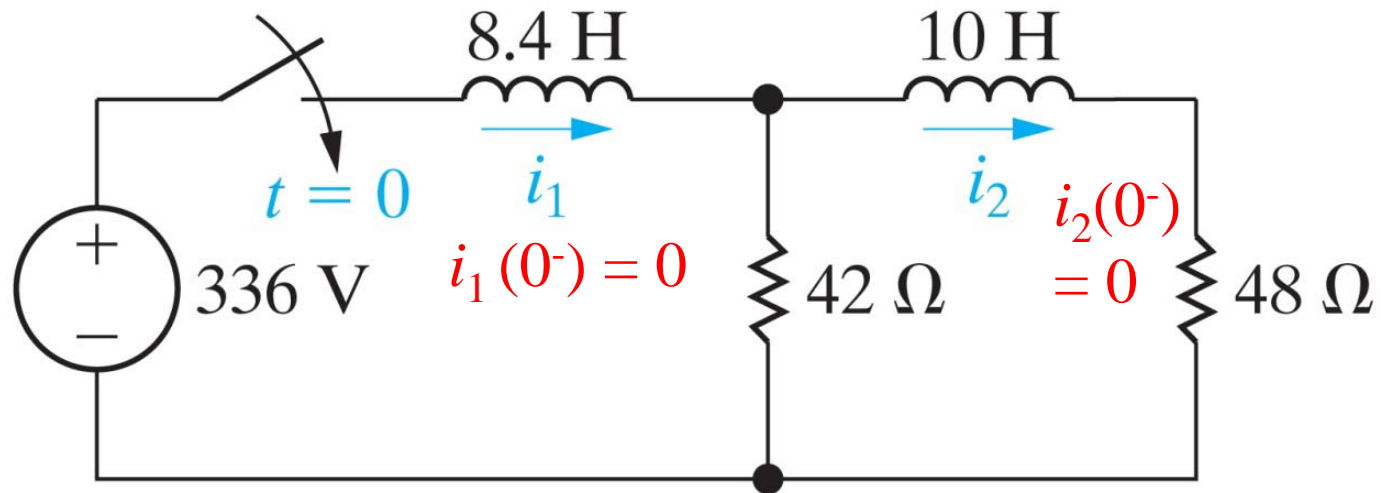

## Step response of a 2-mesh circuit (2)

- MCM,  $\Rightarrow$  2 algebraic equations & solutions:


$$\begin{cases} 8.4sI_1 + 42(I_1 - I_2) = \frac{336}{s} \dots (1) \\ 42(I_2 - I_1) + (10s + 48)I_2 = 0 \dots (2) \end{cases}$$

$$\Rightarrow \begin{bmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{bmatrix} \times \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 336/s \\ 0 \end{bmatrix}.$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{bmatrix}^{-1} \times \begin{bmatrix} 336/s \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{15}{s} - \frac{14}{s+2} - \frac{1}{s+12} \\ \frac{7}{s} - \frac{8.4}{s+2} + \frac{1.4}{s+12} \end{bmatrix}.$$


## Step response of a 2-mesh circuit (3)

- Perform inverse Laplace transform:

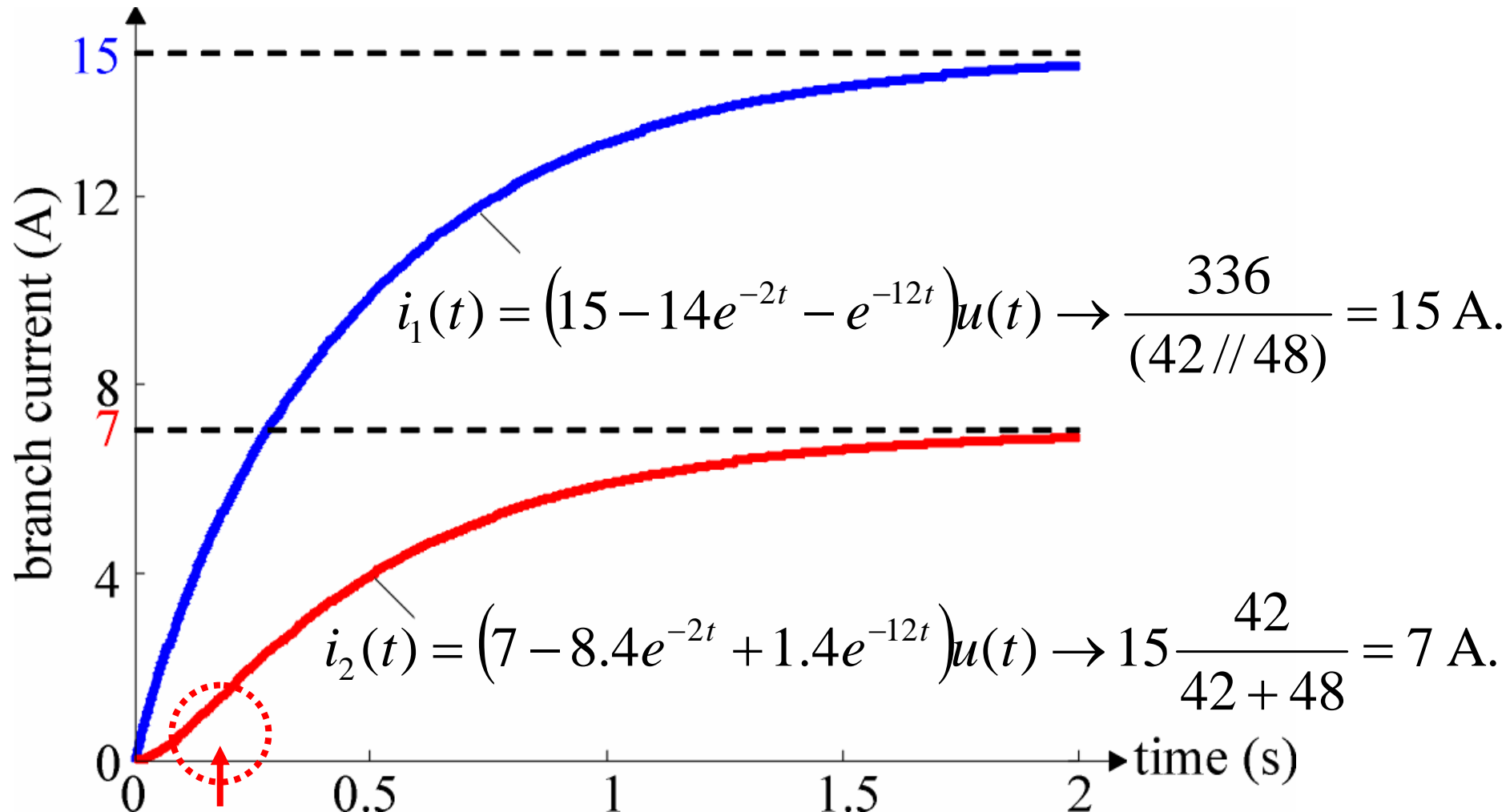

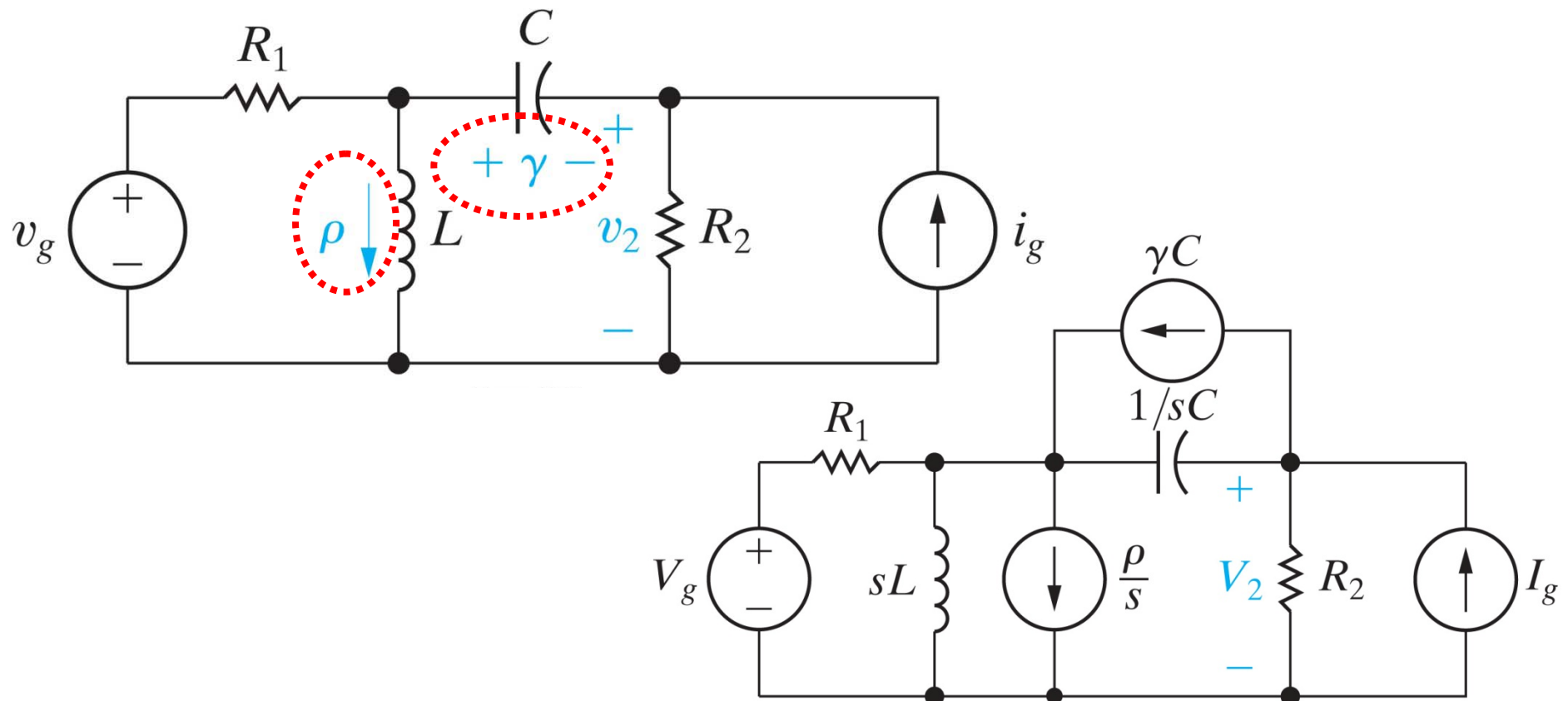
## Use of superposition (1)

- Given 2 independent sources  $v_g$ ,  $i_g$  and initially charged C, L,  $\Rightarrow v_2(t) = ?$


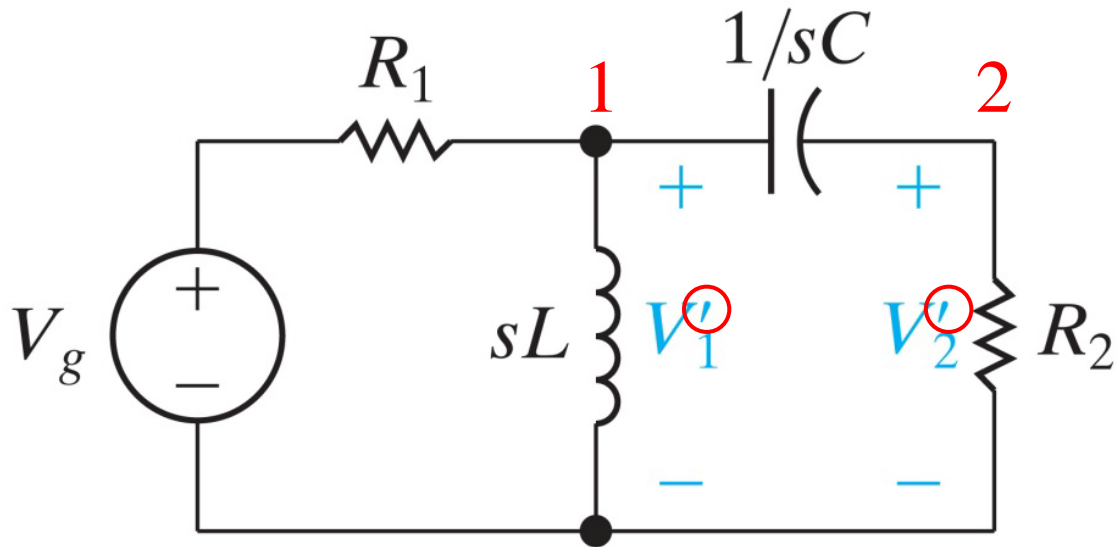
## Use of superposition: $V_g$ acts alone (2)



$$\left\{ \begin{array}{l} \frac{V'_1 - V_g}{R_1} + \frac{V'_1}{sL} + \frac{V'_1 - V'_2}{(sC)^{-1}} = 0, \\ \frac{V'_2 - V'_1}{(sC)^{-1}} + \frac{V'_2}{R_2} = 0. \end{array} \right. \Rightarrow \left\{ \begin{array}{l} \left( \frac{1}{R_1} + \frac{1}{sL} + sC \right) V'_1 - sC V'_2 = \frac{V_g}{R_1}, \\ -sC V'_1 + \left( \frac{1}{R_2} + sC \right) V'_2 = 0. \end{array} \right.$$



## Use of superposition (3)


- For convenience, define admittance matrix:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{sL} + sC & -sC \\ -sC & \frac{1}{R_2} + sC \end{bmatrix} \times \begin{bmatrix} V_1' \\ V_2' \end{bmatrix}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{bmatrix} \times \begin{bmatrix} V_1' \\ V_2' \end{bmatrix} = \begin{bmatrix} V_g/R_1 \\ 0 \end{bmatrix}.$$

$$\Rightarrow V_2' = \frac{-Y_{12}/R_1}{Y_{11}Y_{22} - Y_{12}^2} V_g.$$
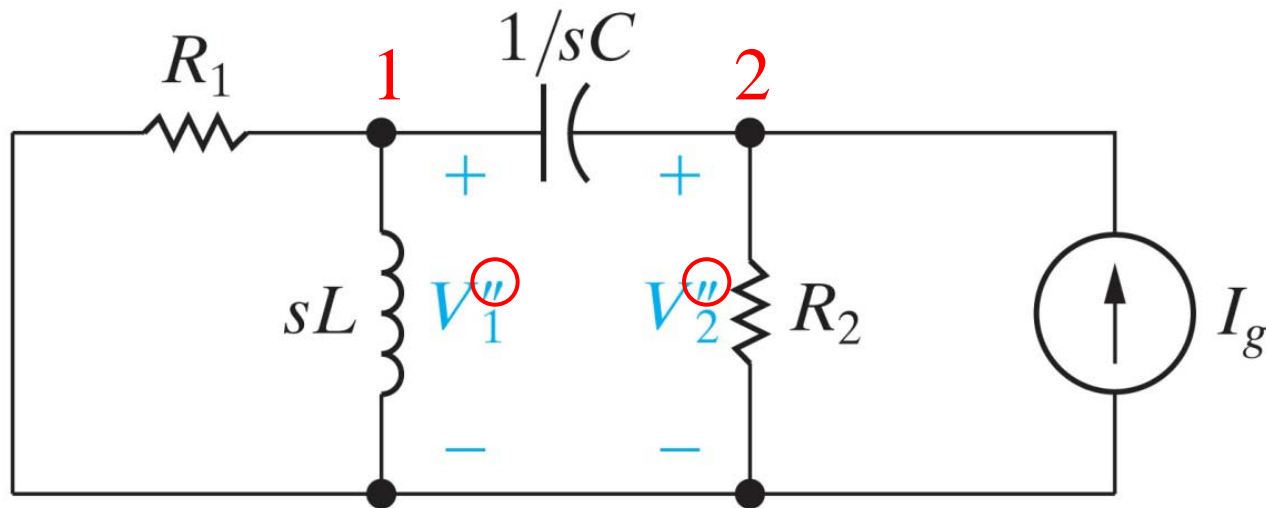
## Use of superposition: $I_g$ acts alone (4)




$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{bmatrix} \times \begin{bmatrix} V_1'' \\ V_2'' \end{bmatrix} = \begin{bmatrix} 0 \\ I_g \end{bmatrix}, \Rightarrow V_2'' = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{12}^2} I_g$$

Same matrix

Same denominator
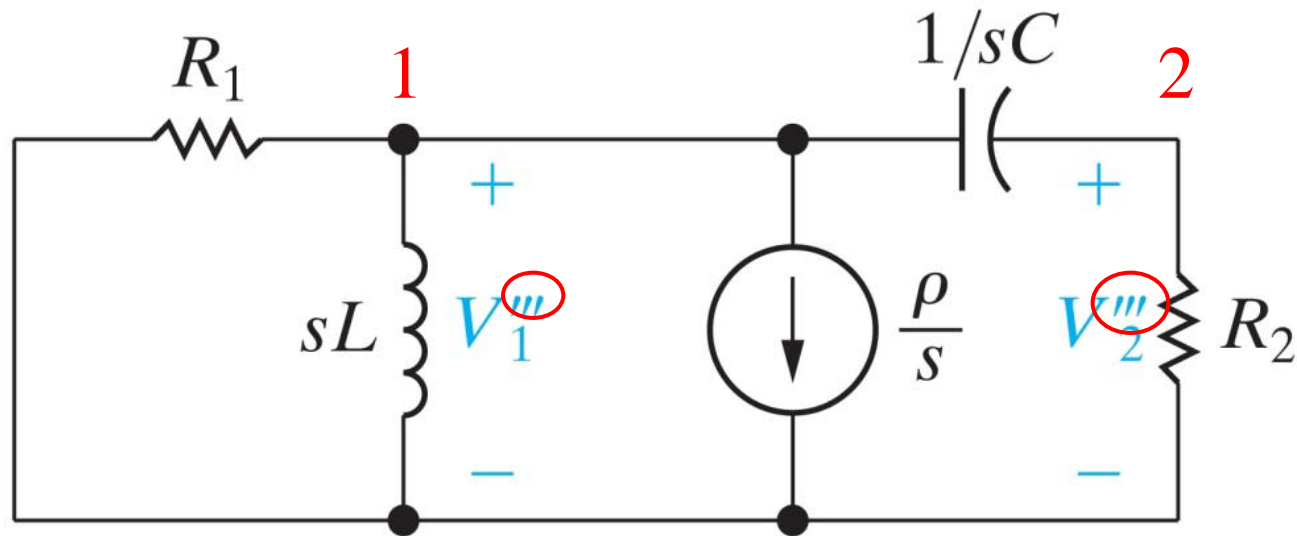
## Use of superposition: Energized L acts alone (5)




$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{bmatrix} \times \begin{bmatrix} V_1''' \\ V_2''' \end{bmatrix} = \begin{bmatrix} -\rho/s \\ 0 \end{bmatrix}, \Rightarrow V_2''' = \frac{Y_{12}/s}{Y_{11}Y_{22} - Y_{12}^2} \rho$$

Same matrix

Same denominator

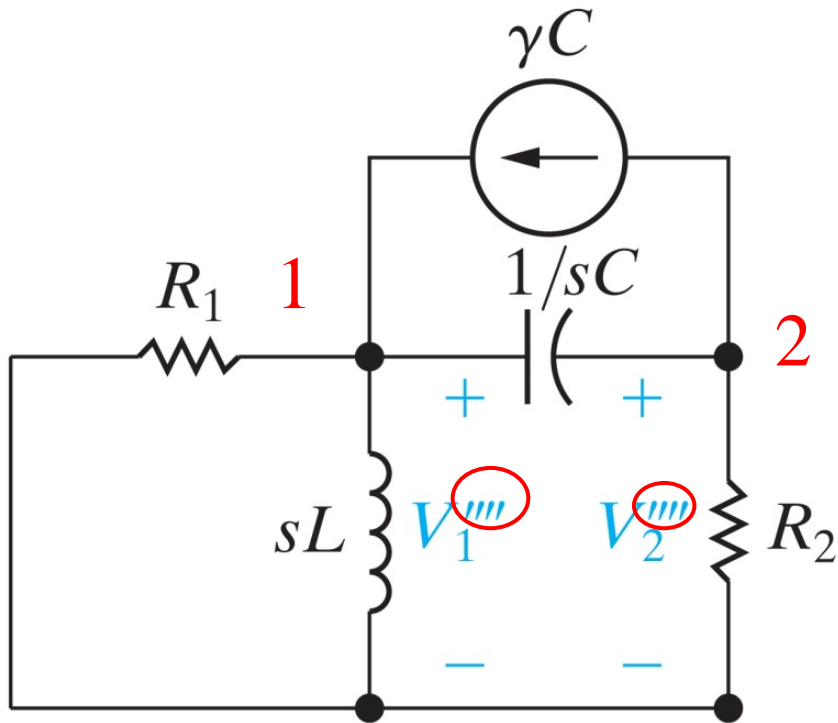
## Use of superposition: Energized C acts alone (6)



$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{bmatrix} \times \begin{bmatrix} V_1'''' \\ V_2'''' \end{bmatrix} = \begin{bmatrix} \gamma C \\ -\gamma C \end{bmatrix},$$

$$\Rightarrow V_2'''' = \frac{-(Y_{11} + Y_{12})C}{Y_{11}Y_{22} - Y_{12}^2} \gamma.$$

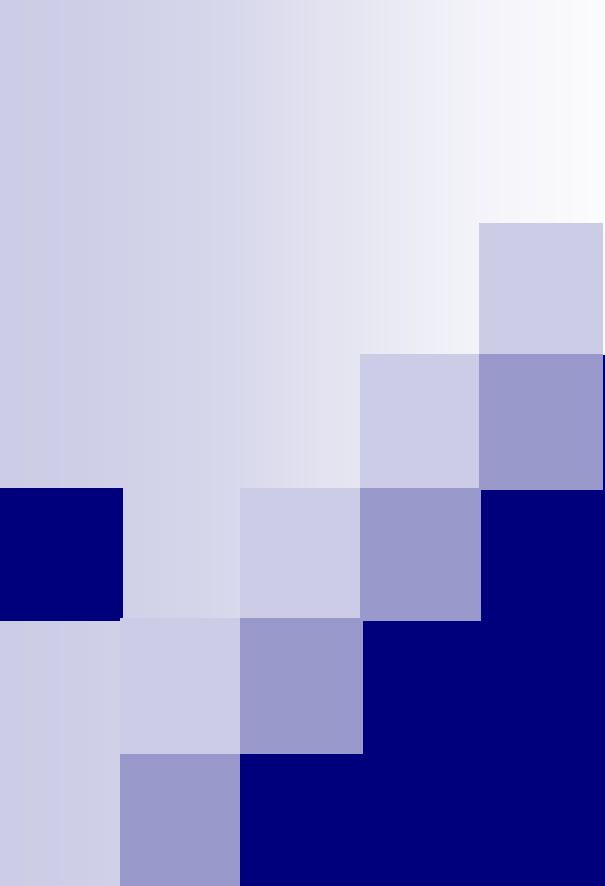- The total voltage is:  $V_2 = V_2' + V_2'' + V_2''' + V_2''''$ .



# Section 13.4, 13.5 The Transfer Function and Natural Response

## What is the transfer function of a circuit?


- The **ratio** of a circuit's output to its input in the s-domain:

$$H(s) = \frac{Y(s)}{X(s)}$$


- A single circuit may have many transfer functions, each corresponds to some specific choices of input and output.
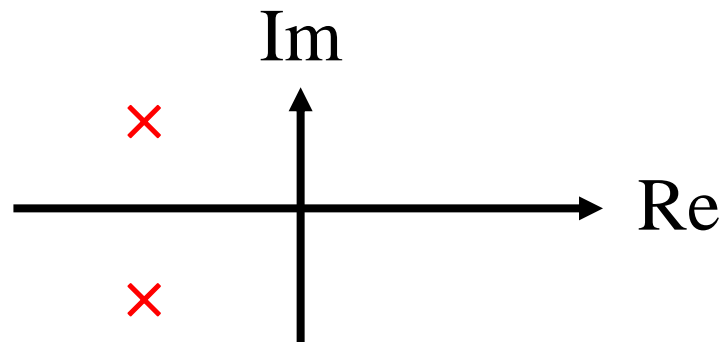
## Poles and zeros of transfer function

- For linear and lumped-parameter circuits,  $H(s)$  is always a **rational** function of  $s$ .
- Poles and zeros always appear in complex conjugate pairs.
- The **poles** must lie in the **left half** of the  $s$ -plane if bounded input leads to bounded output.



## Example: Series RLC circuit

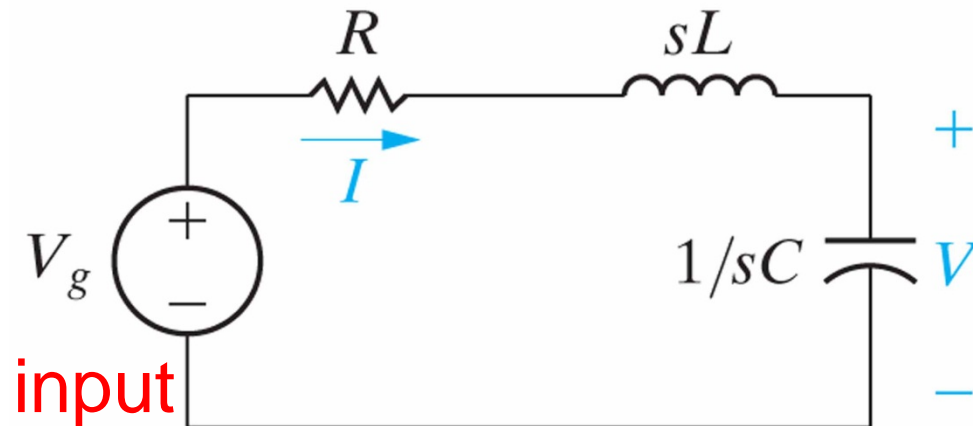

- If the output is the loop current  $I$ :

$$H(s) = \frac{I}{V_g} = \frac{1}{R + sL + (sC)^{-1}} = \frac{sC}{s^2 LC + sRC + 1}.$$

- If the output is the capacitor voltage  $V$ :

$$H(s) = \frac{V}{V_g} = \frac{(sC)^{-1}}{R + sL + (sC)^{-1}} = \frac{1}{s^2 LC + sRC + 1}.$$





## How do poles, zeros influence the solution?

- Since  $Y(s) = H(s)X(s)$ ,  $\Rightarrow$  the partial fraction expansion of the output  $Y(s)$  yields a term  $K/(s-a)$  for each pole  $s=a$  of  $H(s)$  or  $X(s)$ .
- The functional forms of the **transient** (natural) and **steady-state** responses  $y_{tr}(t)$  and  $y_{ss}(t)$  are determined by the poles of  **$H(s)$**  and  **$X(s)$** , respectively.
- The partial fraction coefficients of  $Y_{tr}(s)$  and  $Y_{ss}(s)$  are determined by **both**  $H(s)$  and  $X(s)$ .

## Example 13.2: Linear ramp excitation (1)

- Q:  $v_o(t) = ?$

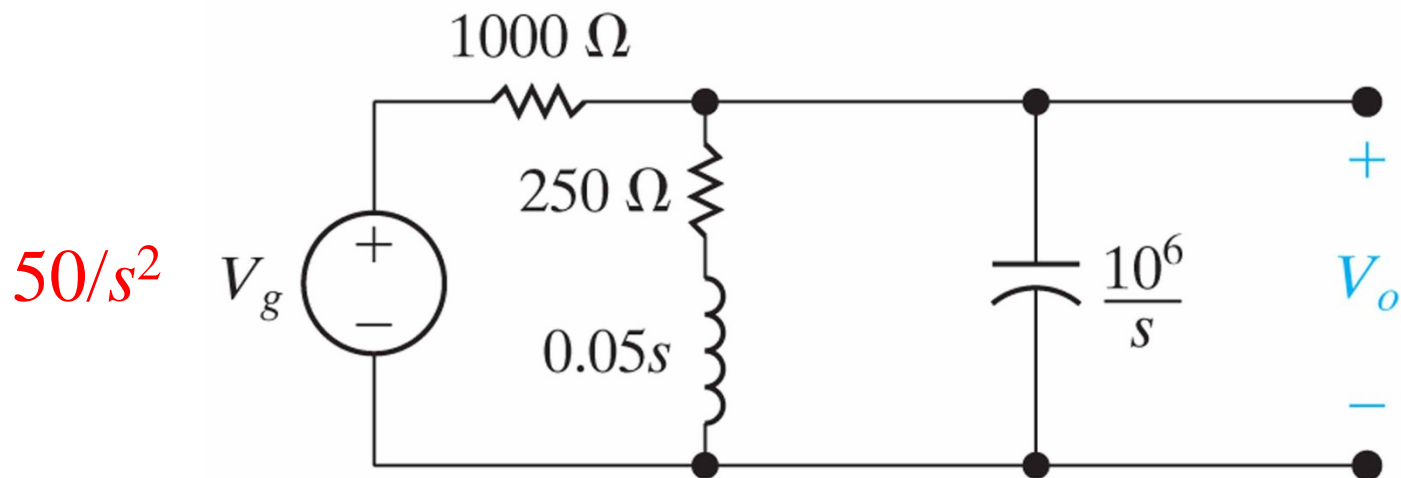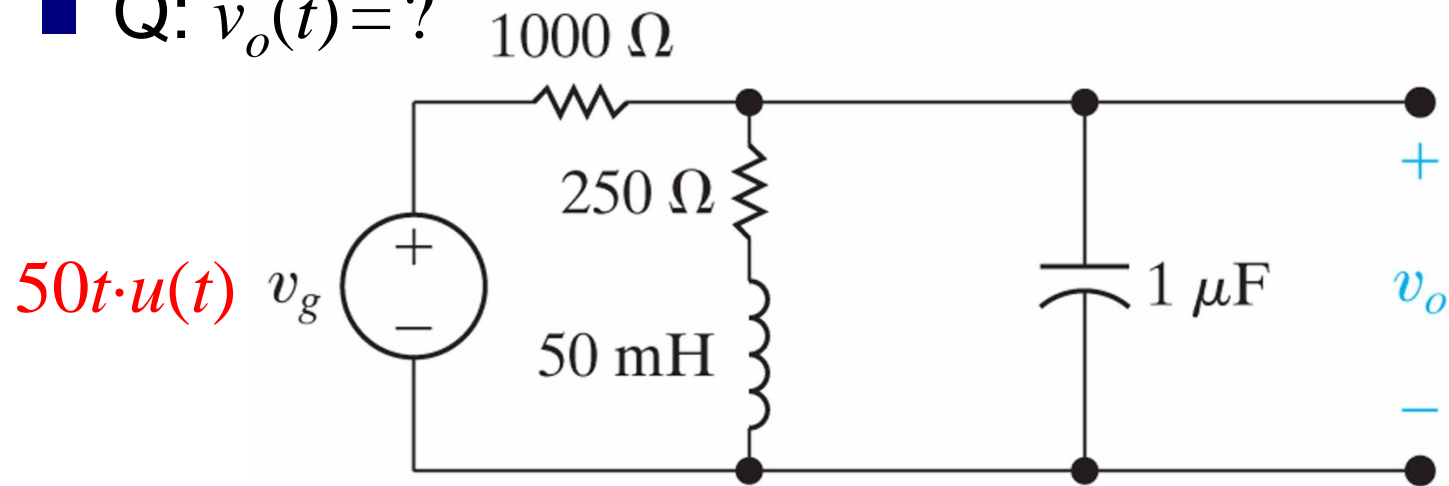

## Example 13.2 (2)

- Only one essential node,  $\Rightarrow$  use NVM:

$$\frac{V_o - V_g}{1000} + \frac{V_o}{250 + 0.05s} + \frac{V_o}{10^6/s} = 0,$$

$$\Rightarrow H(s) = \frac{V_o}{V_g} = \frac{1000(s + 5000)}{s^2 + 6000s + (2.5 \times 10^7)}.$$

- $H(s)$  has 2 complex conjugate poles:

$$s = -3000 \pm j4000.$$

- $V_g(s) = 50/s^2$  has 1 repeated real pole:  $s = 0^{(2)}$ .

## Example 13.2 (3)

- The total response in the s-domain is:

$$V_o(s) = H(s)V_g(s) = \frac{5 \times 10^4 (s + 5000)}{s^2 (s^2 + 6000s + 2.5 \times 10^7)} = Y_{tr} + Y_{ss}$$

expansion coefficients depend on  $H(s)$  &  $V_g(s)$


$$= \frac{5\sqrt{5} \times 10^{-4} \angle 80^\circ}{s + 3000 - j4000} + \frac{5\sqrt{5} \times 10^{-4} \angle -80^\circ}{s + 3000 + j4000} + \frac{10}{s^2} - \frac{4 \times 10^{-4}}{s}$$

poles of  $H(s)$ :  $-3k \pm j4k$       pole of  $V_g(s)$ :  $0^{(2)}$

- The total response in the t-domain:

$$v_o(t) = y_{tr} + y_{ss} = \left[ \sqrt{5} \times 10^{-3} e^{-3,000t} \cos(4,000t + 80^\circ) \right] u(t) + (10t - 4 \times 10^{-4}) u(t).$$

## Example 13.2 (4)

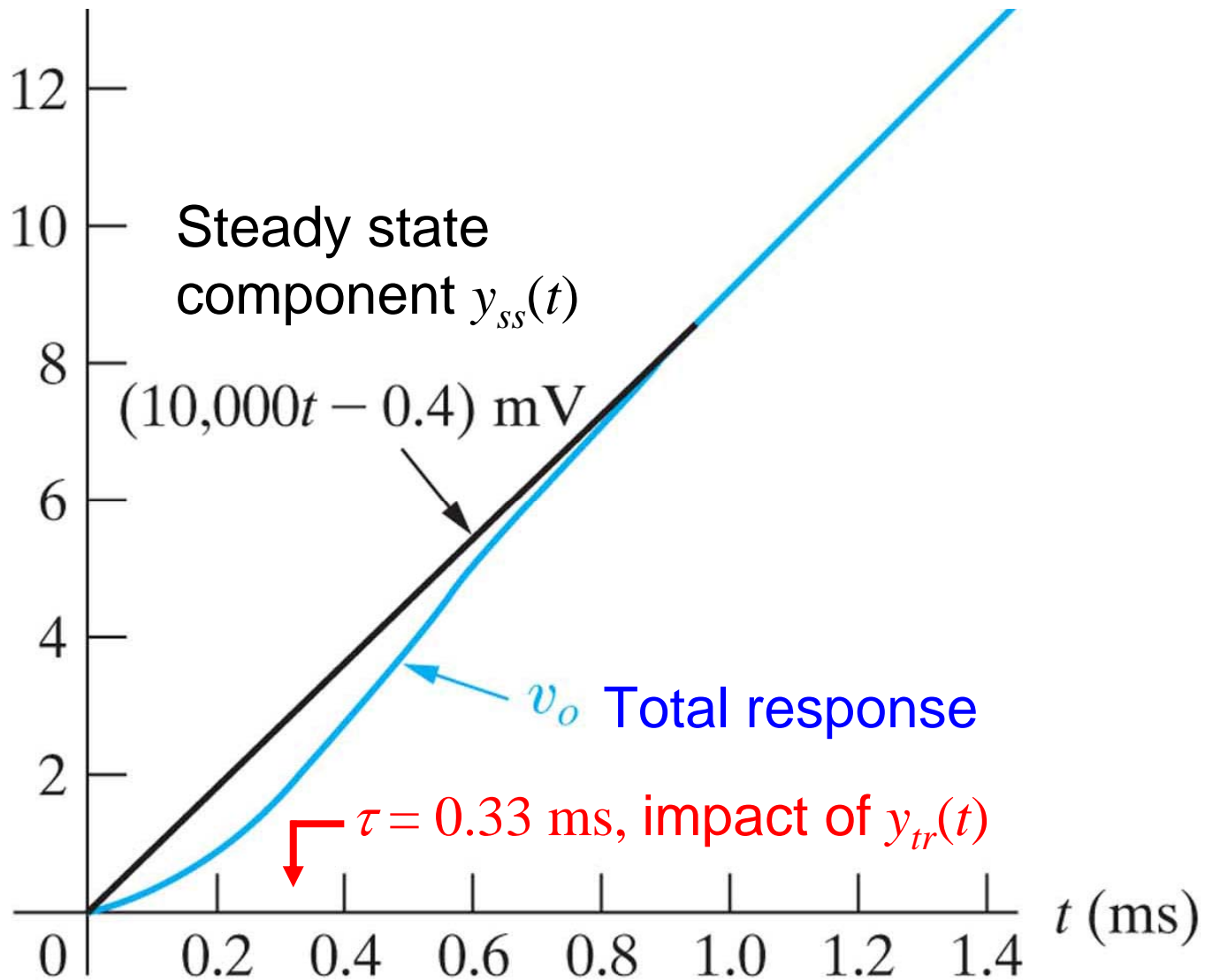



## Section 13.6

# The Transfer Function and the Convolution Integral

1. Impulse response
2. Time invariant
3. Convolution integral
4. Memory of circuit

## Impulse response

- If the input to a linear, lumped-parameter circuit is an impulse  $\delta(t)$ , the output function  $h(t)$  is called impulse response, which happens to be the natural response of the circuit:

$$X(s) = L\{\delta(t)\} = 1, \quad Y(s) = H(s) \times 1 = H(s),$$
$$y(t) = L^{-1}\{Y(s)\} = L^{-1}\{H(s)\} = h(t).$$

- The application of an impulse source is equivalent to **suddenly storing energy** in the circuit. The subsequent release of this energy gives rise to the natural response.

## Time invariant

- For a linear, lumped-parameter circuit, delaying the input  $x(t)$  by  $\tau$  simply delays the response  $y(t)$  by  $\tau$  as well (time invariant):

$$X(s, \tau) = L\{x(t - \tau)u(t - \tau)\} = e^{-\tau s} X(s),$$


$$Y(s, \tau) = H(s)X(s, \tau) = e^{-\tau s} H(s)X(s) = e^{-\tau s} Y(s),$$

$$\begin{aligned} y(t, \tau) &= L^{-1}\{Y(s, \tau)\} = L^{-1}\{Y(s)\} \Big|_{t \rightarrow t - \tau} \\ &= y(t - \tau)u(t - \tau). \end{aligned}$$



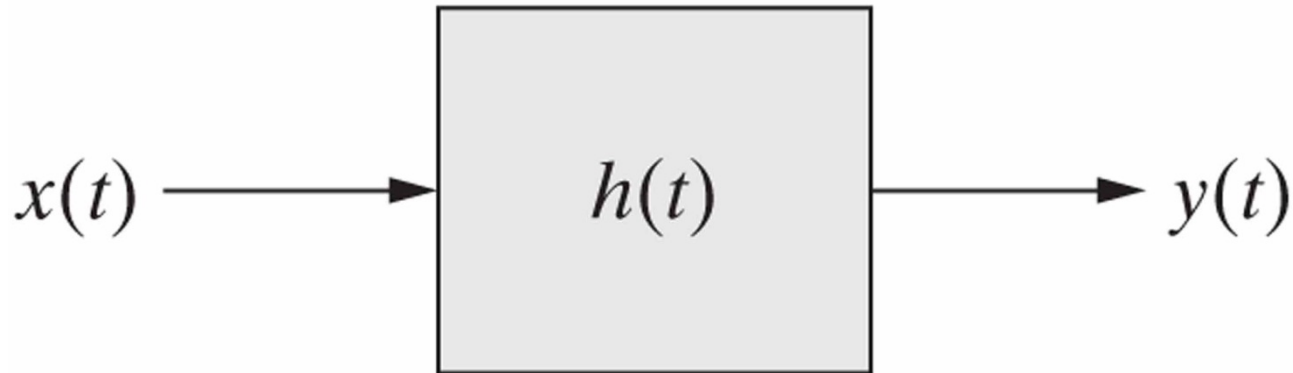
## Motivation of working in the time domain

- The properties of impulse response and time-invariance allow one to calculate the output function  $y(t)$  of a “**linear and time invariant (LTI)**” circuit in the t-domain only.
- This is beneficial when  $x(t)$ ,  $h(t)$  are known only through experimental data.



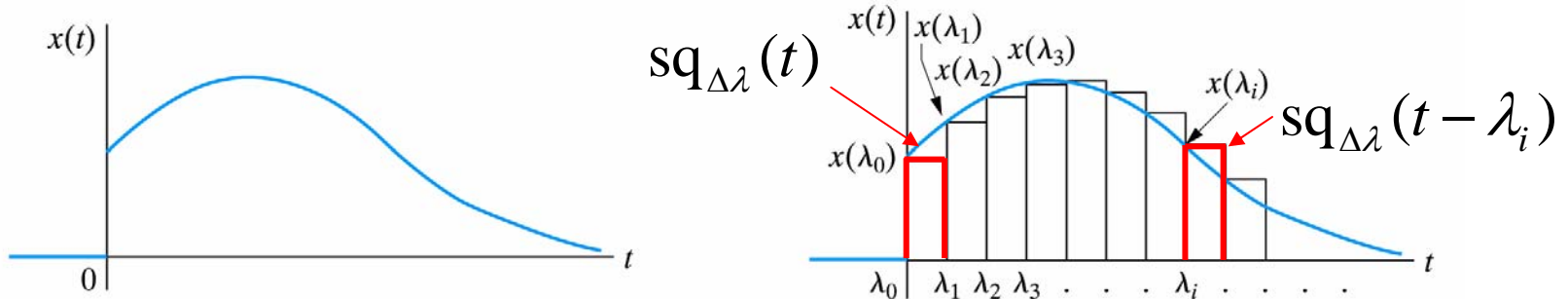
# Decompose the input source $x(t)$

- We can approximate  $x(t)$  by a series of rectangular pulses  $\text{rec}_{\Delta\lambda}(t-\lambda_i)$  of uniform width  $\Delta\lambda$ :



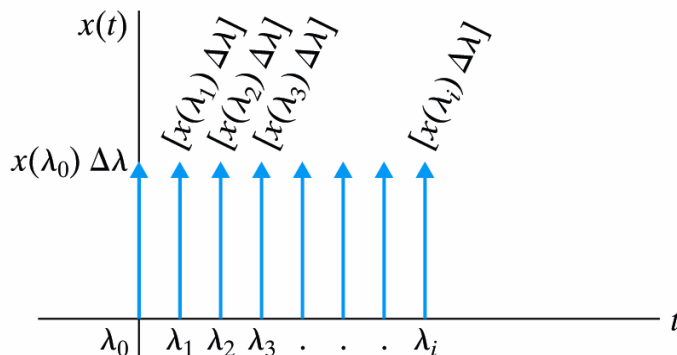- By having  $\Delta\lambda \rightarrow 0$ ,  $\Rightarrow \text{rec}_{\Delta\lambda}(t-\lambda_i)/\Delta\lambda \rightarrow \delta(t-\lambda_i)$ ,  $x(t)$  converges to a **train of impulses**:



$$\begin{aligned}
 x(t) &= \sum_{i=0}^{\infty} x(\lambda_i) \times \lim_{\Delta\lambda \rightarrow 0} \text{rec}_{\Delta\lambda}(t - \lambda_i) \\
 &= \sum_{i=0}^{\infty} x(\lambda_i) \times \Delta\lambda \times \delta(t - \lambda_i).
 \end{aligned}$$



# Synthesize the output $y(t)$ (1)

- Since the circuit is **LTI**:

$$\begin{cases} \delta(t) \rightarrow h(t), \\ \delta(t - \lambda_i) \rightarrow h(t - \lambda_i), \\ \sum a_i x_i(t) \rightarrow \sum a_i y_i(t); \end{cases}$$

$$\Rightarrow \sum_{i=0}^{\infty} x(\lambda_i) \Delta\lambda \cdot \delta(t - \lambda_i)$$
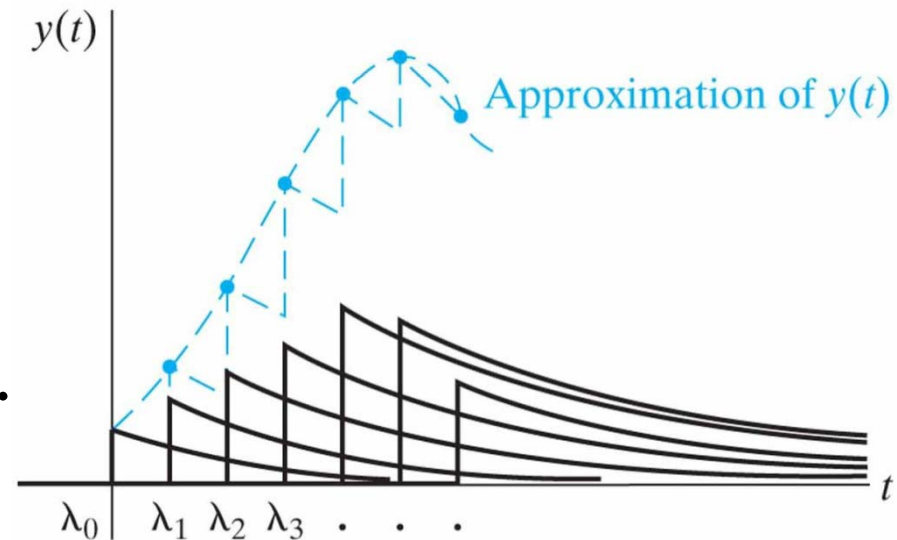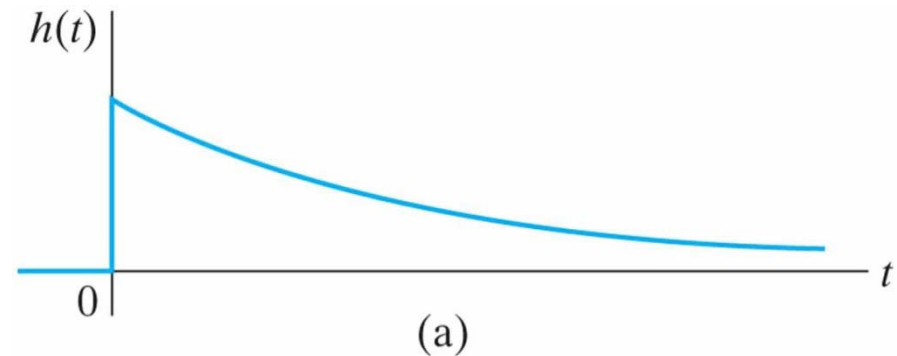
$$\rightarrow \sum_{i=0}^{\infty} x(\lambda_i) \Delta\lambda \cdot h(t - \lambda_i).$$



## Synthesize the output $y(t)$ (2)

- As  $\Delta\lambda \rightarrow 0$ , summation  $\rightarrow$  integration:

$$y(t) = \int_0^{\infty} x(\lambda)h(t-\lambda)d\lambda \xrightarrow{\text{if } x(t) \text{ extends } (-\infty, \infty)} \int_{-\infty}^{\infty} x(\lambda)h(t-\lambda)d\lambda.$$

- By change of variable  $u = t - \lambda$ ,  $\Rightarrow$

$$y(t) = \int_{-\infty}^{\infty} x(t-u)h(u)du.$$

- The output of an LTI circuit is the **convolution** of input and the impulse response of the circuit:


$$\begin{aligned} y(t) &= x(t) * h(t) \\ &= \int_{-\infty}^{\infty} x(\lambda)h(t-\lambda)d\lambda = \int_{-\infty}^{\infty} x(t-\lambda)h(\lambda)d\lambda. \end{aligned}$$

# Convolution of a causal circuit

- For physically realizable circuit, no response can occur prior to the input excitation (**causal**),  $\Rightarrow \{h(t) = 0 \text{ for } t < 0\}$ .
- Excitation is turned on at  $t = 0$ ,  $\Rightarrow \{x(t) = 0 \text{ for } t < 0\}$ .  $\Rightarrow$

$$y(t) = x(t) * h(t)$$
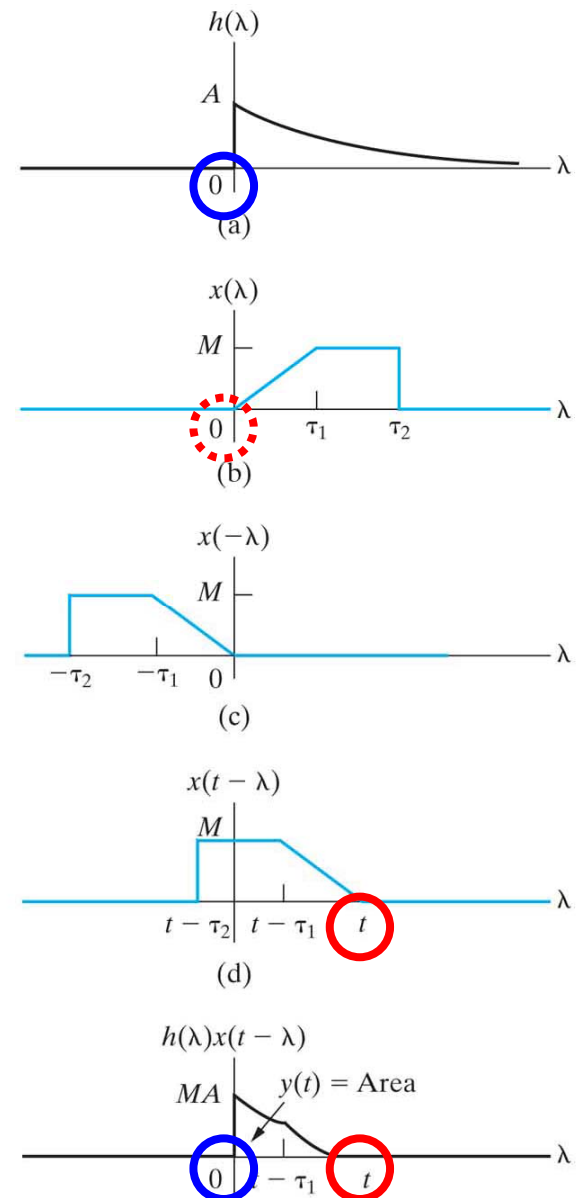
$$= \int_0^t x(t - \lambda) h(\lambda) d\lambda.$$




## Effect of $x(t)$ is weighted by $h(t)$

- The convolution integral

$$y(t) = \int_0^t x(t - \lambda)h(\lambda)d\lambda$$

shows that the value of  $y(t)$  is the weighted average of  $x(t)$  **from  $t=0$  to  $t=t$**  [from  $\lambda = t$  to  $\lambda=0$  for  $x(t-\lambda)$ ].

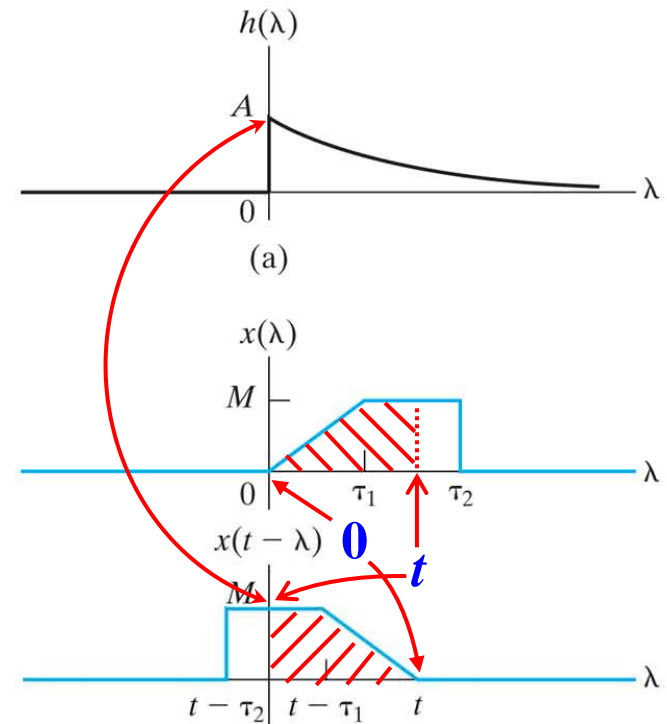- If  $h(t)$  is monotonically decreasing, the highest weight is given to **the present**  $x(t)$ .




## Memory of the circuit

- If  $h(t)$  only lasts from  $t = 0$  to  $t = T$ , the convolution integral

$$y(t) = \int_0^t x(t - \lambda)h(\lambda)d\lambda.$$



implies that the circuit has a **memory** over a finite interval  $t = [t-T, t]$ .

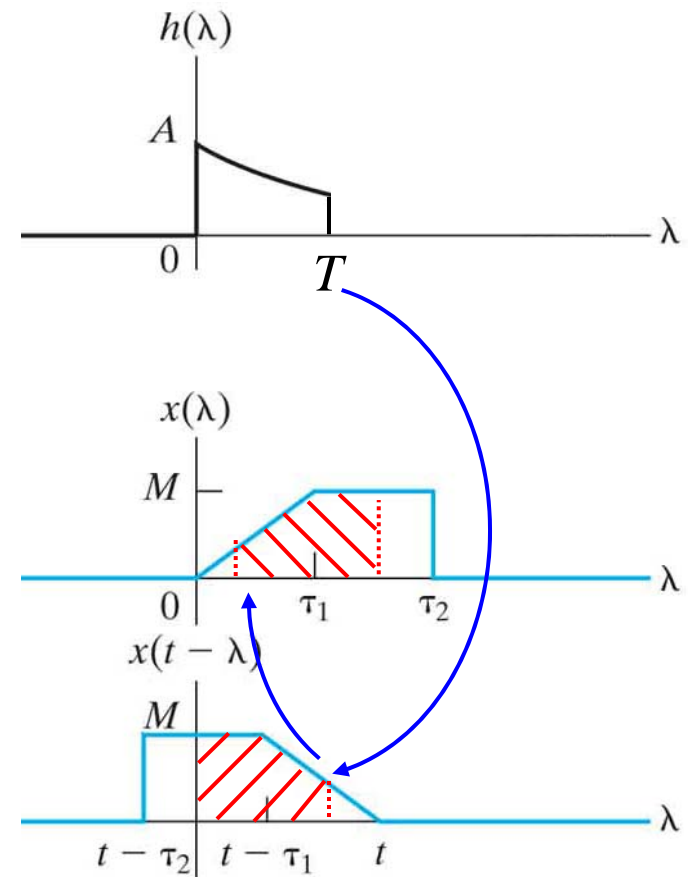- If  $h(t) = \delta(t)$ , no memory, output at  $t$  only depends on  $x(t)$ ,  $\Rightarrow y(t) = x(t) * \delta(t) = x(t)$ , no distortion.



## Example 13.3: RL driven by a trapezoidal source (1)

- Q:  $v_o(t) = ?$

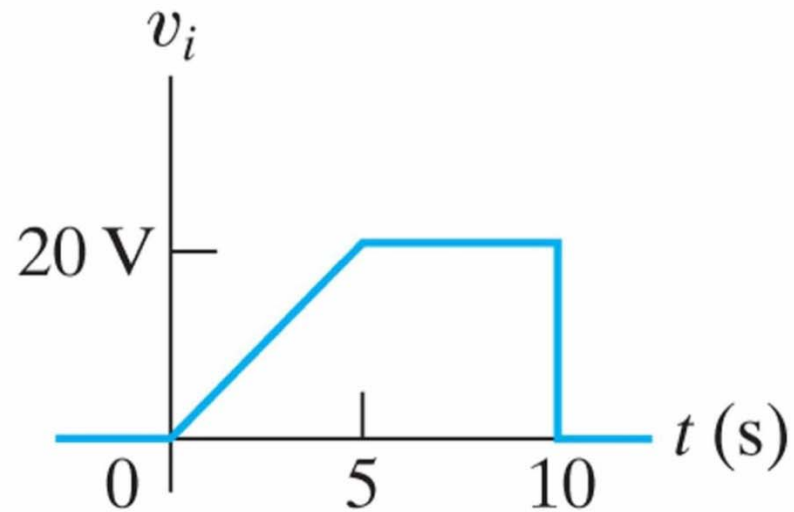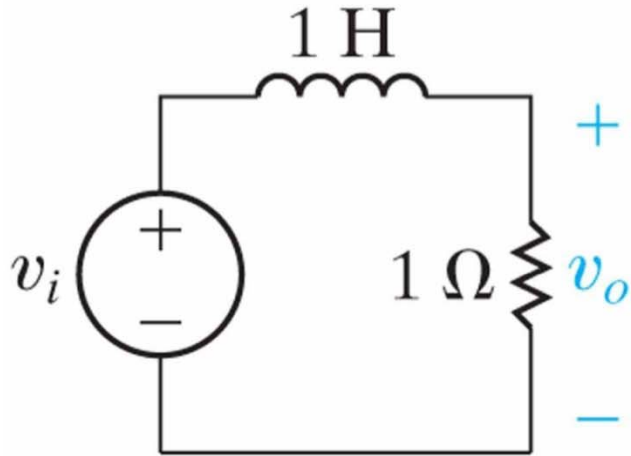



$$V_o = \frac{1}{s+1} V_i, \Rightarrow H(s) = \frac{V_o}{V_i} = \frac{1}{s+1}.$$

$$\Rightarrow h(t) = L^{-1} \left\{ \frac{1}{s+1} \right\} = e^{-t} u(t).$$





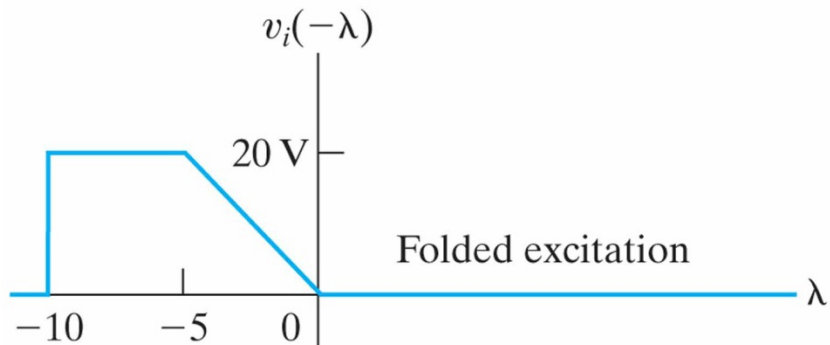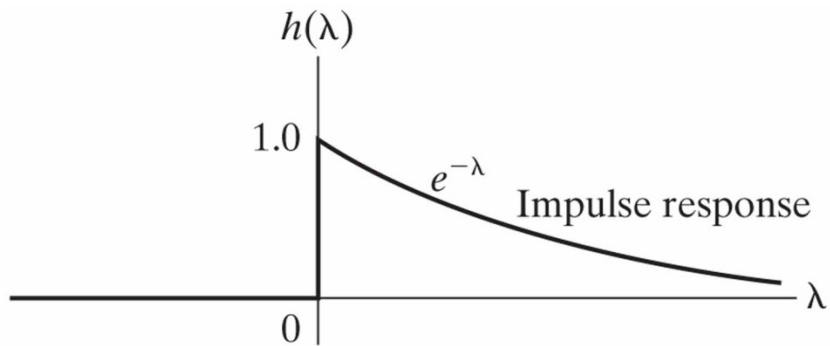
## Example 13.3 (2)

$$v_o(t) = \int_0^t v_i(t - \lambda) h(\lambda) d\lambda.$$





- Separate into 3 intervals:

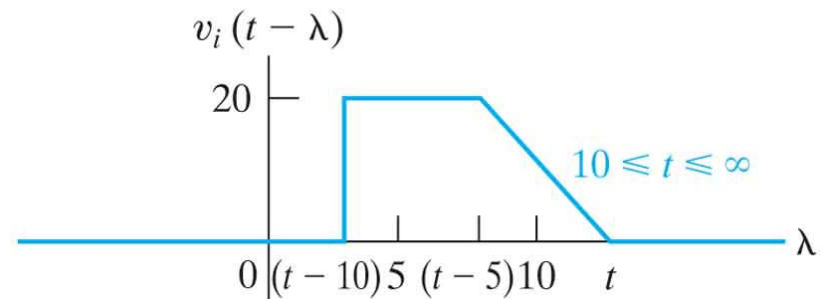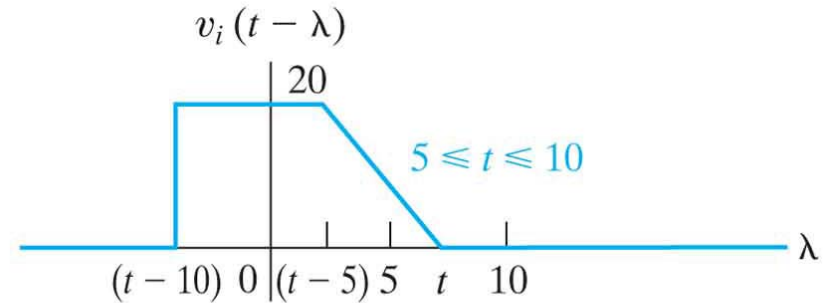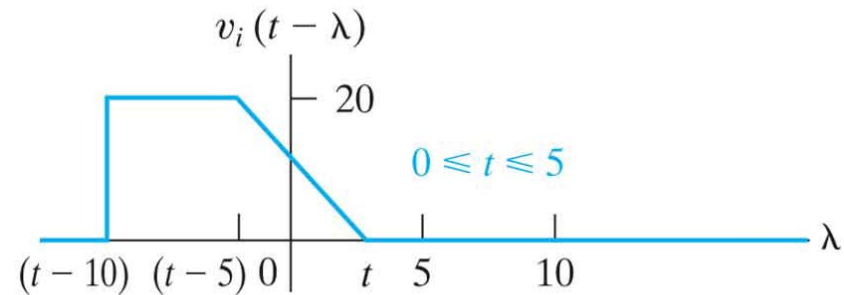
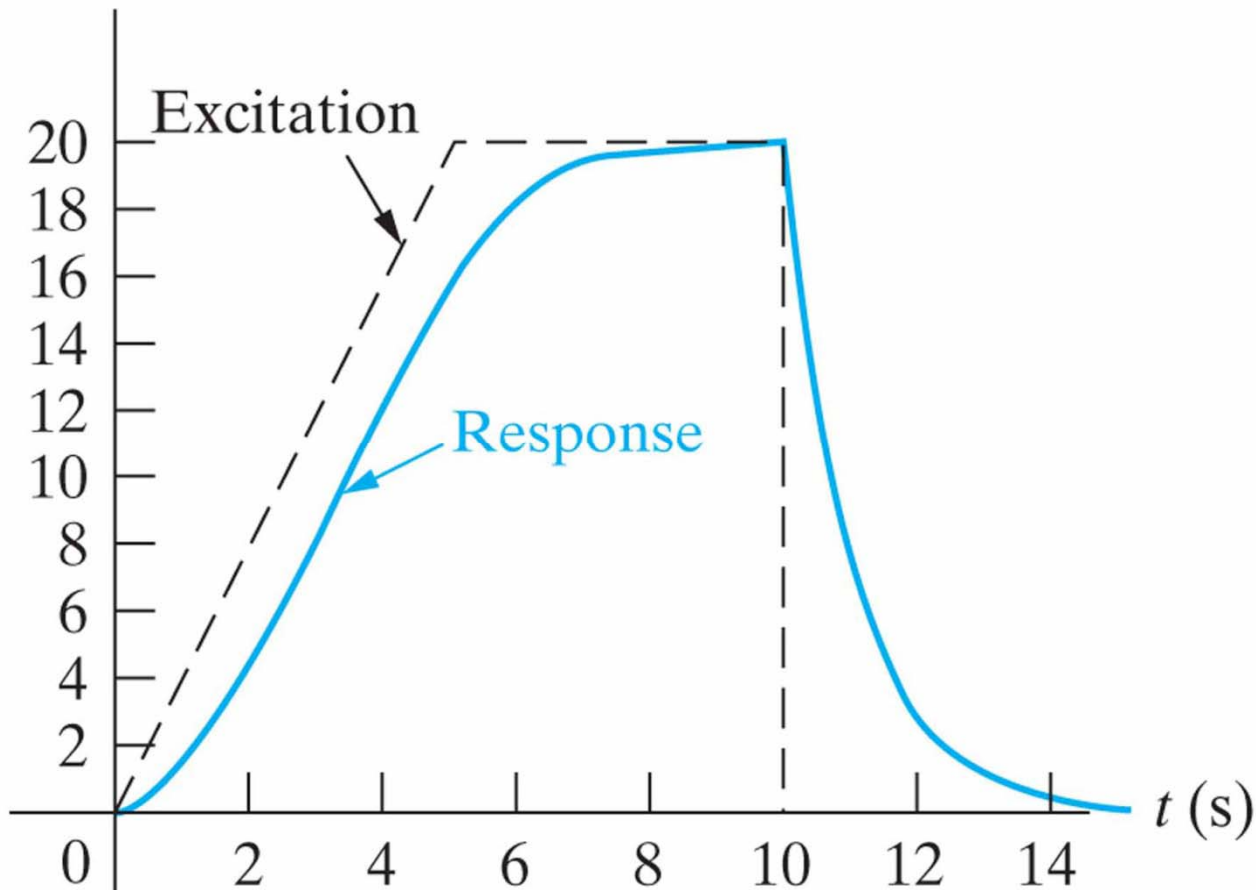
## Example 13.3 (3)

- Since the circuit has certain memory,  $v_o(t)$  has some distortion with respect to  $v_i(t)$ .



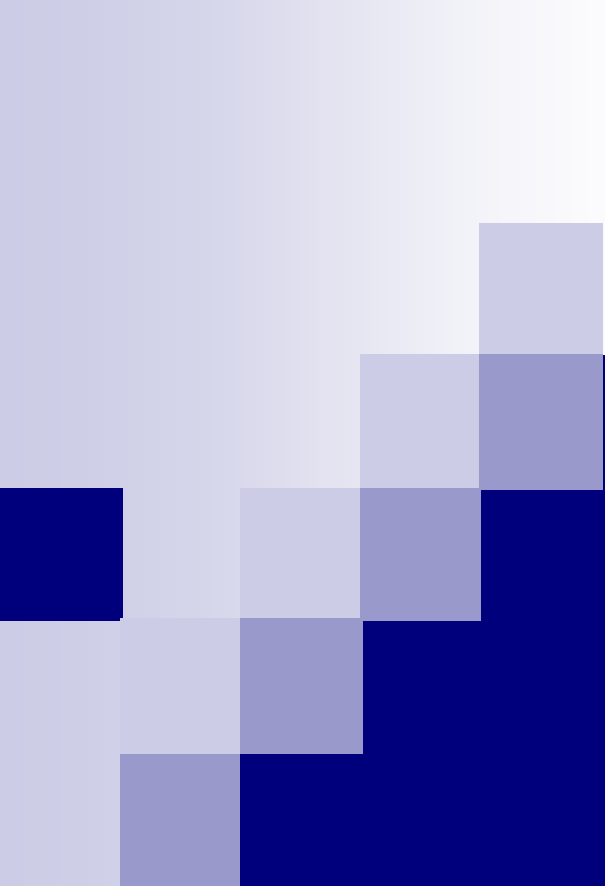

# Section 13.7

## The Transfer Function and the Steady-State Sinusoidal Response

## How to get sinusoidal steady-state response by $H(s)$ ?

- In Chapters 9-11, we used phasor analysis to get steady-state response  $y_{ss}(t)$  due to a sinusoidal input  $x(t) = A\cos(\omega t + \phi)$ .
- If we know  $H(s)$ ,  $y_{ss}(t)$  must be:

$$y_{ss}(t) = |H(j\omega)|A\cos[\omega t + \phi + \theta(\omega)],$$

$$\text{where } H(j\omega) = H(s)|_{s=j\omega} = |H(j\omega)|e^{j\theta(\omega)}.$$

- The changes of amplitude and phase depend on the **sampling** of  $H(s)$  **along the imaginary axis**.

# Proof

$$x(t) = A \cos(\omega t + \phi) = A \cos \phi \cos \omega t - A \sin \phi \sin \omega t.$$

$$X(s) = A \cos \phi \frac{s}{s^2 + \omega^2} - A \sin \phi \frac{\omega}{s^2 + \omega^2} = A \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2}.$$

$$Y(s) = H(s)X(s) = H(s) \cdot A \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2} = Y_{tr}(s) + Y_{ss}(s),$$


where  $Y_{ss}(s) = \frac{K_1}{s - j\omega} + \frac{K_1^*}{s + j\omega}$ ,  $K_1 = Y(s)(s - j\omega)|_{s=j\omega}$

$$= H(s) A \frac{s \cos \phi - \omega \sin \phi}{s + j\omega} \Big|_{s=j\omega} = H(j\omega) A \frac{j\omega \cos \phi - \omega \sin \phi}{2j\omega} = \frac{H(j\omega) A e^{j\phi}}{2}.$$

$$y_{ss}(t) = L^{-1} \left\{ \frac{|H(j\omega)| e^{j\theta(\omega)} A e^{j\phi}}{2(s - j\omega)} \right\} + c.c. = A |H(j\omega)| \cos[\omega t + \phi + \theta(\omega)].$$
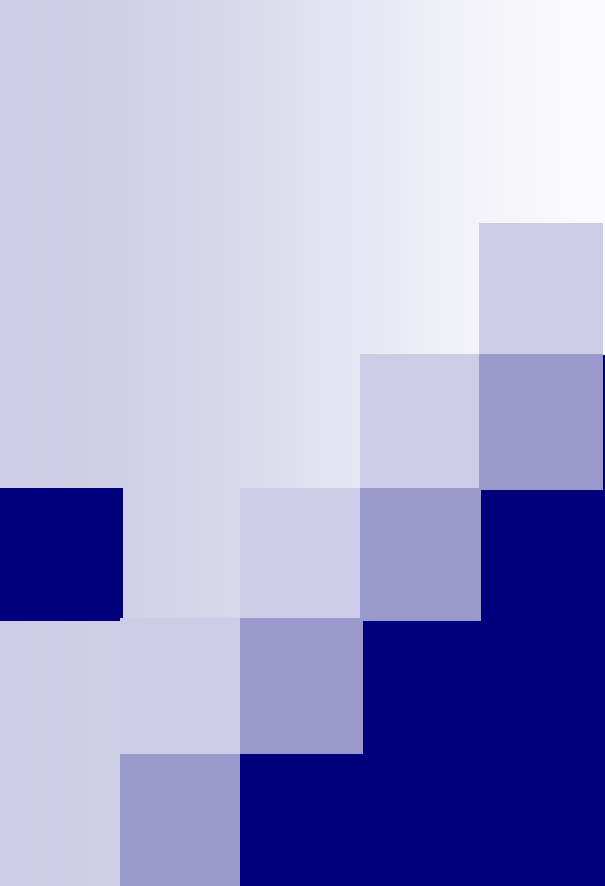
## Obtain $H(s)$ from $H(j\omega)$

- We can reverse the process: determine  $H(j\omega)$  experimentally, then construct  $H(s)$  from the data (not always possible).
- Once we know  $H(s)$ , we can find the response to **other excitation sources**.




# Section 13.8

## The Impulse Function in Circuit Analysis

## E.g. Impulsive inductor voltage (1)


- Q:  $v_o(t) = ?$

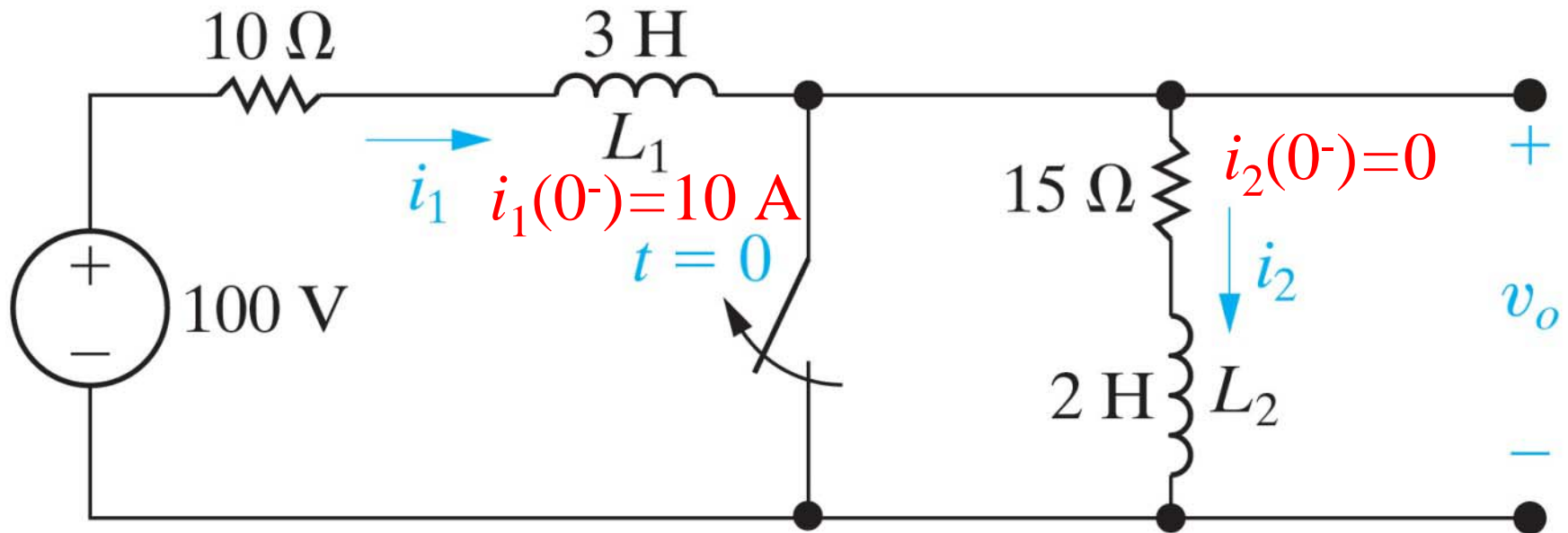

- The opening of the switch forces the two inductor currents  $i_1$ ,  $i_2$  change immediately by inducing an impulsive inductor voltage [ $v = L \cdot i'(t)$ ].


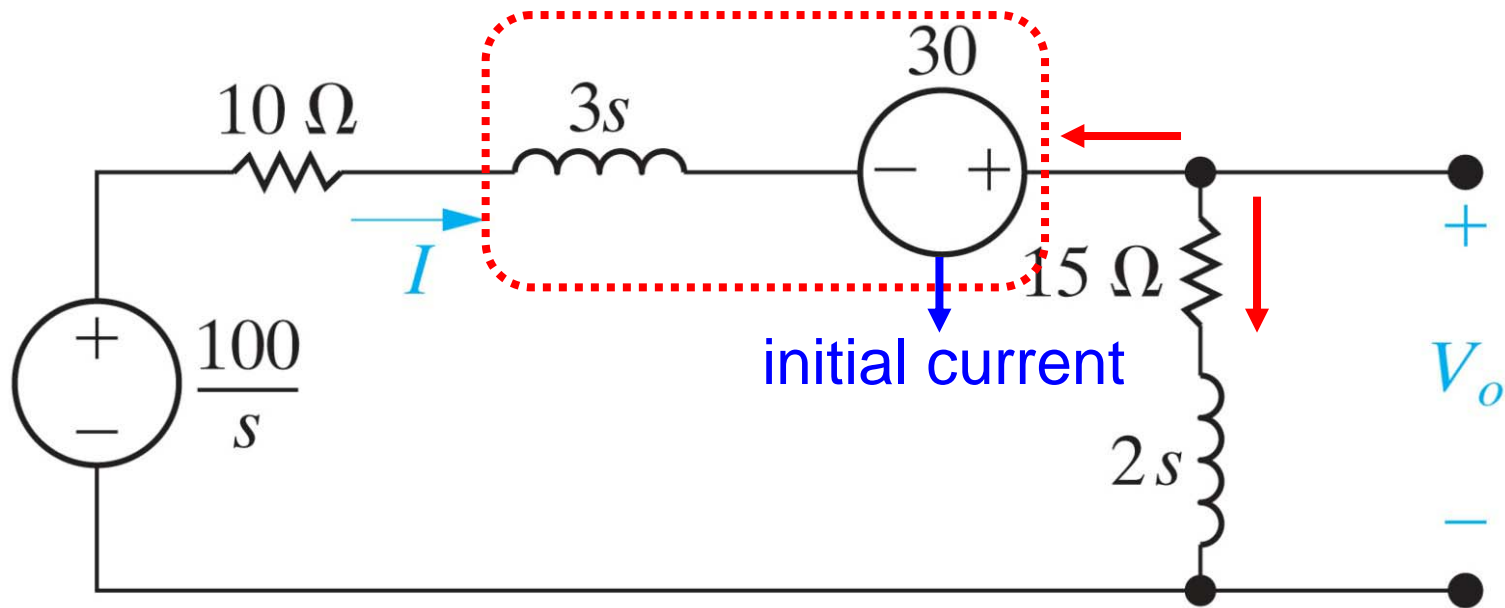
## E.g. Equivalent circuit & solution in the s-domain (2)



$$\frac{V_0 - (100/s + 30)}{10 + 3s} + \frac{V_0}{15 + 2s} = 0,$$

$$\Rightarrow V_0(s) = \frac{2(6s^2 + 65s + 150)}{s(s + 5)} = 12 + \frac{60}{s} + \frac{10}{s + 5}.$$


improper rational

## E.g. Solutions in the t-domain (3)


$$v_o(t) = L^{-1} \left\{ 12 + \frac{60}{s} + \frac{10}{s+5} \right\} = \underline{12\delta(t)} + (60 + 10e^{-5t})u(t).$$

- To **verify** whether this solution  $v_o(t)$  is correct, we need to solve  $i(t)$  as well.
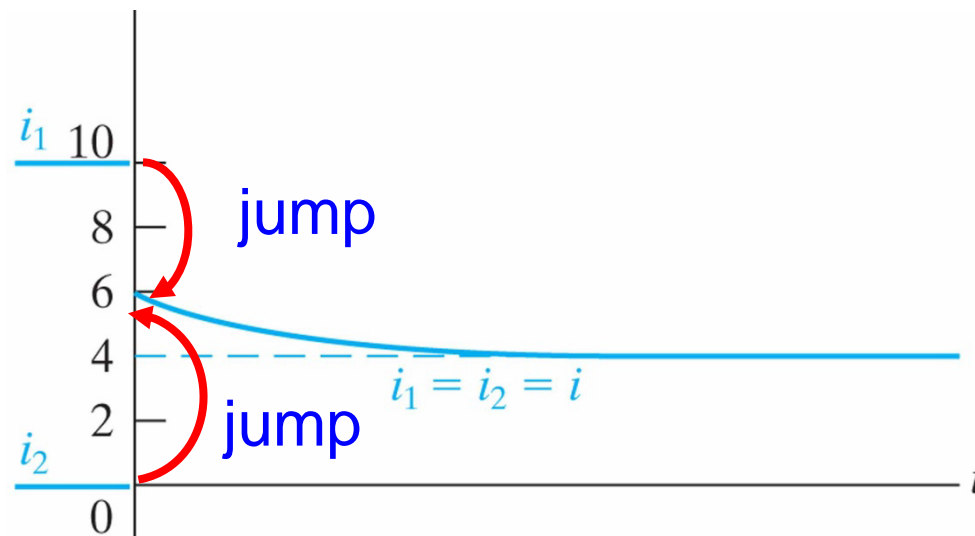
$$I(s) = \frac{100/s + 30}{10 + 3s + 15 + 2s} = \frac{4}{s} + \frac{2}{s+5}, \Rightarrow i(t) = (4 + 2e^{-5t})u(t).$$



## Impulsive inductor voltage (4)

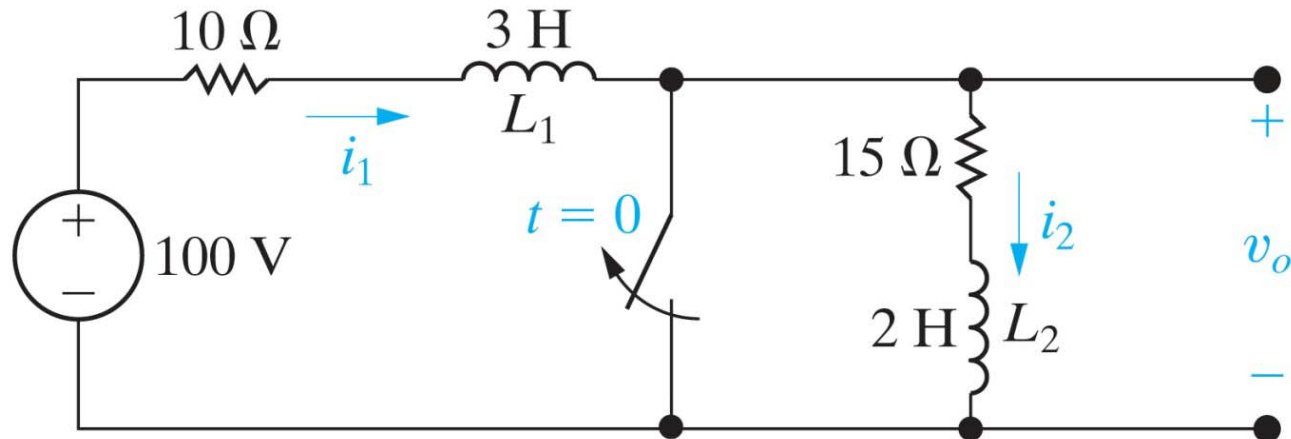

- The jump of  $i_2(t)$  from 0 to 6 A causes  $i_2'(t) = 6\delta(t)$ , contributing to a voltage impulse  $L_2 i_2'(t) = 12\delta(t)$ .
- After  $t > 0^+$ ,
 
$$v_o(t) = (15\Omega)i_2(t) + (2\text{H})i_2'(t)$$

$$= 15(4 + 2e^{-5t}) + 2(-10e^{-5t}) = 60 + 10e^{-5t},$$
 consistent with that solved by Laplace transform.

## Key points


- How to represent the **initial energy** of L, C in the s-domain?
- Why the functional forms of **natural** and **steady-state responses** are determined by the **poles** of transfer function  $H(s)$  and excitation source  $X(s)$ , respectively?
- Why the output of an LTI circuit is the **convolution** of the input and impulse response?  
How to interpret the **memory** of a circuit by convolution?



# Practical Perspective Voltage Surges
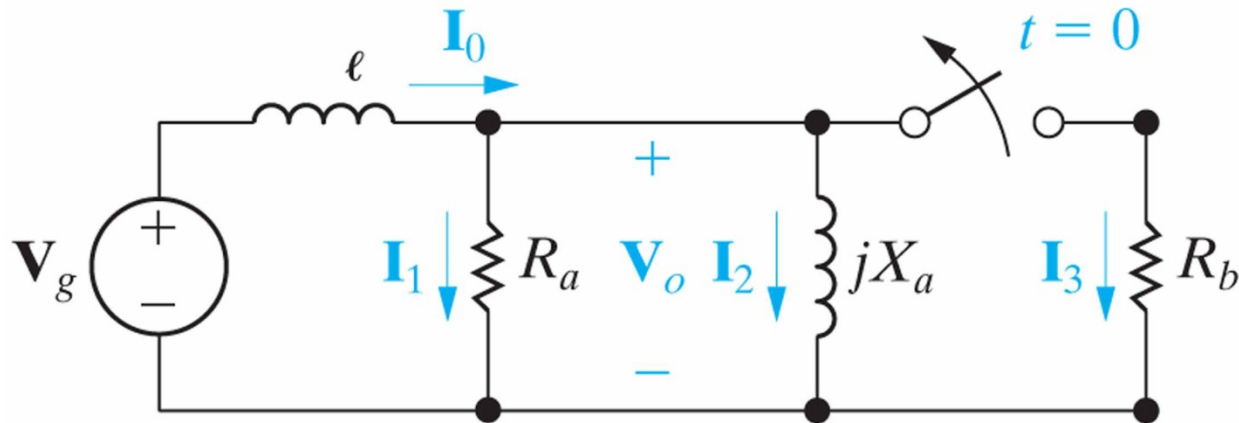
## Why can a voltage surge occur?


- Q: Why a voltage surge is created when a load is switched off?
- Model: A sinusoidal voltage source drives three loads, where  $R_b$  is switched off at  $t=0$ .



- Since  $i_2(t)$  cannot change abruptly,  $i_1(t)$  will jump by the amount of  $i_3(0^-)$ ,  $\Rightarrow$  voltage surge occurs.
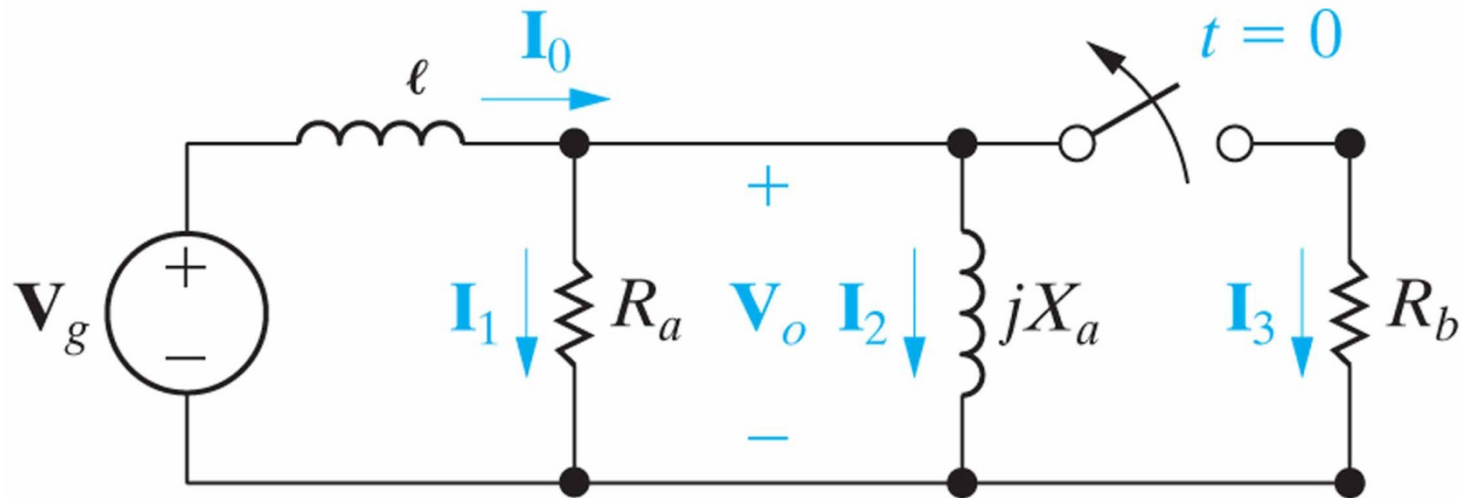
## Example

- Let  $V_o = 120 \angle 0^\circ$  (rms),  $f = 60$  Hz,  $R_a = 12 \Omega$ ,  $R_b = 8 \Omega$ ,  $X_a = 41.1 \Omega$  (i.e.  $L_a = X_a / \omega = 109$  mH),  $X_l = 1 \Omega$  (i.e.  $L_l = 2.65$  mH). Solve  $v_o(t)$  for  $t > 0^-$ .



- To draw the s-domain circuit, we need to calculate the initial inductor currents  $i_2(0^-)$ ,  $i_0(0^-)$ .


## Steady-state before the switching

- The three branch currents (rms phasors) are:  
$$\mathbf{I}_1 = \mathbf{V}_o / R_a = (120 \angle 0^\circ) / (12 \ \Omega) = 10 \angle 0^\circ \text{ A},$$
$$\mathbf{I}_2 = \mathbf{V}_o / (jX_a) = (120 \angle 0^\circ) / (j41.1 \ \Omega) = 2.92 \angle -90^\circ \text{ A},$$
$$\mathbf{I}_3 = \mathbf{V}_o / R_b = (120 \angle 0^\circ) / (8 \ \Omega) = 15 \angle 0^\circ \text{ A},$$
- The line current is:  $\mathbf{I}_0 = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 25.2 \angle -6.65^\circ \text{ A}.$
- Source voltage:  $\mathbf{V}_g = \mathbf{V}_o + \mathbf{I}_0(jX_l) = 125 \angle -11.5^\circ \text{ V}.$
- The two initial inductor currents at  $t=0^-$  are:
  - $i_2(t) = 2.92(\sqrt{2})\cos(120\pi t - 90^\circ), \Rightarrow i_2(0^-) = 0;$
  - $i_0(t) = 25.2(\sqrt{2})\cos(120\pi t - 6.65^\circ), \Rightarrow i_0(0^-) = 35.4 \text{ A}.$



# S-domain analysis

- The s-domain circuit is:

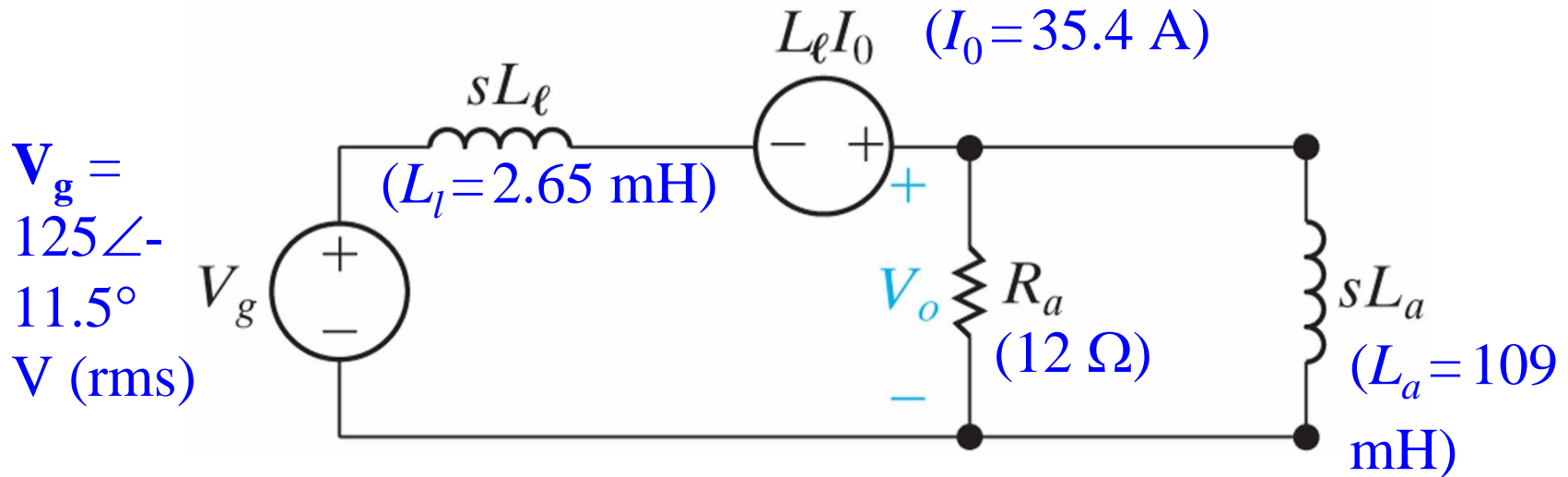

- By NVM: 
$$\frac{V_o - L_l I_0 - V_g}{sL_l} + \frac{V_o}{R_a} + \frac{V_o}{sL_a} = 0,$$

$$V_o = \frac{(R_a/L_l)V_g(s) + I_0 R_a}{s + [R_a(L_a + L_l)]/(L_a L_l)} = \frac{253}{s + 1475\pi} + \frac{86 \angle 6.85^\circ}{s - j120\pi} + \frac{86 \angle -6.85^\circ}{s + j120\pi}$$

## Inverse Laplace transform

■ Given  $V_o(s) = \frac{253}{s + 1475\pi} + \frac{86\angle 6.85^\circ}{s - j120\pi} + \frac{86\angle -6.85^\circ}{s + j120\pi}$ ,

$$\Rightarrow v_o(t) = \left[ 253e^{-1475\pi t} + 173\cos(120\pi t + 6.85^\circ) \right] \cdot u(t).$$

