



CHAPTER 5


Frequency Response

Syllabus


- Basic physics of MOS transistors and their equivalent circuit models (ch. 6)
- Elementary gain stages (ch. 7, ch. 9, and ch. 10)
- Operational amplifier basics (ch. 8)
- **Frequency responses (ch. 11)**
- Noise (ch.7, Design of analog CMOS ICs)
- Feedback, stability and compensation (ch. 12)
- Operational amplifiers (ch.9, Design of analog CMOS ICs)

What is “Frequency Response”

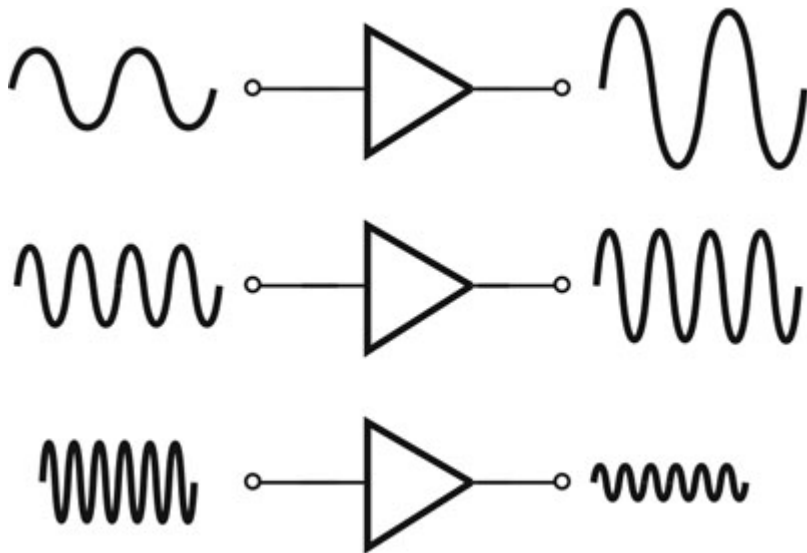Apply a sinusoid at the input of the circuit and observe the output while the input frequency is varied.



Gain roll-off with frequency

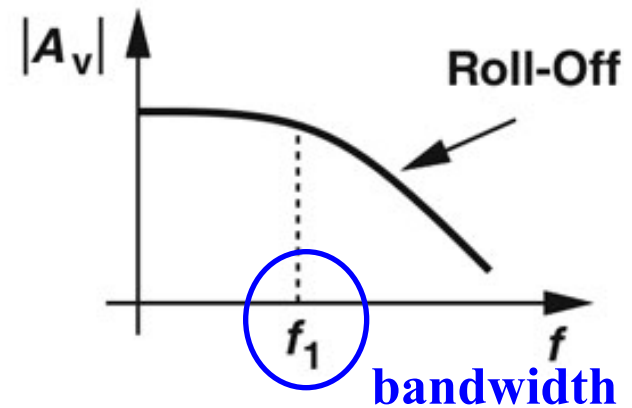


What is the cause??


What Causes the Gain Roll-Off?

Take the low-pass filter for example

The circuit

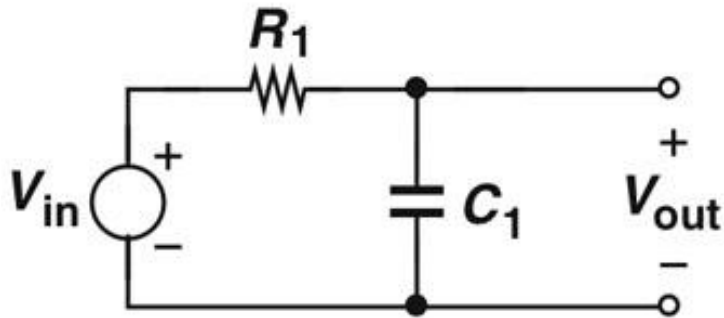


Frequency response

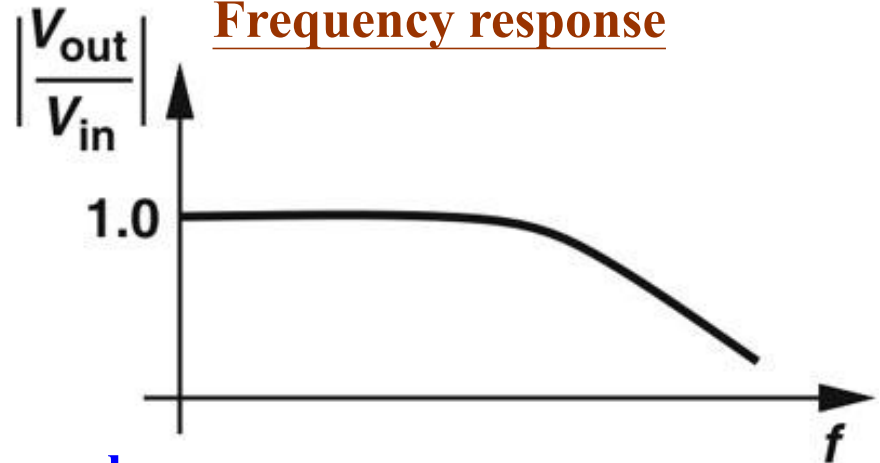


Take the common-source amplifier for example

The circuit

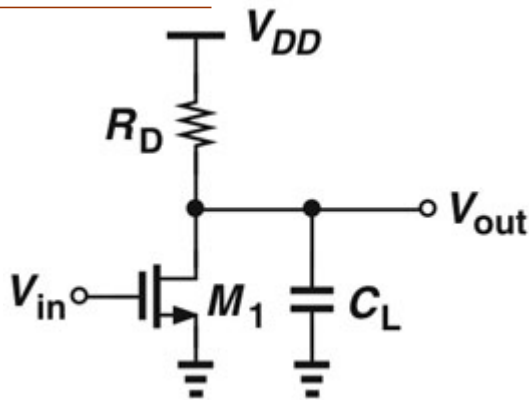

Small-signal model

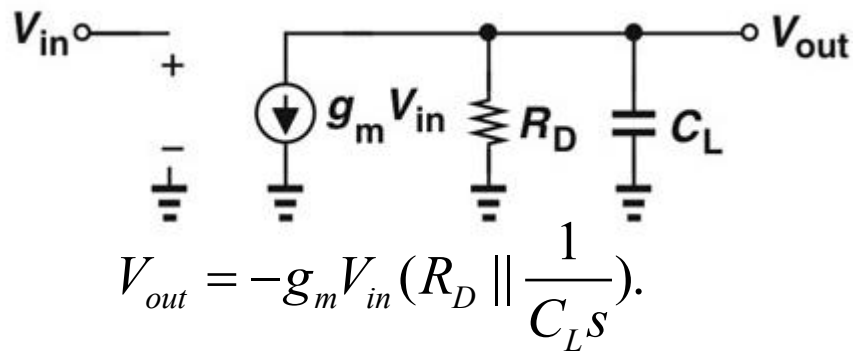

Gain drops at high frequencies!!

Transfer Function

From basic circuit theory, the transfer function of a circuit can be written as:

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \cdots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \cdots}, \quad s \rightarrow 0 \quad H(s) \rightarrow A_0$$

A_0 : the low-frequency gain

ω_z : zeros of the transfer function

ω_p : poles of the transfer function

For input: $x(t) = A \cos(2\pi ft) = A \cos \omega t$

Output: $y(t) = A |H(j\omega)| \cos[\omega t + \angle H(j\omega)],$

$|H(j\omega)|$: magnitude of the transfer function

$\angle H(j\omega)$: phase of the transfer function


f : in Hz

$$\omega = 2\pi f$$

ω : in rad/s

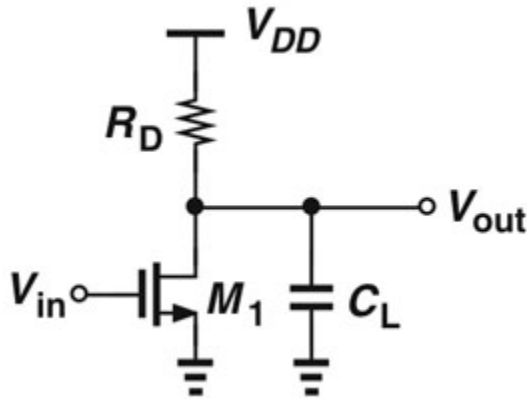Example 11.4

Determine the transfer function and frequency response of the CS stage



$$H(s) = \frac{V_{out}}{V_{in}}(s) = -g_m \left(R_D \parallel \frac{1}{C_L s} \right)$$

$$= \frac{-g_m R_D}{R_D C_L s + 1}.$$

For sinusoid input: $s = j\omega$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{R_D^2 C_L^2 \omega^2 + 1}}.$$

At $\omega = 1/(R_D C_L)$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{2}}.$$


$$20 \log \sqrt{2} \approx 3 \text{ dB}$$

-3dB bandwidth is equal to $1/(R_D C_L)$

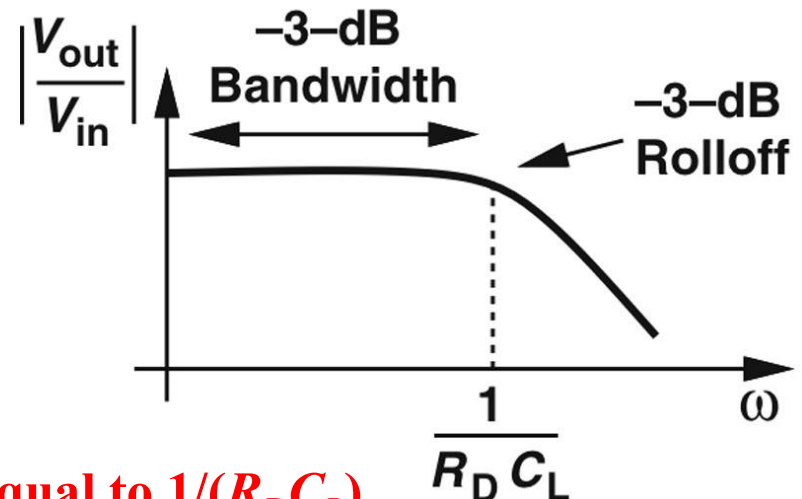

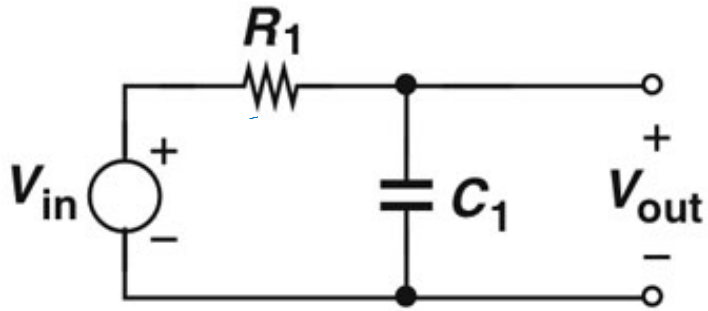Example 11.6

Explain the relationship between the frequency response and step response of the simple low-pass filter.





$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{\frac{1}{C_1 s}}{\frac{1}{C_1 s} + R_1} = \frac{1}{R_1 C_1 s + 1}.$$

$$|H(s = j\omega)| = \frac{1}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}.$$

$$\text{-3dB bandwidth} = 1/R_1 C_1$$

Step response to $V_0 u(t)$:
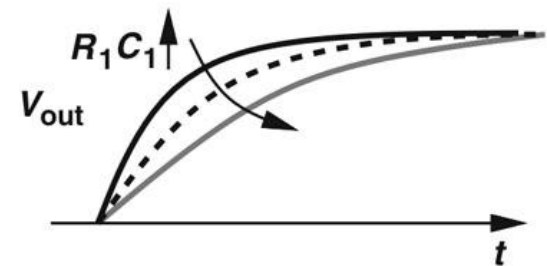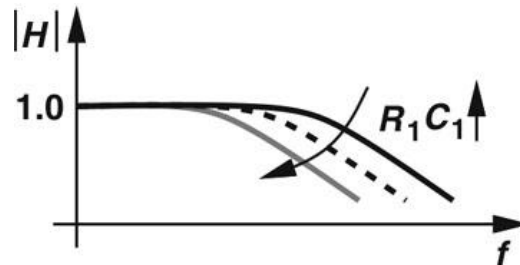
$$V_{out}(t) = V_0 \left(1 - \exp\left(-\frac{t}{R_1 C_1}\right)\right) u(t).$$



➤ The relationship is such that as $R_1 C_1$ increases, the bandwidth *drops* and the step response becomes *slower*.

Bode's Rules

The task of obtaining $|H(j\omega)|$ from $H(s)$ and plotting the result is tedious. We often utilize Bode's rules (approximation) to construct $|H(j\omega)|$ rapidly.




<Bode's rules>

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \cdots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \cdots}$$

- As ω passes each **pole** frequency, the slope of $|H(j\omega)|$ **decreases** by 20 dB/dec.
- As ω passes each **zero** frequency, the slope of $|H(j\omega)|$ **increases** by 20 dB/dec.

<Example 11.7> Construct the Bode plot of $|H(j\omega)|$ for the CS stage.


$$H(s) = \frac{V_{out}}{V_{in}}(s) = -g_m \left(R_D \parallel \frac{1}{C_L s}\right) = \frac{-g_m R_D}{R_D C_L s + 1}. \quad |\omega_{p1}| = \frac{1}{R_D C_L}.$$

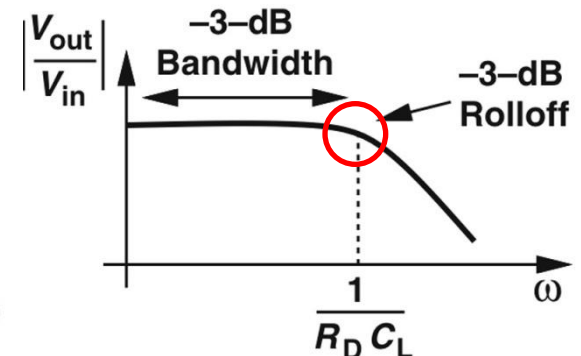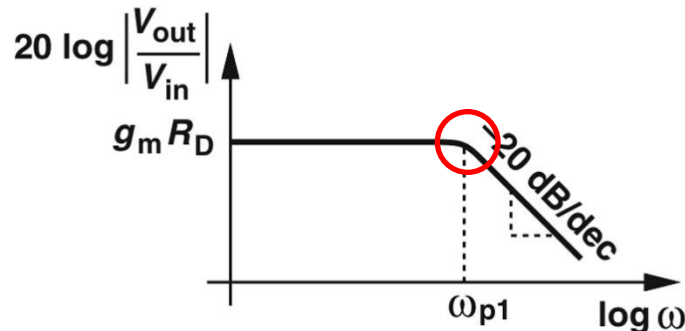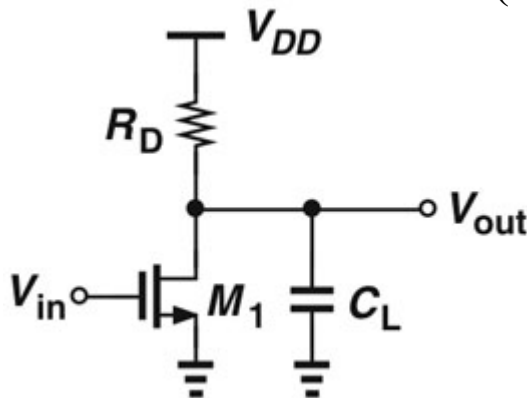

Identify the Poles (Speed Bottleneck)


Generalized from the CS stage: if node j in the signal path exhibits a small-signal resistance of R_j to ground and a capacitance of C_j to ground, then it contributes a pole of magnitude $(R_j C_j)^{-1}$ to the transfer function.
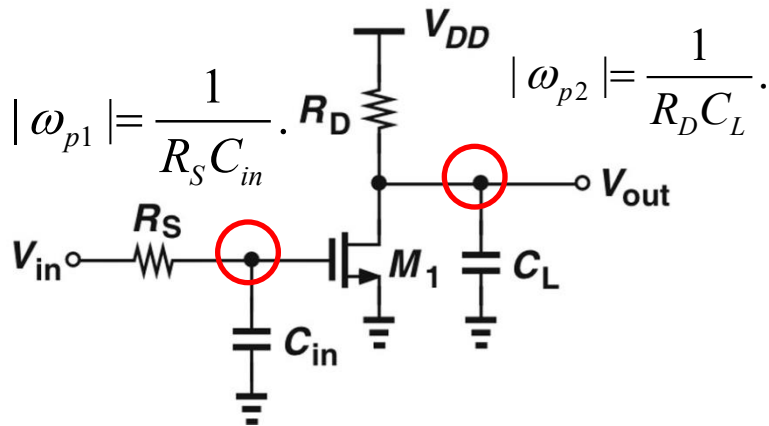
<Example 11.8> Determine the poles of the circuit. Assume $\lambda=0$.



$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{(1 + \omega^2 / \omega_{p1}^2)(1 + \omega^2 / \omega_{p2}^2)}}.$$

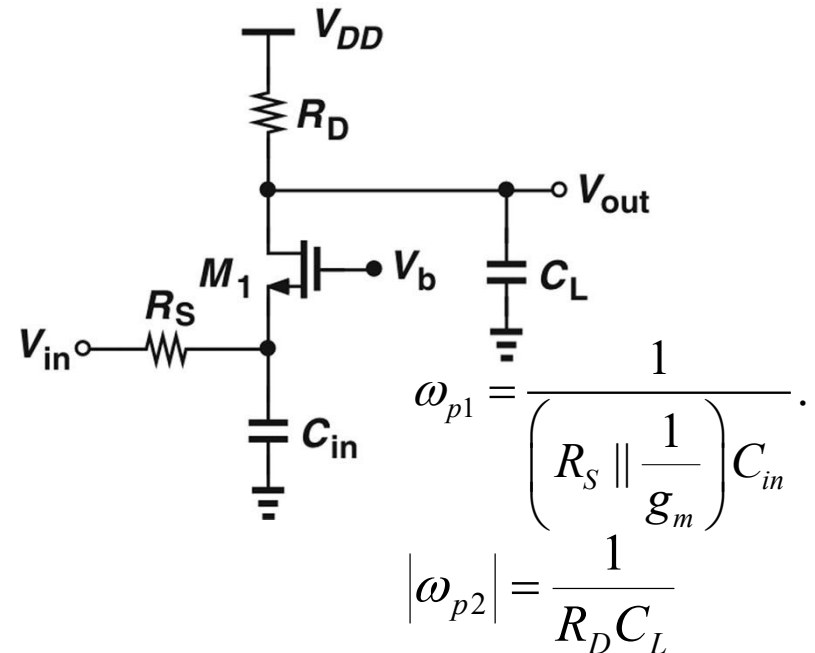
<Example 11.9> Determine the poles of the circuit. Assume $\lambda=0$.



$$\omega_{p1} = \frac{1}{\left(R_S \parallel \frac{1}{g_m} \right) C_{in}}.$$

$$|\omega_{p2}| = \frac{1}{R_D C_L}$$

Circuit with Floating Capacitor

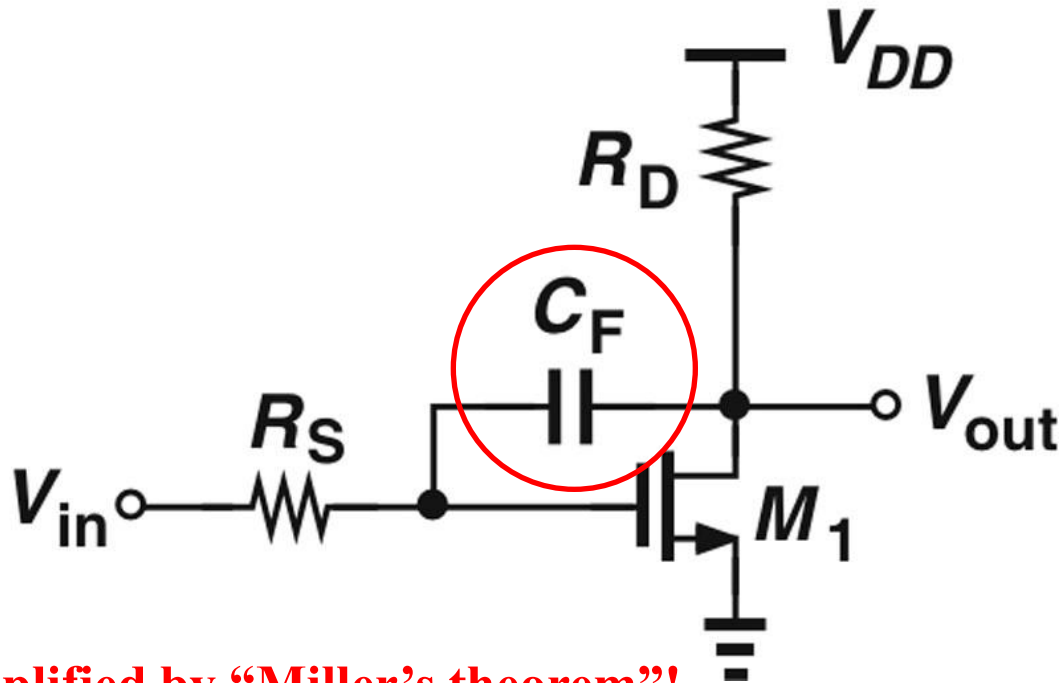


Can be simplified by “Miller’s theorem”!

- The pole of a circuit is computed by finding the effective resistance and capacitance from a node to GROUND.
- The circuit above creates a problem since neither terminal of C_F is grounded.


Miller's Theorem

A method that “transforms” a floating capacitor to two grounded capacitors.

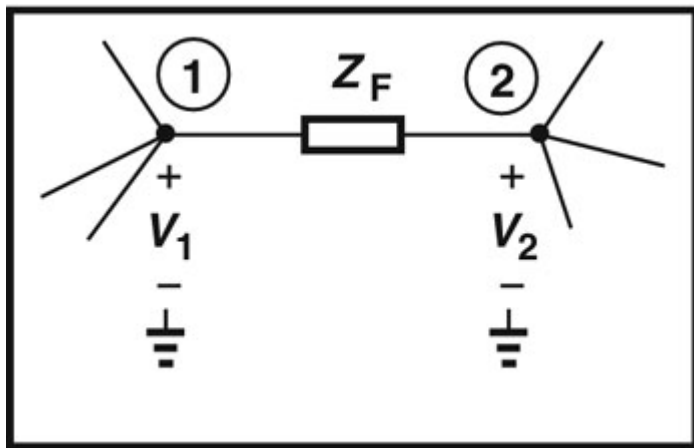General circuit including a floating impedance



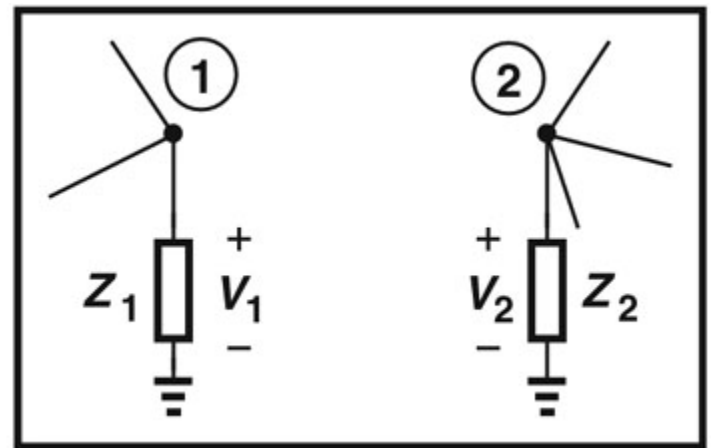Equivalent obtained from Miller's theorem



<Two observations>

- The current drawn by Z_F from node 1 must be equal to that drawn by Z_1
- The current injected to node 2 must be equal to that injected by Z_2

Denote the voltage gain from node 1 to node 2 by A_v

$$Z_1 = Z_F \frac{V_1}{V_1 - V_2} = \frac{Z_F}{1 - A_v}$$

$$Z_2 = Z_F \frac{-V_2}{V_1 - V_2} = \frac{Z_F}{1 - \frac{1}{A_v}}$$


$$\frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_1}$$

$$\frac{V_1 - V_2}{Z_F} = -\frac{V_2}{Z_2}$$

The floating impedance is reduced by a factor of $1 - A_v$, when “seen” at node 1

ZF as a Single Capacitor CF

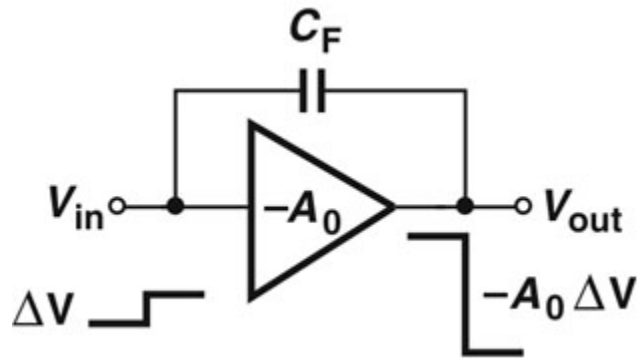Inverting amplifier with floating capacitor




$$Z_1 = \frac{Z_F}{1 - A_v} = \frac{1}{\underline{(1 + A_0)C_F s}},$$

Miller multiplication


$$Z_2 = \frac{Z_F}{1 - \frac{1}{A_v}} = \frac{1}{\left(1 + \frac{1}{A_0}\right) C_F s}, \approx \frac{1}{\underline{C_F s}}$$

Miller effect!!

Equivalent circuit from Miller's theorem

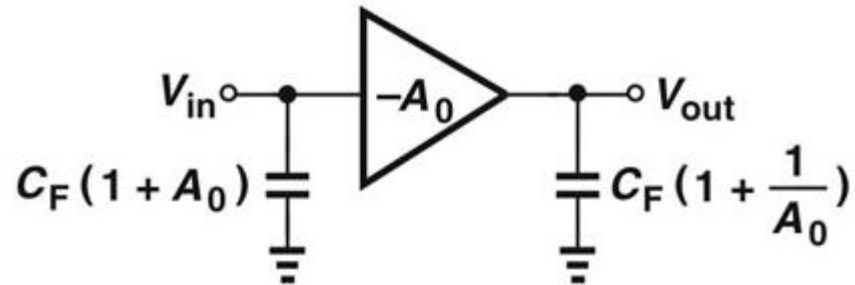
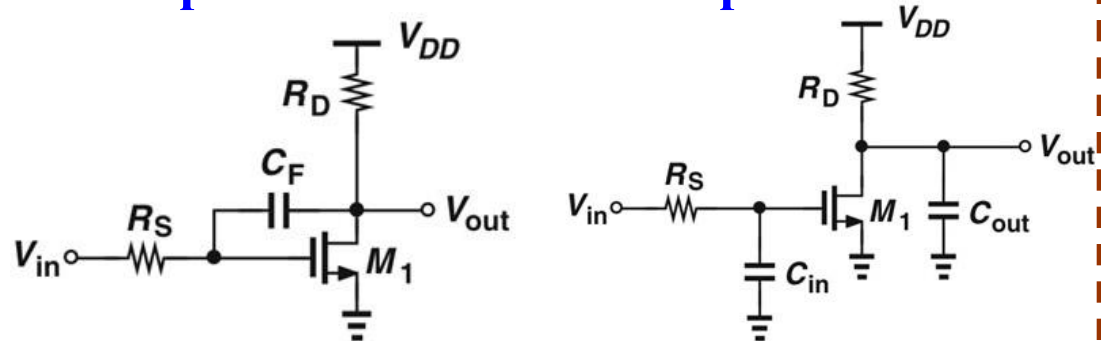
<Example 11.10> Estimate the poles. $\lambda=0$.



$$C_{in} = (1 + A_0)C_F = (1 + g_m R_D)C_F$$


$$C_{out} = \left(1 + \frac{1}{g_m R_D}\right)C_F,$$

$$\omega_{in} = \frac{1}{R_S C_{in}} = \frac{1}{R_S (1 + g_m R_D)C_F}$$

$$\omega_{out} = \frac{1}{R_D C_{out}} = \frac{1}{R_D \left(1 + \frac{1}{g_m R_D}\right)C_F}.$$


High-Pass Filter

The circuit

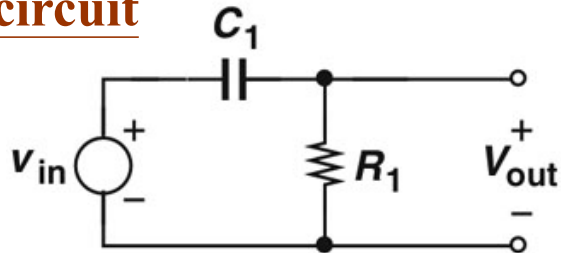


$$\frac{V_{out}}{V_{in}}(s) = \frac{R_1}{R_1 + \frac{1}{C_1 s}} = \frac{R_1 C_1 s}{R_1 C_1 s + 1}, \quad \Rightarrow \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{R_1 C_1 \omega}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}.$$

Frequency response

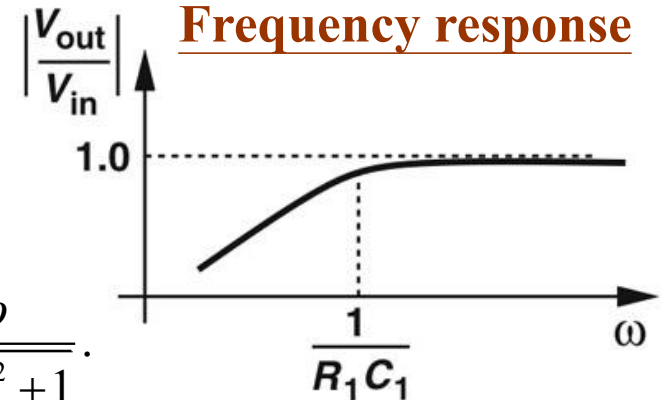
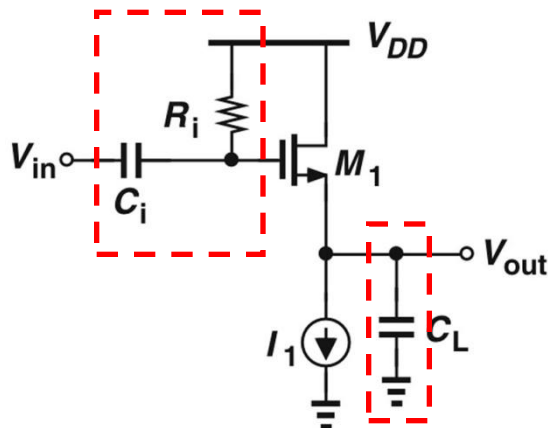
<Example 11.11> Source follower in an audio amplifier. Assume $\lambda=0$, $g_m = 1/(200\Omega)$, and $R_i = 100\text{k}\Omega$. Determine the minimum C_i and maximum C_L .



Audio signal component as low as 20Hz

Set the corner frequency $1/(R_i C_i)$ to $2\pi \times 20\text{Hz}$ $\Rightarrow C_i = 79.6\text{nF}$.


Set the pole frequency to upper end of audio 20kHz

$$\omega_{p,out} = \frac{g_m}{C_L} = 2\pi \times (20\text{kHz}), \quad \Rightarrow C_L = 39.8\text{nF}.$$


Why do we need C_i ??

Capacitor Coupling

With coupling capacitor

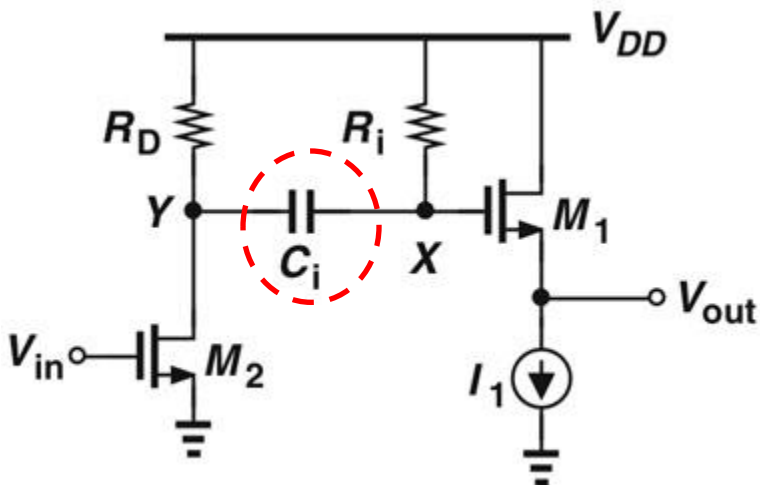

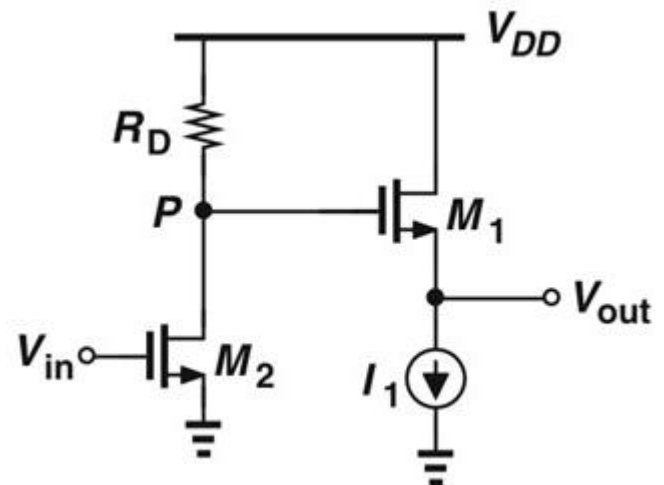Without coupling capacitor (direct coupling)



Maximize the CS voltage gain

Set $V_Y = V_{GS2} - V_{TH2}$ (why?) (200mV)

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D},$$


ω_L : lower corner, lower “cut-off” frequency

ω_H : upper corner, upper “cut-off” frequency




$V_P = V_{GS1} + V_{II}$ (600mV~700mV)

Typical frequency response

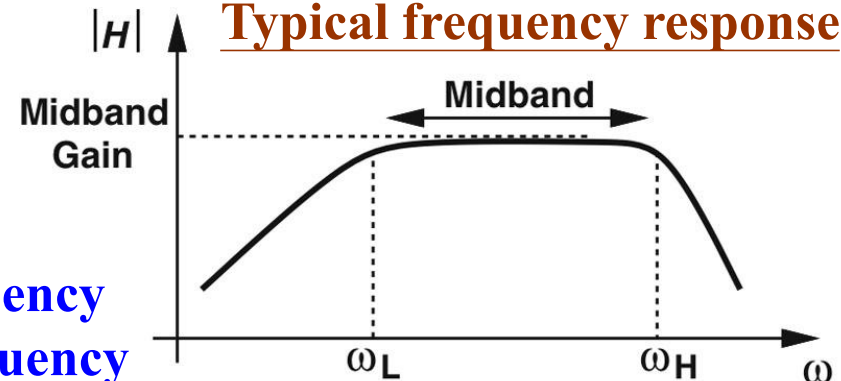


High-Frequency Model of MOSFET


Structure of MOSFET

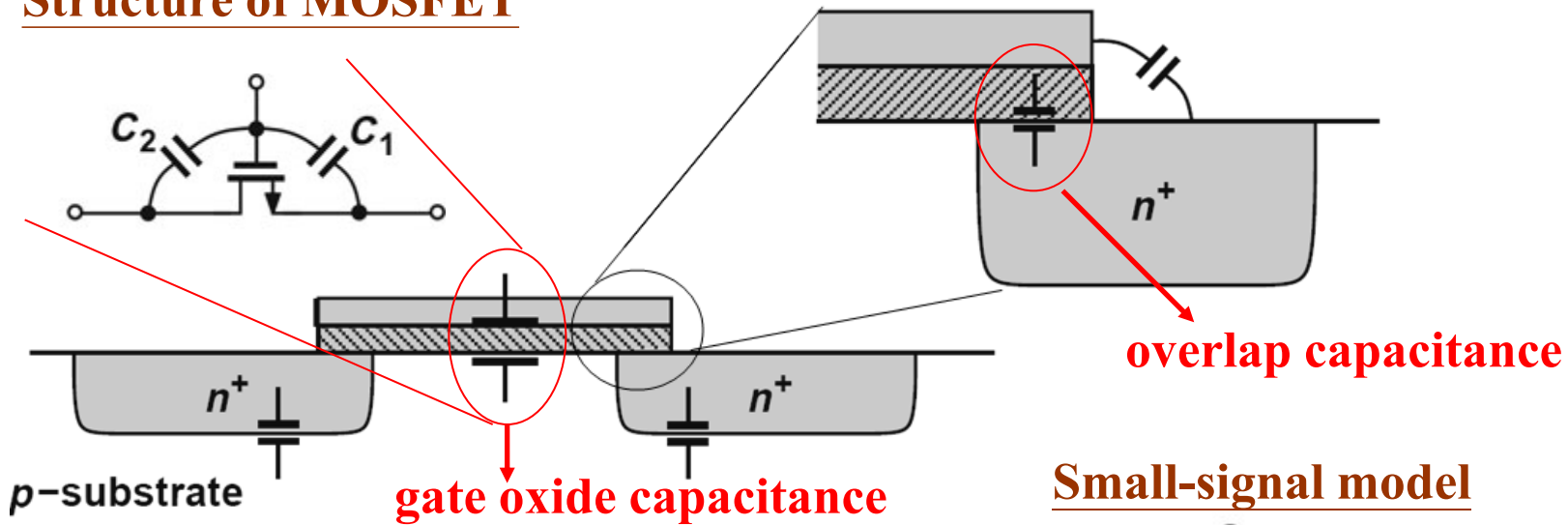

Device symbol with capacitances

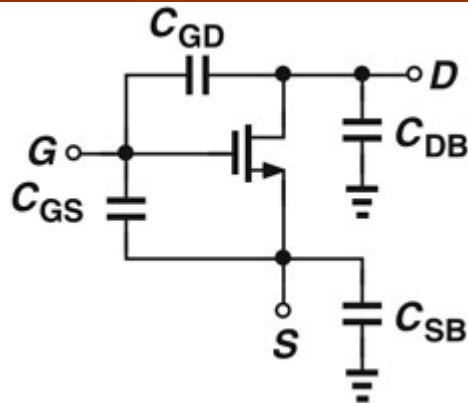


Small-signal model

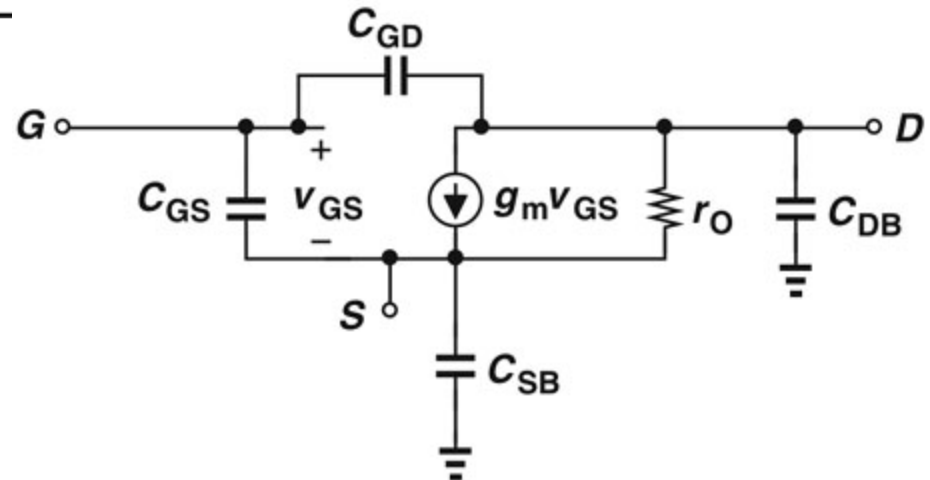

Transit (Cut-Off) Frequency f_T

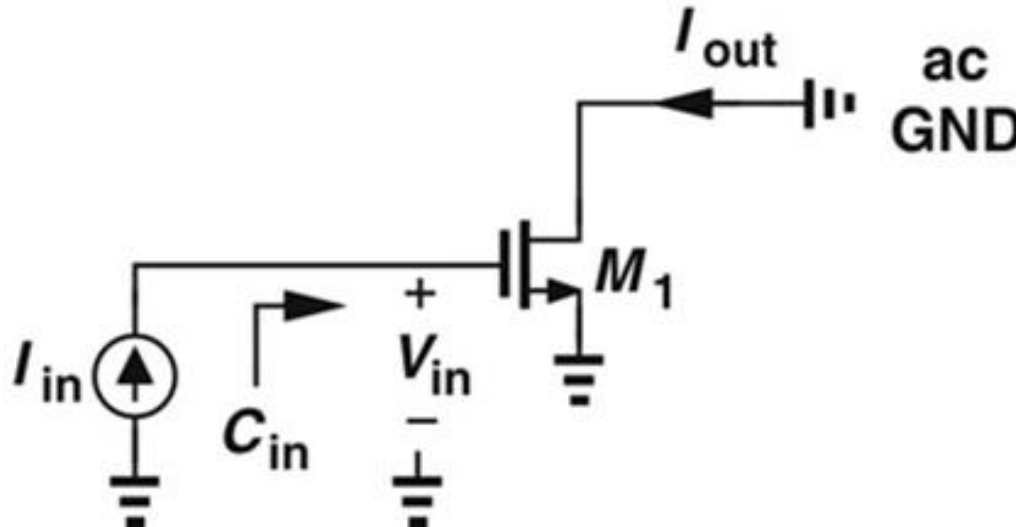Define a quantity that represents the ultimate speed of the transistor
 f_T : the frequency at which the small-signal *current gain* of the device falls to unity



$$Z_{in} = \frac{1}{sC_{GS}} \quad I_{out} = g_m I_{in} Z_{in} \quad \Rightarrow \quad \frac{I_{out}}{I_{in}} = \frac{g_m}{sC_{GS}}$$

$$\omega_T = \frac{g_m}{C_{GS}}$$

➤ Transit frequency, f_T , is defined as the frequency where the current gain from input to output drops to 1.

Concepts We Have Learned So Far


- The frequency response refers to the magnitude of the transfer function of a system.
- Bode's approximation simplifies the task of plotting the frequency response if poles and zeros are known.
- In general, it is possible to associate a pole with each node in the signal path.
- Miller's theorem helps to decompose floating capacitors into grounded elements.
- MOS devices exhibit various capacitances that limit the speed of circuits.

Analysis Procedure


- **Determine which capacitor impact the low-frequency region of the response and calculate the low-frequency pole (neglect transistor capacitance).**
- **Calculate the midband gain by replacing the capacitors with short circuits (neglect transistor capacitance).**
- **Include transistor capacitances.**
- **Merge capacitors connected to AC grounds and omit those that play no role in the circuit.**
- **Determine the high-frequency poles and zeros.**
- **Plot the frequency response using Bode's rules or exact analysis.**

Low-Frequency Response of CS

General CS stage

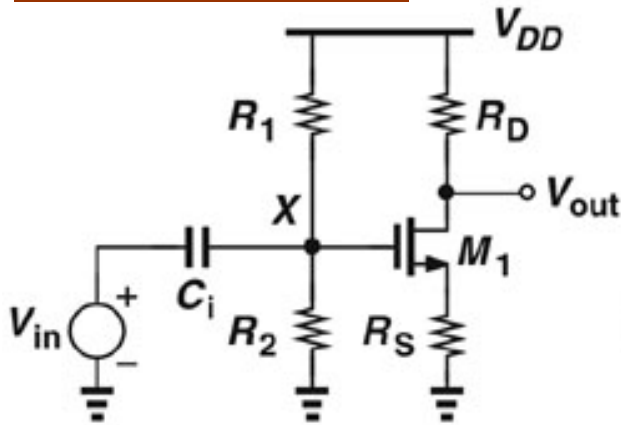

Bypass capacitor added

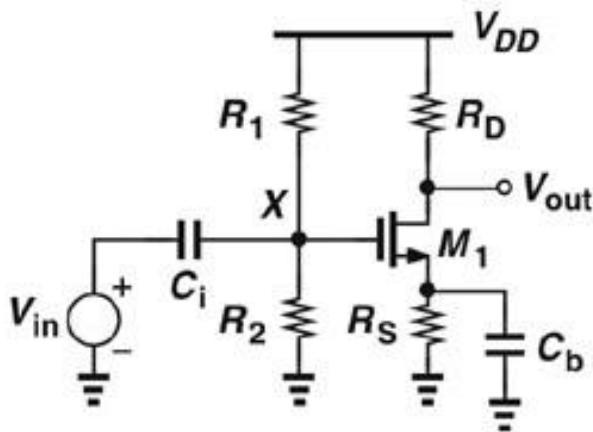

Low frequency response

$$V_{out}/V_{in} = (V_{out}/V_X)(V_X/V_{in})$$

$$V_{out}/V_X = -R_D/(R_S + 1/g_m)$$


$$\frac{V_X}{V_{in}}(s) = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + \frac{1}{C_i s}} = \frac{(R_1 \parallel R_2)C_i s}{(R_1 \parallel R_2)C_i s + 1}$$

$$\begin{aligned} \frac{V_{out}}{V_X}(s) &= \frac{-R_D}{R_S \parallel \frac{1}{C_b s} + \frac{1}{g_m}} \\ &= \frac{-g_m R_D (R_S C_b s + 1)}{R_S C_b s + g_m R_S + 1} \end{aligned}$$

Pole needs to be chosen significantly smaller than the lowest signal frequency of interest


$$\frac{1}{2\pi[(R_1 \parallel R_2)C_i]} < f_{sig,min}$$

Bode plot

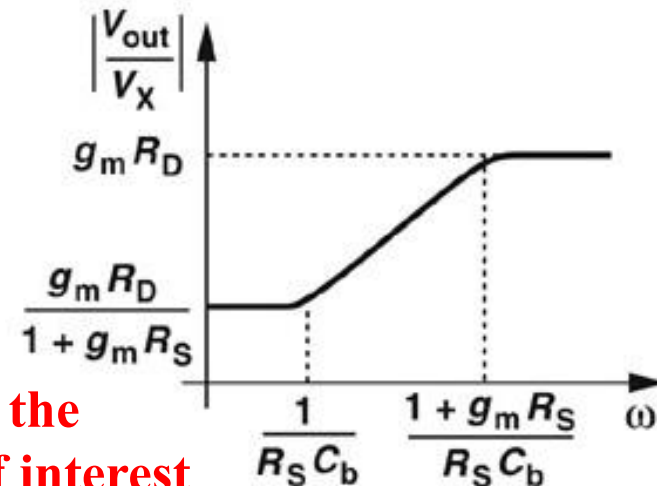


High-Frequency Model of CS


CS amplifier

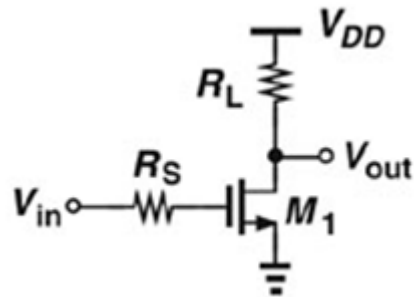


Transistor caps included

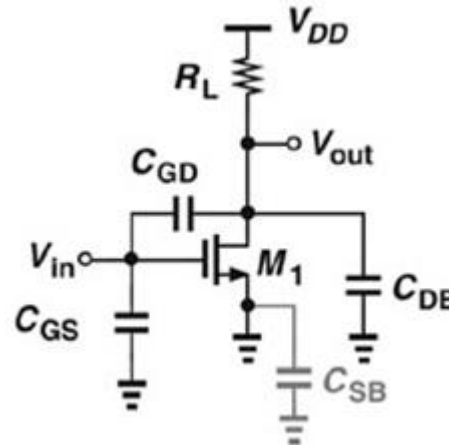

Small-signal equivalents

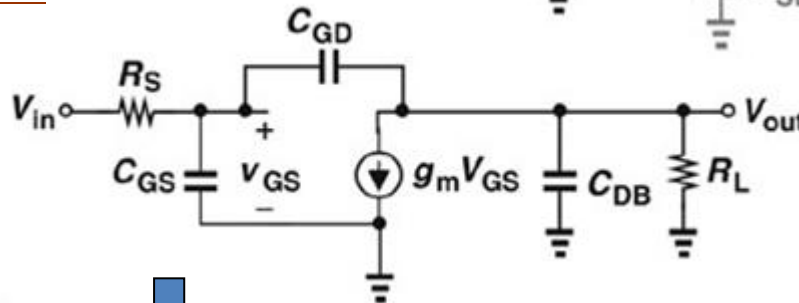

Unified for both

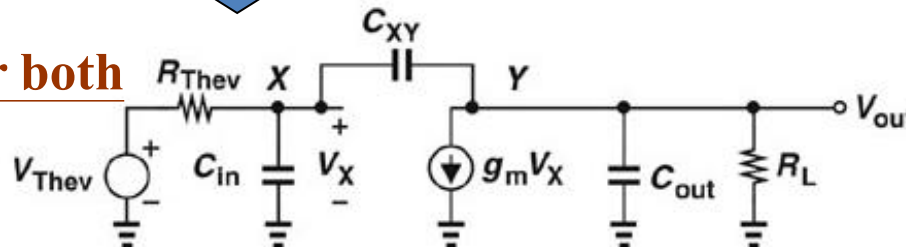


$$R_S \ll r_\pi$$

$$R_{Thev} \approx R_S$$

$$r_o \parallel R_L$$

Use of Miller's Theorem

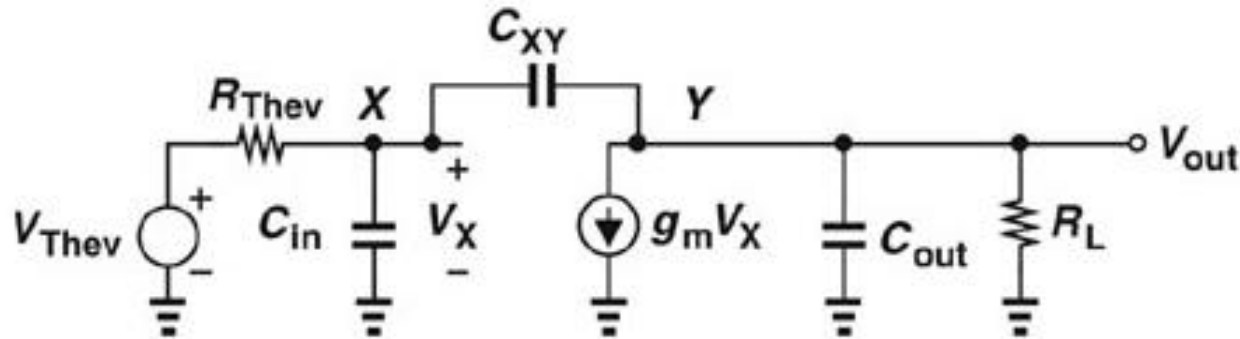


$$C_X = (1 + g_m R_L) C_{XY}$$

$$C_Y = \left(1 + \frac{1}{g_m R_L} \right) C_{XY}$$

$$|\omega_{p,in}| = \frac{1}{R_{Thev} [C_{in} + (1 + g_m R_L) C_{XY}]}$$

$$|\omega_{p,out}| = \frac{1}{R_L \left[C_{out} + \left(1 + \frac{1}{g_m R_L} \right) C_{XY} \right]}$$

Direct Analysis

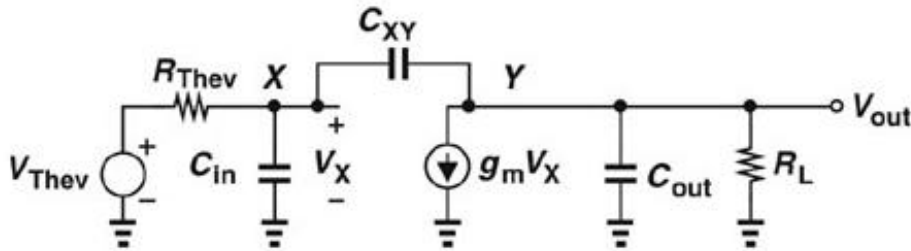

$$\text{At Node X: } (V_{out} - V_X)C_{XY}s = V_X C_{in}s + \frac{V_X - V_{Thev}}{R_{Thev}}$$

$$\text{At Node Y: } (V_X - V_{out})C_{XY}s = g_m V_X + V_{out} \left(\frac{1}{R_L} + C_{out}s \right). \Rightarrow V_X = V_{out} \frac{C_{XY}s + \frac{1}{R_L} + C_{out}s}{C_{XY}s - g_m}$$

$$\Rightarrow V_{out} C_{XY}s - \left(C_{XY}s + C_{in}s + \frac{1}{R_{Thev}} \right) \frac{C_{XY}s + \frac{1}{R_L} + C_{out}s}{C_{XY}s - g_m} V_{out} = \frac{-V_{Thev}}{R_{Thev}}.$$

$$\Rightarrow \frac{V_{out}}{V_{Thev}}(s) = \frac{(C_{XY}s - g_m)R_L}{as^2 + bs + 1}, \quad a = R_{Thev}R_L(C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out})$$

$$b = (1 + g_m R_L)C_{XY}R_{Thev} + R_{Thev}C_{in} + R_L(C_{XY} + C_{out}).$$

More Analysis

$$\frac{V_{out}}{V_{Thev}}(s) = \frac{(C_{XY}s - g_m)R_L}{as^2 + bs + 1}, \quad \begin{aligned} a &= R_{Thev}R_L(C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out}) \\ b &= (1 + g_mR_L)C_{XY}R_{Thev} + R_{Thev}C_{in} + R_L(C_{XY} + C_{out}). \end{aligned}$$

There is a zero

$$\omega_z = \frac{g_m}{C_{XY}}.$$

Miller's theorem fails to predict this zero!!

Usually at very high frequency, so...OK!

There are two poles

$$as^2 + bs + 1 = \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1.$$

Suppose $\omega_{p2} \gg \omega_{p1}$ (dominant pole approximation) $b = \frac{1}{\omega_{p1}}$,

$$|\omega_{p1}| = \frac{1}{\underline{(1 + g_mR_L)C_{XY}R_{Thev} + R_{Thev}C_{in}} + \underline{R_L(C_{XY} + C_{out})}}.$$


$$|\omega_{p2}| = \frac{b}{a} = \frac{(1 + g_mR_L)C_{XY}R_{Thev} + R_{Thev}C_{in} + R_L(C_{XY} + C_{out})}{R_{Thev}R_L(C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out})}.$$

Example 11.18

In the CS stage, $R_S = 200\Omega$, $C_{GS} = 250\text{fF}$, $C_{GD} = 80\text{fF}$, $C_{DB} = 100\text{fF}$, $g_m = 1/(150\Omega)$, $\lambda=0$, $R_L = 2\text{k}\Omega$. Plot the frequency response with (a) Miller's approximation, (b) the exact transfer function, (c) the dominant-pole approximation.

Gain

$$g_m R_L = 13.3$$

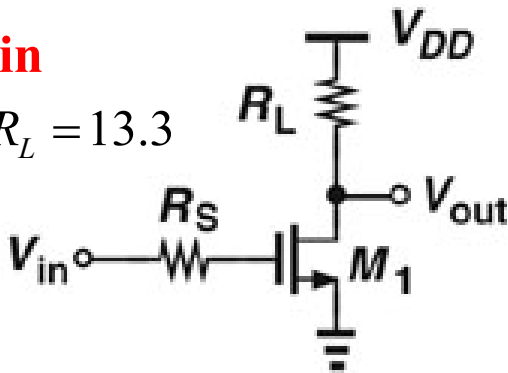

(a)

$$|\omega_{p,in}| = 2\pi \times (571\text{MHz})$$

$$|\omega_{p,out}| = 2\pi \times (428\text{MHz}).$$


(b) zero: $g_m/C_{GD} = 2\pi \times (13.3\text{GHz})$
 $a = 2.12 \times 10^{-20}\text{s}^{-2}$, $b = 6.39 \times 10^{-10}\text{s}$

$$|\omega_{p1}| = 2\pi \times (264\text{MHz})$$


$$|\omega_{p2}| = 2\pi \times (4.53\text{GHz}).$$

Very different!

(c) $|\omega_{p1}| = 2\pi \times (249\text{MHz})$
 $|\omega_{p2}| = 2\pi \times (4.79\text{GHz}).$

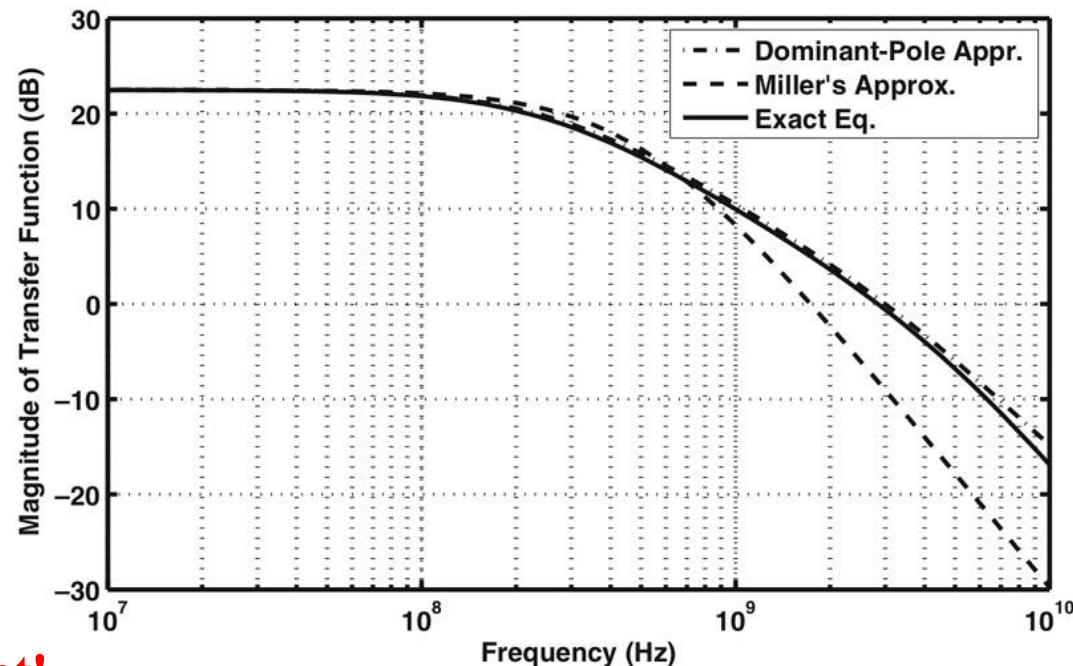

Input Impedance

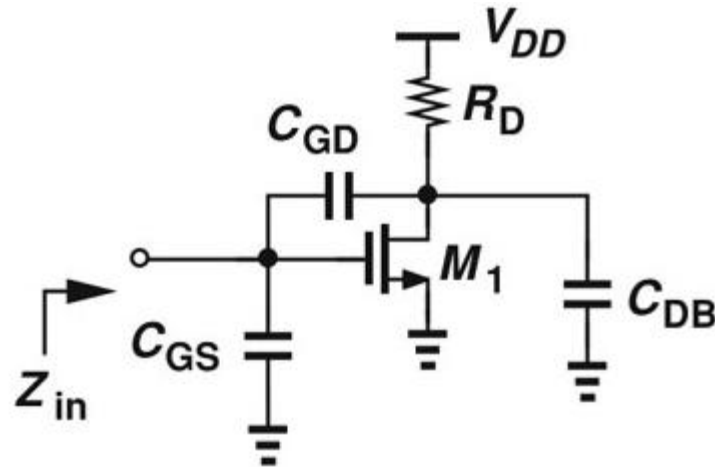


$$Z_{in} \approx \frac{1}{[C_{GS} + (1 + g_m R_D)C_{GD}]s}.$$

- With a high voltage gain, the Miller effect may substantially lower the input impedance at high frequencies

Frequency Response of CG

General CG stage

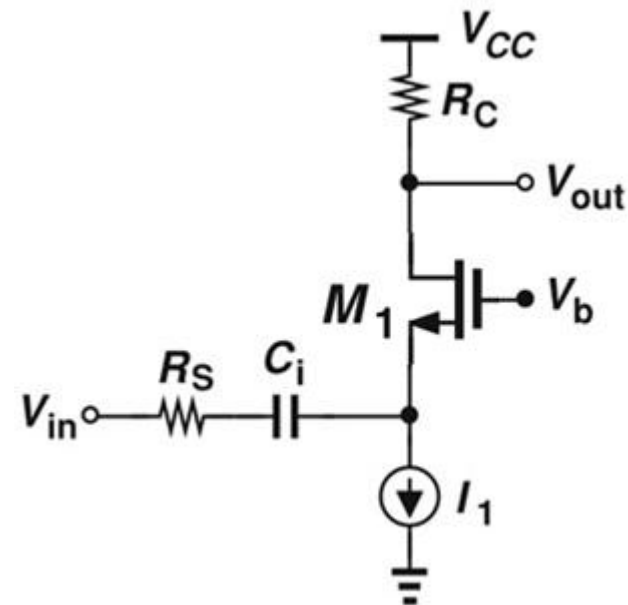


$$|\omega_p| = \frac{g_m}{(1 + g_m R_S) C_i}$$



$$\frac{1}{C_i s} \ll R_S + \frac{1}{g_m}$$

Frequency response

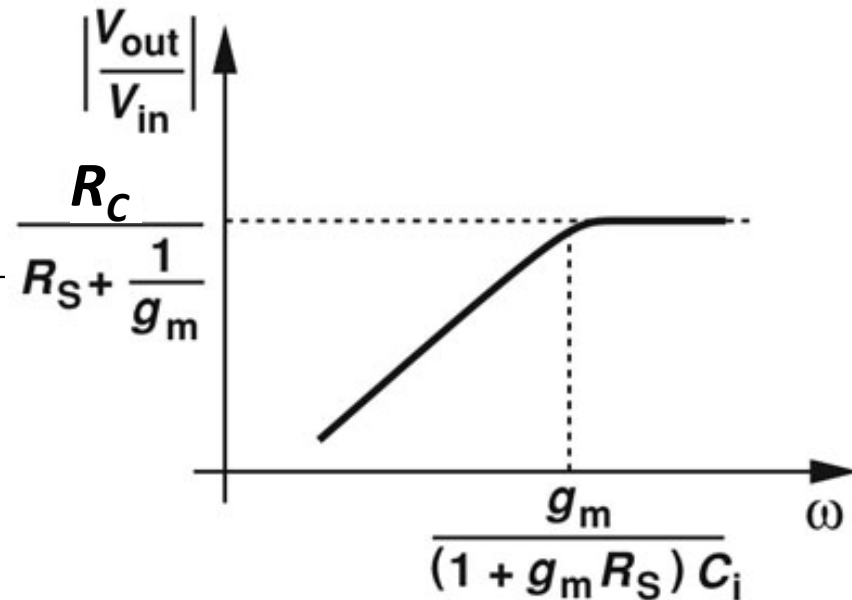


Midband gain: $R_C / (R_S + 1/g_m)$ **Slide 3-31**

Replace R_S with $R_S + (C_i s)^{-1}$

$$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{R_C}{R_S + (C_i s)^{-1} + 1/g_m} = \frac{g_m R_C C_i s}{(1 + g_m R_S) C_i s + g_m}$$

➤ **Capacitive coupling leads to low-frequency roll-off**

Frequency Response of CG

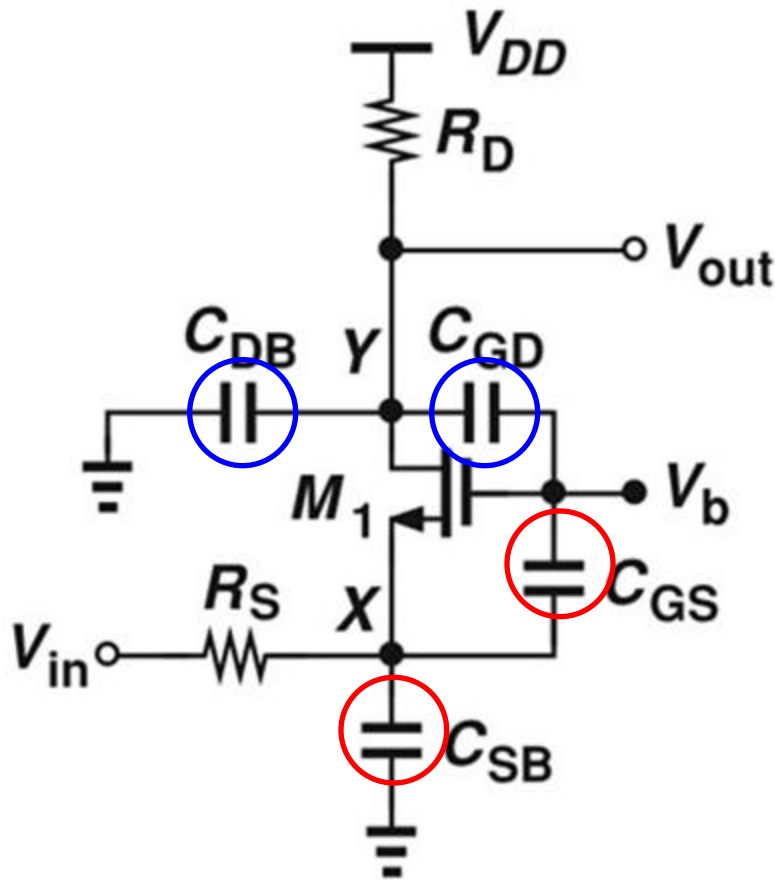

$$|\omega_{p,X}| = \frac{1}{\left(R_S \parallel \frac{1}{g_m}\right) C_X}, \approx \omega_T$$

$$|\omega_{p,Y}| = \frac{1}{R_D C_Y},$$


Node X (C_X): $C_{SB} + C_{GS}$ to ground

Node Y (C_Y): $C_{DB} + C_{GD}$ to ground

No capacitance between input and output: No Miller effect.

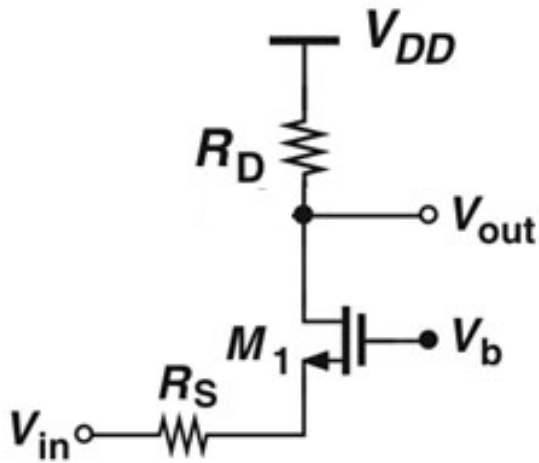Example 11.20

Plot the frequency response of the CG stage using 11.18 parameters.




$$\text{Gain} = R_D / (R_S + 1/g_m) = 5.7 < \text{CS} = 13.3$$

$$|\omega_{p,X}| = \frac{1}{\left(R_S \parallel \frac{1}{g_m}\right) C_X}, \quad |\omega_{p,Y}| = \frac{1}{R_D C_Y},$$


Limitation

$$|\omega_{p,X}| = 2\pi \times (5.31\text{GHz}) \quad |\omega_{p,Y}| = 2\pi \times (442\text{MHz}).$$

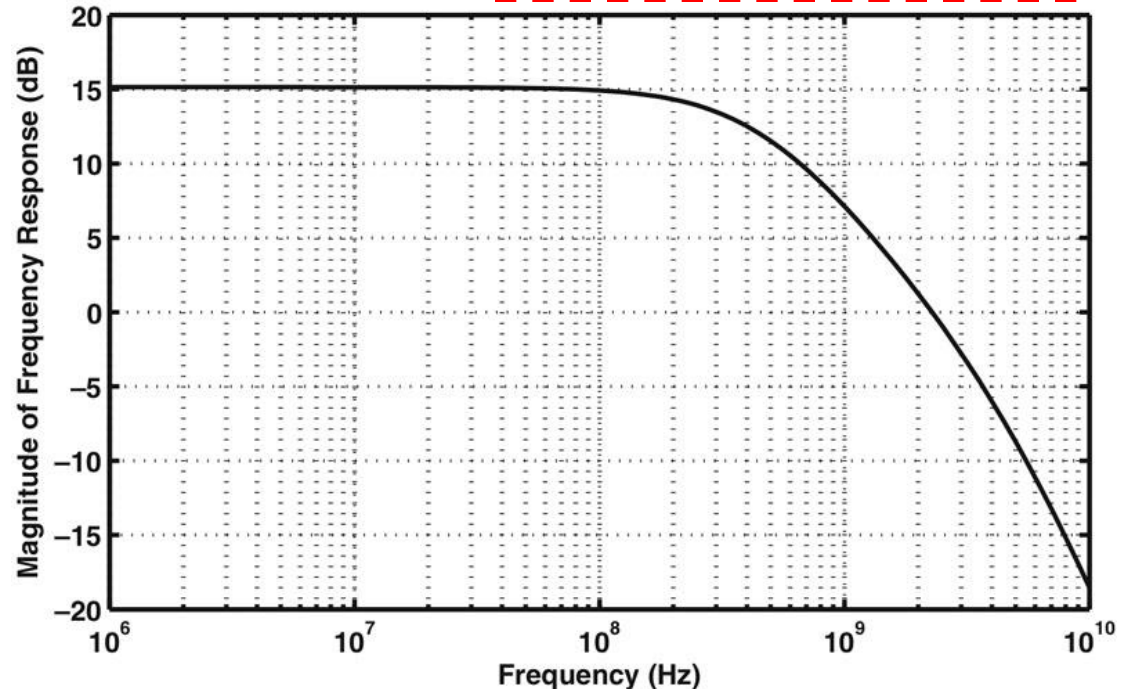

Frequency Response of SF

Source follower

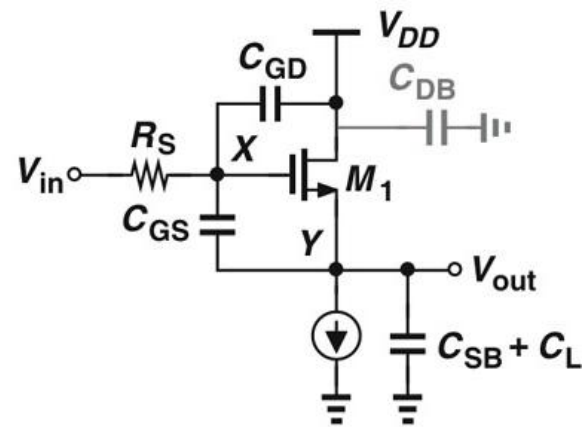

$$\text{Node } X: \frac{v_{out} + v_{GS} - v_{in}}{R_S} + (v_{out} + v_{GS})C_{GD}s + v_{GS}C_{GS}s = 0$$

$$\text{Output node: } v_{GS}C_{GS}s + g_mv_{GS} = v_{out}(C_{SB} + C_L)s$$




$$v_{GS} = \frac{v_{out}(C_{SB} + C_L)s}{C_{GS}s + g_m}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1 + \frac{C_{GS}}{g_m}s}{as^2 + bs + 1},$$

$$a = \frac{R_S}{g_m} [C_{GD}C_{GS} + C_{GD}(C_{SB} + C_L) + C_{GS}(C_{SB} + C_L)]$$

$$b = R_SC_{GD} + \frac{C_{GD} + C_{SB} + C_L}{g_m}.$$

Input Impedances of SF

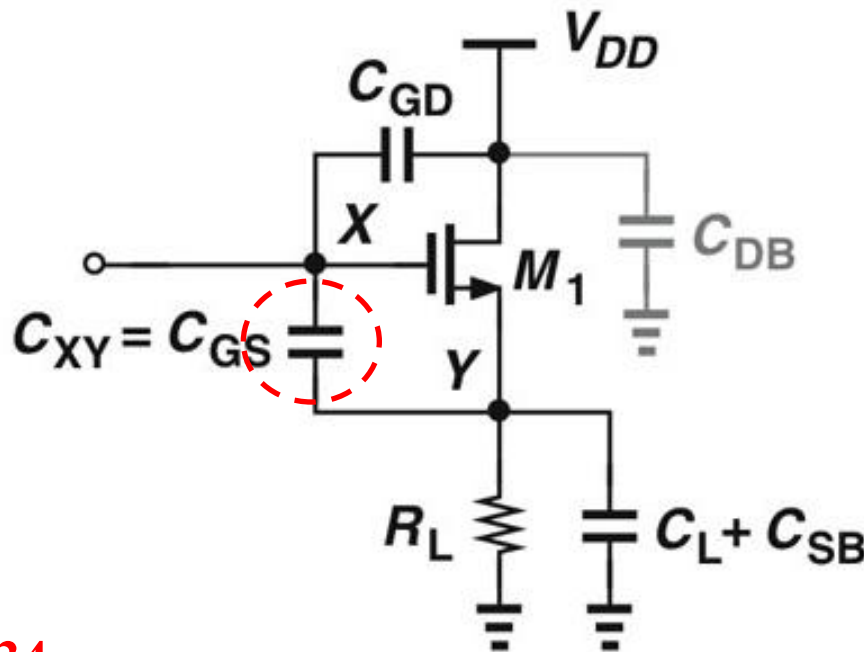


**Miller's
theorem!!**

Slide 3-34


$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}}, \quad C_X = (1 - A_v)C_{XY} = \frac{1}{1 + g_m R_L} C_{XY}.$$

$$C_{in} = C_{GD} + \frac{C_{GS}}{1 + g_m R_L}$$

Poles of MOSFET Cascode

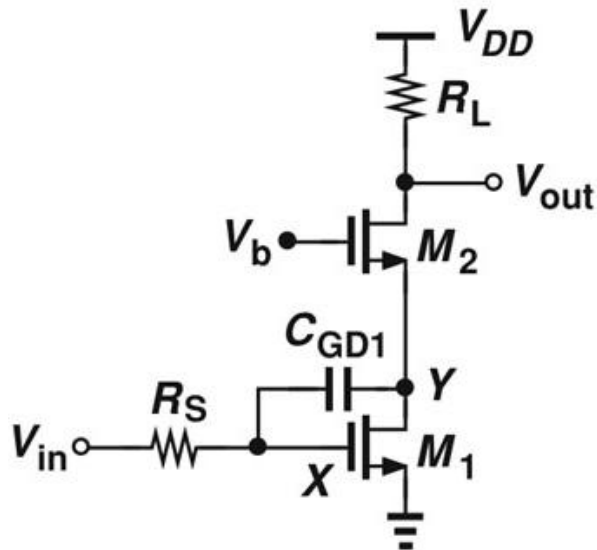
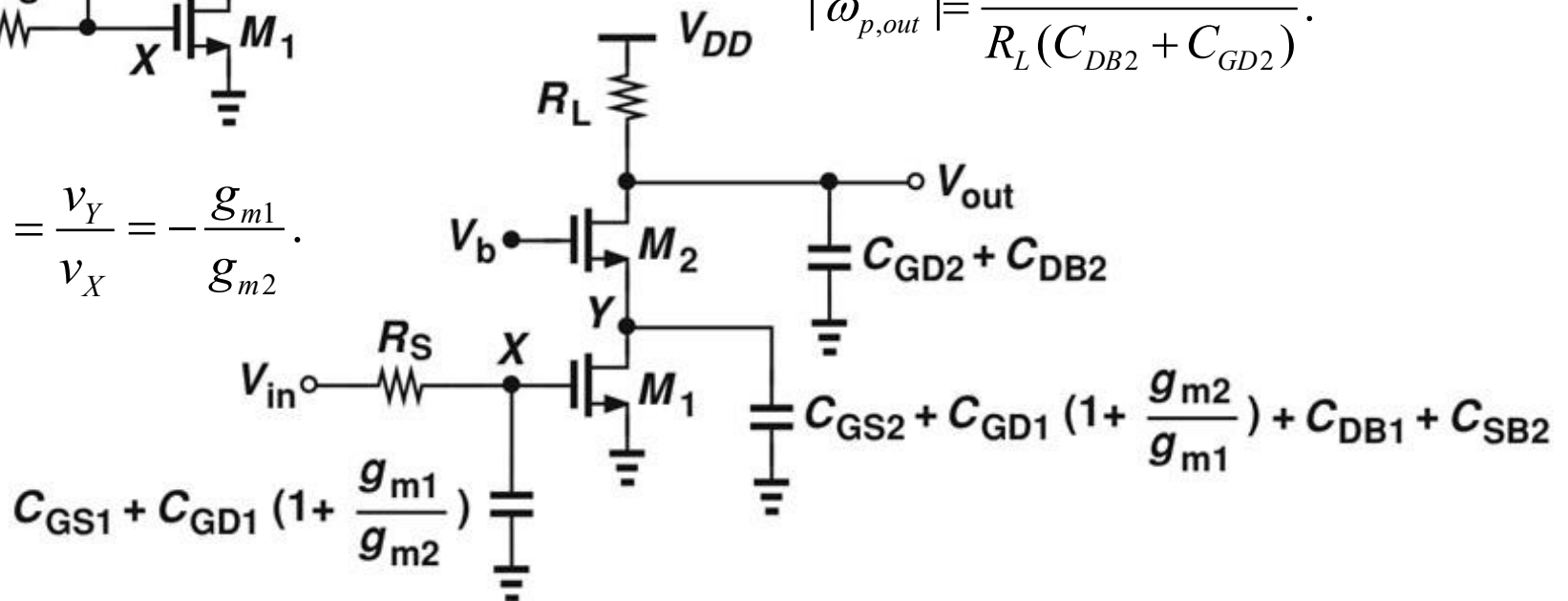
$$A_{v,XY} = \frac{v_Y}{v_X} = -\frac{g_{m1}}{g_{m2}}.$$




$$|\omega_{p,X}| = \frac{1}{R_S [C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}}\right) C_{GD1}]}$$

$$|\omega_{p,Y}| = \frac{1}{\frac{1}{g_{m2}} [C_{DB1} + C_{GS2} + \left(1 + \frac{g_{m2}}{g_{m1}}\right) C_{GD1} + C_{SB2}]}$$

$$|\omega_{p,out}| = \frac{1}{R_L (C_{DB2} + C_{GD2})}.$$


Input and Output Impedances

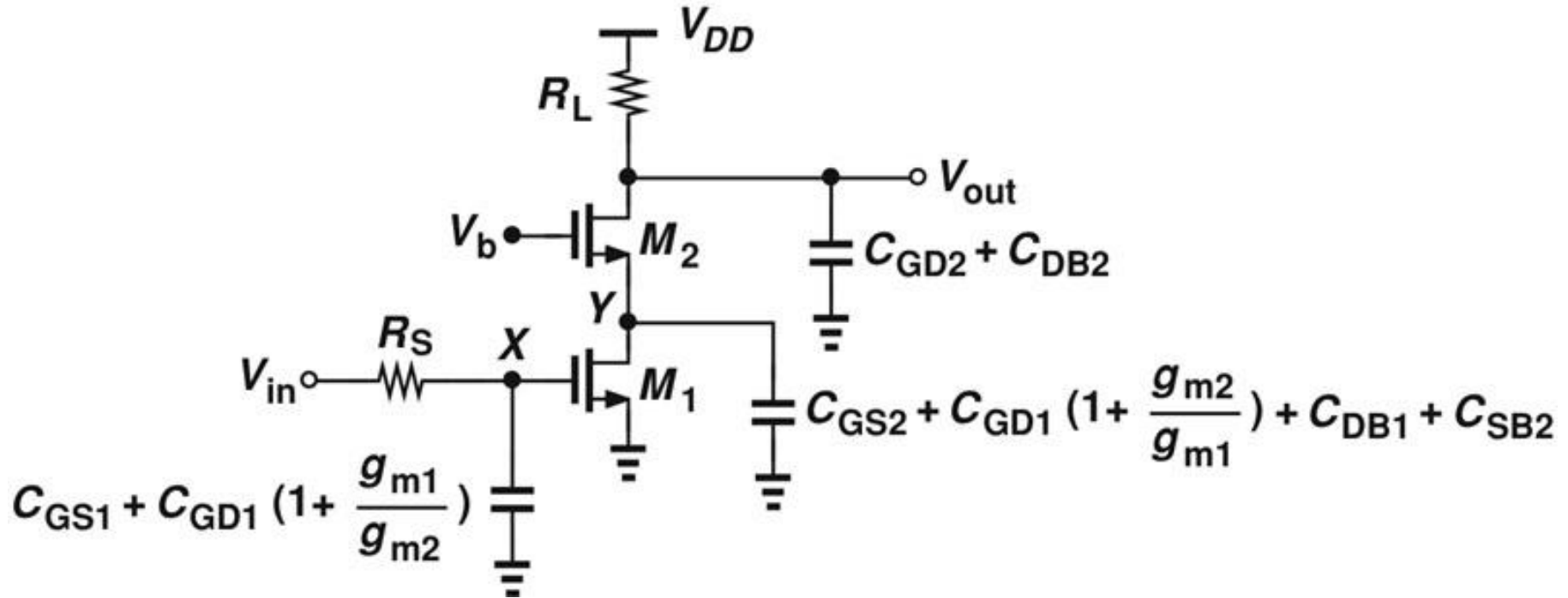


$$Z_{in} = \frac{1}{[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}}\right) C_{GD1}]s}$$

$$Z_{out} = \frac{1}{s(C_{GD2} + C_{DB2})} \parallel R_L$$

Frequency Response of DP

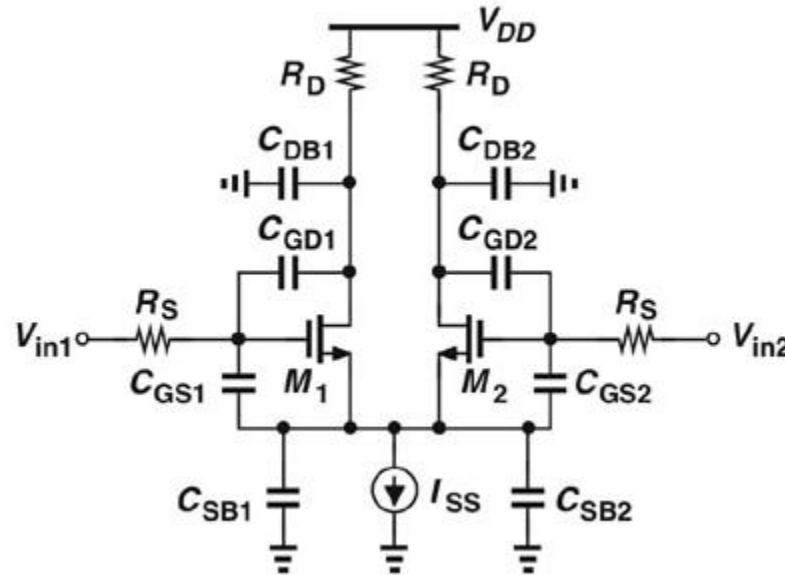

Half circuit

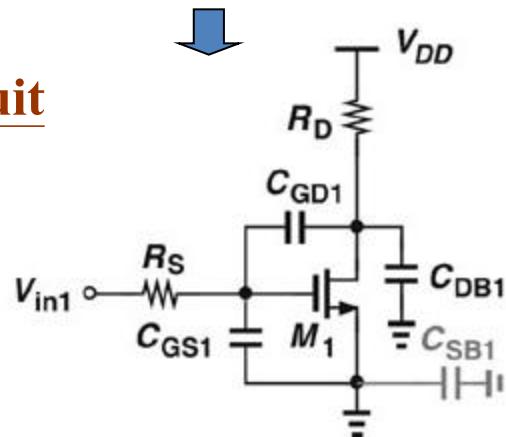


Slide 5-23

$$\frac{V_{out}}{V_{Thev}}(s) = \frac{(C_{XY}s - g_m)R_L}{as^2 + bs + 1},$$

Same as CS!


Common-Mode Frequency Response

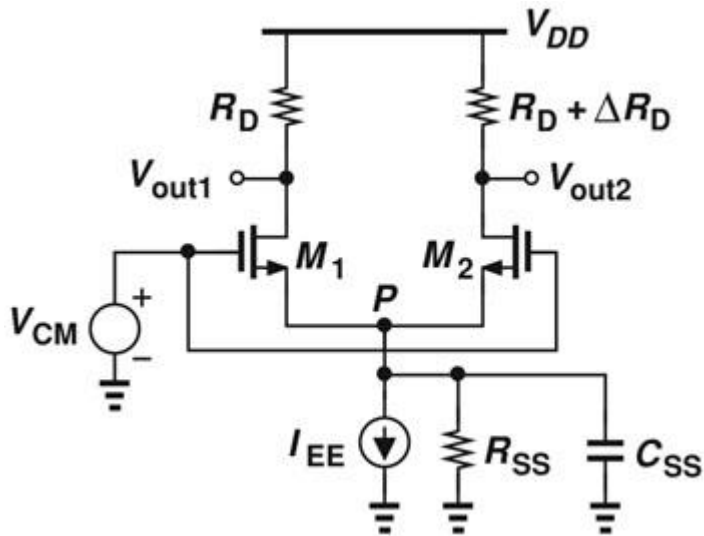


$$\left| \frac{\Delta V_{out}}{\Delta V_{CM}} \right| = \frac{\Delta R_D}{\frac{1}{g_m} + 2(R_{SS} \parallel \frac{1}{C_{SS}s})} = \frac{g_m \Delta R_D (R_{SS} C_{SS} s + 1)}{R_{SS} C_{SS} s + 2g_m R_{SS} + 1}.$$

$$2g_m R_{SS} \gg 1 \quad |\omega_z| = \frac{1}{R_{SS} C_{SS}} \quad |\omega_p| = \frac{2g_m}{C_{SS}},$$



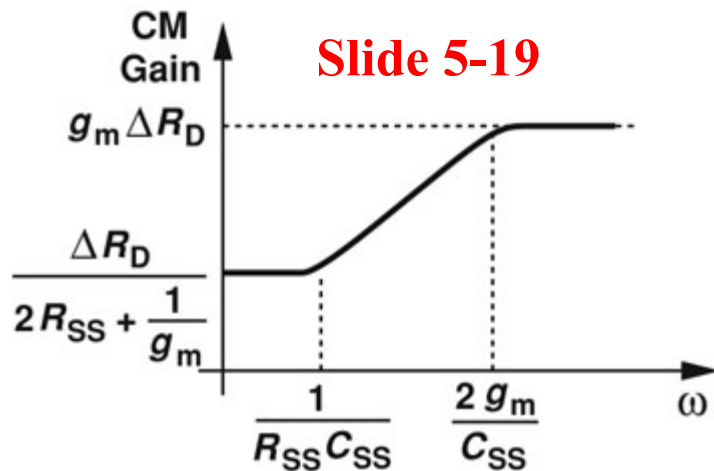
➤ C_{SS} will lower the total impedance between point P to ground at high frequency, leading to higher CM gain which degrades the CM rejection ratio.



Source of C_{SS}

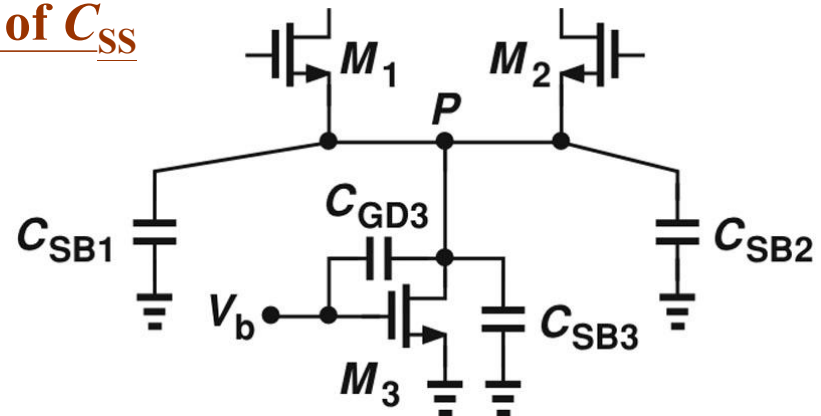

DP with Active Current Mirror

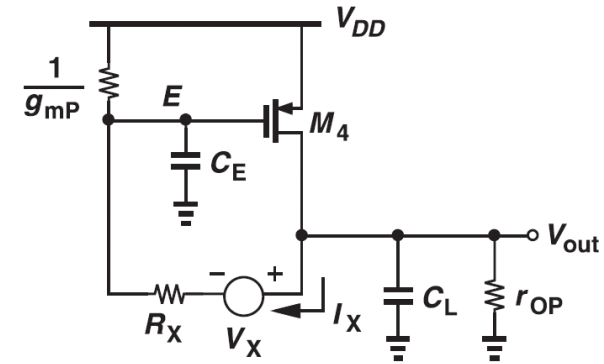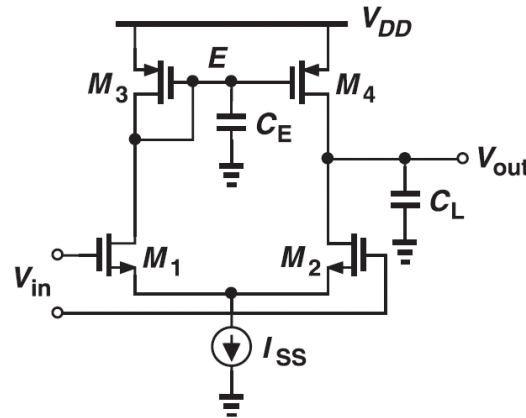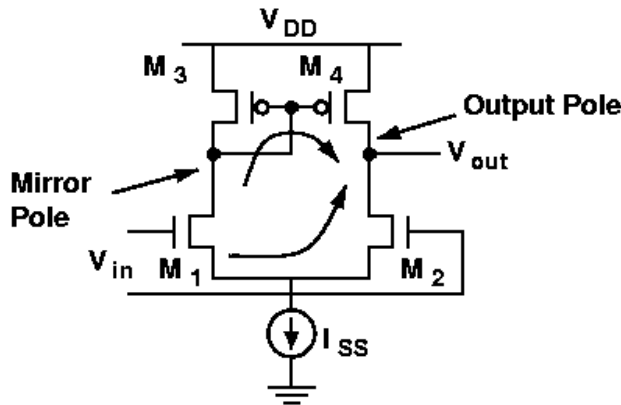

- This topology contains two signal paths with different transfer functions.
- Pole at node E (*Mirror pole*)

$$\omega_{pE} = \frac{g_{m3}}{C_E}, \quad C_E \approx C_{GS3} + C_{GS4} + C_{DB3} + C_{DB1} + 2C_{GD1} + g_{m4}(r_{O4} \parallel r_{O2})C_{GD4}$$

$$V_X = g_{mN}r_{ON}V_{in}, \quad R_X = 2r_{ON}, \quad V_E = (V_{out} - V_X) \frac{(C_E s + g_{mP})^{-1}}{(C_E s + g_{mP})^{-1} + R_X}, \quad -g_{m4}V_E - I_X = V_{out}(sC_L + r_{OP}^{-1})$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{mN}r_{ON}r_{OP}(2g_{mP} + sC_E)}{2r_{OP}r_{ON}C_EC_Ls^2 + [(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L]s + 2g_{mP}(r_{ON} + r_{OP})}$$

$$\omega_{p1} \approx \frac{2g_{mP}(r_{ON} + r_{OP})}{(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L} \approx \frac{1}{(r_{ON} \parallel r_{OP})C_L} \quad \text{if } 2g_{mP}r_{ON} \gg 1 \quad \omega_{p2} \approx \frac{g_{mP}}{C_E}$$

DP with Active Current Mirror

- To find zero

- Consider that the circuit consists of a “slow path” (M_1 , M_3 , and M_4) in parallel with a “fast path” (M_1 , and M_2)

- Slow path

$$A_{v1} = \frac{A_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)}$$


- Fast path

$$A_{v2} = \frac{A_0}{\left(1 + \frac{s}{p_1}\right)}$$


- We have

$$\frac{V_{out}}{V_{in}} = A_{v1} + A_{v2} = \frac{A_0}{1 + \frac{s}{p_1}} \left(1 + \frac{1}{1 + \frac{s}{p_2}}\right) = \frac{A_0 \left(2 + \frac{s}{p_2}\right)}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)} \Rightarrow z = 2p_2$$

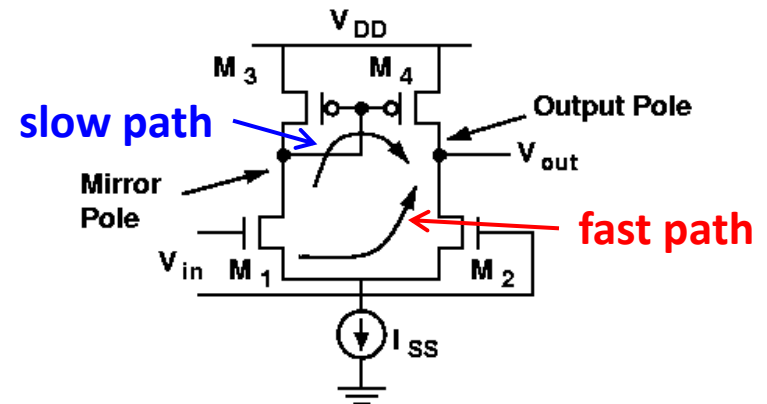- Fully differential pair has no mirror pole, which is better than differential-to-single ended amp.



G_m Frequency Response

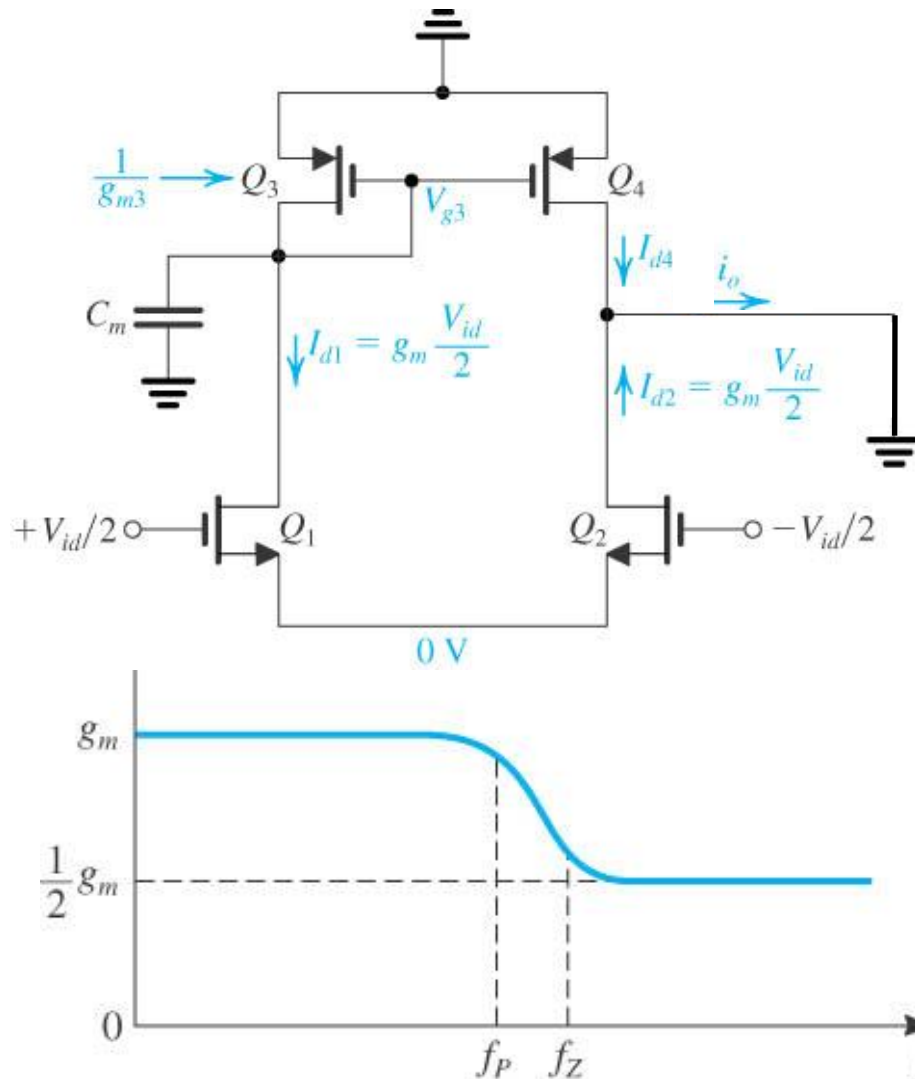

At low frequency: C_m is OPEN

$$i_{d4} = i_{d1} = g_m \frac{V_{id}}{2}, i_{d2} = g_m \frac{V_{id}}{2}$$

$$i_o = i_{d4} + i_{d2} = g_m V_{id}$$

$$G_m = i_o / V_{id} = g_m$$

At high frequency: C_m is SHORT

$$V_{g3} = 0, i_{d4} = 0, i_o = i_2 = g_m \frac{V_{id}}{2}$$

$$G_m = i_o / V_{id} = g_m / 2$$

G_m transfer function

$$G_m \equiv \frac{i_o}{V_{id}} = g_m \left(\frac{1 + sC_m / 2g_{m3}}{1 + sC_m / g_{m3}} \right)$$

$$f_P = \frac{g_{m3}}{2\pi C_m}, f_Z = \frac{2g_{m3}}{2\pi C_m}$$