

A close-up, high-contrast image of a green printed circuit board (PCB) with intricate white and gold circuit traces and various electronic components.

CHAPTER 6

Noise




Syllabus

- Basic physics of MOS transistors and their equivalent circuit models (ch. 6)
- Elementary gain stages (ch. 7, ch. 9, and ch. 10)
- Operational amplifier basics (ch. 8)
- Frequency responses (ch. 11)
- **Noise (ch.7, Design of analog CMOS ICs)**
- Feedback, stability and compensation (ch. 12)
- Operational amplifiers (ch.9, Design of analog CMOS ICs)

Outline

- 1. Statistical Characteristics of Noise**
2. Types of Noise
3. Representation of Noise in Circuits
4. Noise in Single-Stage Amplifiers
5. Noise in Differential Pairs

Statistical Behavior of Noise

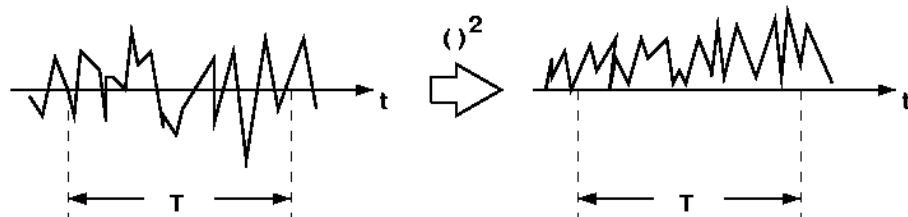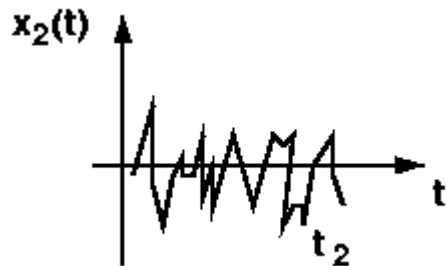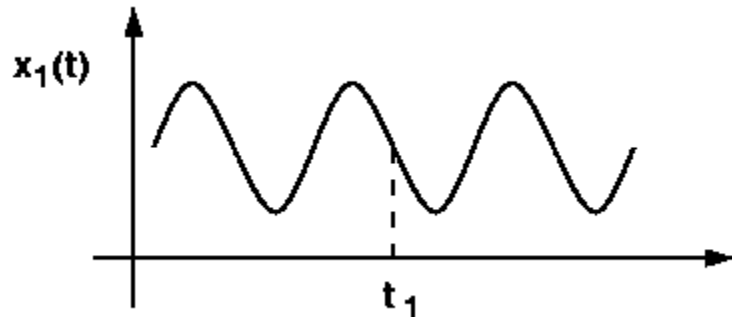

- Noise is a random process.
 - The value of noise can not be predicted at any time even if the past values are known.
 - Observe the noise for a long time and using the measured results to construct a “statistical model”.
 - In many cases, the average power of noise is predictable.


$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} \frac{v^2(t)}{R_L} dt = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} x^2(t) dt$$

unit : (V²) in stead of (W)

Normalize the area under waveform to T

Noise Spectrum

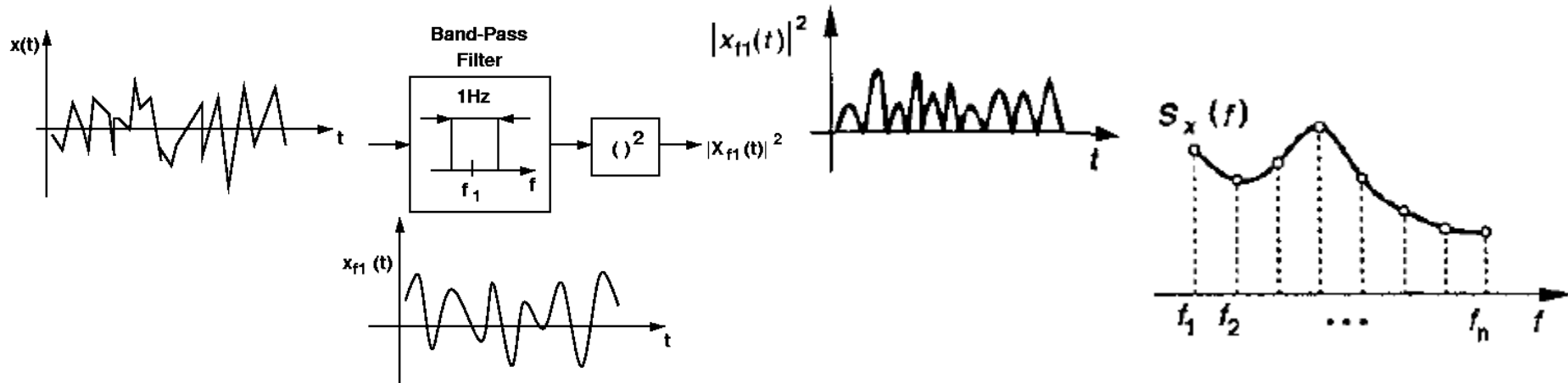
- The concept of noise power becomes more versatile if defined with regard to the *frequency content of noise* – *Power spectral density (PSD)*



- The PSD, $S_x(f)$, of a noise waveform $x(t)$ is defined as the average power carried by $x(t)$ in a one-Hertz bandwidth around f , expressed in V^2/Hz .
- The square root of $S_x(f)$ expressed in $V / \sqrt{Hz}$.
- Input noise = $3n \text{ V} / \sqrt{Hz}$ at 100Mhz means average power in a 1Hz bandwidth at 100Mhz = $(3e-9)^2 V^2$.



Spectral Shaping

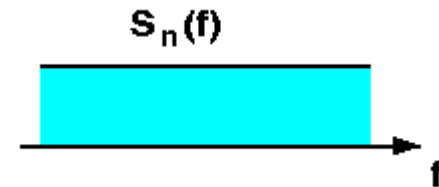- White noise – the PSD displays the same value at all frequencies.




- If a signal with spectrum $S_x(f)$ is applied to a linear time-invariant system with transfer function $H(s)$, then the output spectrum is given by

$$S_Y(f) = S_X(f) |H(f)|^2 \quad \text{where} \quad H(f) = H(s = j2\pi f)$$

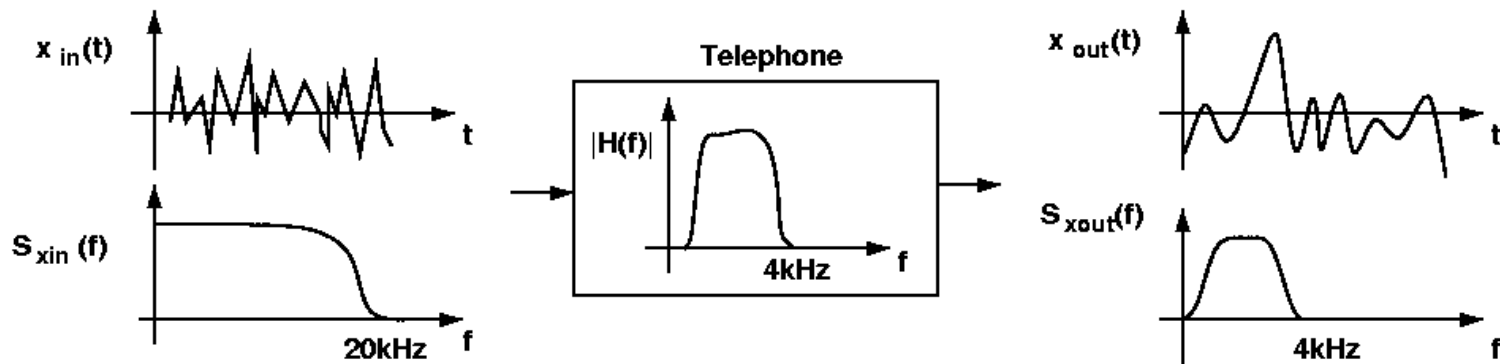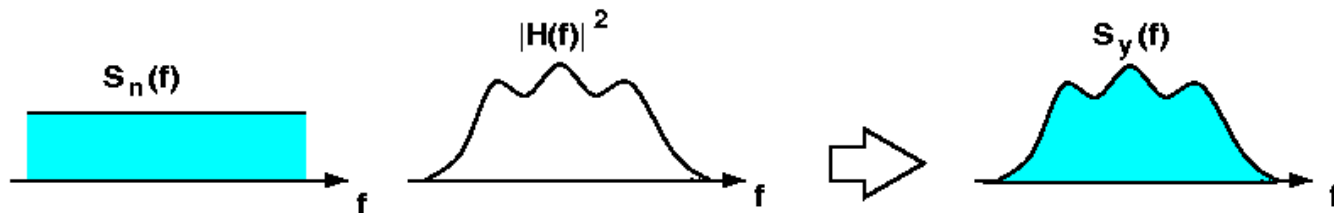


Noise Spectra

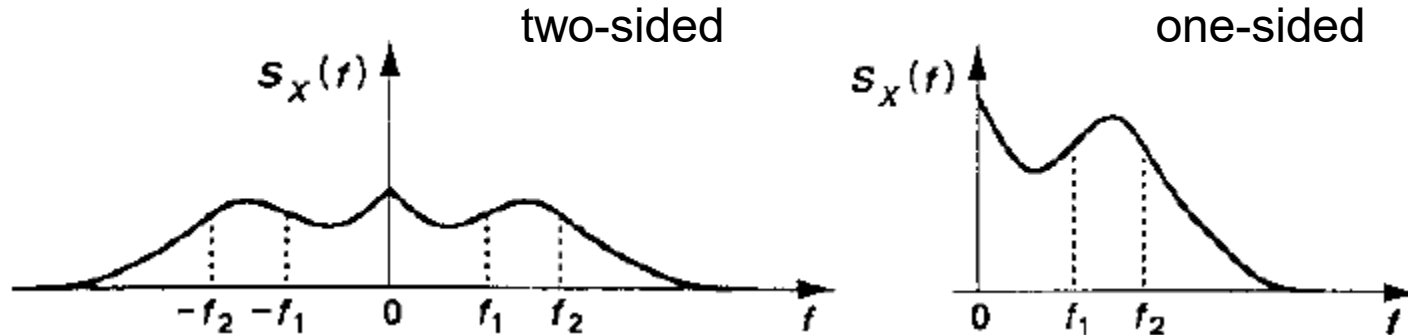- Since $S_x(f)$ is an even function of f for real $x(t)$.



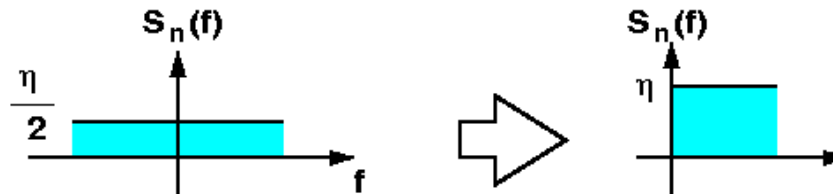
- The negative frequency part of the spectrum is folded around the vertical axis and added to the positive frequency part.



$$P_{f_1, f_2} = \int_{-f_2}^{-f_1} S_X(f) df + \int_{f_1}^{f_2} S_X(f) df = 2 \int_{f_1}^{f_2} S_X(f) df$$

Amplitude Distribution

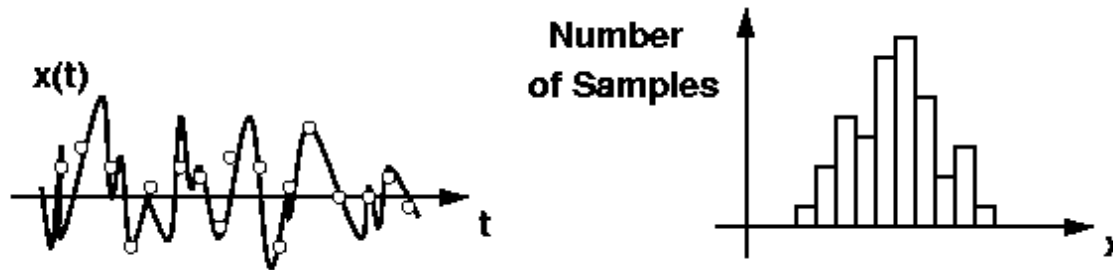- Distribution of amplitude – *Probability density function (PDF)*.
- The distribution of $x(t)$ is defined as
 - $p_x(x)dx = \text{probability of } x < X < x + dx$, X is the measured value of $x(t)$




- *Gaussian (Normal) Distribution*
 - The *central limit theorem* states that if many independent random process with arbitrary PDFs are added, the PDF of the sum approaches a *Gaussian distribution*.
 - The *Gaussian PDF is defined as*
$$p_x(f) = \frac{1}{\sigma\sqrt{2\pi}} \exp \frac{-(x-m)^2}{2\sigma^2}$$

Correlated and Uncorrelated Sources


- For deterministic voltages and currents, use the superposition principle.
- In noise analysis, the average noise power is of interest.

$$\begin{aligned} P_{av} &= \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} [x_1(t) + x_2(t)]^2 dt \\ &= \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} x_1^2(t) dt + \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} x_2^2(t) dt + \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} 2x_1(t)x_2(t) dt \\ &= P_{av1} + P_{av2} + \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} 2x_1(t)x_2(t) dt \end{aligned}$$

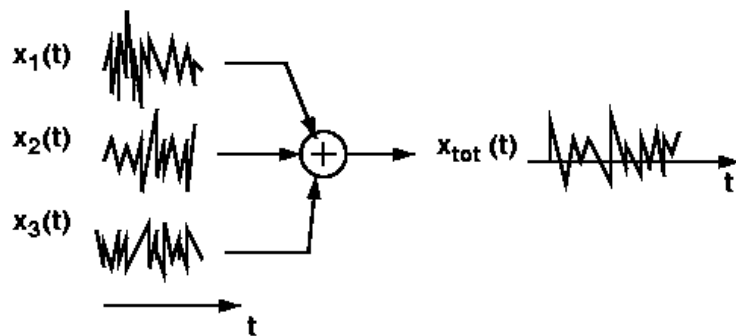- P_{av1} and P_{av2} denote the average power of $x_1(t)$ and $x_2(t)$.
- The third term is the “**correlation**” between $x_1(t)$ and $x_2(t)$.
- If generated by independent devices, the correlation = 0.



uncorrelated noise

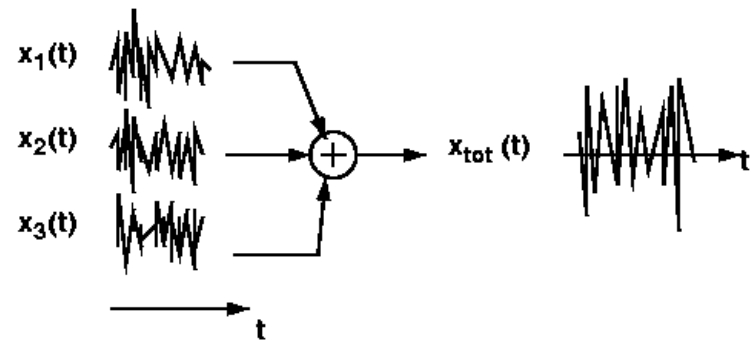

correlated noise

Outline


1. Statistical Characteristics of Noise
- 2. Types of Noise**
3. Representation of Noise in Circuits
4. Noise in Single-Stage Amplifiers
5. Noise in Differential Pairs

Types of Noise

- Device electronics
 - Thermal noise
 - Flicker noise
- Environmental noise
 - Supply
 - Ground
 - Substrate

Thermal Noise

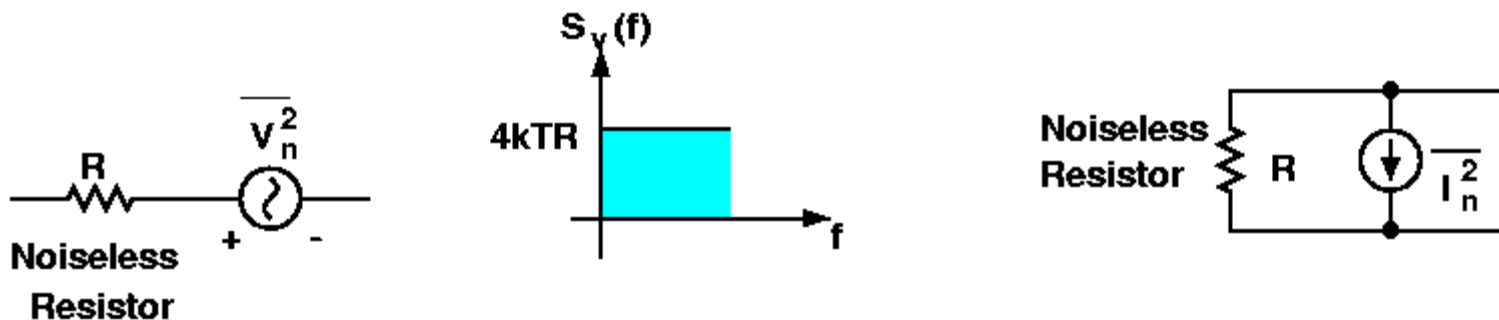- Thermal noise (white noise)
 - Resistor thermal noise - the random motion of electrons in a conductor introduces fluctuations in the voltage measured across the conductor even if the average current is zero.
 - The spectrum of thermal noise is proportional to the absolute temperature.



$$S_v(f) = 4kTR \text{ (V}^2/\text{Hz)} \quad f \geq 0, \quad \overline{V_n^2} = 4kTR \times 1\text{Hz (V}^2), \quad k = 1.38 \times 10^{-23} \text{ (J / K)} \text{ Boltzmann constant}$$


- Example : a $50 \, \Omega$ resistor at $T = 300^\circ \text{K}$ exhibits $8.28 \times 10^{-19} \text{ V}^2/\text{Hz}$ of thermal noise, or $0.91 \text{ nV}/\sqrt{\text{Hz}}$
- The thermal noise of a resistor can be represented by a parallel current source as well.

$$\overline{I_n^2} = 4kT / R \text{ (A}^2 / \text{Hz)}$$

Thermal Noise

- The thermal noise is white. In reality, $S_v(f)$ is flat for up to roughly 100 THz, dropping at higher frequencies.
- The polarity used for the voltage source is unimportant.

Thermal Noise

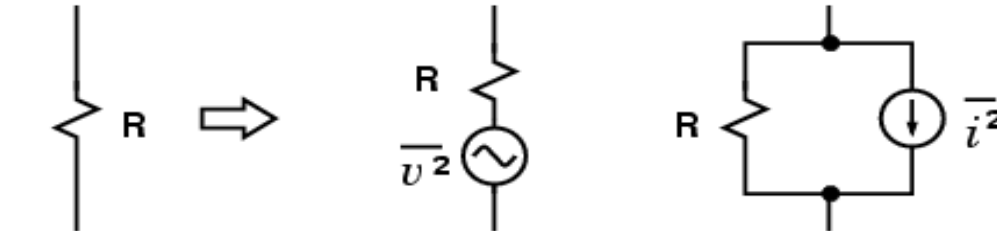


T = Absolute temperature in Kelvins
 k = 1.38×10^{-23} watt/K-Hz (Boltzmann's constant)
 Δf = Bandwidth per Hertz

$$\frac{\overline{v^2}}{\Delta f} = 4kTR$$

$$\frac{\overline{i^2}}{\Delta f} = 4kT \frac{1}{R}$$

$$f = 0 - \infty$$

Noise Spectrum Shaping : LP Filter

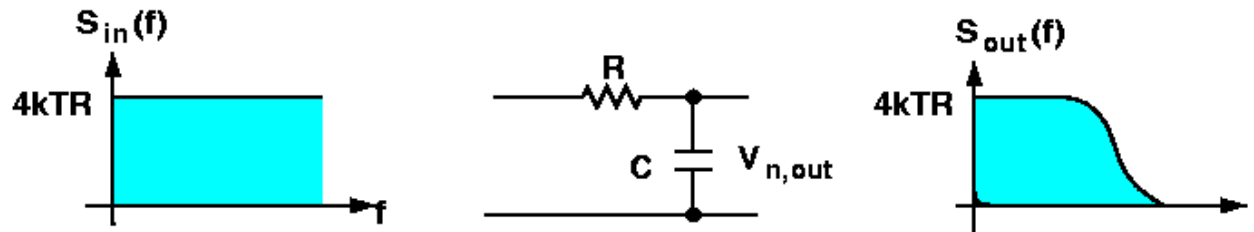

- Modeling the noise of R by a series voltage source V_R . The transfer function from V_R to V_{out}

$$\frac{V_{out}}{V_R}(s) = \frac{1}{1 + sRC}$$

- We have

$$S_{out}(f) = S_R(f) \left| \frac{V_{out}}{V_R}(j\omega) \right|^2 = 4kTR \frac{1}{4\pi^2 R^2 C^2 f^2 + 1}$$

- The total noise power at the output

$$P_{n,out} = \int_0^\infty \frac{4kTR}{4\pi^2 R^2 C^2 f^2 + 1} df = \frac{2kT}{\pi C} \tan^{-1} u \Big|_{u=0}^{u=\infty} = \frac{kT}{C} \text{ (V}^2\text{)} \quad \text{for} \quad \int \frac{dx}{x^2 + 1} = \tan^{-1} x$$


- Example : for a 1 pF capacitor, the total noise voltage is equal to $64.3 \mu\text{V}_{\text{rms}}$.
- The total noise at the output of the circuit is independent of the value R .
- Low temperature operation can decrease noise in analog circuits. The mobility of charge carriers in MOS devices also increase at low temperatures.

Thermal Noise in MOSFET

- For long-channel MOS devices operating in saturation region, the channel noise can be modeled by


$$\overline{I_n^2} = 4kT\gamma g_m$$

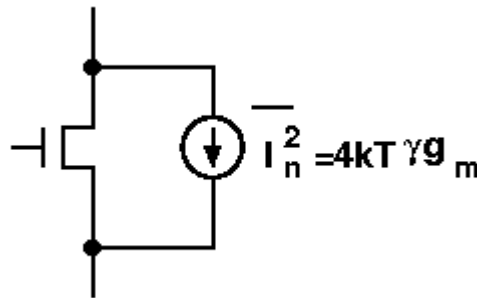- The coefficient γ is derived to be equal to $2/3$ for long channel transistors and may need to be replaced by a larger value for submicron MOSFETs. (ex. 2.5 for 0.25-um MOS devices)




Thermal Noise in MOSFET

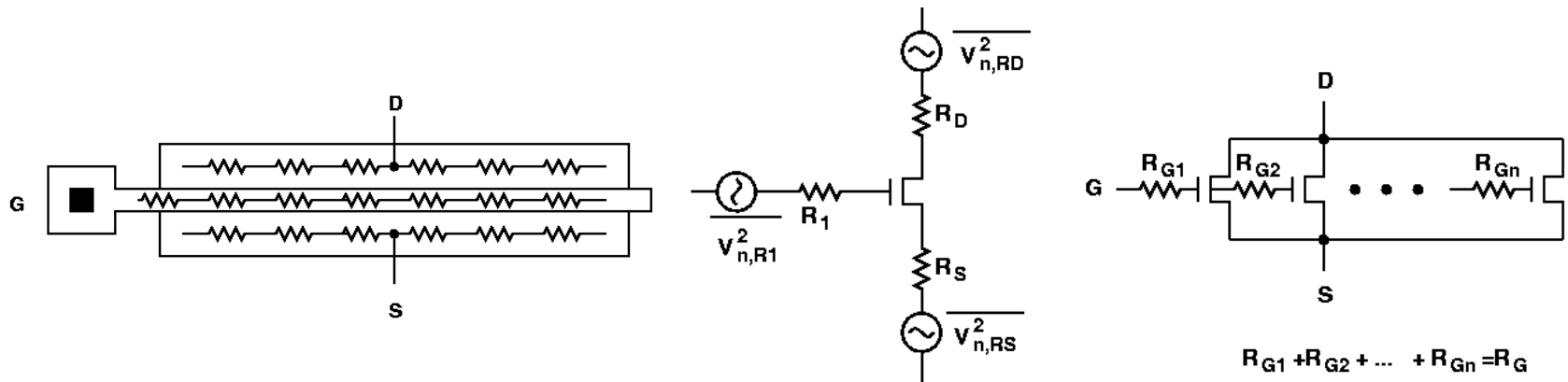- The ohmic sections of a MOSFET also contribute thermal noise.
- For a relatively wide transistor, the gate distributed resistance may become noticeable.





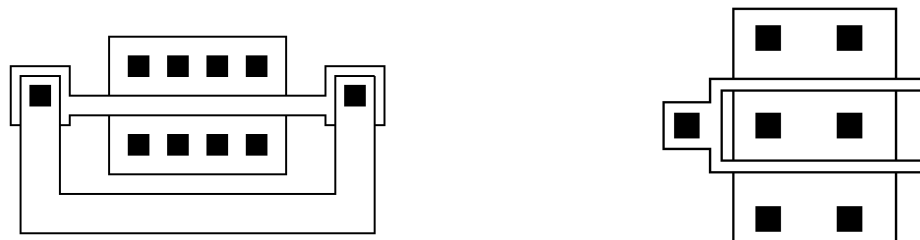- A lumped resistor R_1 represents the distributed gate resistance. $R_1 = R_G / 3$
- Reduction of gate resistance by adding contacts to both sides or folding.



Flicker Noise

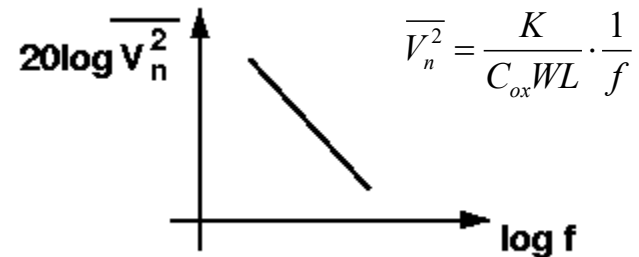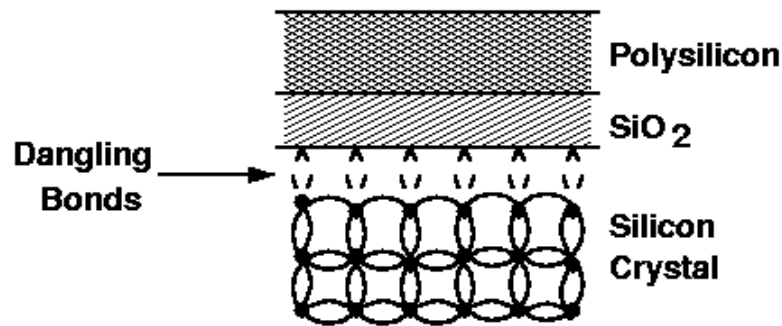- Since the silicon crystal reaches an end at the interface, many dangling bonds appear, give rise to extra energy states.
- As carriers move to the interface, some are randomly trapped and later released by such energy states, introducing “flicker” noise in the drain current.




- The flicker noise is modeled as a voltage source series with the gate :

$$\overline{V_n^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}, \quad WL \uparrow, \quad f \uparrow, \quad \overline{V_n^2} \downarrow$$

- Where K is a process-dependent constant on the order of $10^{-25} \text{ V}^2 \text{ F}$.
- Our notation assumes a bandwidth of 1 Hz .
- The trap-and-release phenomenon occurs at low frequencies more often. ($1/f$ noise)
- PMOS devices exhibits less $1/f$ noise than NMOS.

Flicker Noise Corner Frequency

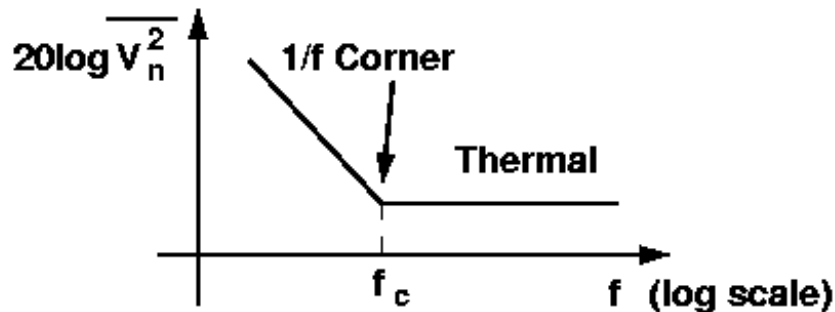
- As f approaches DC, noise becomes indistinguishable from thermal drift or aging of devices.
- Corner frequency : the intersection point serves as a measure of what part of the band is mostly corrupted by flicker noise.



$$4kT\left(\frac{2}{3}g_m\right) = \frac{K}{C_{ox}WL} \cdot \frac{1}{f_c} \cdot g_m^2$$
$$f_c = \frac{K}{C_{ox}WL} g_m \frac{3}{8kT}$$

- f_c generally depends on device dimensions and bias current. However, for a given L , the dependence is relatively weak.
- The $1/f$ noise corner is relatively constant, falling in the vicinity of 500 kHz to 1 MHz for submicron transistors.

Noise Bandwidth

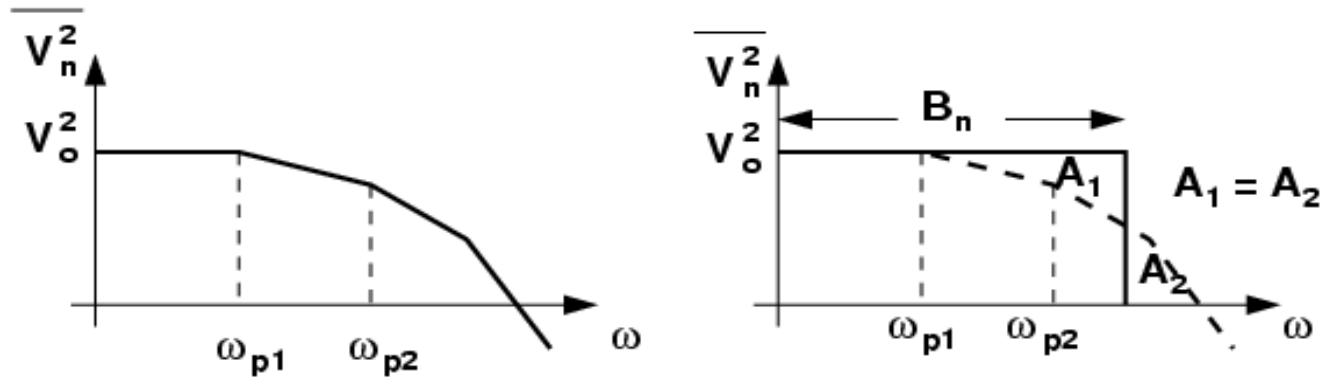

- Noise bandwidth B_n : allows a fair comparison of circuits that exhibit the same low-frequency noise V_o^2 , but different high-frequency transfer functions.

$$\overline{V_{n,out,tot}^2} = \int_0^{\infty} \overline{V_{n,out}^2} df, \quad V_o^2 \bullet B_n = \int_0^{\infty} \overline{V_{n,out}^2} df, B_n \equiv \text{Noise Bandwidth}$$

- The total noise must be evaluated by calculating the total area under the spectral density, for a single-pole filter


$$H(s) = (1 + s / \omega_0)^{-1}, B_n = \int_0^{\infty} |H(j2\pi f)|^2 df = \int_0^{\infty} \left[1 + \left(\frac{f}{f_0} \right)^2 \right]^{-1} df = \frac{\pi}{2} f_0$$

Outline


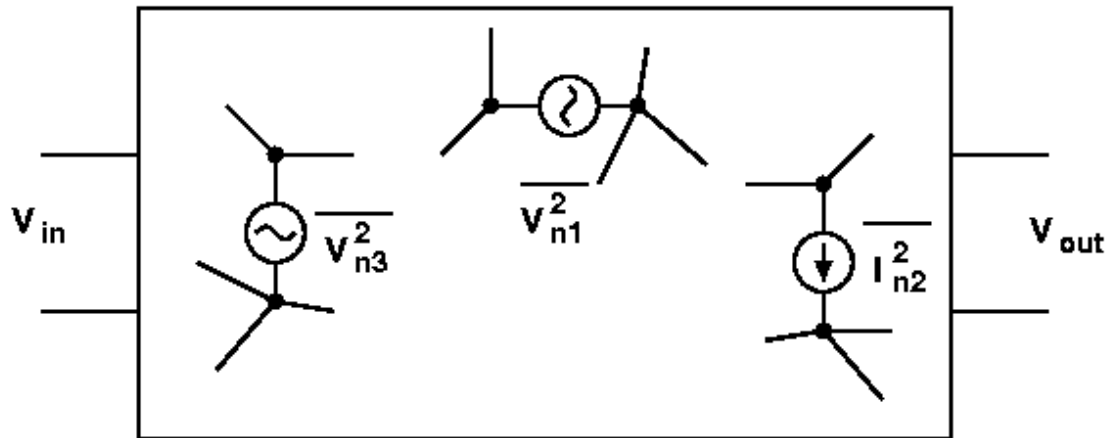
1. Statistical Characteristics of Noise
2. Types of Noise
- 3. Representation of Noise in Circuits**
4. Noise in Single-Stage Amplifiers
5. Noise in Differential Pairs

Representation of Noise in Circuits

- Set the input to zero and calculate the total noise at the output due to various sources of noise in the circuit.




Representation of Noise in Circuits

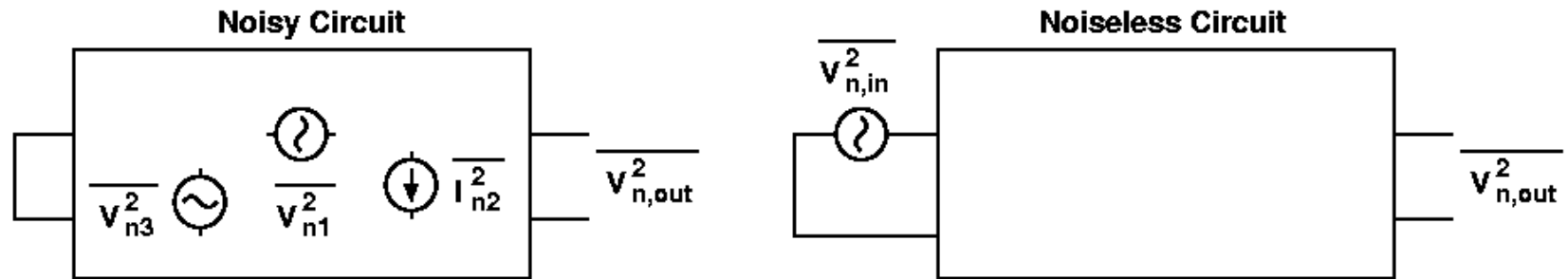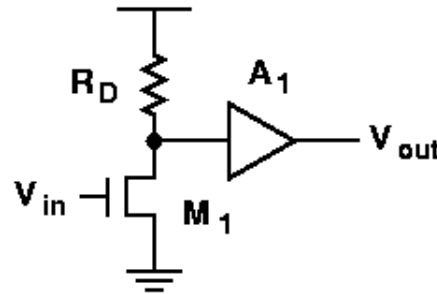


- A_1 amplifies the noise and signal also at the output.
- **Input referred noise** : to represent the effect of all noise sources in the circuit by a single source, $\overline{V_{n,in}^2}$.
 - If the voltage gain is A_v , then we must have $\overline{V_{n,out}^2} = A_v^2 \overline{V_{n,in}^2}$
 - Indicating how much the input signal is corrupted by the circuit's noise.

Representation of Noise by V/I Sources

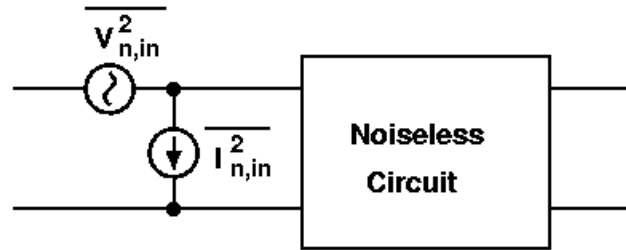
- Consider two extreme cases : zero and infinite source impedances.



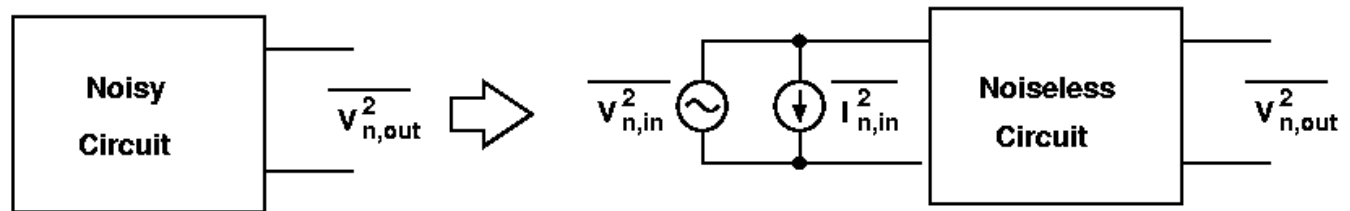- If the source impedance is zero, $\overline{I_{n,in}^2}$ flows through $\overline{V_{n,in}^2}$ and has no effect on the output.



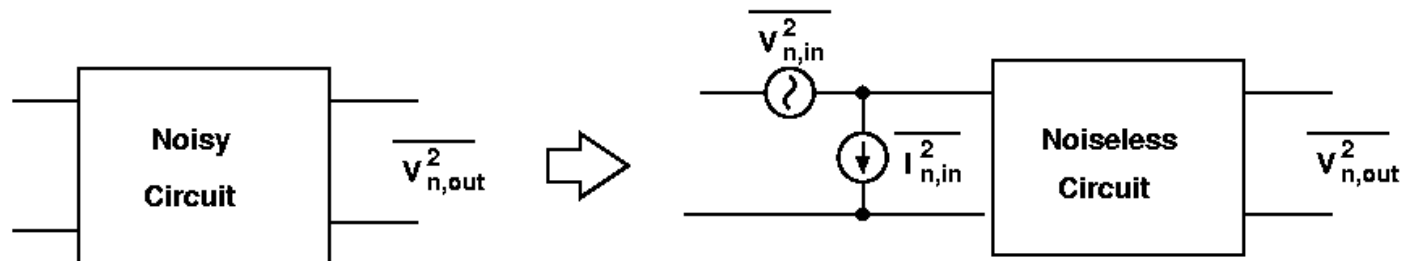- If the input is open, then $\overline{V_{n,in}^2}$ has no effect and the $\overline{V_{n,out}^2}$ is due to only $\overline{I_{n,in}^2}$



Outline

1. Statistical Characteristics of Noise
2. Types of Noise
3. Representation of Noise in Circuits
- 4. Noise in Single-Stage Amplifiers**
5. Noise in Differential Pairs



Common Source Stage

- The input-referred noise voltage per unit bandwidth of CS



$$\overline{V_{n,in}^2} = 4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox}WL} \frac{1}{f}$$

- To reduce the input-referred noise voltage

- The g_m of M_1 must be maximized if the transistor is to amplify a voltage signal applied to its gate.
- If $g_{m1} \uparrow \rightarrow I_D \uparrow \rightarrow$ greater power dissipation and limited voltage swings.
- If $g_{m1} \uparrow \rightarrow W/L \uparrow \rightarrow$ larger input and output capacitance.
- The transconductance of M_1 must be minimized if the transistor operates as a current source.
- Noise contributed by R_D decreases as R_D increases.
 - Limiting the voltage headroom and lowering the speed.
- The noise voltage due to R_D at the output proportional to $(R_D)^{0.5}$
- The voltage gain of the circuit is proportional to R_D .
- Trade-off between noise, power dissipation, voltage headroom, and speed.

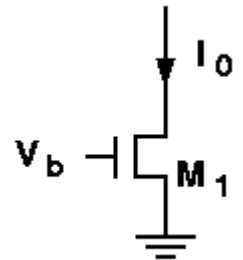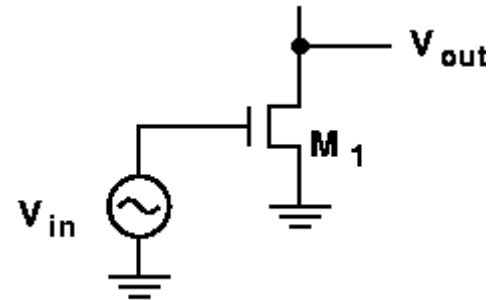

SNR of CS Stage

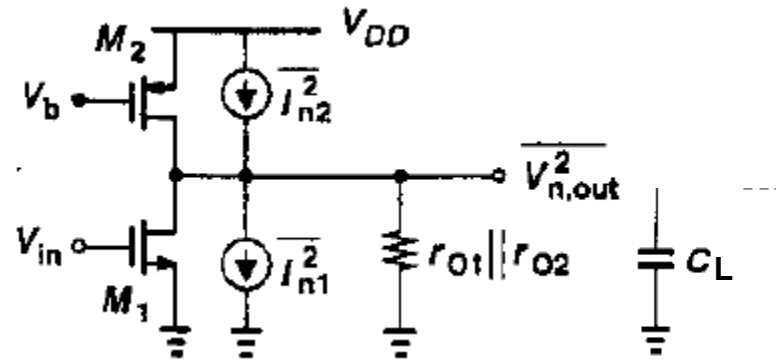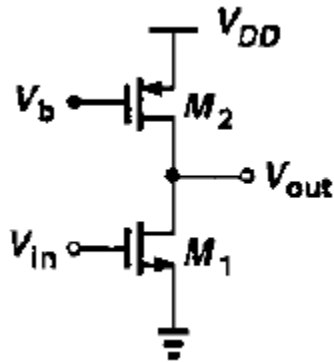


$$\overline{V_{n,out}^2} = 4kT \frac{2}{3} (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})^2 = \overline{V_{n,in}^2} (g_{m1})^2 (r_{O1} \parallel r_{O2})^2, \quad \overline{V_{n,in}^2} = 4kT \frac{2}{3} \frac{(g_{m1} + g_{m2})}{(g_{m1})^2}$$

$$\overline{V_{n,out,tot}^2} = \int_0^\infty 4kT \frac{2}{3} (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})^2 \frac{df}{1 + (r_{O1} \parallel r_{O2})^2 C_L^2 (2\pi f)^2} = \frac{2}{3} (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2}) \frac{kT}{C_L}$$

$$SNR_{out} = \left[\frac{g_{m1}(r_{O1} \parallel r_{O2})V_m}{\sqrt{2}} \right]^2 \frac{1}{(2/3)(g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})(kT / C_L)} = \frac{3C_L}{4kT} \frac{g_{m1}^2(r_{O1} \parallel r_{O2})}{g_{m1} + g_{m2}} V_m^2$$

- $C_L \uparrow$ bandwidth $\downarrow$ $SNR \uparrow$
- $g_{m1} \uparrow$ $g_{m2} \downarrow$ $V_m \uparrow$ $SNR \uparrow$ (V_m : amplitude of sinusoid input)


Common-Gate Stage

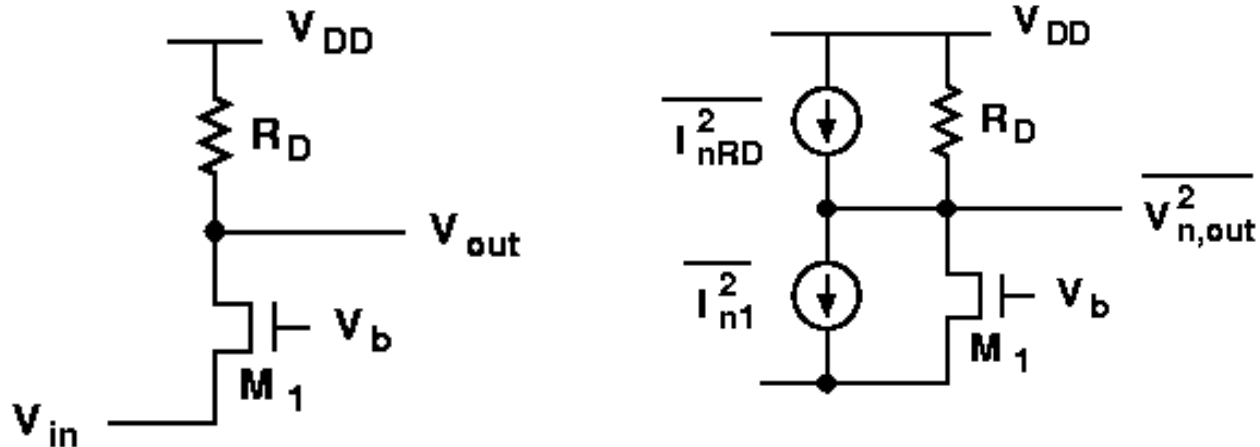


- Neglect channel length modulation effect. Represent the thermal noise of M_1 and R_D by two current sources.
- Due to low input impedance of CG, the input-referred noise current is not negligible at low frequencies
- They directly refer the noise current produced by the load to the input (current-gain = 1).

Input-referred Noise of CG

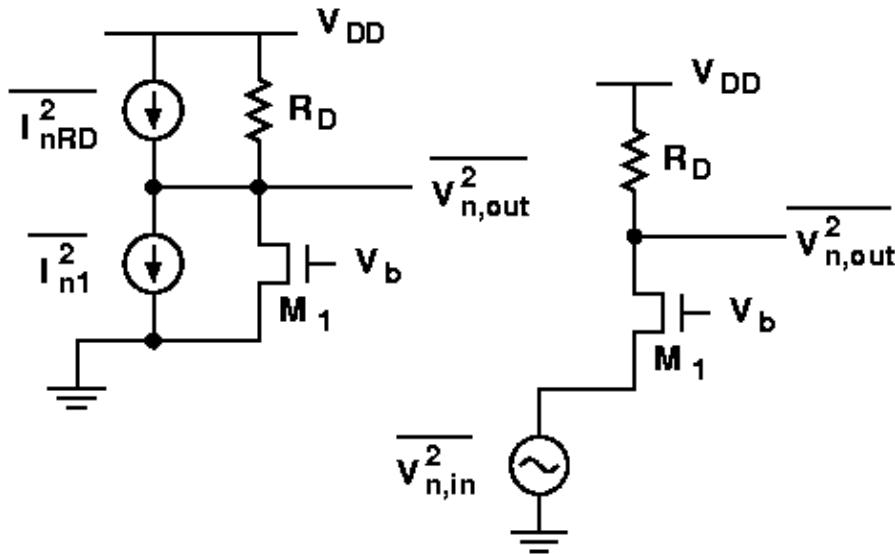- To calculate input referred noise V_n :



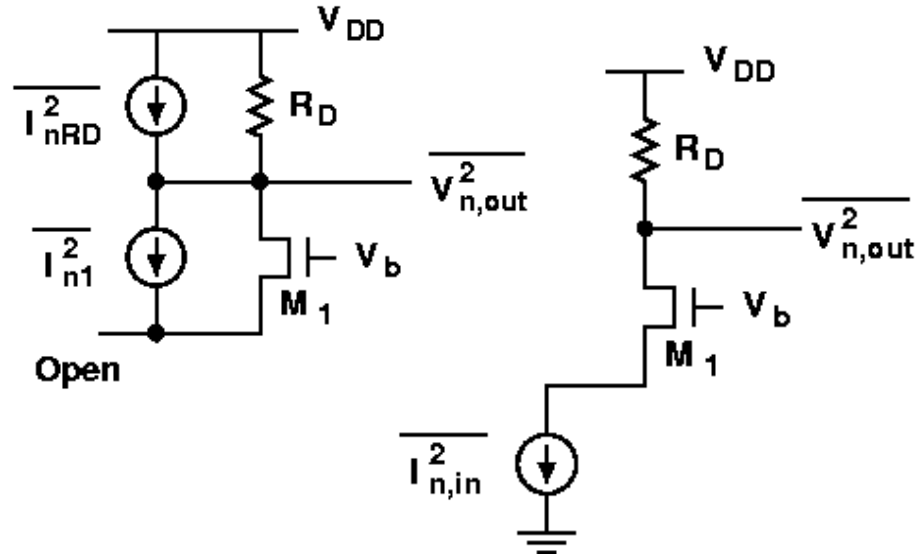- To calculate input referred noise I_n :




$$4kT \left(\frac{2}{3} g_m + \frac{1}{R_D} \right) R_D^2 = \overline{V_{n,in}^2} (g_m + g_{mb})^2 R_D^2, \quad \overline{V_{n,in}^2} = \frac{4kT \left(\frac{2}{3} g_m + \frac{1}{R_D} \right)}{(g_m + g_{mb})^2}$$

$$I_{n1} + I_{D1} = 0, \quad \overline{I_{n,in}^2 R_D^2} = 4kTR_D, \quad \overline{I_{n,in}^2} = \frac{4kT}{R_D}$$

- They directly refer the noise current produced by the load to the input (I-gain = 1).

Noise Contributed by Current Source

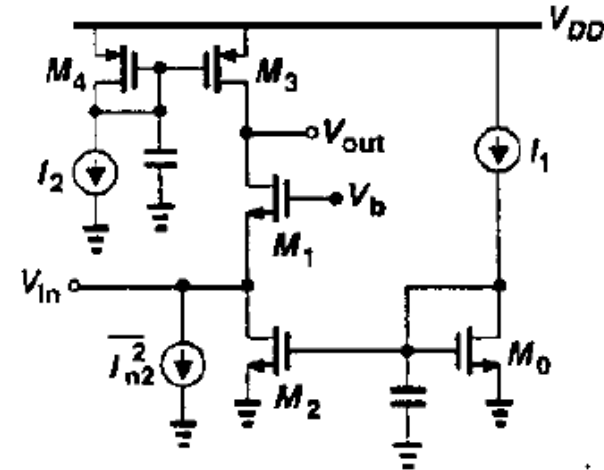- The drain noise current of M_2 directly adds to the input referred noise current of $\overline{I_{n2}^2}$.
- For low noise performance, $g_{m2} \downarrow$, $g_{m2} = \frac{2I_{D2}}{(V_{GS2} - V_{TH2})}$
- For a given bias current, this requires a high voltage of V_b and limiting the voltage swing at the output node.



- For input-referred noise voltage, short the input to ground



$$\overline{V_{n,out}^2} = 4kT \frac{2}{3} (g_{m1} + g_{m3})(r_{O1} \parallel r_{O3})^2 = \overline{V_{n,in}^2} (g_{m1} + g_{mb1})^2 (r_{O1} \parallel r_{O3})^2$$

$$\overline{V_{n,in}^2} = 4kT \frac{2}{3} \frac{(g_{m1} + g_{m3})}{(g_{m1} + g_{mb1})^2} \propto g_{m3}$$

- For input-referred noise current, open the input

$$\overline{V_{n,out}^2} = (\overline{I_{n2}^2} + \overline{I_{n3}^2}) R_{out}^2 = \overline{I_{n,in}^2} R_{out}^2, \quad \overline{I_{n,in}^2} = (\overline{I_{n2}^2} + \overline{I_{n3}^2}) = 4kT \frac{2}{3} (g_{m2} + g_{m3}) \propto g_{m2}, g_{m3}$$

Source Followers

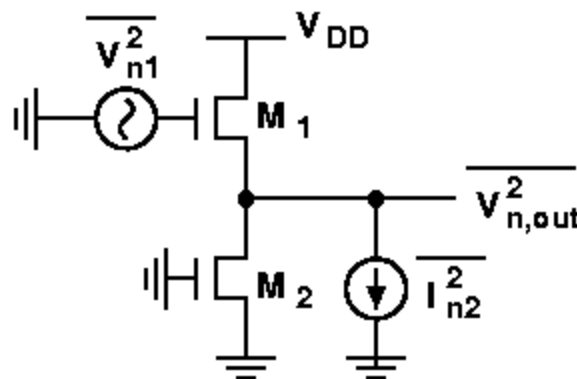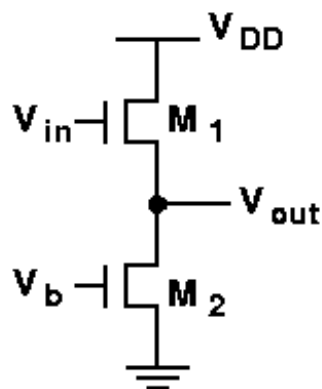


$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \frac{\overline{V_{n,out}^2}|_{M2}}{A_v^2} = 4kT \frac{2}{3} \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$

or $\overline{V_{n,in}^2} = \frac{(\overline{I_{n1}^2} + \overline{I_{n2}^2}) R_{out}^2}{A_v^2}, \quad \frac{R_{out}}{A_v} = \frac{1}{g_{m1}}$

$$R_{out} = \left(\frac{1}{g_{m1}} \parallel R_o \right), \quad A_v = \frac{R_o}{R_o + 1/g_{m1}}$$

- M_2 serves as the bias current source .
- Since the input impedance of the circuit is quite high, even at relatively high frequencies, the input-referred noise current can usually be neglected for moderate driving source impedances.
- Since source followers add noise to the input signal while providing a voltage gain less than unity, **they are usually avoided in low-noise amplification.**

Cascode Stage

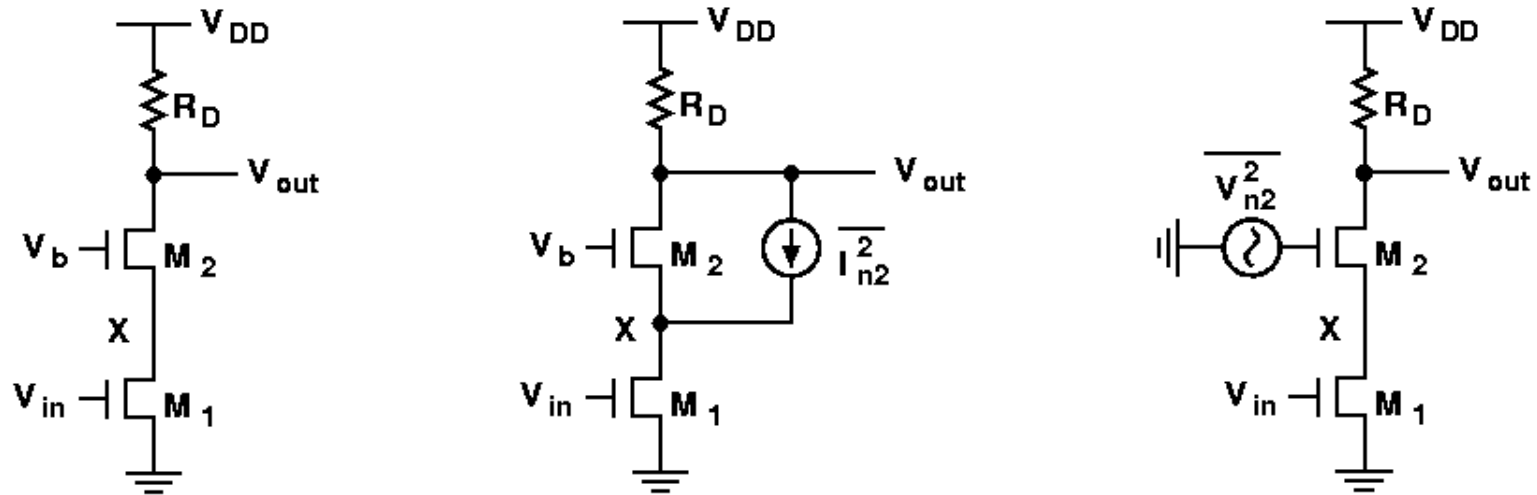

- Consider the noise current of M_1 and R_D . At low frequencies, the noise currents of M_1 and R_D flow through R_D


$$\overline{V_{n,in}^2} \Big|_{M1, R_D} = 4kT \left(\frac{2}{3g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right)$$

- Consider the noise current of M_2 , (CS + Source degeneration)

$$\frac{V_{n,out}}{V_{n2}} \approx \frac{-R_D}{1/sC_X + 1/g_{m2}}$$


- The input referred noise of a cascode stage may rise considerably at high freq.

Noise in Differential Pairs

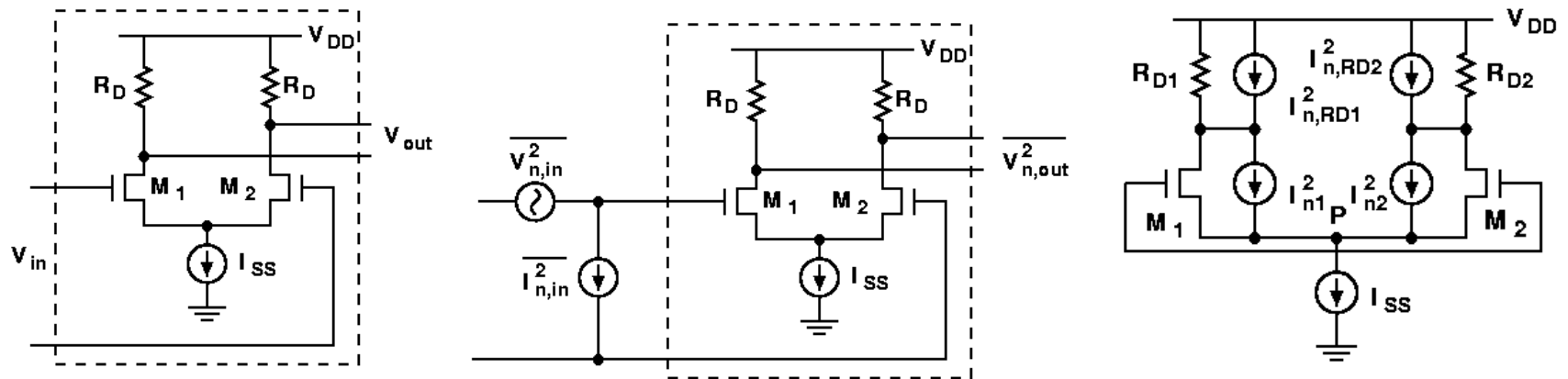

- For low frequency operation, the magnitude of $\overline{I_{n,in}^2}$ is typically negligible.
- To calculate the thermal component of $\overline{V_{n,in}^2}$, short input
 - Since $\overline{I_{n1}^2}$ and $\overline{I_{n2}^2}$ are uncorrelated, node P can not be considered a virtual ground.

Input Referred Noise of DP

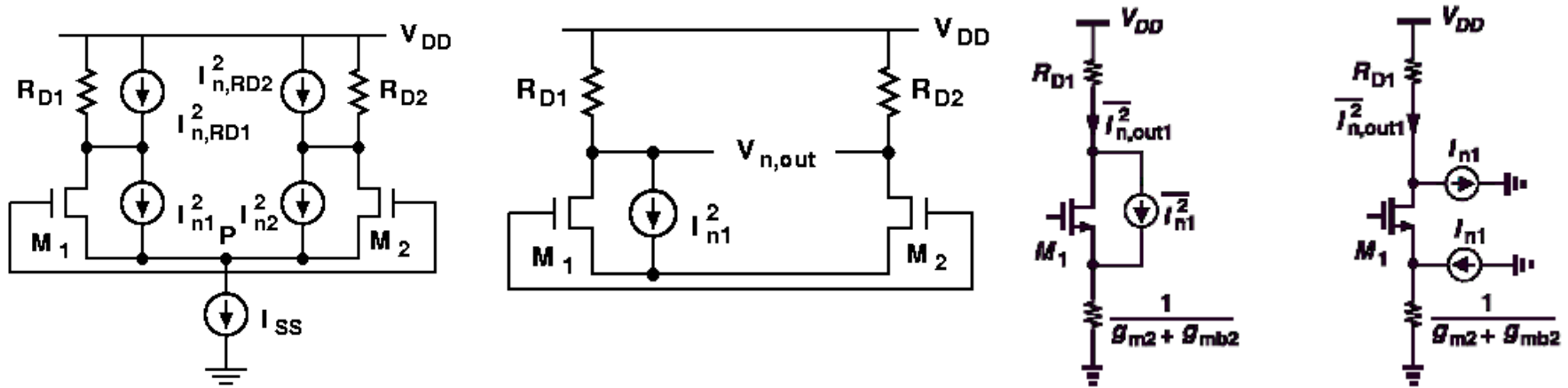

- Decomposing I_{n1} into two (correlated) current sources and calculating their effect at the output.

$$V_{n,out}|_{M1} = \frac{I_{n1}}{2} R_{D1} + \frac{I_{n1}}{2} R_{D2}$$

- If $R_{D1} = R_{D2} = R_D$ $\overline{V_{n,out}^2}|_{M1} = \overline{I_{n1}^2} R_D^2$, $\overline{V_{n,out}^2}|_{M2} = \overline{I_{n2}^2} R_D^2$, $\overline{V_{n,out}^2}|_{M1,M2} = (\overline{I_{n1}^2} + \overline{I_{n2}^2}) R_D^2$
- Taking into account the noise of $R_{D1} = R_{D2}$

$$\overline{V_{n,out}^2} = (\overline{I_{n1}^2} R_D^2 + \overline{I_{n2}^2} R_D^2) + 2(4kTR_D) = 8kT \left(\frac{2}{3} g_m R_D^2 + R_D \right)$$

$$\overline{V_{n,in}^2}(CS) = 4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right)$$

- Dividing the result by the square of the differential gain: $\overline{V_{n,in}^2} = 8kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right)$

Input-Referred Noise of DP

- Placing the voltage sources given by $K/(C_{ox}WL)$ in series with each gate

$$\overline{V_{n,in}^2} = 8kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{2K}{C_{ox}WL} \frac{1}{f}$$

- The noise of tail current modulates the transconductance of each device

$$\Delta I_{D1} - \Delta I_{D2} = g_m \Delta V_{in} = \sqrt{2\mu_n C_{ox} \frac{W}{L} \left(\frac{I_{SS} + I_n}{2} \right)} \Delta V_{in}$$

- In essence, the noise modulates the transconductance of each device

$$\Delta I_{D1} - \Delta I_{D2} \approx \sqrt{2\mu_n C_{ox} \frac{W}{L} \cdot \frac{I_{SS}}{2}} \left(1 + \frac{I_n}{2I_{SS}} \right) \Delta V_{in} = g_{m0} \left(1 + \frac{I_n}{2I_{SS}} \right) \Delta V_{in}$$

$g_{m0} : g_m$ of noiseless circuit

- The effect is nonetheless usually negligible.

$$\overline{V_{n,in}^2}(CS) = 4kT \left(\frac{2}{3g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox}WL} \frac{1}{f}$$

