

A dark background with a light gray circuit board pattern, featuring various traces, pads, and a central rectangular component.

CHAPTER 6

Analog Front End

Outline

- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- 6.3 SC Application
- 6.4 Noise in SC
- 6.5 Non-ideal Effects in SC
- 6.6 Practical Issues


Outline

- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- 6.3 SC Application
- 6.4 Noise in SC
- 6.5 Non-ideal Effects in SC
- 6.6 Practical Issues


Introduction

- Analog front end
 - Correlated double sampling (CDS) : optional
 - Programmable gain amplifier (PGA)
 - Digital to analog converter (DAC)
 - Analog to digital converter (ADC)

AFE for CCD

 


Commercial CIS Product

 

Correlated Double Sampling

 - Purpose of CDS
 - Inter-chip signal sampling, signal clamp (CCD + AFE)
 - Offset cancellation
 - Fixed pattern cancellation
 - KTC cancellation
 - Signal buffering & level shifting




Programmable Gain Amplifier

- Purpose of PGA
 - CDS implementation
 - Single-to-differential conversion
 - Signal amplification
 - Color balance in analog domain (white balance)
 - ADC input level fitting : signal full-swing tuning

Digital to Analog Converter

 - Purpose of DAC
 - Signal path offset cancellation
 - Optical black calibration (analog domain)
 - SC implementation with PGA




Analog to Digital Converter

- Purpose of ADC
 - Digitization for subsequent signal processing
 - 8b ~ 12b depends on application
 - Single / Column-parallel / Pixel-parallel implementation depends on required bandwidth
 - Pipeline / Single-slope / SAR / Cyclic ...

Outline

- 6.1 Introduction
- **6.2 Switched-Capacitor Circuit**
- 6.3 SC Application
- 6.4 Noise in SC
- 6.5 Non-ideal Effects in SC
- 6.6 Practical Issues

Continuous-Time Integrator

 


$$v_o(t) = -\frac{1}{R_1 \cdot C_2} \int_{-\infty}^t v_{in}(\xi) d\xi$$

$$H(s) = \frac{V_o}{V_i}(s) = -\left(\frac{1}{R_1 \cdot C_2}\right) \cdot \frac{1}{s}$$




$$\tau = R_1 \cdot C_2$$

Goal:

 


Approach: emulating resistors with switched capacitors

Concept of Switched Capacitor

 


$$i = \frac{1}{R} (V_A - V_B)$$

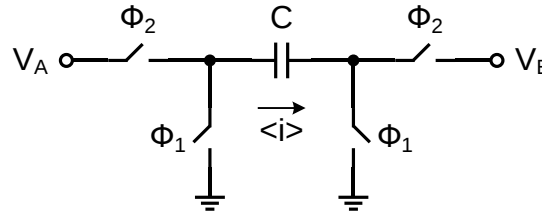

$$\langle i \rangle = \frac{q}{T} = \frac{C}{T} (V_A - V_B)$$

Non-overlapping
two-phase clock

 


$$\Rightarrow \boxed{R_{eq} = \frac{T}{C}} \quad \text{so,} \quad \tau = R_{eq,1} \cdot C_2 = \frac{T}{C_1} \cdot C_2 = T \cdot \frac{C_2}{C_1}$$


- A switched capacitor is a discrete-time “resistor”
- RC time constant set by capacitor ratio C_2/C_1 (match considerably better than R and C) and clock period T (flexibility)

Switched Capacitors



Shunt-type

 

Series-type

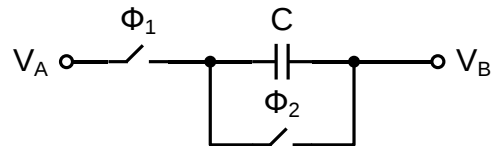

2-phase clock

  


Stray-insensitive


- Shunt- and series-type SCs are simple and cheap to implement
- Stray-insensitive SC requires 2 more switches

Discrete-Time Integrator (DTI)


Shunt-type

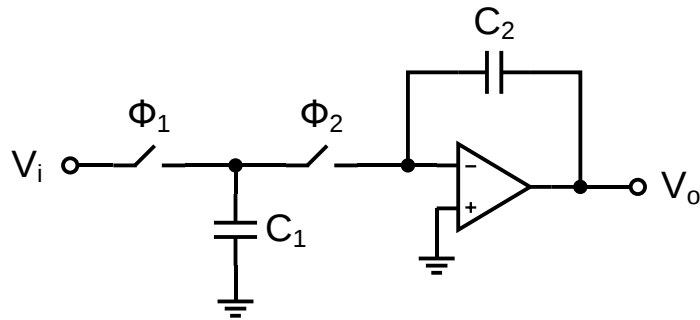



Series-type

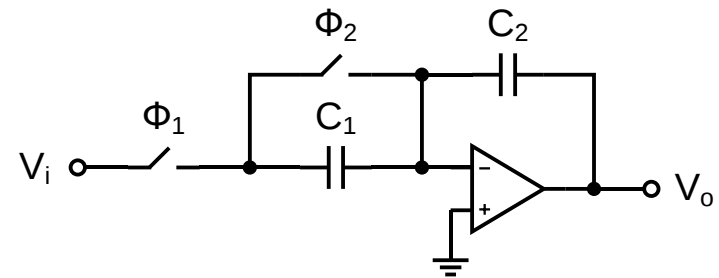

2-phase clock

 


Shunt-Type DTI

 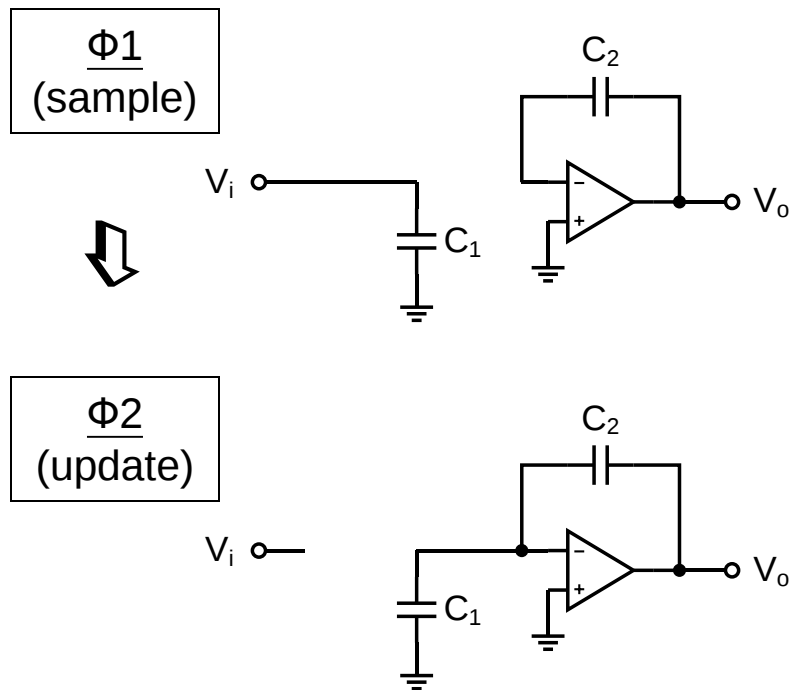

Charge conservation law (ideal):

Total charge on C_1 and C_2 during $\Phi_1 \rightarrow \Phi_2$ transition must remain unchanged!

Shunt-Type DTI

 

$$\sum Q(\varphi_1) = V_i(n) \cdot C_1 - V_o(n) \cdot C_2$$

$$\sum Q(\varphi_2) = 0 \cdot C_1 - V_o(n+1) \cdot C_2$$

$$\sum Q(\varphi_1) = \sum Q(\varphi_2) \Rightarrow V_i(n) \cdot C_1 - V_o(n) \cdot C_2 = 0 \cdot C_1 - V_o(n+1) \cdot C_2$$

$$V_i(z) \cdot C_1 - V_o(z) \cdot C_2 = -z \cdot V_o(z) \cdot C_2$$



$$H(z) = \frac{V_o(z)}{V_i(z)} = -\frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$$

Series-Type DTI

Φ_1
(sample/update)



Φ_2
(reset C_1)

 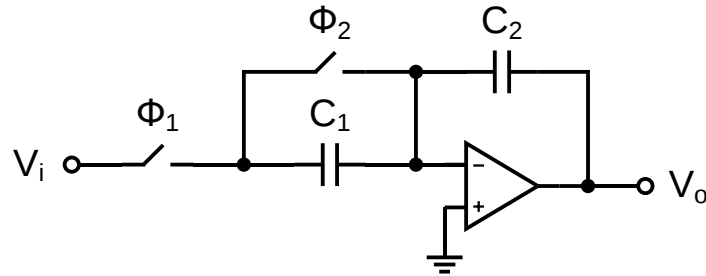

$$\sum Q(\phi_2) = \sum Q(\phi_1) \Rightarrow 0 \cdot C_1 - V_o(n) \cdot C_2 = -V_i(n+1) \cdot C_1 - V_o(n+1) \cdot C_2$$


$$V_o(z) \cdot C_2 = z \cdot V_i(z) \cdot C_1 + z \cdot V_o(z) \cdot C_2$$

VTF:


$$H(z) = \frac{V_o(z)}{V_i(z)} = -\frac{C_1}{C_2} \frac{1}{1 - z^{-1}}$$

Stray Capacitance





Shunt-type

 

Series-type

 


$$\frac{C_2}{C_1} = 4$$

    

- Strays derive from D/S diodes and wiring capacitance
- VTF is modified due to strays
- Strays at the summing node is of no significance (virtual ground)

Stray-Insensitive SC Integrator

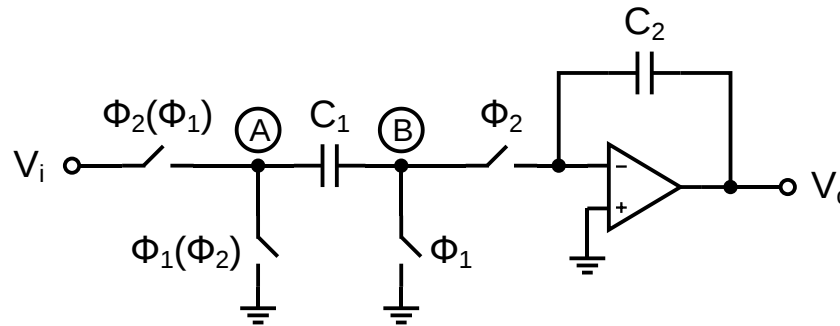

“Inverting”


VTF:
$$H(z) = -\frac{C_1}{C_2} \frac{1}{1-z^{-1}}$$

“Non-inverting”

VTF:
$$H(z) = +\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}}$$

- Capacitors can be significantly sized down to save power/area
- Sizes are eventually limited by kT/C noise, mismatch, etc.

SC Amplifier

 


VTF:


$$H(z) = +\frac{C_1}{C_2} \cdot z^{-1}$$

- Gain implemented by C ratio
- No resistive loading of amplifier (high gain)


SC Unit Gain Buffer

 

(a)

 


(b)

 


(c)

Early Sampling

 


- S_2 turning OFF a little earlier than S_1
- Reduce signal dependent switching error


Switching Error

 

(a)

 



(b)

 

(c)


- V_X is floating by turning off S_2 , and define the charge on C_H
- S_1 turning OFF will not change the charge on C_H

Differential Realization

 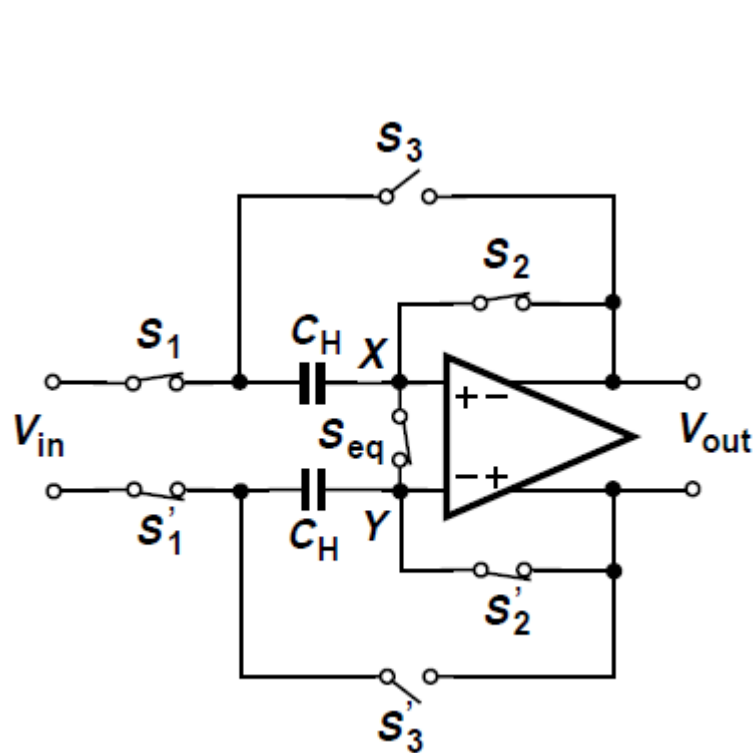

- S_{eq} turning OFF a little after S_2 and earlier than S_1
- To solve the mismatch of S_2 and S_2'

Finite Gain Effect

 



$$V_X = \frac{V_X}{A_{v1}} = 0$$

$$V_X = -\frac{V_{out}}{A_{v1}}$$

$$Q[n] = C_H (0 - V_{in}) = C_{in} V_X + C_H (V_X - V_{out}) = Q[n+1]$$

$$V_{out} = \frac{V_{in}}{1 + \frac{1}{A} \left(1 + \frac{C_{in}}{C_H} \right)} \approx V_{in} \left[1 - \frac{1}{A} \left(1 + \frac{C_{in}}{C_H} \right) \right]$$


Bottom Plate Sampling

  


- Bottom plate sampling
- Minimize C_{in} , increase SC gain precision

SC Gain Stage

Early sampling

 

Finite gain

 


$$\frac{V_{out}}{V_{in}} = \frac{-C_1}{C_2 + \frac{C_2 + C_1 + C_{in}}{A}} \approx -\frac{C_1}{C_2} \left(1 - \frac{C_2 + C_1 + C_{in}}{C_2} \frac{1}{A} \right)$$


Outline

- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- **6.3 SC Application**
- 6.4 Noise in SC
- 6.5 Non-ideal Effects in SC
- 6.6 Practical Issues

CT Filter

 


RLC prototype

 


Active-RC
Tow-Thomas
CT biquad

SC DT Filter

 


Active-RC
Tow-Thomas
CT biquad

 


SC DT
biquad

Sigma-Delta ($\Sigma\Delta$) Modulator

 

DTI + 1-bit comparator + 1-bit DAC = first-order $\Sigma\Delta$ ADC

Pipelined ADC

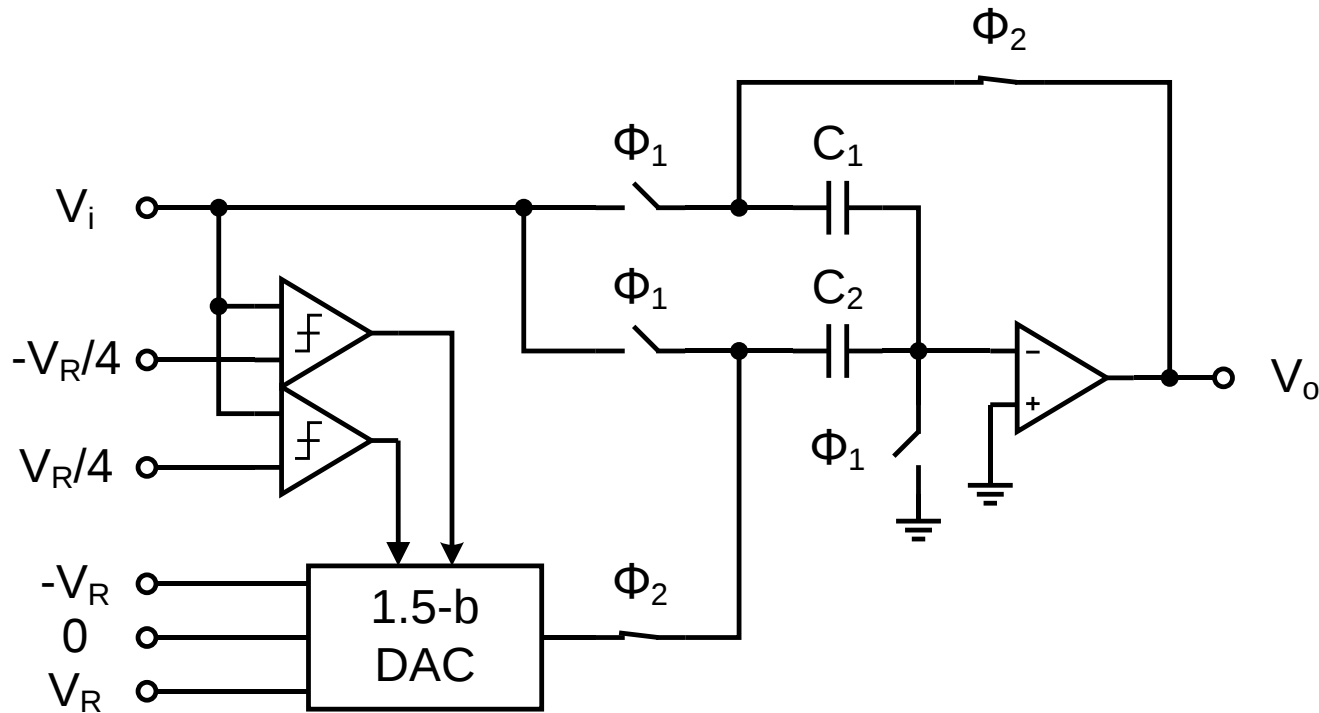


SC amplifier + 2 comparators + 3-level DAC = 1.5-bit pipelined ADC

Outline

- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- 6.3 SC Application
- **6.4 Noise in SC**
- 6.5 Non-ideal Effects in SC
- 6.6 Practical Issues


Noise of CT Integrator

 

$$\overline{V_{oN}}^2 = \int \frac{\overline{V_{N1}}^2}{\Delta f}(f) \cdot |H_1(f)|^2 df + \int \frac{\overline{V_{N2}}^2}{\Delta f}(f) \cdot |H_2(f)|^2 df + \dots$$


Noise in CT circuits can be simulated with SPICE (.noise)

Noise of SC Integrator

 

SC circuits are **NOT** noise-free! Switches and op-amps introduce noise.


Sampling (Φ_1) Ideal Voltage Source

 

$$\begin{aligned}\overline{V_N^2}(\phi_1) &= \int_0^\infty \left[\frac{\overline{V_{N1}^2}}{\Delta f}(f) + \frac{\overline{V_{N2}^2}}{\Delta f}(f) \right] \cdot |H_1(f)|^2 df \\ &= \int_0^\infty [4kTR_1 + 4kTR_2] \cdot \left| \frac{1}{1 + j2\pi f \cdot (R_1 + R_2)C} \right|^2 df \\ &= \frac{kT}{C}\end{aligned}$$

- Noise is indistinguishable from signal after sampling
- The noise acquired by C_1 will be amplified in Φ_2 just like signal

Integration (Φ_2)

 


$$\overline{V_N}^2(\phi_2) = \int \left[\frac{\overline{V_{N3}}^2}{\Delta f}(f) + \frac{\overline{V_{N4}}^2}{\Delta f}(f) \right] \cdot |H_{34}(f)|^2 df + \int \frac{\overline{V_{N5}}^2}{\Delta f}(f) \cdot |H_5(f)|^2 df + \dots$$

$$\boxed{\overline{V_{oN}}^2 = \left(\frac{C_1}{C_2} \right)^2 \cdot \overline{V_N}^2(\phi_1) + \overline{V_N}^2(\phi_2)}$$


No simulator can directly simulate the aggregated output noise!

Sampling (Φ_1) Noise – Cascaded Stages

 

- Finite op-amp BW limits the noise bandwidth, resulting in less overall kT/C noise (noise filtering).
- But parasitic loop delay may introduce peaking in freq. response, resulting in more integrated noise (noise peaking).

Sampled Noise Spectrum

 

- Total integrated noise power remains constant
- SNR remains constant



Outline

- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- 6.3 SC Application
- 6.4 Noise in SC
- **6.5 Non-ideal Effects in SC**
- 6.6 Practical Issues

Nonideal Effects in SC Circuits

- Capacitors (poly-poly, metal-metal, MIM, MOM, sandwich, gate cap, accumulation-mode gate cap, etc.)
 - PP, MIM, and MOM are linear up to 14-16 bits (nonlinear voltage coefficients negligible for most applications)
 - Gate caps are typically good for up to 8-10 bits
- Switches (MOS transistors)
 - Nonzero on-resistance (voltage dependent)
 - (Nonlinear) stray capacitance added (C_{gs} , C_{gd} , C_{gb} , C_{db} , C_{sb})
 - Switch-induced sampling errors (charge injection, clock feedthrough, junction leakage, drain-source leakage, and gate leakage)
- Operational amplifiers
 - Offset
 - Finite-gain effects (voltage dependent)
 - Finite bandwidth and slew rate (measured by settling speed)


Nonzero On-Resistance

  


$$R_{on}^{-1} = \mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_{out})$$

- FET channel resistance (thus tracking bandwidth) depends on signal level
- Usually $(R_{on} C_S)^{-1} \geq (3-5) \cdot \omega_{-3dB}$ of closed-loop op-amp for settling purpose

Clock Bootstrapping

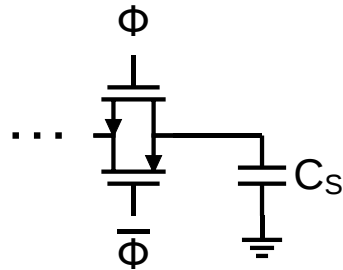


CMOS

 

Bootstrapped NMOS

- Small on-resistance leads to large switches → large parasitic caps and large clock buffers
- Clock bootstrapping keeps V_{GS} of the switch constant → constant on-resistance (body effect?) and less parasitics w/o the PMOS

Simplified Clock Bootstrapper

 


Pros

- Linearity
- Bandwidth


Cons

- Device reliability
- Complexity

Double Bootstrapper

 




Switch-Induced Errors

 

- Clock feedthrough
- Charge injection


Channel charge injection and clock feedthrough (on drain side) result in charge trapped on C_S after switch is turned off.

Clock Feedthrough / Charge Injection

 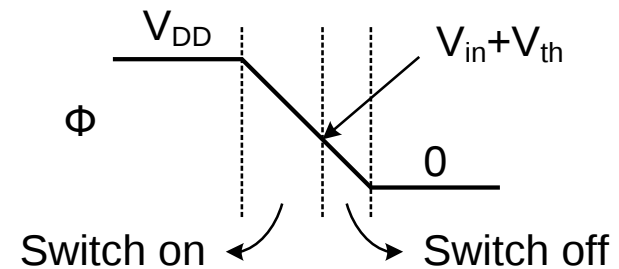 


- Both phenomena sensitive to Z_i , C_S , and clock rise/fall time
- Offset, gain error, and nonlinearity introduced to the sampling
- Clock feedthrough can be simulated by SPICE, but charge injection **cannot** be simulated with lumped transistor models

Clock Rise/Fall-Time Dependence

 

 
$$Q_{ch} = C_{ox}WL(V_{DD} - V_{th} - V_{in})$$




	Clock feedthrough	Charge injection
Fast turn-off	$\Delta V = -\frac{C_{gs}}{C_{gs} + C_S} V_{DD}$	$\Delta V = -\frac{C_{ox}WL(V_{DD} - V_{th} - V_{in})}{2(C_{gs} + C_S)}$
Slow turn-off	$\Delta V = -\frac{C_{gs}}{C_{gs} + C_S} (V_{in} + V_{th})$	$\Delta V = 0$

Dummy Switch


 


- Difficult to achieve precise cancellation due to the nonlinear dependence of ΔV on Z_i , C_S , and clock rise/fall time
- Sensitive to the phase alignment between Φ and Φ_{-}

Dummy Switch

 


  Charge injection cancellation
(Signal dependent)



Clock feedthrough cancellation (Depend on W/L only)





CMOS Switch

 



Same size for
P and N FETs

- Very sensitive to phase alignment between Φ and Φ_{-}
- Subject to threshold mismatch between PMOS and NMOS
- Exact cancellation occurs only for one specific V_{in} (which one?)

CMOS Switch

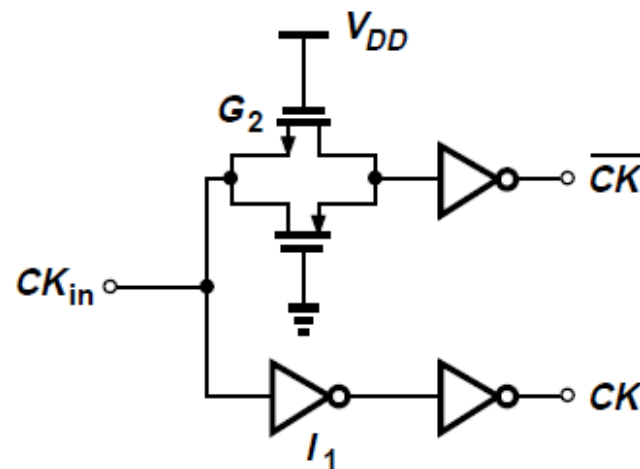   

Differential Signaling

  

Balanced diff. input

- Signal-independent errors (offset) and even-order distortions cancelled
- Gain error and odd-order nonlinearities remain

Switch Performance

On-resistance: $R_{\text{on}} = \frac{1}{\mu C_{\text{ox}} \frac{W}{L} (V_{\text{DD}} - V_{\text{th}} - V_i)} = \frac{L^2}{\mu C_{\text{ox}} W L (V_{\text{DD}} - V_{\text{th}} - V_i)} = \frac{L^2}{\mu Q_{\text{ch}}}$

Bandwidth: $BW \approx \frac{1}{R_{\text{on}} C_S} = \frac{\mu Q_{\text{ch}}}{L^2 C_S}$



Charge injection: $\Delta V \approx \frac{1}{2} \frac{Q_{\text{ch}}}{C_S}$

Performance FoM: $\boxed{\frac{\Delta V}{BW} \approx \frac{1}{2} \frac{Q_{\text{ch}}}{C_S} \cdot \frac{L^2 C_S}{\mu Q_{\text{ch}}} = \frac{L^2}{2\mu}}$

Technology scaling improves switch performance!

Leakage in SC Circuits

 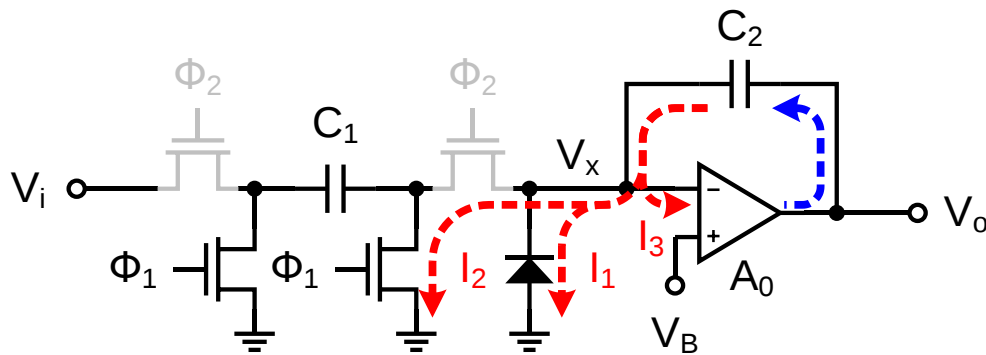$\Phi_1 = \text{"high"} , \Phi_2 = \text{"low"}$



- **I1** – diode leakage (existing in the old days too)
- **I2** – sub-threshold drain-source leakage of summing-node switch
- **I3** – gate leakage (FN tunneling) of amplifier input transistors
- Leakage currents are highly temperature- and process-dependent; the lower limit of clock frequency is often determined by leakage

Gate Leakage

$$I_{GS} \propto WL \cdot \exp(-t_{ox}) \cdot \exp(V_{GS})$$

- Direct tunneling through the thin gate oxide
- Short-channel MOSFET behaves increasingly like BJT's
- Violates the high-impedance assumption of the summing node

Switch Size Optimization

- To minimize switch-induced error voltages, small transistor size, slow turn-off, low source impedance should be used.
- For fast settling (high-speed design), large W/L should be used, and errors will be inevitably large as well.


Guidelines

- Always use minimum channel length for switches as long as leakage allows.
- For a given speed, switch sizes can be optimized w/ simulation.
- Be aware of the limitations of simulators (SPICE etc.) using lumped device models.

Nonideal Effects of Op-Amps


- Offset
- Finite-gain effects (voltage dependent)
- Finite bandwidth and slew rate (measured by settling speed)

Offset Voltage

 

$$\sum Q(\phi_1) = V_i(n)C_1 + [V_o(n) - V_{os}]C_2$$
 
$$\sum Q(\phi_2) = -V_{os}C_1 + [V_o(n+1) - V_{os}]C_2$$




$$V_i = 0$$

$$V_i = 0 \rightarrow V_o(n+1) - V_o(n) = \left(\frac{C_1}{C_2} \right) V_{os}$$

$$V_o(z) = \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}} V_i(z)$$

Autozeroing

 


$$\sum Q(\varphi_1) = [V_i(n) - V_{os}]C_1 - V_{os}C_2$$

$$\sum Q(\varphi_2) = -V_{os}C_1 + [V_o(n) - V_{os}]C_2$$

$$H(z) = \frac{V_o(z)}{V_i(z)} = \frac{C_1}{C_2}$$


- Also eliminates low-frequency noise, e.g., $1/f$ noise
- A.k.a. **correlated double sampling (CDS)**

Chopper Stabilization

 


Ref: K. C. Hsieh, P. R. Gray, D. Senderowicz, and D. G. Messerschmitt, "A low-noise chopper-stabilized differential switched-capacitor filtering technique," *IEEE Journal of Solid-State Circuits*, vol. 16, issue 6, pp. 708-715, 1981.


Chopper Stabilization

 

Also eliminates DC offset
voltage of A_1

 


Chopper-Stabilized Diff. Op-Amp

 

- Integrators/amplifiers can be built using these op-amps
- Some oversampling is useful to facilitate the implementation


Ideal SC Amplifier

 

$$A_{CL} = \frac{C_1}{C_2}$$

- Closed-loop gain is determined by the capacitor ratio by design
- But this is assuming X is an ideal summing node (the op-amp is ideal)

Finite-Gain Effect in SC Amplifier

 

$$A_{CL} = \frac{V_o}{V_i} = \frac{C_1}{C_2} \cdot \frac{1}{1 + \frac{C_1 + C_2}{C_2 A}} \approx \frac{C_1}{C_2} \cdot \left(1 - \frac{C_1 + C_2}{C_2 A} \right)$$

$$\sum Q(\phi_1) = [V_i(\phi_1) - V_x(\phi_1)] \cdot C_1 + 0 \cdot C_2$$

$$V_x(\phi_1) = V_o(\phi_1) = -V_x(\phi_1) \cdot A$$

$$\sum Q(\phi_2) = -V_x(\phi_2) \cdot C_1 + [V_o(\phi_2) - V_x(\phi_2)] \cdot C_2$$

$$V_o(\phi_2) = -V_x(\phi_2) \cdot A$$


$$\sum Q(\phi_1) = \sum Q(\phi_2) \Rightarrow V_i \cdot C_1 = -V_x \cdot C_1 + (V_o - V_x) \cdot C_2$$

$$V_o = -V_x \cdot A$$

Outline


- 6.1 Introduction
- 6.2 Switched-Capacitor Circuit
- 6.3 SC Application
- 6.4 Noise in SC
- 6.5 Non-ideal Effects in SC
- **6.6 Practical Issues**

Analog vs. Digital Supply Lines

 


Sharing sensitive analog supplies with digital ones is a very bad idea.

Analog vs. Digital Supply Lines

 

- Dedicated pads for analog and digital supplies
- On-chip bypass capacitors help (watch ringing)
- Off-chip chokes (large inductors) can stop noise propagation at board level


“Supply” Capacitance

 

$$\Delta V_o = \Delta V \cdot \frac{C_{stray}}{C_2}$$


- Any summing-node stray capacitance can be a potential coupling path.
- V_{DD} , V_{SS} , substrate, clock line, and digital noises, body effect, etc.
- Fully differential circuits help to reject common-mode noise and coupling.

“Supply” Capacitance

 

- Avoid connecting bottom-plate parasitics to the summing node
- Avoid crossing other signal lines with the summing node
- Shielding can mitigate substrate noise coupling


Clock Generation

 

- Clock-gated ring structure
- Non-overlapping time determined by inverter delays, sensitive to process, voltage, and temperature (PVT) variations
- DLL is an alternative, often used in high-speed designs

Review of CMOS Operational Amplifiers

Negative Feedback

 


$$A_{CL} = \frac{V_o}{V_i} = \frac{A(V_o)}{1 + \beta A(V_o)} \quad \xrightarrow{A(V_o) = \infty} \quad \frac{1}{\beta}$$

$$\begin{aligned} \frac{\delta A_{CL}}{A_{CL}} &= \frac{\delta A(V_o)}{A(V_o)} \cdot \frac{1}{\beta A(V_o)} \\ &= \frac{\delta A(V_o)}{A(V_o)} \cdot \frac{1}{T} \end{aligned}$$

$$THD \sim \frac{1}{\beta A(V_o)} = \frac{1}{T}$$

- Closed-loop linearity is achieved by negative feedback with large loop gain
- Negative feedback reduces gain sensitivity and harmonic distortion


Folded-Cascode Op-Amp

 

- Differential
- $A_0 \sim (g_m \cdot r_o)^2 \sim 40\text{-}50\text{dB}$
- $V_{o,pp} \sim 2(V_{DD} - 4V_{DSAT})$
- Noise factor ~ 3
- $\omega_{p2} \sim f_T/3$
- Efficiency $\sim 50\%$
- Load-compensated
- Flexible input CM

Most often used single-stage topology, easy to bias


Telescopic Op-Amp

 

- Differential
- $A_0 \sim (g_m \cdot r_o)^2 \sim 40\text{-}50\text{dB}$
- $V_{o,pp} \sim 2(V_{DD} - 5V_{DSAT})$
- Noise factor ~ 2
- $\omega_{p2} \sim f_T/2$
- Efficiency $\sim 100\%$
- Load-compensated
- Fixed input CM

2X more power-efficient than the folded-cascode topology, fast


Two-Stage Op-Amp

 

- Differential
- $A_0 \sim (g_m \cdot r_o)^3 \sim 60\text{-}70\text{dB}$
- $V_{o,pp} \sim 2(V_{DD} - 3V_{DSAT})$
- $N_2 = N_1 \cdot \beta \cdot C_M / C_L$
- Noise factor $\sim 2 + 2\beta$
- $\omega_{p2} \sim g_{m2} / C_L$
- Efficiency $< 50\%$
- Miller-compensated
- Fixed input CM

Not as power-efficient as single stage, suitable for low V_{DD}



Pseudo-Differential Op-Amp

 

- Differential
- $A_0 \sim (g_m \cdot r_o)^2 \sim 40\text{-}50\text{dB}$
- $V_{o,pp} \sim 2(V_{DD} - 4V_{DSAT})$
- Noise factor ~ 2
- $\omega_{p2} \sim f_T/2$
- Efficiency $\sim 100\%$
- Load-compensated
- Fixed input CM
- No CMFB point


As power-efficient and fast as telescopic, but V_{ocm} is a problem

CMOS Gain-Boosting

  

- $A_0 \sim A_a \cdot (g_m \cdot r_o)^2 \sim 60\text{-}100\text{dB}$, limited by substrate current
- Single-stage design, same output swing, suitable for SC circuits
- Auxiliary amplifiers introduce pole-zero doublet (slow settling), additional noise

Nested CMOS Gain-Boosting

 

- Two levels of recursive gain-boosting $\rightarrow A_0 \approx (g_m \cdot r_o)^6 \geq 120\text{ dB}$
- Pseudo-differential architecture $\rightarrow$ p-p differential output swing $\geq 2\text{ V}$

Reference

- Y. Chiu, Data Converters Lecture Slides, UT Dallas 2012.
- Omnivision Product Datasheet
- J. Ohta, Smart CMOS Image Sensor and Applications, 2008