



CHAPTER 9

Successive Approximation ADC


Outline

1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation

Outline





1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation

SAR ADC

 

- SAR ADC is composed of sample & hold, DAC, comparator and SAR control logic
- Conversion procedure
 - Sampling phase
 - S&H sample the input and reset DAC to initial value
 - Conversion phase
 - Comparator compare the input signal and DAC output, then control the SAR logic to perform the binary search from MSB to LSB




Single Ended SAR ADC

    





$$V_{in} = b_0\left(\frac{1}{2}\right)V_{ref} + b_1\left(\frac{1}{4}\right)V_{ref} + b_2\left(\frac{1}{8}\right)V_{ref} + b_3\left(\frac{1}{16}\right)V_{ref} + Nq$$

$$VDAC = V_{ref}$$

Single Ended SAR ADC

   





Single Ended SAR ADC

    

$$V_{in} = b_0\left(\frac{1}{2}\right)V_{ref} + b_1\left(\frac{1}{4}\right)V_{ref} + b_2\left(\frac{1}{8}\right)V_{ref} + b_3\left(\frac{1}{16}\right)V_{ref} + N_q$$



$$VDAC = V_{ref} - V_{in} + \left(\frac{1}{2}\right)V_{ref}$$

Single Ended SAR ADC

    

$$\begin{aligned} V_{in} &= b_0\left(\frac{1}{2}\right)V_{ref} + b_1\left(\frac{1}{4}\right)V_{ref} + b_2\left(\frac{1}{8}\right)V_{ref} \\ &\quad + b_3\left(\frac{1}{16}\right)V_{ref} + Nq \\ V_{DAC} &= V_{ref} - V_{in} + \left(\frac{1}{2}\right)V_{ref} + \left(\frac{1}{4}\right)V_{ref} \end{aligned}$$

Single Ended SAR ADC

 
 


The timing diagram shows three signals: 'clk' (clock), 'sample' (sample-and-hold control), and 'invert' (DAC output control). The 'clk' signal is a periodic square wave. The 'sample' signal is a single pulse that occurs during a specific clock cycle. The 'invert' signal is a square wave that is high during the 'sample' pulse and low otherwise.

$$V_{in} = b_0\left(\frac{1}{2}\right)V_{ref} + b_1\left(\frac{1}{4}\right)V_{ref} + b_2\left(\frac{1}{8}\right)V_{ref} + b_3\left(\frac{1}{16}\right)V_{ref} + Nq$$

$$VDAC = V_{ref} - V_{in} + \left(\frac{1}{2}\right)V_{ref} + \left(\frac{1}{8}\right)V_{ref}$$

Single Ended SAR ADC

  

Timing diagram showing the clock (clk), sample, and invert signals. The clock is a square wave. The sample signal is a pulse that occurs during the clock high period. The invert signal is a square wave that is high during the sample period and low otherwise.

$$V_{in} = b_0 \left(\frac{1}{2} \right) V_{ref} + b_1 \left(\frac{1}{4} \right) V_{ref} + b_2 \left(\frac{1}{8} \right) V_{ref} + b_3 \left(\frac{1}{16} \right) V_{ref} + Nq$$



$$VDAC = V_{ref} - V_{in} + \left(\frac{1}{2} \right) V_{ref} + \left(\frac{1}{16} \right) V_{ref}$$

$b_0=1, b_1=0, b_2=0, b_3=1$

Outline



1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation
7. Low Power Design Case Study

Sample and Hold

  


- Simple S/H concept using a NMOS and a capacitor
- When Clk is high, V_{in} is sampled on the sampling capacitor (C_{load})
- Clk becomes low, V_{in} is held on C_{load} to perform conversion

Sample and Hold – On-Resistance

  

- Because of threshold drop, NMOS only can pass the signal from 0 to $V_{DD}-V_{th}$
- $$R_{on} = \frac{L}{W} \frac{1}{\mu_n C_{ox} (V_{gs} - V_{th})}$$
- On resistance is signal-dependent, which leads to non-linearity error

Sample and Hold – Charge Injection

 


- When MOS turns off, stored charges are injected into Vin and Cload, results in voltage change across capacitor

$$Q = C_{ox} \cdot W \cdot L \cdot (V_{gs} - V_{th})$$
$$\Delta V = \frac{C_{ox} \cdot W \cdot L \cdot (VDD - V_{in} - V_{th})}{2C_{load}}$$

- Voltage change across Cload is signal-dependent, which leads to nonlinearity and harmonic distortion

Sample and Hold – Clock Feedthrough

 


- When Clk goes from high to low, the capacitance between the gate and source or drain will couple the voltage onto the loading capacitance

$$\Delta V = \frac{C_{overlap} \cdot VDD}{C_{load} + C_{overlap}}$$
$$C_{overlap} = C_{ox} \cdot W \cdot LD$$

- LD is the length of the gate that overlap the drain/source


Sample and Hold – kT/C noise

 

$$V_n^2 = \frac{kT}{C_{load}}$$


- To achieve higher precision and lower noise, larger sampling capacitor is better
- Larger sampling capacitance needs more settling time
- Trade-off between speed and precision

Sample and Hold – Bootstrapped

 


- Under low voltage operation, the gate-source voltage of sampling switch is limited and increases the on-resistance
- The on-resistance results in sampled signal loss
- By the bootstrapped technique, the gate-source of sampling switch is boosted and signal independent

Digital-Analog Converter

 

- N-bits($b_0, b_1, b_2, \dots, b_{N-2}, b_{N-1}$)
- Reference voltage V_{REF}
- b_0 is most significant bit(MSB)
- b_{N-1} is least significant bit(LSB)
- $$D = \frac{b_0}{2^1} + \frac{b_1}{2^2} + \frac{b_2}{2^3} + \dots + \frac{b_{N-1}}{2^N}$$
- $$V_{out} = KV_{REF} \left(\frac{b_0}{2^1} + \frac{b_1}{2^2} + \frac{b_2}{2^3} + \dots + \frac{b_{N-1}}{2^N} \right)$$

Static Characteristic of DAC

 

- Ideal input-output of a 3-bit DAC

- $LSB = \frac{V_{ref}}{2^N}$

- Full scale(FS) = $V_{ref} - LSB$


$$= V_{ref} \left(1 - \frac{1}{2^N} \right)$$

- $FSR = \lim_{N \rightarrow \infty} FS = V_{ref}$


- Dynamic range(DR) = $\frac{FSR}{LSB} =$

$$\frac{FSR}{(FSR/2^N)} = 2^N = 6.02N \text{ dB}$$

Static Characteristic of DAC

 

Quantization Noise

 

- Quantization noise
 - Analog output of infinite-bit DAC minus the output of finite-bit DAC
- Signal-to-noise ration(SNR)
 - Ratio of the full scale value to the rms value of the quantization noise



$$\begin{aligned} \text{rms} &= \sqrt{\frac{1}{T} \int_0^T LSB^2 \left(\frac{t}{T} - 0.5\right)^2 dt} \\ &= \frac{LSB}{\sqrt{12}} = \frac{FSR}{2^N \sqrt{12}} \end{aligned}$$

$$SNR = \frac{FSR / (2\sqrt{2})}{FSR / (2^N \sqrt{12})} = \frac{2^N \sqrt{6}}{2}$$

$$SNR(dB) = 20 \log \left(\frac{2^N \sqrt{6}}{2} \right) = 6.02N + 1.76$$


$$ENOB = \frac{SNR - 1.76}{6.02}$$

Static Characteristic of DAC

  

- Integral nonlinearity(INL)
 - $((V_i - V_{i,ideal})/V_s) \text{ LSB}$ V_s is the ideal change of bit-to-bit
- Differential nonlinearity(DNL)
 - $((V_i - V_{i-1})/V_s - 1) \text{ LSB}$ V_s is the ideal change of bit-to-bit

Charge Redistribution DAC


 


- Operate by binary dividing the total charge applied to a capacitor array
- By charge conservation

$$- V_{ref} C_{eq} = V_{ref} \left(b_0 C + \frac{b_1 C}{2^1} + \dots + \frac{b_{N-1} C}{2^{N-1}} \right) = C_{tot} V_{out} = 2C V_{out}$$



$$- V_{out} = V_{ref} \left(\frac{b_0}{2^1} + \frac{b_1}{2^2} + \frac{b_2}{2^3} + \dots + \frac{b_{N-1}}{2^N} \right)$$

Comparator

  

- A comparator is defined as a circuit that has a binary output whose value is based on a comparison of two analog inputs
- $\text{Gain} = A_v = \lim_{\Delta V \rightarrow 0} \frac{V_{OH} - V_{OL}}{\Delta V}$

Comparator – Input Offset

  


- $$V_{OS} = \Delta V_{TH1,2} + \frac{(V_{gs} - V_{TH})_{1,2}}{2} \left(\frac{\Delta S_{1,2}}{S_{1,2}} + \frac{\Delta R}{R} \right)$$
- $\Delta S_{1,2}$ is the dimension mismatch between M1 and M2
- ΔR is the loading difference induced by M3-M6
- The input common-mode varies the input pair effective voltage which results the dynamic offset and degrades the performance

Outline

 1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation

Switching Energy

- Assume that at time 0^- , the input voltage has been sampled on the capacitor array and all switches are open. At time 0 , the bottom plate of C_2 is switched to V_{REF} . The capacitor array is then charged to reach the final value. If the capacitor array settles in time T_p , the total energy drawn from V_{REF} is



$$\begin{aligned}
 E_{0 \rightarrow 1} &= \int_{0^+}^{T_P} i_{REF}(t) V_{REF} dt = V_{REF} \int_{0^+}^{T_P} i_{REF}(t) dt \\
 E_{0 \rightarrow 1} &= -V_{REF} \int_{0^+}^{T_P} \frac{dQ_{C_2}}{dt} dt = -V_{REF} \int_{Q_{C_2}(0^+)}^{Q_{C_2}(T_P)} dQ_{C_2} \\
 &= -V_{REF} (Q_{C_2}(T_P) - Q_{C_2}(0^+)) \\
 &= -V_{REF} 2C_0 ((V_X[1] - V_{REF}) - V_X[0])
 \end{aligned}$$

An Energy-Efficient Charge Recycling Approach
for a SAR Converter With Capacitive DAC, ISCAS'05

Switching Energy

- The capacitor switched from ground to V_{REF} consumes $E_{0 \rightarrow 1}$

$$E_{0 \rightarrow 1} = CV_{REF}(V_{REF} - \Delta V_X) \quad (1)$$

- The remaining capacitor connected to V_{REF} consumes E_{TOP}

$$E_{TOP} = CV_{REF}(-\Delta V_X) \quad (2)$$


Example

- The first step switches 4C to V_{REF} and consumes
- The second step switches 1C from V_{REF} to ground on non-inverting input, and 1C from ground to V_{REF} on inverting input. That consumes


$$CV_{REF}(V_{REF}-V_{cm})\times 4=2CV_{REF}^2$$

$$CV_{REF}\left(-\left(-\frac{1}{4}V_{REF}\right)\right)=\frac{1}{4}CV_{REF}^2$$
 
$$CV_{REF}\left(V_{REF}-\left(\frac{1}{4}V_{REF}\right)\right)+CV_{REF}\left(-\left(\frac{1}{4}V_{REF}\right)\right)\times 2=\frac{1}{4}CV_{REF}^2$$



Reset Energy

 


- Reset energy is defined as DAC energy consumed before the next sampling
- Some switching method consumes zero reset energy. Ex: V_{cm} -based and set-and-down switching method
- Some switching method consumes reset energy. Ex: CAS switching method

Outline

1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation

Conventional Switching

 

3-bit Conventional DAC switching procedure

Split Capacitor Switching

 


Fig. (a) 2-bit Split capacitor DAC (b) MSB capacitor C_2 has been split into $C_{2,1}$ and $C_{2,2}$

- Split the MSB capacitor into sub-array which is same as the remaining capacitor array
- “down” transition is power-efficient

Set-and-Down Switching

 


Fig. 3-bit set-and-down DAC switching procedure

- Reset to reference high, V_{REF} , then monotonically switch down
- Common mode voltage varies with every transition

Vcm-Based Switching

 


Fig. 3-bit Vcm-based DAC switching procedure

- Additional voltage source V_{cm} is needed
- Common mode voltage is fixed

Capacitor Average Switching


 


Fig. 4-bit CAS DAC switching procedure

- Efficient switching energy but has reset energy

Switching Energy Comparison

 

10-bit DAC switching energy

Switching Energy Comparison

	Conventional	Split cap	Set-and-down	Vcm-based	CAS
Normalized Energy(%)	100	62.5	18.75	12.5	8.37
No. of switches	$6n+6$	$12n-2$	$4n-2$	$6n-4$	$8n-8+2m$
No. of binary caps	$2n+2$	$4n$	$2n$	$2n$	$4n-4$
No. of unit caps	2^n	2^n	2^{n-1}	2^{n-1}	2^{n-1}

† “m” depends on how many steps using CAS technique

Table. Comparison of switching schemes for N-bit SAR ADC

Outline

1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation



Single-Pole Amplifier

- The comparator amplification gain is

$$U = \frac{V_o}{V_i} = A_o [1 - e^{-t_a/(RC)}] \quad A_o = g_m R \quad \tau_m = \frac{C}{g_m}$$

- The relation between amplification gain U and time t_a is
  
$$\frac{t_a}{\tau_m} = A_o \times \ln\left(\frac{1}{1 - \frac{U}{A_o}}\right)$$





Positive-Feedback Regeneration

- The comparator amplification gain is

$$\begin{aligned}
 C \frac{dV_{O1}}{dt} + \frac{V_{O1}}{R} + g_m V_{O2} &= 0 & C \frac{dV_O}{dt} + \frac{V_O}{R} + g_m V_O &= 0 \\
 C \frac{dV_{O2}}{dt} + \frac{V_{O1}}{R} + g_m V_{O1} &= 0 & V_O &= V_{O1} - V_{O2}
 \end{aligned}
 \Rightarrow
 \begin{aligned}
 U = \frac{V_O(t_a)}{V_O(0)} &= e^{t_a/\tau_r} & A_O &= g_m R \\
 \tau_r = \frac{RC}{A_O - 1} &= \frac{\tau_m}{1 - 1/A_O} & \tau_m &= \frac{C}{g_m}
 \end{aligned}$$

- The relation between amplification gain U and time t_a is
  
$$\frac{t_a}{\tau_m} = \frac{1}{1 - \frac{1}{A_O}} \times \ln(U)$$




Offset of a Source-Coupled Pair

- The equivalent input offset is

$$\sigma^2(V_{OS}) = \sigma^2(\Delta V_t) + \left(\frac{V_{OV}}{2}\right)^2 \times \frac{\sigma^2(\Delta\beta)}{\beta^2} = \frac{1}{W \times L} \left(A_{V_t}^2 + \frac{V_{OV}^2}{4} \times A_{\beta}^2 \right)$$
 
$$\beta = \mu C_{ox} \frac{W}{L} \quad \sigma^2(\Delta V_t) = \frac{A_{V_t}^2}{W \times L} \quad \frac{\sigma^2(\Delta\beta)}{\beta^2} = \frac{A_{\beta}^2}{W \times L}$$





Comparator Typical Architecture

- The equivalent input offset is


$$V_{OS} = V_{OSA} + \frac{V_{OSL}}{A} \quad \sigma^2(V_{OS}) = \sigma^2(V_{OSA}) + \frac{\sigma^2(V_{OSL})}{A^2}$$

  - The preamplifier provides:
 - Input common-mode rejection
 - Kick-back noise reduction




Regenerative Latch

 - When CLK=0, latch is disable and no power dissipation.
- When CLK=1
 - The M1-M2 pair is activated first
 - The M3-M4 pair is then activated
 - The M5-M6 pair is last activated.



Kickback-Noise

 - After comparison, one of the comparator output would force to ground and the other to supply voltage
- The comparator inputs coupled with different voltage resulting a equivalent noise source.
- The coupled value is corresponding to the ratio of parasitic capacitance of comparator input device and the loading capacitance of comparator input



Comparator Trade-Off

- For a MOS pair, mismatch and input-referred offset are modeled as

$$\sigma^2(V_{OS}) = \frac{1}{W \times L} \left(A_{V_t}^2 + \frac{V_{OV}^2}{4} \times A_{\beta}^2 \right)$$

- For a comparator


$$\text{Speed} \propto \frac{g_m}{C} \approx \frac{2I / V_{OV}}{(2/3) \cdot WL \cdot C_{OX}} \quad \frac{1}{\text{Accuracy}^2} \propto \frac{\sigma^2(V_{OS})}{V_{DD}^2} \approx \frac{A_{V_t}^2 + \frac{V_{OV}^2}{4} \times A_{\beta}^2}{WL \times V_{DD}^2}$$

$$\text{Power} \propto I \cdot V_{DD} \Rightarrow \frac{\text{Speed} \times \text{Accuracy}^2}{\text{Power}} \propto \frac{1}{C_{OX} \cdot \left(A_{V_t}^2 + \frac{V_{OV}^2}{4} \times A_{\beta}^2 \right)} \times \frac{V_{DD}}{V_{OV}}$$

K. Uyttenhove and M. Steyaert, "Speed-power-accuracy tradeoff in high-speed CMOS ADCs," TCAS-II, 2002/4, pp. 280–286.


Variable-Offset Regenerative Latch

 - Comparator offset is adjusted by varying C_1 and C_2 , or I_1 and I_2 .



Comparator offset Calibration

 - During Calibration, $V_i = V_{i1} - V_{i2} = 0$.




Outline

 1. Basic Operation Principle of SAR ADC
2. Block Introduction (S/H, DAC, Comparator, SAR)
3. DAC Switching Energy Calculation
4. DAC Switching Method
5. Comparator Requirement (Matching)
6. SAR Logic Implementation

SAR ADC Architecture



- The SAR ADC is composed of a sample and hold (S/H), DAC, comparator and digital SAR control logic.
- N comparisons per conversion
- DAC voltage is converged to input voltage by SAR Control, which is determined by comparison results



Traditional SAR Logic

- The function of SAR is determined by the value of each bit in a sequential manner, based on the output of comparator.
- Minimized the amount of DFF.

A	B	
1	-	Memorization
0	1	Data load
0	0	Shift right

  


FSM of SAR Logic

Conversion step	Input D/A word									Comparator output
0	1	0	0	0	0	0	0	0	0	a7
1	a7	1	0	0	0	0	0	0	0	a6
2	a7	a6	1	0	0	0	0	0	0	a5
3	a7	a6	a5	1	0	0	0	0	0	a4
4	a7	a6	a5	a4	1	0	0	0	0	a3
5	a7	a6	a5	a4	a3	1	0	0	0	a2
6	a7	a6	a5	a4	a3	a2	1	0	0	a1
7	a7	a6	a5	a4	a3	a2	a1	1	0	a0
result	a7	a6	a5	a4	a3	a2	a1	a0	-	-


Rossi, A., "Nonredundant successive approximation register for A/D converters," *Electronics Letters* , no.12, pp.1055,1057, 6 Jun 1996

Full Custom Register Logics

Resettable shift register

 


Switch drive register

 

B.P. Ginsburg, A.P. Chandrakasan, "Dual Time-Interleaved Successive Approximation Register ADCs for an Ultra-Wideband Receiver," *JSSC*, vol.42, no.2, pp.247,257, Feb. 2007.



SAR ADC Flow Chart

 - First, SAR ADC samples input signal on DAC by the S/H.
- Next, after the S/H is turn-off, the comparator directly performs the first comparison.
- According to the comparator output, the digital output B_1 is determined and the DAC voltage is switched to converged.
- The ADC repeats the procedure until the MSB to LSB is decided.



Asynchronous SAR Logic

  - To avoid using a high-frequency clock generator, the asynchronous control circuit uses to internally generate necessary clock signals.



CLK_S : sampling clock

CLK_C : control signal of comp.

Valid : NAND of comp. outputs

CLK_i : CLK to store comp. output
& control SAR