Introduction to permanent-magnet synchronous motor drive and brushless DC motor drive

- Motor types and section (SPMSM, IPMSM, SynRM?).
- Governing equations.
- Key parameters and variables measurements.'
- Inverter-fed PMSM drives:
  - (Sinewave PMSM + sinewave inverter): Complicated control scheme.
  - (Square-wave PMSM + square-wave inverter).
  - Hybrid: e.g., (Square-wave PMSM + sine-wave inverter).
- Control schemes and realized environments?
- Filter between inverter and motor.
- AC/DC front-end converter.

#### Motor types and selection

Some typical rotor structures of synchronous motors (SMs): (a), (b), (c) SPMSM; (d), (e), (f) IPMSM; (g) PMASynRM; (h) SynRM; (i) SRM.



#### Some typical stator structures

- (a) 如圖(a),為salient pole,係集中式電樞
   繞組(Concentrated winding)之定子結構:
   具有短的end turns,相與相間之 coupling
   較小,每一相之線圈不同時,與所有轉
   子磁鐵作用時,導致性能之降低。
- (b) 如圖(b),沒有slot (Slot-less),故沒 有齒隙轉矩(Cogging torque),但線圖 與後鐵間之熱導低,不利負荷之增 加。又因沒有靜子齒,使得氣隙增長 成轉子表面至後鐵,為維持適當大之 PC值,磁鐵之長度須增長。
- (c) 如圖(c),為槽式用以容置分佈式繞組
   (Distributed winding),具有shoes在氣隙
   處,可減少氣隙磁導隨位置之變化,而
   減少Cogging torque。







## Difference between square-wave and sine-wave BDCMs

#### ■ Square-wave BDCM:

- -- Rectangular distribution of air-gap magnet flux;
- -- Rectangular winding current waveforms;
- -- Concentrated stator armature winding.

### ■ Sine-wave BDCM:

- -- Sinusoidal or quasi-sinusoidal distribution of air-gap magnet flux;
- -- Sinusoidal or quasi-sinusoidal winding current waveforms;
- -- Quasi-sinusoidal stator armature conductors, i.e., short-pitched and distributed stator armature conductors.

If the stator winding current is not pure sine wave, and if the stator winding distribution is not purely sinusoidal, the time harmonics of the current can interact the space-harmonics of the conductor distribution to produce large torque ripple with only a slight increase of average torque.

<u>Concentrated armature winding</u> (Square-wave motor)



#### Distributed armature winding (Sine-wave motor)



*<u>Three-phase</u> armature currents* 





# **Classification of BDCMs**

# Speed servo drive (square-wave BDCM): not suited for lower operation speeds

(a) Normally: concentrated armature windings.(b) Usually called BDCM.

- Using photo sensor
- Using Hall sensor

# **Notice Serve Arive: Sine-wave BDCM**

(a) Normally: distributed armature windings.(b) Usually called PMSM.

Sine-wave motor driven by square-wave inverter: theoretical torque ripple at low speed >= 13%.

#### BDCM PWM switching signal waveforms





#### Sine-wave BDCM Operation principle and commutation instant tuning

**Brushless DC Motors (BDCMs):** PMSM with winding commutation according to the sensed rotor position.



- Special application cases:
  - The SPMSMs are also found in high-speed applications. However, some key affairs should be treated:
  - The permanent-magnet volume and thus the back-EMF at the maximum speed must be properly determined.
  - (2) Inverter DC-link voltage must be properly set.
  - (3) The demagnetization risk in real operation must be cared, especially for the position sensorless controlled PMSM drive.

#### Effects of non-ideal current waveforms



## 永磁同步馬達之參數估測 (Parameter estimation of PMSM)

Experimental mechanism for making parameter estimation



- Equivalent circuit parameter estimation: rotor is locked at a particular position and the winding is excited with a variable-frequency and variable-current AC source.
- Slip test: the rotor is driven at a speed slightly different from synchronous speed.
- The voltage, current and power are recorded.
- Back-EMF: measure motor open-circuit terminal voltages at different driven speeds.

## 换相時刻調整



▶ 機械對位調整

● 電氣對位調整

霍爾位置感測信號相位調校之機構



#### 調整後量測所得之感測馬達之開路端電壓



# Per-phase equivalent circuit model



- $\boxtimes$  Back EMF constant estimation:  $e_d = k_t \omega_r$
- $\boxtimes$  Flux linkage amplitude estimation:  $\lambda'_m$
- (a) Considering the correct measurement;(b) observing the wave shape of the back EMF.

# $\boxtimes$ Winding inductances

$$\begin{aligned} L_{asas} &= L_{ls} + L_A + L_B \cos 2\theta_r \\ L_{bsbs} &= L_{ls} + L_A + L_B \cos 2(\theta_r - \frac{2\pi}{3}) \\ L_{cscs} &= L_{ls} + L_A + L_B \cos 2(\theta_r + \frac{2\pi}{3}) \\ L_{asbs} &= L_{bsas} = -\frac{1}{2}L_A + L_B \cos 2(\theta_r - \frac{\pi}{3}) \\ L_{ascs} &= L_{csas} = -\frac{1}{2}L_A + L_B \cos 2(\theta_r + \frac{\pi}{3}) \\ L_{bscs} &= L_{csbs} = -\frac{1}{2}L_A + L_B \cos 2(\theta_r + \pi) \end{aligned}$$







## Y-connected with non-isolated neutral



$$\begin{split} \boxed{\mathbf{X}} \quad v_s = v_{as} = r_s i_{as} + \frac{d}{dt} \Big[ \big( L_{ls} + L_A + L_B \cos 2\theta_r \big) i_{as} \Big] = r_s i_{as} + \frac{d}{dt} \Big[ L_{asas} \left( \theta_r \right) i_{as} \Big] \\ L_{asas, \max} = L_{asas} \left( \theta_r = 0 \right) = L_{ls} + L_A + L_B \\ L_{asas, \min} = L_{asas} \left( \theta_r = 0.5\pi \right) = L_{ls} + L_A - L_B \\ L_q \approx \frac{3}{2} L_{asas, \max}, \quad L_d \approx \frac{3}{2} L_{asas, \min} \\ L_q \approx \frac{3}{2} (L_A + L_B), \quad L_d \approx \frac{3}{2} (L_A - L_B) \end{split}$$

## Y-connected with non-isolated neutral



$$v_{s} = v_{as} - v_{bs} \quad i_{bs} = -i_{as} \quad i_{cs} = 0 \quad \omega_{r} = 0$$

$$R_{s} = \frac{1}{2}R_{ab}$$

$$L_{q} = \frac{1}{2}L_{asbs,max}$$

$$R_{ab} = 2R_{s}$$

$$L_{ab}(\theta_{r}) = 2L_{ls} + 3L_{A} - 3L_{B}\cos(2\theta_{r} - 2\pi/3)$$

17

#### **Estimation of Key Motor Parameters: Example**

#### **PM Flux Linkage** $\lambda'_m^r$ and **Back EMF Constant** $k_e$ .

- Three Y-connected resistors with reasonably high resistance ( $100k\Omega$ ) are connected at the stator terminals to measure the motor phase back-EMF at no-load.
- Let the PMSM be driven at a constant speed with terminal open-circuited.

$$i_{as} = i_{bs} = i_{cs} = 0$$

$$\implies v_{as} = \omega_r \lambda_m^r \cos \theta_r \underline{\Delta} \hat{E}_d \cos \theta_r \underline{\Delta} e_{as}$$

$$\implies \lambda_m^r = \frac{\hat{E}_d}{\omega_r}, \qquad E_d = k_e \omega_r$$

Estimated parameters:

$$\lambda_m^{'r} = 0.00858$$
 Web,  $k_e = 3.81$  V<sub>rms</sub>/krpm



• For simplicity, the parameters  $R_{ab}$  and  $L_{ab}(\theta_r)$  are measured using off-the-shelf LCR meter (3532-50 LCR HiTester, HIOKI)



**Estimated parameters** (f = 200 Hz):

 $\overline{R}_s = 0.60625\Omega$ 

$$L_q = 1/2(L_{ab,max}) = 328.415 \mu H$$
  
 $L_d = 1/2(L_{ab,min}) = 214.635 \mu H$ 

- The parameters measured using LCR meter will not be accurate owing to its small-signal level excitation.
- The effects of inaccuracy and variations of motor parameters on the motor driving control performance will be handled by the proposed robust control approaches.

## Possible control schemes for BDCMs

Square-wave BDCM drive using direct duty ratio control (without current-mode control)





Without current control loops.
Simple implementation.
Lower driving performance.

### Measured results



Measured waveforms of Hall sensor signal *HA*, motor line current  $i_{as}$ , the switching signals  $GT_1$  and  $GT_4$  of squarewave type BDCM drive with 120° conduction: (a) 1000 *rpm*,  $R_L = 32.7\Omega$ ; (b) 2500 *rpm*,  $R_L = 32.7\Omega$ .

#### Sine-wave BDCM Operation principle and commutation instant tuning



# BDCM drive using sine-wave current-mode control (abc-domain)



## Measured results



Fig. 2.16. Measured waveforms of Hall sensor signal HA, motor line current  $i_{as}$  and command  $i_{as}^*$ , the switching signals  $GT_1$  and  $GT_4$  of sine-wave type BDCM drive with current-controlled PWM switching control: (a) 1000 rpm,  $R_L = 32.7\Omega$ , (b) 2500 rpm,  $R_L = 32.7\Omega$ .

# BDCM drive using robust sine-wave current-mode control with d-axis excitation control (dq-domain)



Fig. 4.3. Configuration of the CCPWM scheme in dq-domain.

## Measured results



Fig. 4.12. Measured winding currents and commands due to a step speed command change ( $R_L = 21.6\Omega$ ,  $\omega_r = 2700$ rpm  $\rightarrow 3000$ rpm) in dq-domain:(a) PI controller (W=0); (b) robust controller (W=0.9).

### Measured results





Reference frame transformation

$$\begin{array}{c} \bullet \quad abc \ to \ dq \quad \begin{bmatrix} f_{qs}^r \\ f_{ds}^r \\ f_{ds}^r \\ f_{ds}^r \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos \theta_r & \cos(\theta_r - \frac{2\pi}{3}) & \cos(\theta_r + \frac{2\pi}{3}) \\ \sin \theta_r & \sin(\theta_r - \frac{2\pi}{3}) & \sin(\theta_r + \frac{2\pi}{3}) \\ \frac{1}{2} & \frac{1}{2} & \frac{1}{2} \end{bmatrix} \begin{bmatrix} f_{as} \\ f_{bs} \\ f_{cs} \end{bmatrix} \\ \begin{array}{c} \theta_r = \text{rotor absolute} \\ \text{angular position} \end{bmatrix} \\ \begin{array}{c} \theta_r = \text{rotor absolute} \\ \theta_r = \text{rotor absolute} \\ \text{angular position} \end{bmatrix} \\ \begin{array}{c} \theta_r = \text{rotor absolute} \\ \theta_r = \text{rotor absolute}$$

The sine-wave winding current can also be roughly obtained by applying SPWM voltage mode excitation:

- Without current control loops.
- Simple implementation (however, how to realize SPWM schemes?).
- Lower current and thus torque dynamic performances.
- The driving performance can be improved via commutation instant shift (Example IPMs: Toshiba: TB6551 sine-wave controller, TB6581H 3-Phase full-wave sine-wave PWM brushless motor rriver = TB6551 + TPD4103AK high-voltage driver.

# Some example commercialized sine BDCM drives



PID: Proportional-Integral-Derivative
dq/UVW: Conversion from the dq axis to
the UVW phase *Q*: Supplementary control added to
PID control *Q*rat: Motor's angular speed target
Idrt,Iqrt: Motor current target in the dq axis
Iu,Iv,Iw: Motor current in the U, V and W
phases of a three-phase alternating current
PWM: Pulse width modulation
UVW/dq: Conversion from the UVW phase
to the dq axis
(*Q*: Motor current in the dq axis
Vd,Vq: Motor current in the dq axis

\* Coordinate system where the magnetic pole direction of a motor's rotor is the d axis and the direction orthogonal to it is in the q axis



B. Standard Square-wave PMSM Driven Cooling Fan



#### SMR Application examples: Front-end of motor drives

- 對於一變頻器供電之交流馬達而言,雖然變頻器之PWM控制具有變頻變 壓控制能力,但在變頻器之前端加裝一切換式整流器(Switching-mode rectifier, SMR)以建立直流鏈電壓,更具調壓彈性,可得良好之高速驅動 特性,及提升入電之電力品質。(The equipment of SMR front-end: can provide well-regulated and boosted DC-link voltage to improve the operation performance of a motor drive, particularly the high speed operations.)
- 變頻器直流鏈之電壓如為可調變一般稱為 (Pulse-width modulated, PAM) 變頻器,藉由直流鏈電壓之調變可使方波變頻器之輸出成為近乎弦波。 然而PAM之操控性能較差,僅適用於速度驅動。但如將PWM佐以PAM, 可得較佳之控制彈性及性能。((PAM + PWM) >> can increase the control flexibility and performance of a motor drive.)



#### Some typical single-phase SMRs:

(a) boost SMR; (b) buck SMR; (c) buck- boost SMR; (d) Ćuk SMR; (e) buck-boost cascade SMR; (f) boost-buck hybrid SMR; (g) flyback SMR; (h) isolated ZETA SMR.



33

## Flyback SMR (Flyback 切換式整流器)



