


Chapter 1

Circuit Variables

- 1.1 Electrical Engineering: An Overview
- 1.2 The International System of Units
- 1.3 Circuit Analysis: An Overview*
- 1.4 Voltage and Current
- 1.5 The Ideal Basic Circuit Element
- 1.6 Power and Energy

Key points

- What is the **lumped-parameter assumption** upon which all the circuit analysis methods introduced in this course are founded?
- What is the **passive sign convention** that is used in unambiguously defining the sign of each formula in circuit analysis?

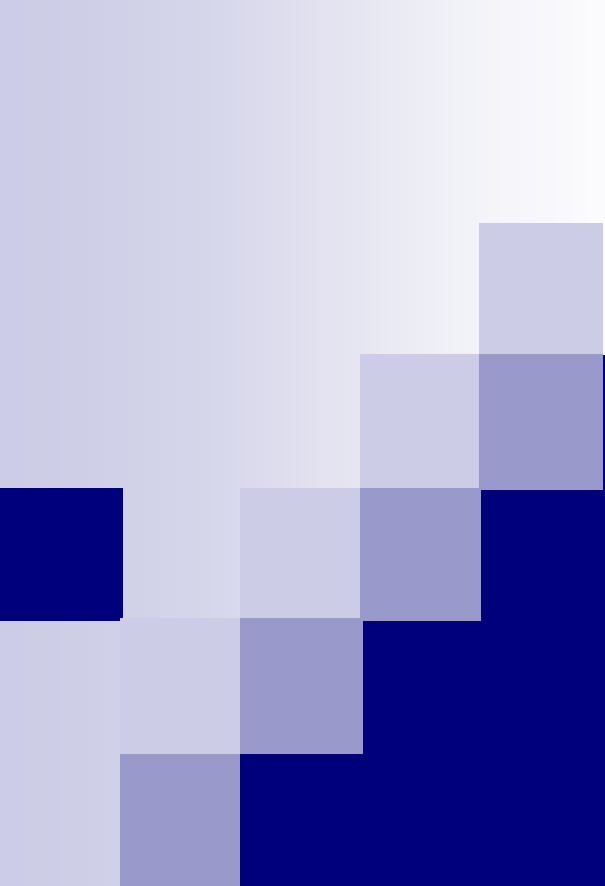

Section 1.1


Electrical Engineering: An Overview

1. Electric circuits
2. Lumped-parameter assumption

What is an electric circuit?

- A **mathematical model** that approximates the behavior of an actual electrical system.

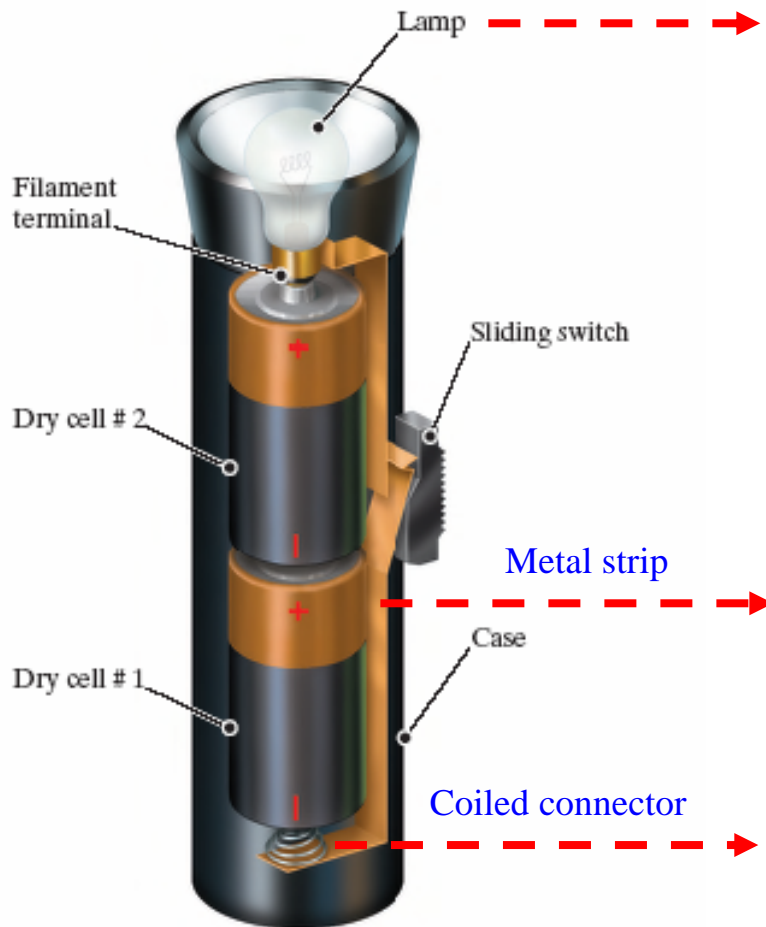Example: Electric Circuit of a Flash Lamp (1)



Physics: Filament is heated to a temperature high enough to radiate the visible light.

Modeling: a resistor R_l (only accounts for conversion of electric energy to thermal energy, not light energy).



Physics: Conductive connection.

Modeling: a resistor R_c

Physics: Conductive connection.

Modeling: a resistor R_1

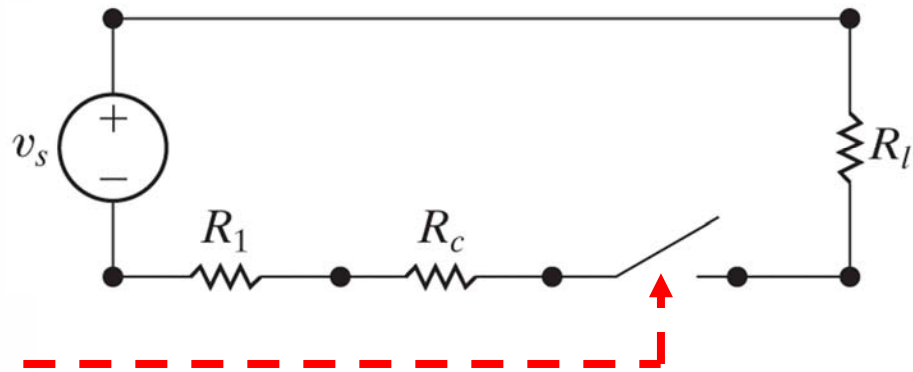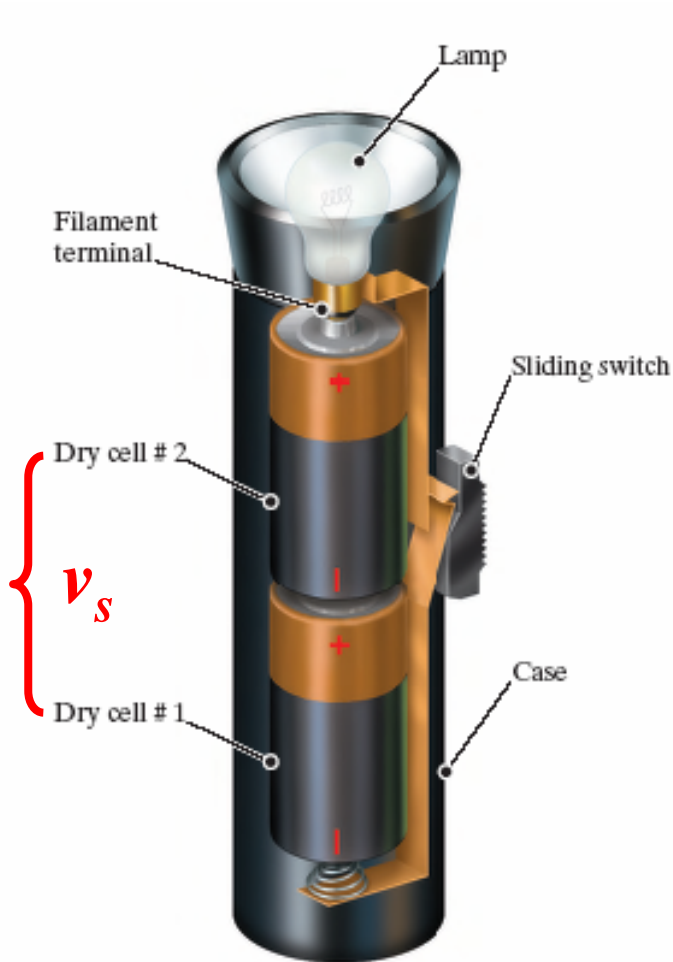Example: Electric Circuit of a Flash Lamp (2)



- Only electric behavior is accounted: lamp, coiled connector, metal strip are modeled by the same element (resistor).
- Modeling requires approximations: ignore internal dissipation of the dry cells.


What is the circuit theory?

- A simplified version of electromagnetic field theory, which is accurate under **low frequency** condition.

What is the electromagnetic theory?

- Electric charge \rightarrow electric field.
- Electric current (moving charge) \rightarrow magnetic field.
- Time-varying fields \rightarrow electromagnetic wave with properties of propagation, reflection, ...

E.g.

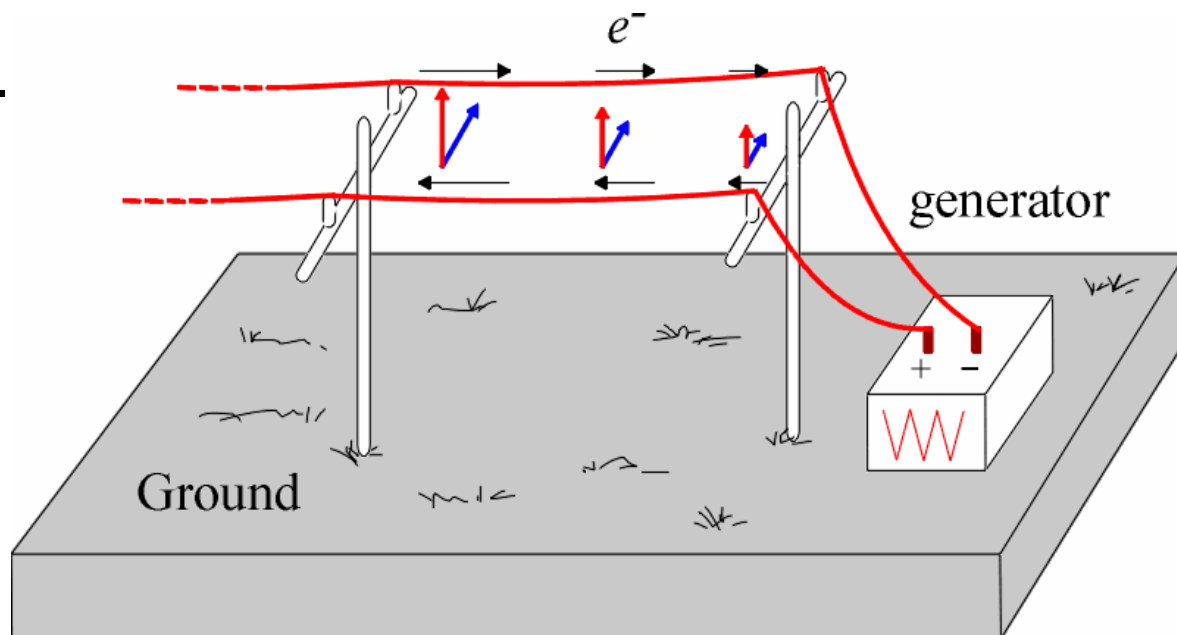

Lumped-parameter assumption

- If the circuit size is $< \lambda/10$ ($\lambda = c/f$), electrical effects are supposed to reach every corner of the circuit instantaneously. \Rightarrow Electric signals do not change along the wire. All changes take place across the “lumped” elements.
- E.g. Electric power is distributed with $f = 60$ Hz, $\Rightarrow \lambda = (3 \times 10^8)/60 = 5 \times 10^6$ m. Power distribution networks smaller than $\lambda/10 = 500$ km can be treated by circuit theory.

Taiwan




Russia



Pacific Ocean



Example: A resistive circuit

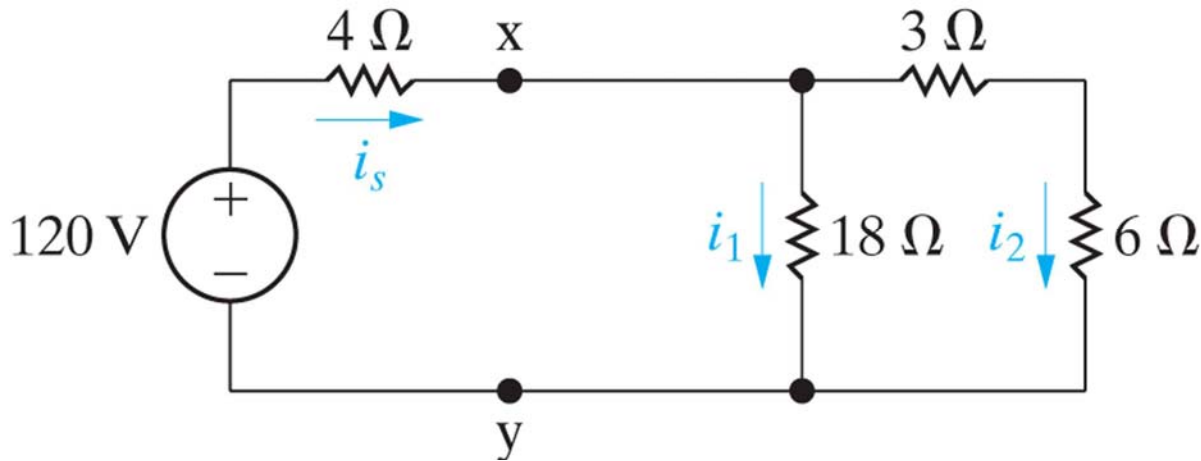

- Once the 120-V voltage is connected, currents $i_1 = 4 \text{ A}$, $i_2 = 8 \text{ A}$ are assumed to **immediately** flow through the 18-Ω and 6-Ω resistors.
- According to electromagnetic theory, different resistors will sense the 120-V at different times.



Section 1.2

The International System (SI) of Units

1. Units
2. Prefixes

What are SI units?

- Abbreviation from French “Système international d'unités”, established in 1960.
- The SI Units are based on 7 defined quantities: length (m), mass (kg), time (s), current (A), temperature (K), amount (mol), luminous intensity (cd).
- SI units enable engineers to communicate in a meaningful way about quantitative results.

Derived units in SI

Quantity	Unit Name (Symbol)	Formula
Frequency	hertz (Hz)	s^{-1}
Force	newton (N)	$kg \cdot m/s^2$
Energy or work	joule (J)	$N \cdot m$
Power	<u>watt (W)</u>	J/s
Electric charge	coulomb (C)	$A \cdot s$
Electric potential	volt (V)	J/C
Electric resistance	ohm (Ω)	V/A
Electric conductance	siemens (S)	A/V
Electric capacitance	farad (F)	C/V
Magnetic flux	weber (Wb)	$V \cdot s$
Inductance	henry (H)	Wb/A

Prefixes to signify powers of 10 (1)


- Engineers often use powers divisible by 3, and base numbers between 1 and 1,000.

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}

Prefixes to signify powers of 10 (2)

Prefix	Symbol	Power
deka	da	10
hecto	h	10 ²
kilo	k	10 ³
mega	M	10 ⁶
giga	G	10 ⁹
tera	T	10 ¹²

- E.g. 10^{-5} s is denoted by 10 μ s, instead of 0.01 ms.

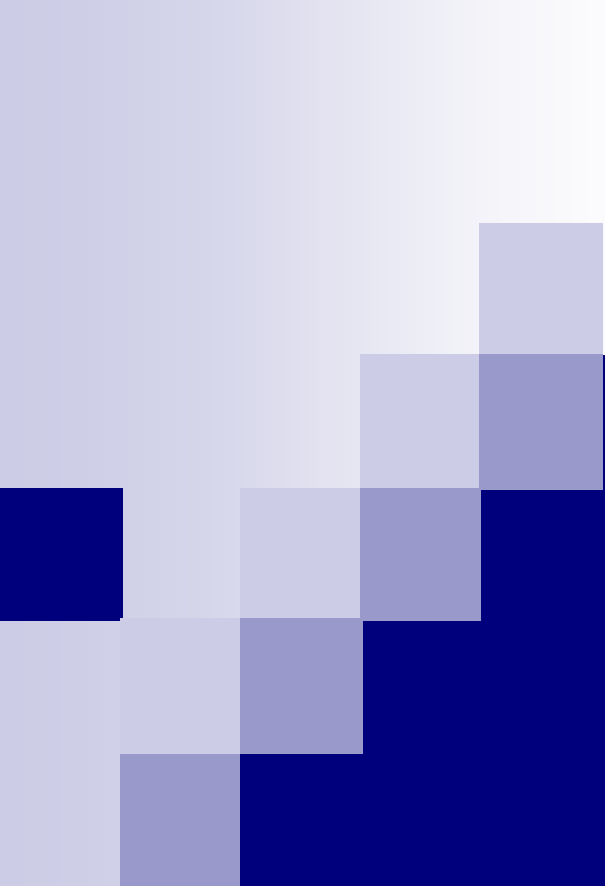

Section 1.4

Voltages and Currents

1. Definition of voltage
2. Definition of current

Voltages

- Voltage is the energy per unit charge.

$$v = \frac{dw}{dq} \quad \dots \text{definition of magnitude}$$

v = the voltage in volts

w = the energy in joules

q = the charge in coulombs ($e = 1.6022 \times 10^{-19}$ C)

Currents

- Current is the rate of charge flow.

$$i = \frac{dq}{dt} \text{ ...definition of magnitude}$$

i = the current in amperes

q = the charge in coulombs

t = the time in seconds




Section 1.5

The Ideal Basic Circuit Element

1. Definition of basic circuit element
2. Passive sign convention


Three attributes & symbol

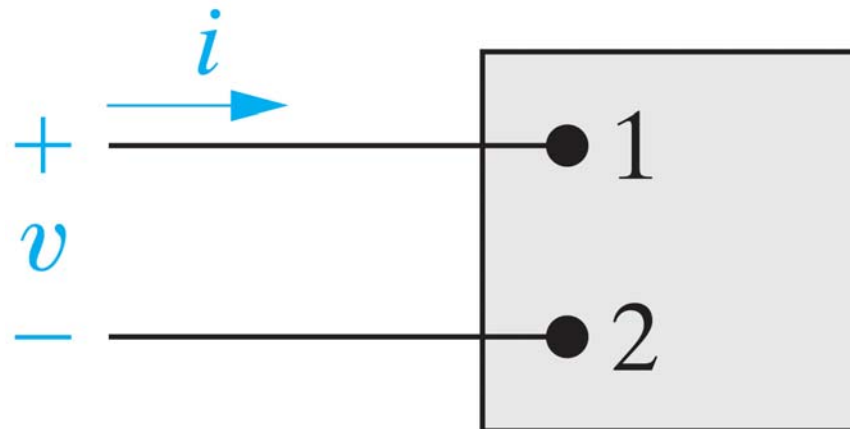
1. Only **two terminals**, which are points of connection to other circuit components.
2. Described mathematically in terms of the voltage across it and/or the current through it.
3. Cannot be subdivided into other elements.



Passive sign convention

- If the reference current through the element is in the direction of the reference **voltage drop** across the element, we can use a **positive sign** in the i - v relation of the element.
- E.g. Let the reference current and voltage of the resistor satisfy the passive sign convention, \Rightarrow we have $v = +R \times i$, though the values of v , i can be >0 or <0 .

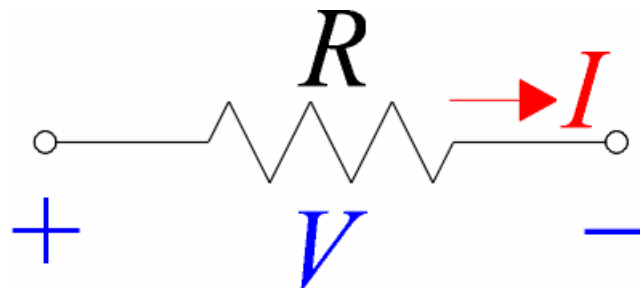

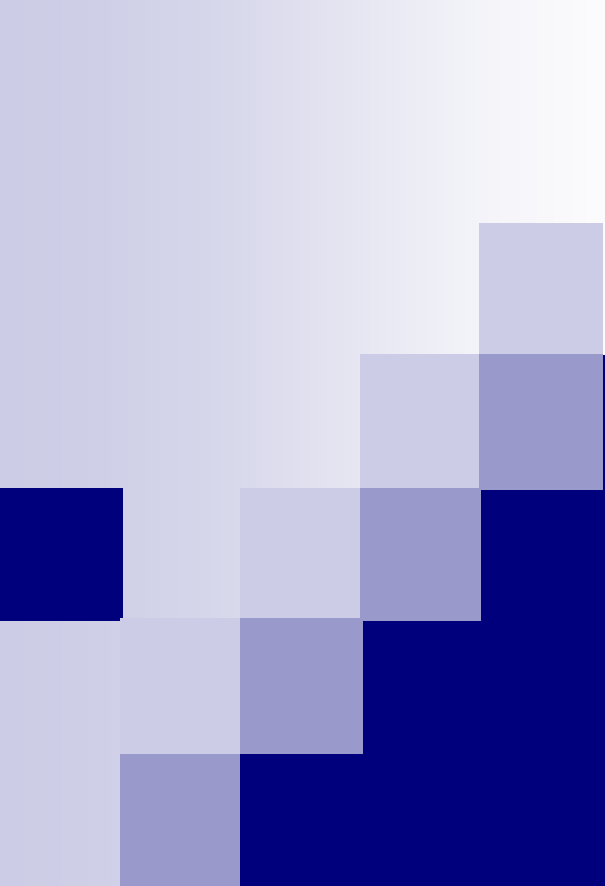

Section 1.6

Power and Energy

1. Definition and formula of power
2. Sign of power

Powers

- Power is the energy per unit time.

$$p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = v \times i.$$

p = the power in watts

w = the energy in joules


t = the time in seconds

v = voltage in volts


i = current in amperes

- Power is associated with **two** terminals.

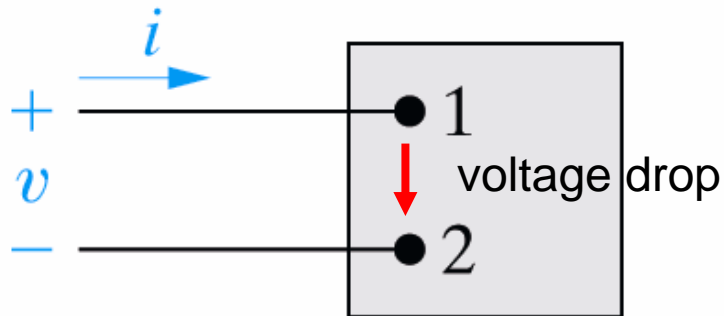
Polarity references and power expressions




(a) $p = vi$

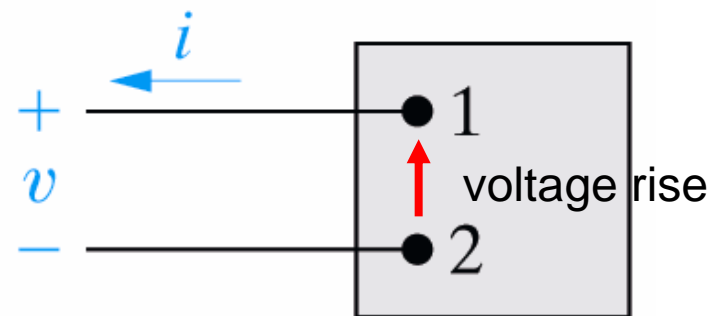

(b) $p = -vi$

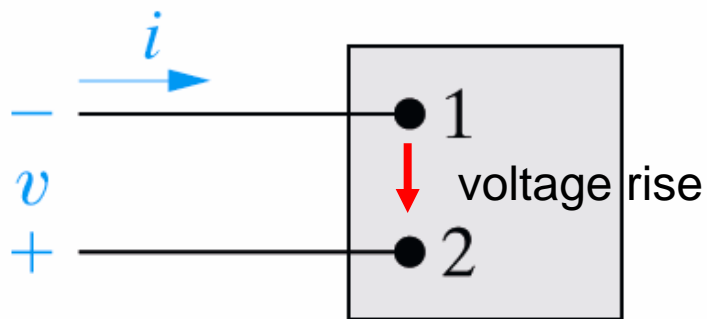

(c) $p = -vi$

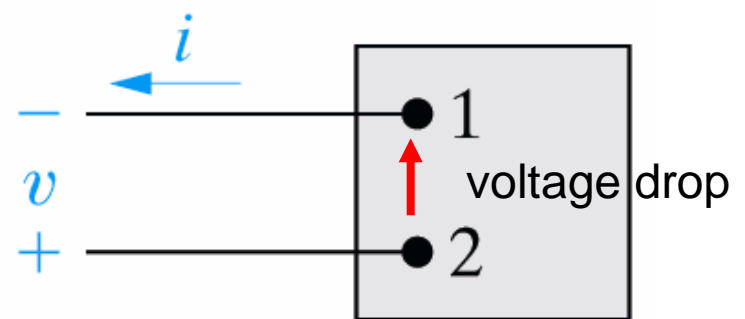

(d) $p = vi$

Power dissipation and extraction

- As positive charges experience voltage drop, they lose energy.
- $p > 0$ (not $p = +vi$): power is **dissipated** by the circuit inside the box.
- $p < 0$ (not $p = -vi$): power is being **extracted**.

Key points

- What is the **lumped-parameter assumption** upon which all the circuit analysis methods introduced in this course are founded?
- What is the **passive sign convention** that is used in unambiguously defining the sign of each formula in circuit analysis?