# Chapter 2 Circuit Elements

- 2.1 Voltage and Current Sources
- 2.2 Electrical Resistance (Ohm's Law)
- 2.3 Construction of a Circuit Model
- 2.4 Kirchhoff's Laws
- 2.5 Analysis of a Circuit Containing Dependent Sources



- Microscopic view of Ohm's law.
- Physics of Kirchhoff's laws.

Section 2.1 Voltage and Current Sources

- 1. Ideal sources
- 2. Real sources
- 3. Dependent sources

Ideal voltage and current sources

- Ideal voltage source: maintains a prescribed voltage regardless of the current in the device.
- Ideal current source: maintains a prescribed current regardless of the voltage in the device.



# Real voltage sources

- The output voltage  $V_o$  will change with the (1) the output current  $I_o$ , (2) the load resistance  $R_L$ .
- The entire source is modeled by an ideal one plus a series resistor  $R_S$ .



# **Real current sources**

- The output current  $I_o$  will change with the (1) the output voltage  $V_o$ , (2) the load resistance  $R_L$ .
- The entire source is modeled by an ideal one plus a parallel resistor  $R_{S}$ .



### Independent vs. dependent sources

- Independent sources: The output voltage (current) is not influenced by any other voltage or current in the circuit. All the cases shown above belong to this category.
- Dependent sources: The output voltage (current) is determined by some other voltage or current in the circuit. This happens when the circuit has active devices (e.g. transistors).

# Symbols of dependent sources



Section 2.2 Electrical Resistance (Ohm's Law)

- 1. Physics
- 2. Electric power

Microscopic view of conductors

- A conductor is made of (1) immobile ions, and (2) free electrons that move fast (Fermi speed,  $v_F \sim 10^6$  m/s) and randomly.
- When an external E-field is applied, electrons have slow (~mm/s) drift velocity v<sub>d</sub> statistically.



#### Ohm's law

The drift velocity v<sub>d</sub> (∞ net current i) is proportional to the applied electric field E (∞ applied voltage v), resulting in:

$$v = iR$$

if passive sign convention is held:



#### Comments

- The Ohm's law is valid for good conductors, instead of every material. Counter examples: vacuum tubes ( $I \propto V^{1.5}$ ), transistors ( $I \propto e^{\alpha V}$ ).
- Resistance depend on material, shape, and the way of connection. E.g. washer resistor:



# **Electric power consumption**

- Microscopically, frequent collisions between free electrons and immobile ions transfer energy from electric field to thermal vibration.
- Power in a resistor in terms of current:

$$p = vi = (iR)i = i^2R$$

Power in a resistor in terms of voltage:

$$p = \frac{v^2}{R}$$

#### Example 2.3



$$v_a = 1 \times 8 = 8 \text{ V}$$
  
 $p = vi = 8 \times 1 = 8 \text{ W}$ 



$$v_c = iR = (-1) \times 20 = -20 \text{ V}$$
  
 $p = vi = (-20) \times (-1) = 20 \text{ W}$ 

• vi > 0, power is always dissipated in a resistor.

# Section 2.4 Kirchhoff's Laws

- 1. Nodes & loops
- 2. Kirchhoff's laws & the physics

# Nodes and loops

- Electric circuits consist of connected basic circuit elements.
- A node is a point where two or more circuit elements join.
- A loop is a closed path, starting and ending at the same node without passing through any intermediate node more than once.

# Example:



Kirchhoff's current law (KCL)

- The algebraic sum of all the currents at any node in a circuit equals zero.
- Microscopic equivalent: Conservation of charges.

Kirchhoff's voltage law (KVL)

- The algebraic sum of all the voltages around any loop in a circuit equals zero.
- Microscopic equivalent: Static electric field is conservative

$$\oint \vec{E} \cdot d\vec{l} = 0,$$

which is not true in time-varying cases!

#### Example 2.6: KCL



Apply KCL over Node b:

 $(-i_1) + i_2 + (-i_a) + i_3 + (-i_b) = 0$ 

Example 2.7: KVL



Apply KVL over Loop a:

$$(-v_1) + v_2 + v_4 + (-v_b) + (-v_3) = 0$$

Section 2.5 Analysis of a Circuit Containing Dependent Sources

# Step 1: Specify unknowns



3 branch currents:  $\{i_{ab} = i_{\Delta}, i_{bc} = i_o, i_{cb} = 5i_{\Delta}\}, \Rightarrow$ only 2 independent unknowns,  $\Rightarrow$  need 2 independent equations.



- KVL for Loop cabc:  $500 = 5i_{\Delta} + 20i_o \dots (1)$
- KVL for Loop cbc: -20i<sub>o</sub>+(??) = 0, failed for voltage across a current source is undetermined.

• KCL for Node b:  $i_{\Delta} + 5i_{\Delta} = i_o \dots (2) \implies i_o = 24 \text{ A}.$ 

# Practical Perspective: Electrical Safety





- Burns is not the major electrical injury.
- Current can disturb the electrochemical signals of nerves that control oxygen supply to the brain or regulate heartbeat.
- Barely perceptible: 5 mA.
- Heart stoppage: 500 mA.



- Microscopic view of Ohm's law.
- Physics of Kirchhoff's laws.