# Chapter 7 Response of First-order RL and RC Circuits

- 7.1-2 The Natural Response of *RL* and *RC* Circuits
- 7.3 The Step Response of *RL* and *RC* Circuits
- 7.4 A General Solution for Step and Natural Responses
- 7.5 Sequential Switching
- 7.6 Unbounded Response

#### **Overview**

- Ch9-10 discuss "steady-state response" of linear circuits to "sinusoidal sources". The math treatment is the same as the "dc response" except for introducing "phasors" and "impedances" in the algebraic equations.
- From now on, we will discuss "transient response" of linear circuits to "step sources" (Ch7-8) and general "time-varying sources" (Ch12-13). The math treatment involves with differential equations and Laplace transform.

#### **First-order circuit**

A circuit that can be simplified to a Thévenin (or Norton) equivalent connected to either a single equivalent inductor or capacitor.



In Ch7, the source is either none (natural response) or step source.

# Key points

- Why an RC or RL circuit is charged or discharged as an exponential function of time?
- Why the charging and discharging speed of an RC or RL circuit is determined by RC or L/R?
- What could happen when an energy-storing element (C or L) is connected to a circuit with dependent source?

Section 7.1, 7.2 The Natural Response of RL and RC Circuits

- 1. Differential equation & solution of a discharging RL circuit
- 2. Time constant
- 3. Discharging RC circuit

# What is natural response?

- It describes the "discharging" of inductors or capacitors via a circuit of no dependent source.
- No external source is involved, thus termed as "natural" response.
- The effect will vanish as t→∞. The interval within which the natural response matters depends on the element parameters.

Circuit model of a discharging RL circuit

• Consider the following circuit model:



- For t < 0, the inductor L is short and carries a current  $I_s$ , while  $R_0$  and R carry no current.
- For t > 0, the inductor current decreases and the energy is dissipated via R.

Ordinary differential equation (ODE), initial condition (IC)

For t > 0, the circuit reduces to:

IC depends on initial energy of the inductor:  $i(0^+) = i(0^-) \equiv I_0 = I_s$ 



By KVL, we got a first-order ODE for i(t):

$$L\frac{d}{dt}i(t) + Ri(t) = 0.$$

where L, R are independent of both i, and t.

## Solving the loop current

$$\begin{aligned} \text{ODE} &: L \frac{d}{dt} i(t) + Ri(t) = 0, \quad \text{IC} : i(0^+) \equiv I_0 = I_s; \\ \Rightarrow L(di) + Ri(dt) = 0, \quad \frac{di}{i} = -\frac{R}{L} dt, \\ \Rightarrow \int_{i(0)}^{i(t)} \frac{di'}{i'} = -\frac{R}{L} \int_0^t dt', \quad \ln i' \Big|_{i(0)}^{i(t)} = -\frac{R}{L} t' \Big|_0^t, \\ \Rightarrow \ln i(t) - \ln i(0) = \ln \frac{i(t)}{I_0} = -\frac{R}{L} t, \\ \Rightarrow i(t) = I_0 e^{-(t/\tau)}, \text{ where } \tau = \frac{L}{R} \quad \dots \text{ time constant} \end{aligned}$$

Time constant describes the discharging speed

- The loop current *i*(*t*) will drop to *e*<sup>-1</sup> (≈37%) of its initial value *I*<sub>0</sub> within one time constant *τ*. It will be <0.01*I*<sub>0</sub> after elapsing 5*τ*.
- If *i*(*t*) is approximated by a linear function, it will vanish in one time constant.



Solutions of the voltage, power, and energy

• The voltage across R (or L) is:

$$v(t) = Ri(t) = \begin{cases} 0, \text{ for } t \leq 0^{-}, \\ RI_0 e^{-(t/\tau)}, \text{ for } t \geq 0^{+}. \end{cases}$$
 ...abrupt change at  $t = 0$ .

The instantaneous power dissipated in R is:

$$p(t) = i^{2}(t)R = I_{0}^{2}Re^{-(2t/\tau)}, \text{ for } t \ge 0^{+}.$$

The energy dissipated in the resistor R is:

$$w = \int_{0}^{t} p(t')dt' = I_{0}^{2}R\int_{0}^{t} e^{-(2t'/\tau)}dt'$$
  
=  $w_{0} \left[1 - e^{-(2t/\tau)}\right], \quad w_{0} = LI_{0}^{2}/2, \text{ for } t \ge 0^{+}.$   
initial energy stored in L

Example 7.2: Discharge of parallel inductors (1)

• Q: Find  $i_1(t)$ ,  $i_2(t)$ ,  $i_3(t)$ , and the energies  $w_1$ ,  $w_2$  stored in  $L_1$ ,  $L_2$  in steady state  $(t \rightarrow \infty)$ .



For t < 0: (1)  $L_1, L_2$  are short, and (2) no current flows through any of the 4 resistors,  $\Rightarrow$ 

 $i_1(0^-) = -8 \text{ A}, \ i_2(0^-) = -4 \text{ A}, \ i_3(0^-) = 0,$  $w_1(0^-) = (5 \text{ H})(8 \text{ A})^2/2 = 160 \text{ J}, w_2(0^-) = (20)(4)^2/2 = 160 \text{ J}.$  Example 7.2: Solving the equivalent RL circuit (2)

For t>0, switch is open, the initial energy stored in the 2 inductors is dissipated via the 4 resistors.

The equivalent circuit becomes:



• The solutions to i(t), v(t) are:

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{4}{8} = 0.5 \,\mathrm{s}, \implies \begin{cases} i(t) = I_0 e^{-(t/\tau)} = 12e^{-2t} \,\mathrm{A}, \\ v(t) = Ri(t) = 96e^{-2t} \,\mathrm{V}. \end{cases}$$

Example 7.2: Solving the inductor currents (3)



Example 7.2: Solutions in steady state (4)

Since  

$$i_1(t) = 1.6 - 9.6e^{-2t} \rightarrow 1.6 \text{ A},$$
  
 $i_2(t) = -1.6 - 2.4e^{-2t} \rightarrow -1.6 \text{ A},$ 

the two inductors form a closed current loop!

The energies stored in the two inductors are:

$$w_1(t \to \infty) = \frac{1}{2} (5 \text{ H})(1.6 \text{ A})^2 = 6.4 \text{ J},$$
  
 $w_2(t \to \infty) = \frac{1}{2} (20)(-1.6)^2 = 25.6 \text{ J},$ 

which is  $\sim 10\%$  of the initial energy in total.

Example 7.2: Solving the resistor current (5)

By current division,  $i_3(t) = 0.6i_{4\Omega}(t)$ , while  $i_{4\Omega}(t)$  can be calculated by v(t):



Circuit model of a discharging RC circuit

Consider the following circuit model:



- For t < 0, C is open and biased by a voltage  $V_g$ , while  $R_1$  and R carry no current.
- For t>0, the capacitor voltage decreases and the energy is dissipated via R.

#### ODE & IC

For t > 0, the circuit reduces to:

IC depends on initial energy of the capacitor:  $v(0^+) = v(0^-) \equiv V_0 = V_g$ 



**By KCL**, we got a first-order **ODE** for v(t):

$$C\frac{d}{dt}v(t) + \frac{v(t)}{R} = 0.$$

where C, R are independent of both v, and t.

#### Solving the parallel voltage

ODE: 
$$C \frac{d}{dt} v(t) + \frac{v(t)}{R} = 0$$
, IC:  $v(0^+) \equiv V_0 = V_g$ ;

$$\Rightarrow v(t) = V_0 e^{-(t/\tau)}$$
, where  $\tau = RC$  ...time constant



Solutions of the current, power, and energy

The loop current is:

$$i(t) = \frac{v(t)}{R} = \begin{cases} 0, \text{ for } t \le 0^-, \\ (V_0/R)e^{-(t/\tau)}, \text{ for } t \ge 0^+. \end{cases}$$
...abrupt change at  $t = 0$ .

The instantaneous power dissipated in R is:

$$p(t) = \frac{v^2(t)}{R} = \frac{V_0^2}{R} e^{-(2t/\tau)}, \text{ for } t \ge 0^+.$$

The energy dissipated in the resistor R is:

$$w = \int_0^t p(t')dt' = w_0 \left[ 1 - e^{-(2t/\tau)} \right], \quad w_0 = \frac{CV_0^2}{2}, \text{ for } t \ge 0^+.$$

initial energy stored in C

Procedures to get natural response of RL, RC circuits

- 1. Find the equivalent circuit.
- 2. Find the initial conditions: initial current  $I_0$ through the equivalent inductor, or initial voltage  $V_0$  across the equivalent capacitor.
- 3. Find the time constant of the circuit by the values of the equivalent R, L, C:

$$\tau = L/R$$
, or  $RC$ ;

4. Directly write down the solutions:

$$i(t) = I_0 e^{-(t/\tau)}, v(t) = V_0 e^{-(t/\tau)}.$$

Section 7.3 The Step Response of RL and RC Circuits

- 1. Charging an RC circuit
- 2. Charging an RL circuit

## What is step response?

- The response of a circuit to the sudden application of a constant voltage or current source, describing the charging behavior of the circuit.
- Step (charging) response and natural (discharging) response show how the signal in a digital circuit switches between Low and High with time.

#### ODE and IC of a charging RC circuit



IC depends on initial energy of the capacitor:

 $v(0^+)=v(0^-)\equiv V_0$ 

Derive the governing ODE by KCL:

$$I_{s} = \frac{v(t)}{R} + C\frac{d}{dt}v(t), \Rightarrow \frac{dv}{dt} = -\frac{1}{\tau}(v - V_{f}),$$

where  $\tau = RC$ ,  $V_f = I_s R$  are the time constant and final (steady-state) parallel voltage. Solving the parallel voltage, branch currents

$$\begin{aligned} \frac{dv}{dt} &= -\frac{1}{\tau} \left( v - V_f \right), \Rightarrow \frac{dv}{v - V_f} = -\frac{1}{\tau} dt, \\ \int_{V_0}^{v(t)} \frac{dv'}{v' - I_s R} &= -\frac{1}{\tau} \int_0^t dt', \quad \ln \frac{v(t) - V_f}{V_0 - V_f} = -\frac{t}{\tau}, \quad \frac{v(t) - V_f}{V_0 - V_f} = e^{-t/\tau}, \\ &\Rightarrow v(t) = V_f + \left( V_0 - V_f \right) e^{-t/\tau}. \end{aligned}$$

The charging and discharging processes have the same speed (same time constant  $\tau = RC$ ).

• The branch currents through C and R are:  $i_C(t) = C \frac{d}{dt} v(t) = \left(I_s - \frac{V_0}{R}\right) e^{-t/\tau}, i_R(t) = \frac{v(t)}{R}, \text{ for } t > 0.$ 

#### Example 7.6 (1)





For t <0, the switch is connected to Terminal 1 for long, the capacitor is an open circuit:

$$v_o(0^-) = (40 \text{ V}) \frac{60 \text{ k}\Omega}{(20+60) \text{ k}\Omega} = 30 \text{ V}, \ i_o(0^-) = 0.$$

#### Example 7.6 (2)

At  $t \ge 0^+$ , the "charging circuit" with two terminals 2 and G can be reduced to a Norton equivalent:



#### Example 7.6 (3)

- The time constant and the final capacitor voltage of the charging circuit are:  $\tau = RC = (40 \text{ k}\Omega)(0.25 \ \mu\text{F}) = 10 \text{ ms},$  $V_f = I_s R = (-1.5 \text{ mA})(40 \text{ k}\Omega) = -60 \text{ V}.$  $\Rightarrow v_{o}(t) = V_{f} + (V_{0} - V_{f})e^{-t/\tau} = -60 + 90e^{-100t}$  V.  $\Rightarrow i_{0}(t) = (I_{s} - V_{0}/R)e^{-t/\tau} = -2.25e^{-100t} \text{ mA.}$
- At the time of switching, the capacitor voltage is continuous:  $v_o(0^-) = 30$  V =  $v_0(0^+) = (-60 + 90)$  V, while the current  $i_o$  jumps from 0 to -2.25 mA.

#### Charging an RL circuit

$$\begin{array}{c} R \\ + \\ V_{s} \\ - \\ - \\ \end{array} \begin{array}{c} i \\ V_{s} \end{array} \begin{array}{c} t = 0 \\ L \\ - \\ \end{array} \begin{array}{c} v(t) \\ + \\ v(t) \end{array} \begin{array}{c} \text{initial energy of} \\ \text{the inductor:} \\ i(0^{+}) = i(0^{-}) \equiv I_{0} \end{array} \\ V_{s} = Ri(t) + L \frac{d}{dt}i(t), \Rightarrow i(t) = I_{f} + (I_{0} - I_{f})e^{-t/\tau}, \\ \text{where } \tau = \frac{L}{R}, \quad I_{f} = \frac{V_{s}}{R}. \end{array}$$

The charging and discharging processes have the same speed (same time constant  $\tau = L/R$ ).

# Section 7.5 Sequential Switching

## What is and how to solve sequential switching?

- Sequential switching means switching occurs  $n \geq 2$ times.
- It is analyzed by dividing the process into n+1 time intervals. Each of them corresponds to a specific circuit.
- Initial conditions of a particular interval are determined from the solution of the preceding interval. Inductive currents and capacitive voltages are particularly important for they cannot change abruptly.
- Laplace transform (Ch12) can solve it easily.

Example 7.12: Charging and discharging a capacitor (1)



For  $0 \le t \le 15$  ms, the 400-V source charges the capacitor via the 100-k $\Omega$  resistor,  $\Rightarrow V_f = 400$  V,  $\tau = RC = 10$  ms, and the capacitor voltage is:  $v_1(t) = V_f + (V_0 - V_f)e^{-t/\tau} = 400 - 400e^{-100t}$  V.

#### Example 7.12 (2)

• For t > 15 ms, the capacitor is disconnected from the 400-V source and is discharged via the 50 $k\Omega$  resistor,  $\Rightarrow V_0 = v_1(15 \text{ ms}) = 310.75 \text{ V}, V_f = 0, \tau$ = RC = 5 ms. The capacitor voltage is:  $v_2(t) = V_0 e^{-(t-t_0)/\tau} = 310.75 e^{-200(t-0.015)}$  V.  $\begin{vmatrix} v(V) \\ 300 \end{vmatrix} = 400 - 400e^{-100t}$  $v = 310.75e^{-200(t - 0.015)}$ 200 100 *t* (ms) 5 1015 20

# Section 7.6 Unbounded Response

# Definition and reason of unbounded response

- An unbounded response means the voltages or currents increase with time without limit.
- It occurs when the Thévenin resistance is negative (R<sub>Th</sub> < 0), which is possible when the first-order circuit contains dependent sources.



For t>0, the capacitor seems to "discharge" (not really, to be discussed) via a circuit with a current-controlled current source, which can be represented by a Thévenin equivalent.

#### Example 7.13 (2)

Since there is no independent source,  $V_{Th} = 0$ , while  $R_{Th}$  can be determined by the test source method:  $i_T$ 



#### Example 7.13 (3)

■ For t≥0, the equivalent circuit and governing differential equation become:



$$V_0 = v_o(0^+) = 10 \text{ V}, \ \tau = RC = -25 \text{ ms} < 0,$$

 $\Rightarrow v_o(t) = V_0 e^{-t/\tau} = 10 e^{+40t}$  V...grow without limit.

Why the voltage is unbounded?

Since 10-k $\Omega$ , 20-k $\Omega$  resistors are in parallel,  $\Rightarrow i_{10k\Omega} = 2i_{\Delta}$ , the capacitor is actually charged (not discharged) by a current of  $4i_{\Delta}$ !

• Charging effect will increase  $v_o$ , which will in turn increase the charging current ( $i_{\Delta} = v_o/20 \text{ k}\Omega$ ) and  $v_o$  itself. The positive feedback makes  $v_o$  soaring.



# Lesson for circuit designers & device fabrication engineers

 Undesired interconnection between a capacitor and a sub-circuit with dependent source (e.g. transistor) could be catastrophic!

# Key points

- Why an RC or RL circuit is charged or discharged as an exponential function of time?
- Why the charging and discharging speed of an RC or RL circuit is determined by RC or L/R?
- What could happen when an energy-storing element (C or L) is connected to a circuit with dependent source?