

# Chapter 8

## Natural and Step Responses of RLC Circuits

---

- 8.1-2 The Natural Response of a Parallel *RLC* Circuit
- 8.3 The Step Response of a Parallel *RLC* Circuit
- 8.4 The Natural and Step Response of a Series *RLC* Circuit

## Key points

- What do the **response curves** of over-, under-, and critically-damped circuits look like? How to choose  $R$ ,  $L$ ,  $C$  values to achieve fast switching or to prevent overshooting damage?
- What are the **initial conditions** in an RLC circuit? How to use them to determine the expansion coefficients of the complete solution?
- Comparisons between: (1) natural & step responses, (2) parallel, series, or **general RLC**.




## Section 8.1, 8.2

# The Natural Response of a Parallel RLC Circuit

1. ODE, ICs, general solution of parallel voltage
2. Over-damped response
3. Under-damped response
4. Critically-damped response

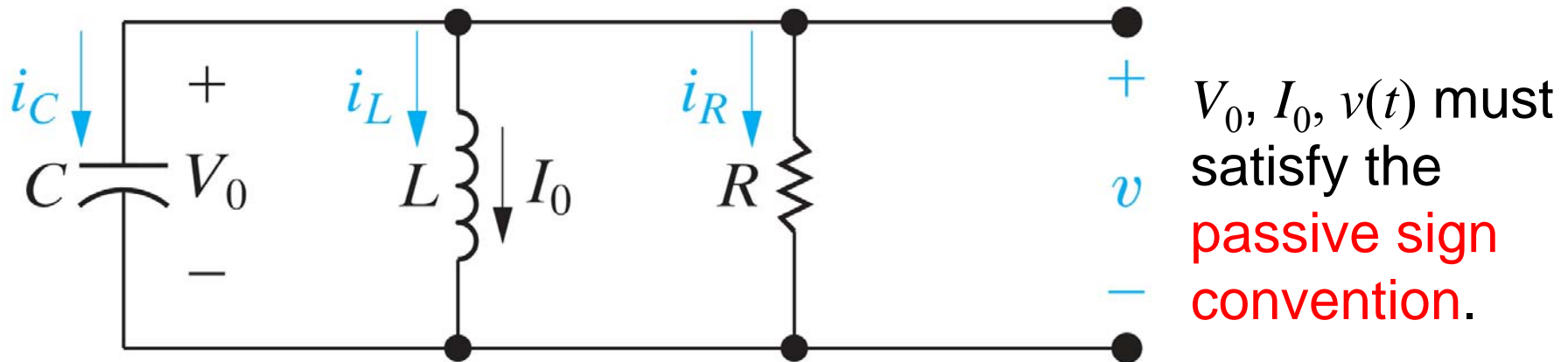
## The governing ordinary differential equation (ODE)



- By KCL:  $C \frac{dv}{dt} + \left[ I_0 + \frac{1}{L} \int_0^t v(t') dt' \right] + \frac{v}{R} = 0.$
- Perform time derivative, we got a linear 2nd-order ODE of  $v(t)$  with constant coefficients:

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0.$$

## The two initial conditions (ICs)

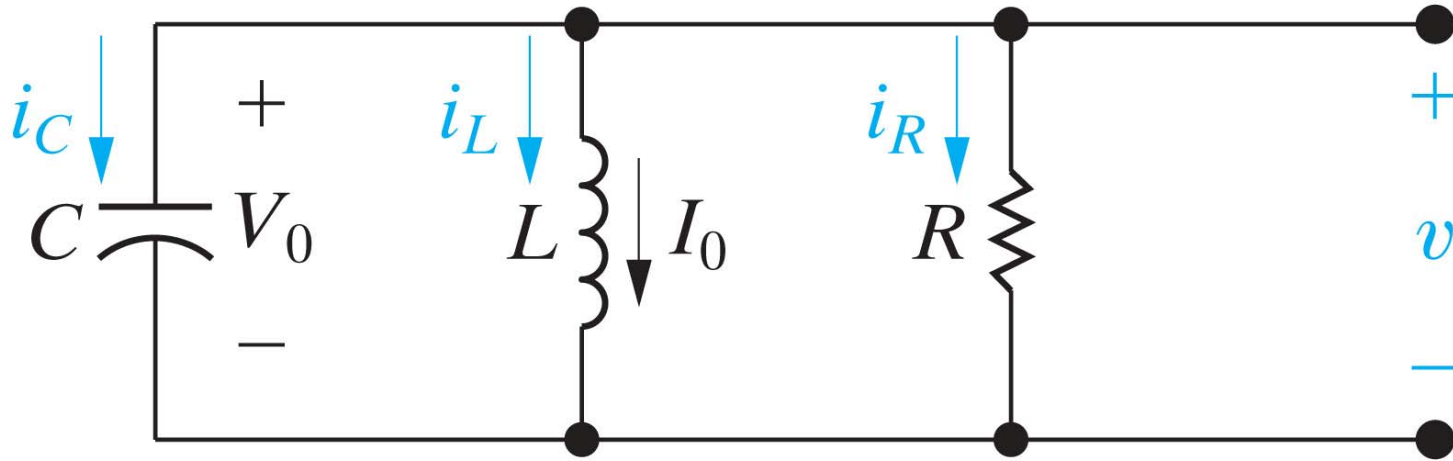

- The capacitor voltage cannot change abruptly,

$$\Rightarrow v(0^+) = V_0 \cdots (1)$$

- The inductor current cannot change abruptly,

$$\Rightarrow i_L(0^+) = I_0, \quad i_C(0^+) = -i_L(0^+) - i_R(0^+) = -I_0 - V_0/R,$$

$$\because i_C(0^+) = C \frac{dv_C}{dt} \Big|_{t=0^+}, \quad \Rightarrow v'_C(0^+) = v'(0^+) = -\frac{I_0}{C} - \frac{V_0}{RC} \cdots (2)$$

## General solution

- Assume the solution is  $v(t) = Ae^{st}$ , where  $A, s$  are unknown constants to be solved.
- Substitute into the ODE, we got an **algebraic** (characteristic) equation of  $s$  determined by the circuit parameters:

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0.$$

- Since the ODE is **linear**,  $\Rightarrow$  linear combination of solutions remains a solution to the equation. The general solution of  $v(t)$  must be of the form:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t},$$

where the expansion constants  $A_1, A_2$  will be determined by the two initial conditions.

## Neper and resonance frequencies

- In general,  $s$  has two roots, which can be (1) distinct real, (2) degenerate real, or (3) complex conjugate pair.

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2},$$

where

$$\alpha = \frac{1}{2RC}, \quad \dots \text{neper frequency}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \dots \text{resonance (natural) frequency}$$

## Three types of natural response

- How the circuit reaches its steady state depends on the relative magnitudes of  $\alpha$  and  $\omega_0$ :

The Circuit is	When	Solutions
Over-damped	$\alpha > \omega_0$	real, distinct roots $s_1, s_2$
Under-damped	$\alpha < \omega_0$	complex roots $s_1 = (s_2)^*$
Critically-damped	$\alpha = \omega_0$	real, equal roots $s_1 = s_2$



## Over-damped response ( $\alpha > \omega_0$ )

- The complete solution and its derivative are of the form:

$$\begin{cases} v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \\ v'(t) = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}. \end{cases}$$


where  $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$  are distinct real.

- Substitute the two ICs:

$$\begin{cases} v(0^+) = A_1 + A_2 = V_0 \cdots (1) \\ v'(0^+) = s_1 A_1 + s_2 A_2 = -\frac{I_0}{C} - \frac{V_0}{RC} \cdots (2) \end{cases} \Rightarrow \text{solve } A_1, A_2.$$
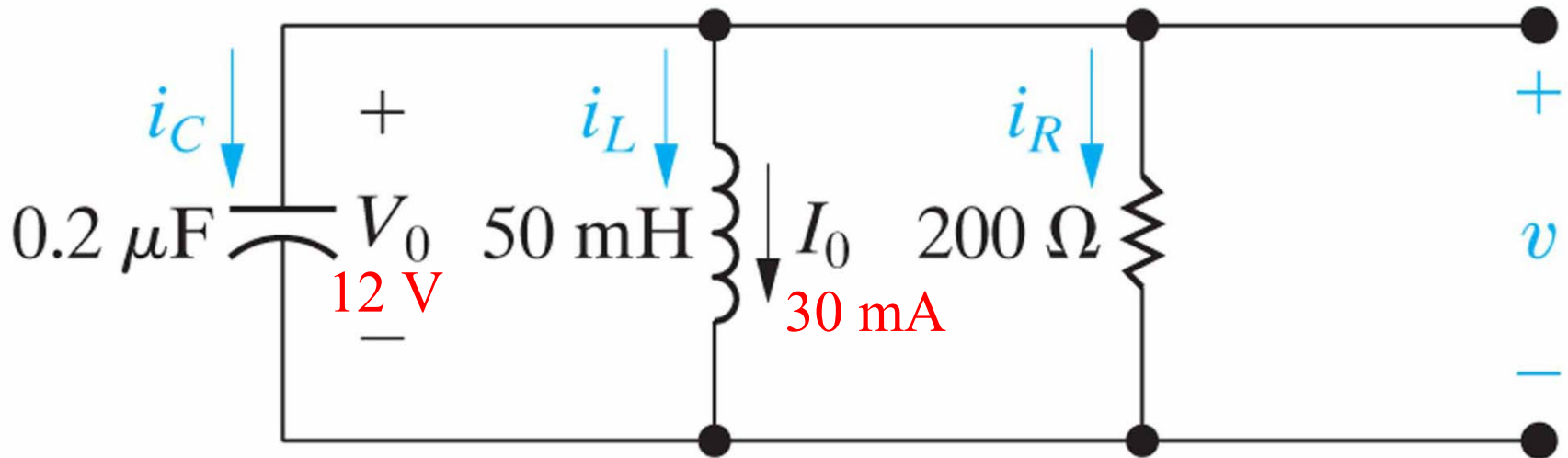
## Example 8.2: Discharging a parallel RLC circuit (1)

- Q:  $v(t)$ ,  $i_C(t)$ ,  $i_L(t)$ ,  $i_R(t) = ?$



$$\begin{cases} \alpha = \frac{1}{2RC} = \frac{1}{2(200)(2 \times 10^{-7})} = 12.5 \text{ kHz}, \\ \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(5 \times 10^{-2})(2 \times 10^{-7})}} = 10 \text{ kHz}. \end{cases} \Rightarrow \alpha > \omega_0, \text{ over-damped}$$

## Example 8.2: Solving the parameters (2)

- The 2 distinct real roots of  $s$  are:

$$\begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -5 \text{ kHz}, \dots |s_1| < \alpha \text{ (slow)} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -20 \text{ kHz}, \dots |s_2| > \alpha \text{ (fast)} \end{cases}$$


- The 2 expansion coefficients are:

$$\begin{cases} A_1 + A_2 = V_0 \\ s_1 A_1 + s_2 A_2 = -\frac{I_0}{C} - \frac{V_0}{RC} \end{cases} \Rightarrow \begin{cases} A_1 + A_2 = 12 \\ -5A_1 - 20A_2 = -450 \end{cases}$$

$$\Rightarrow A_1 = -14 \text{ V}, A_2 = 26 \text{ V}.$$
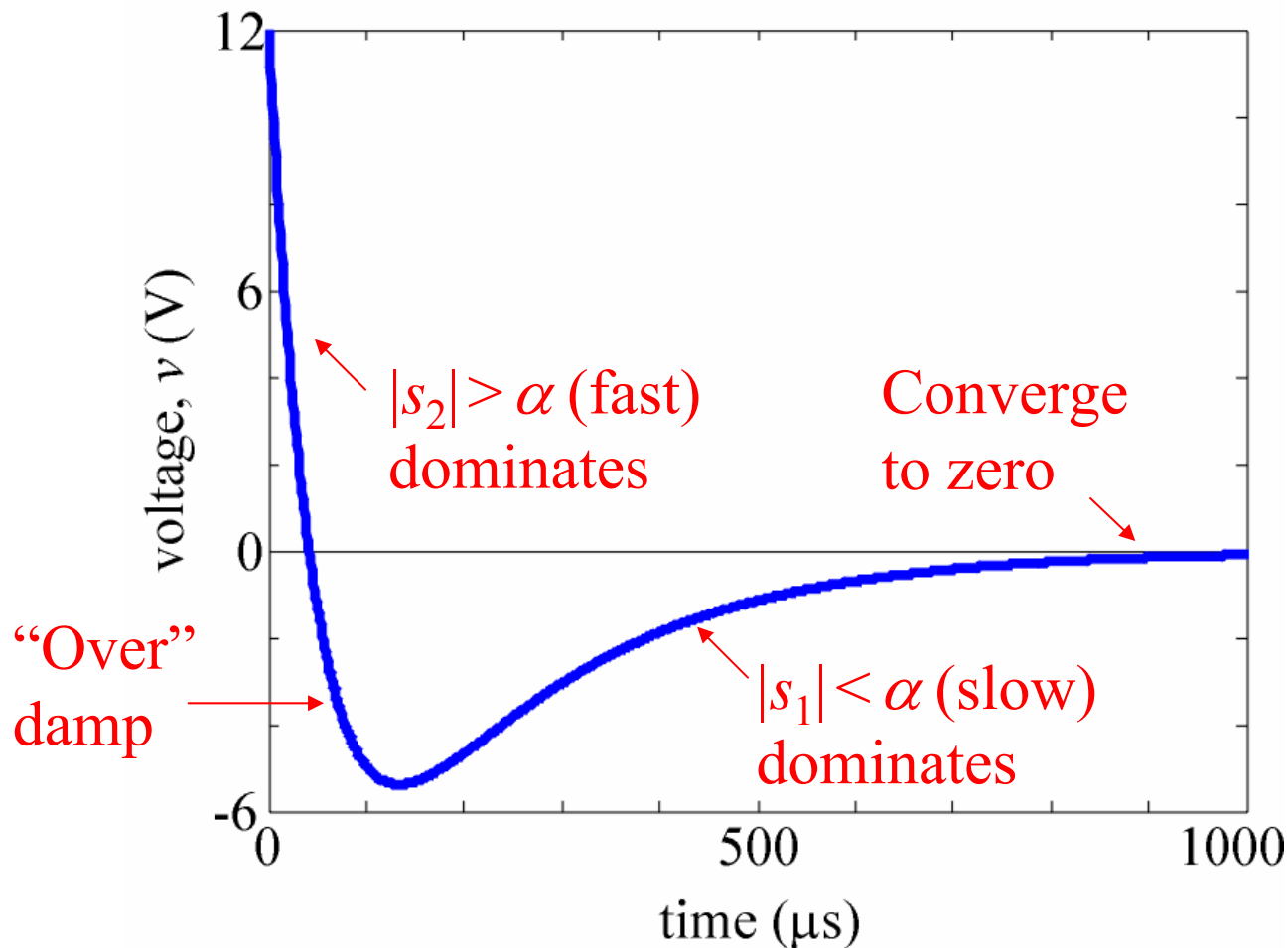
## Example 8.2: The parallel voltage evolution (3)

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = \left( -14e^{-5000t} + 26e^{-20000t} \right) \text{V}.$$



## Example 8.2: The branch currents evolution (4)

- The branch current through R is:

$$i_R(t) = \frac{v(t)}{200 \Omega} = \left( -70e^{-5000t} + 130e^{-20000t} \right) \text{mA}.$$


- The branch current through L is:

$$i_L(t) = 30 \text{ mA} + \frac{1}{50 \text{ mH}} \int_0^t v(t') dt' = \left( 56e^{-5000t} - 26e^{-20000t} \right) \text{mA}.$$

- The branch current through C is:

$$i_C(t) = (0.2 \mu\text{F}) \frac{dv}{dt} = \left( 14e^{-5000t} - 104e^{-20000t} \right) \text{mA}.$$
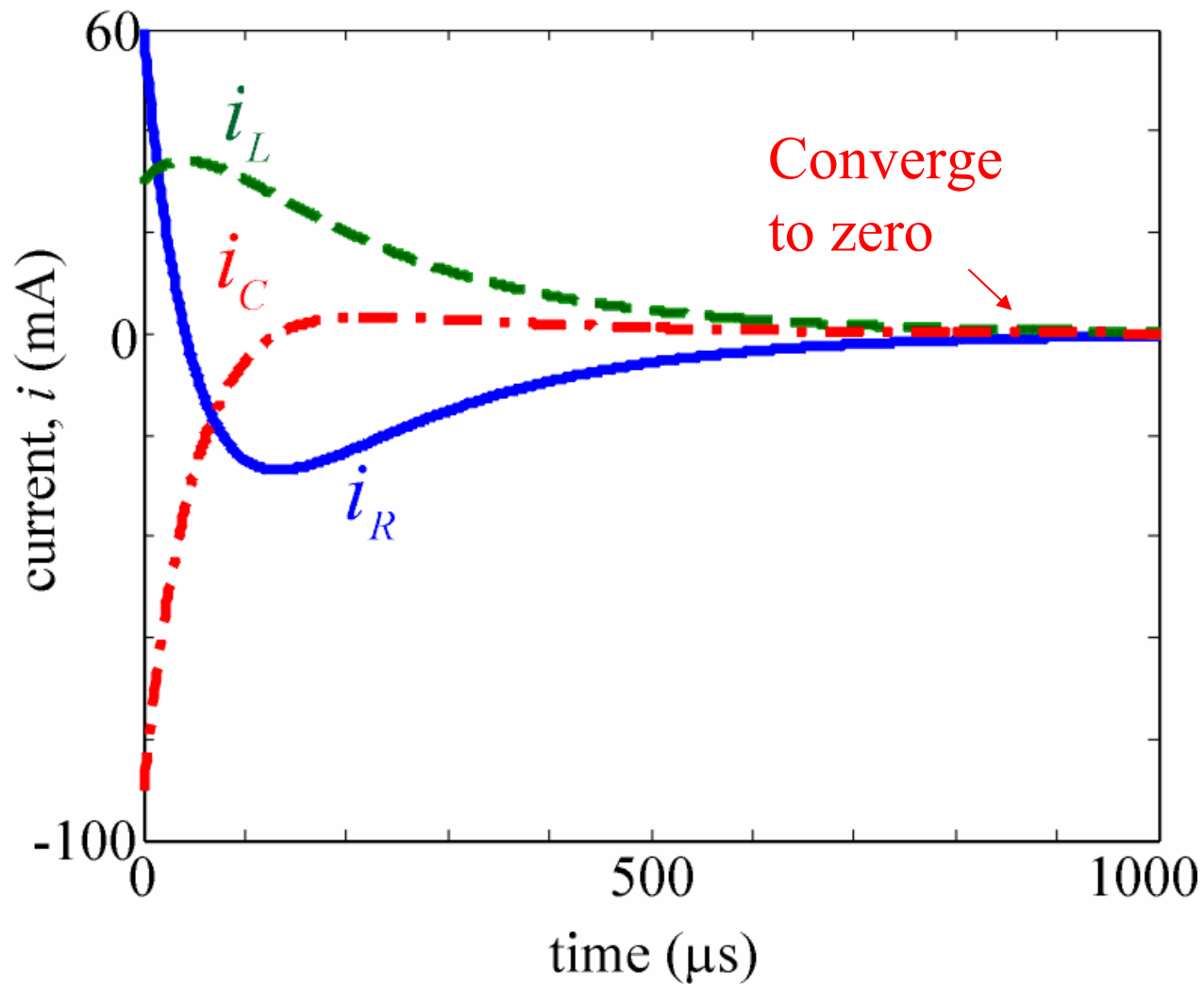
## Example 8.2: The branch currents evolution (5)



## General solution to under-damped response ( $\alpha < \omega_0$ )

- The two roots of  $s$  are complex conjugate pair:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\omega_d,$$

where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  is the damped frequency.

- The general solution is reformulated as:

$$\begin{aligned} v(t) &= A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t} \\ &= e^{-\alpha t} [A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t)] \\ &= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t] \\ &= e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t). \end{aligned}$$

## Solving the expansion coefficients $B_1, B_2$ by ICs

- The derivative of  $v(t)$  is:

$$\begin{aligned} v'(t) &= B_1 \left( -\alpha e^{-\alpha t} \cos \omega_d t - \omega_d e^{-\alpha t} \sin \omega_d t \right) \\ &+ B_2 \left( -\alpha e^{-\alpha t} \sin \omega_d t + \omega_d e^{-\alpha t} \cos \omega_d t \right) \\ &= e^{-\alpha t} \left[ (-\alpha B_1 + \omega_d B_2) \cos \omega_d t - (\alpha B_2 + \omega_d B_1) \sin \omega_d t \right]. \end{aligned}$$


- Substitute the two ICs:

$$\begin{cases} v(0^+) = B_1 = V_0 \cdots (1) \\ v'(0^+) = -\alpha B_1 + \omega_d B_2 = -\frac{I_0}{C} - \frac{V_0}{RC} \cdots (2) \end{cases} \Rightarrow \text{solve } B_1, B_2.$$


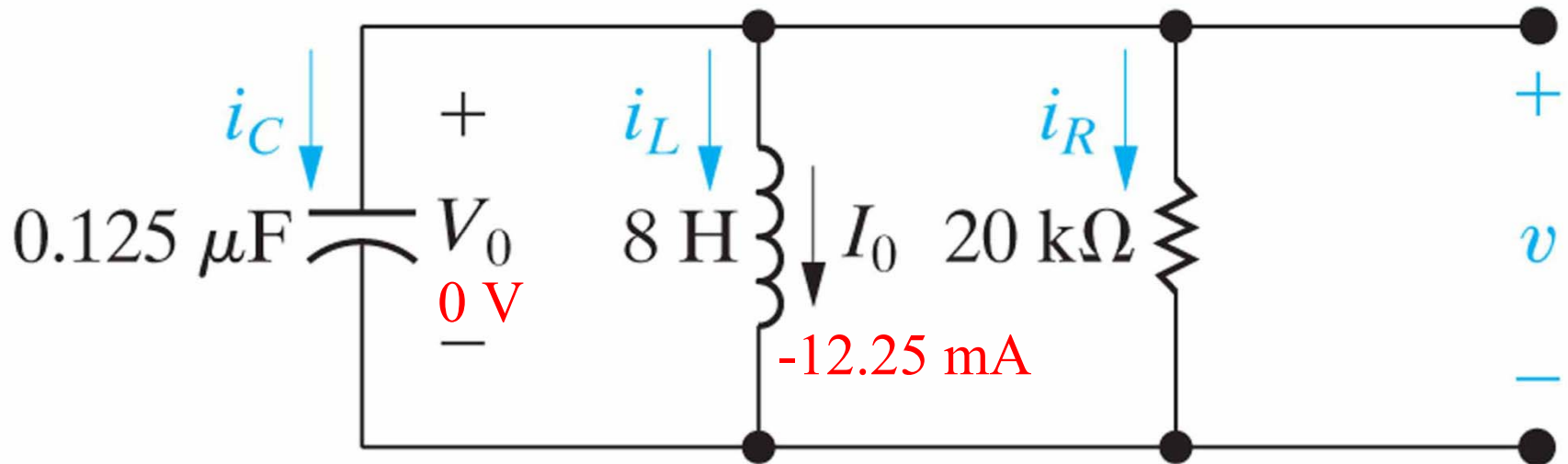
## Example 8.4: Discharging a parallel RLC circuit (1)

- Q:  $v(t)$ ,  $i_C(t)$ ,  $i_L(t)$ ,  $i_R(t) = ?$



$$\begin{cases} \alpha = \frac{1}{2RC} = \frac{1}{2(2 \times 10^4)(1.25 \times 10^{-7})} = 0.2 \text{ kHz}, \\ \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(8)(1.25 \times 10^{-7})}} = 1 \text{ kHz}. \end{cases} \Rightarrow \alpha < \omega_0, \text{ under-damped}$$

## Example 8.4: Solving the parameters (2)

- The damped frequency is:


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{1^2 - 0.2^2} \approx 0.98 \text{ kHz.}$$

- The 2 expansion coefficients are:

$$\begin{cases} B_1 = V_0 = 0 \dots (1) \\ -\alpha B_1 + \omega_d B_2 = -\frac{I_0}{C} - \frac{V_0}{RC} \dots (2) \end{cases} \Rightarrow \begin{cases} B_1 = 0, \\ B_2 \approx 100 \text{ V} \end{cases}$$
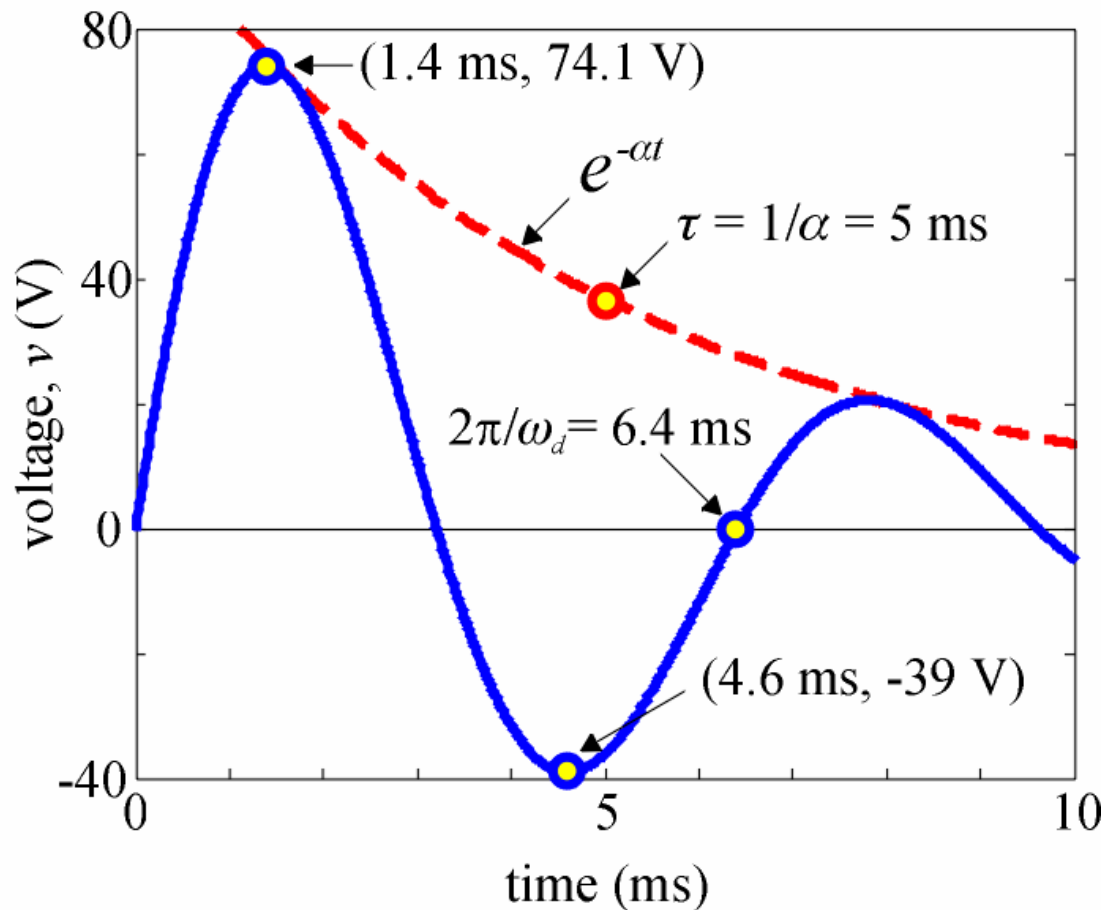
## Example 8.4: The parallel voltage evolution (3)


$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \approx (100 e^{-200t} \sin 980t) \text{ V.}$$



- The voltage oscillates ( $\sim \omega_d$ ) and approaches the final value ( $\sim \alpha$ ), different from the over-damped case (no oscillation, 2 decay constants).

## Example 8.4: The branch currents evolutions (4)

- The three branch currents are:

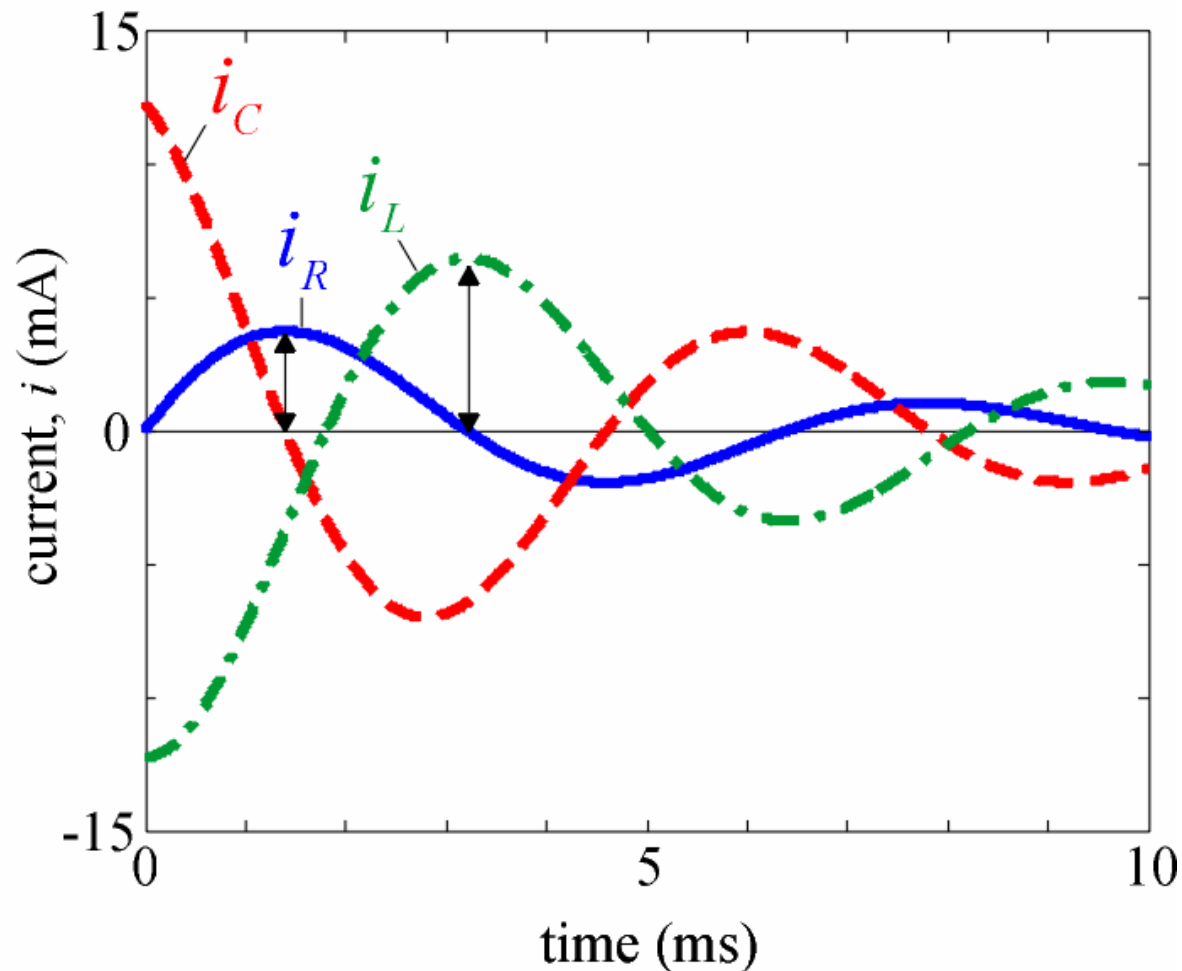

## Rules for circuit designers

- If one desires the circuit reaches the final value as **fast** as possible while the minor oscillation is of less concern, choosing  $R$ ,  $L$ ,  $C$  values to satisfy **under-damped** condition.
- If one concerns that the response not exceed its final value to **prevent potential damage**, designing the system to be **over-damped** at the cost of slower response.

## General solution to critically-damped response ( $\alpha = \omega_0$ )

- Two identical real roots of  $s$  make

$$v(t) = A_1 e^{st} + A_2 e^{st} = (A_1 + A_2) e^{st} = A_0 e^{st},$$

not possible to satisfy 2 independent ICs ( $V_0, I_0$ ) with a single expansion constant  $A_0$ .

- The general solution is reformulated as:

$$v(t) = e^{-\alpha t} (D_1 t + D_2).$$

- You can prove the validity of this form by substituting it into the ODE:

$$v''(t) + (RC)^{-1} v'(t) + (LC)^{-1} v(t) = 0.$$

## Solving the expansion coefficients $D_1, D_2$ by ICs

- The derivative of  $v(t)$  is:


$$v'(t) = D_1(e^{-\alpha t} - \alpha t e^{-\alpha t}) - \alpha D_2 e^{-\alpha t} = [(D_1 - \alpha D_2) - \alpha D_1 t] e^{-\alpha t}.$$

- Substitute the two ICs:

$$\begin{cases} v(0^+) = D_2 = V_0 \cdots (1) \\ v'(0^+) = D_1 - \alpha D_2 = -\frac{I_0}{C} - \frac{V_0}{RC} \cdots (2) \end{cases} \Rightarrow \text{solve } D_1, D_2.$$
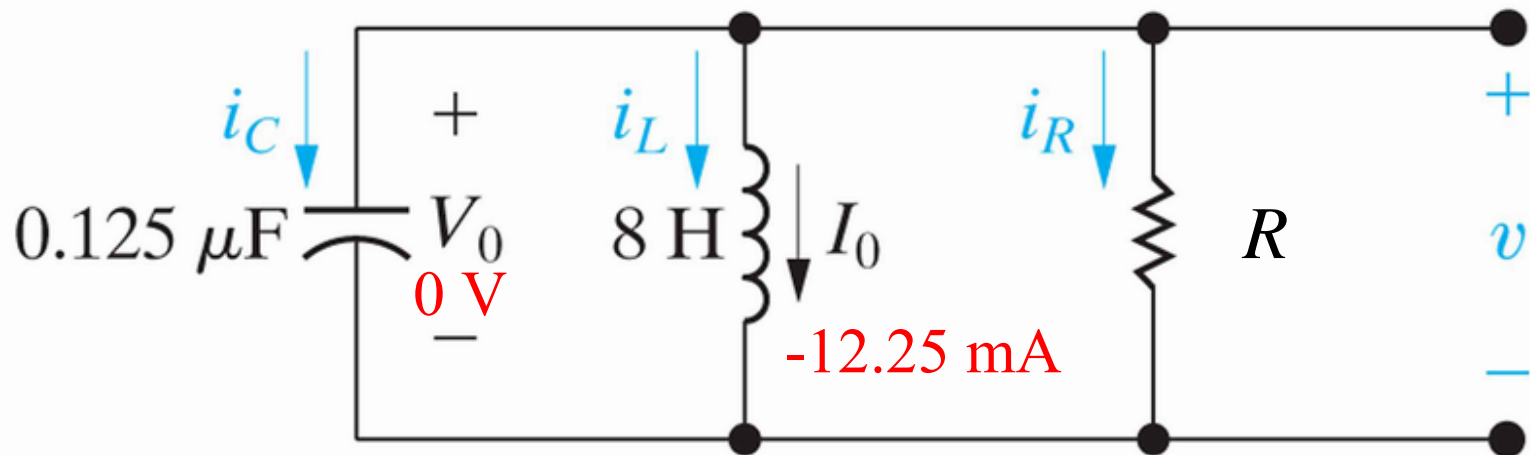
## Example 8.5: Discharging a parallel RLC circuit (1)

- Q: What is  $R$  such that the circuit is critically-damped? Plot the corresponding  $v(t)$ .



$$\alpha = \omega_0, \quad \frac{1}{2RC} = \frac{1}{\sqrt{LC}}, \quad R = \frac{1}{2} \sqrt{\frac{L}{C}} = \frac{1}{2} \sqrt{\frac{8}{1.25 \times 10^{-7}}} = 4 \text{ k}\Omega.$$

- Increasing  $R$  tends to bring the circuit from over-to critically- and even under-damped.



## Example 8.5: Solving the parameters (2)

- The neper frequency is:

$$\alpha = \frac{1}{2RC} = \frac{1}{2(4 \times 10^3)(1.25 \times 10^{-7})} = 1 \text{ kHz},$$

$$\Rightarrow \tau = \frac{1}{\alpha} = 1 \text{ ms}.$$


- The 2 expansion coefficients are:

$$\begin{cases} D_2 = V_0 = 0 \dots (1) \\ D_1 - \cancel{\alpha D_2} = -\frac{I_0}{C} - \frac{\cancel{V_0}}{RC} \dots (2) \end{cases} \Rightarrow \begin{cases} D_1 = 98 \text{ kV/s} \\ D_2 = 0 \end{cases}$$

-12.25 mA  
0.125 μF
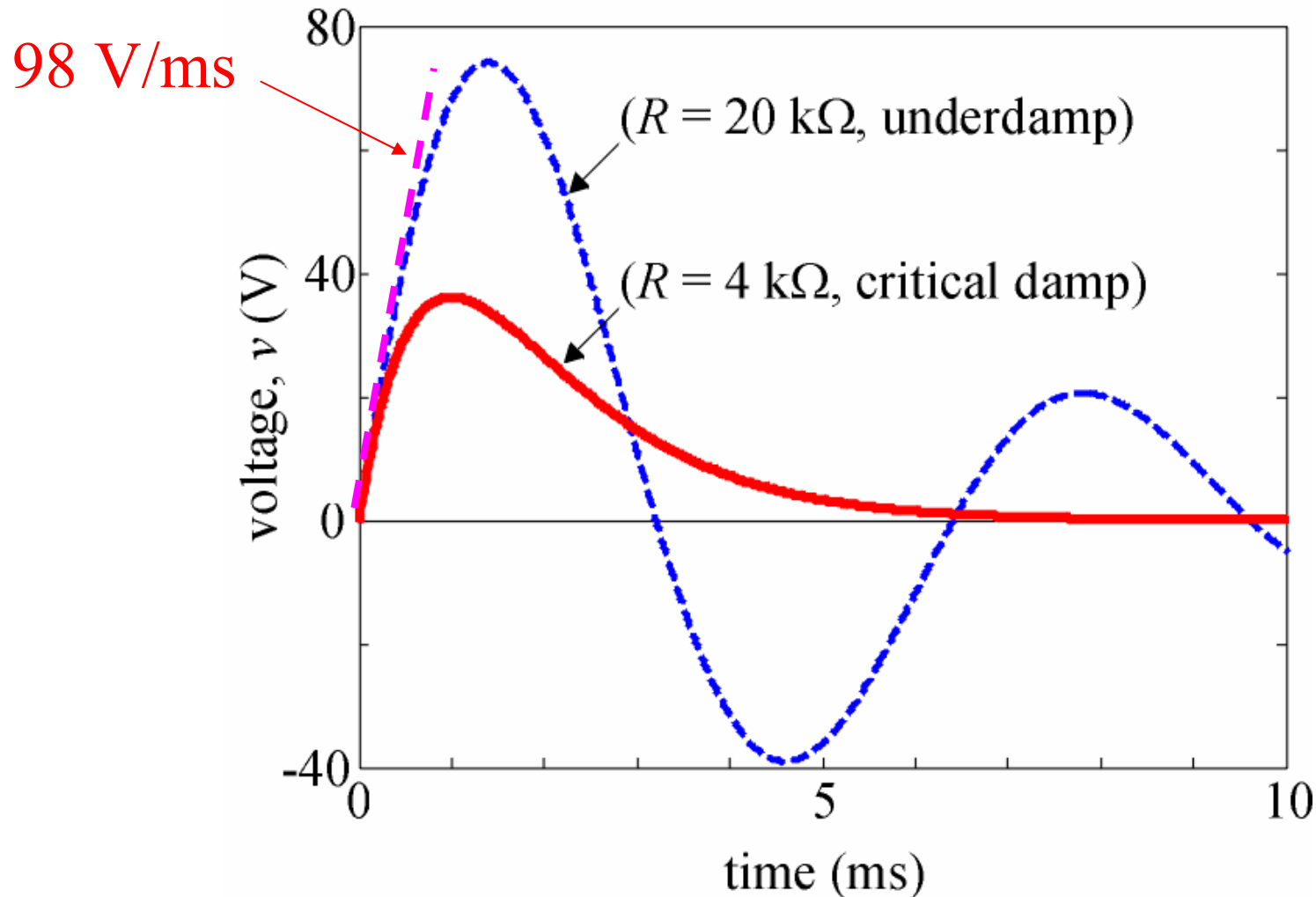
## Example 8.5: The parallel voltage evolution (3)

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} = (98,000 t e^{-1000 t}) \text{ V}.$$



## Procedures of solving nature response of parallel RLC

- Calculate parameters  $\alpha = (2RC)^{-1}$  and  $\omega_0 = 1/\sqrt{LC}$ .

- Write the form of  $v(t)$  by comparing  $\alpha$  and  $\omega_0$ :

$$v(t) = \begin{cases} A_1 e^{s_1 t} + A_2 e^{s_2 t}, s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \text{ if } \alpha > \omega_0, \\ e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t), \omega_d = \sqrt{\omega_0^2 - \alpha^2}, \text{ if } \alpha < \omega_0, \\ e^{-\alpha t} (D_1 t + D_2), \text{ if } \alpha = \omega_0. \end{cases}$$

- Find the expansion constants  $(A_1, A_2)$ ,  $(B_1, B_2)$ , or  $(D_1, D_2)$  by two ICs: 
$$\begin{cases} v(0^+) = V_0 \cdots (1), \\ v'(0^+) = -\frac{I_0}{C} - \frac{V_0}{RC} \cdots (2) \end{cases}$$




## Section 8.3

# The Step Response of a Parallel $RLC$ Circuit

1. Inhomogeneous ODE, ICs, and general solution


# The homogeneous ODE

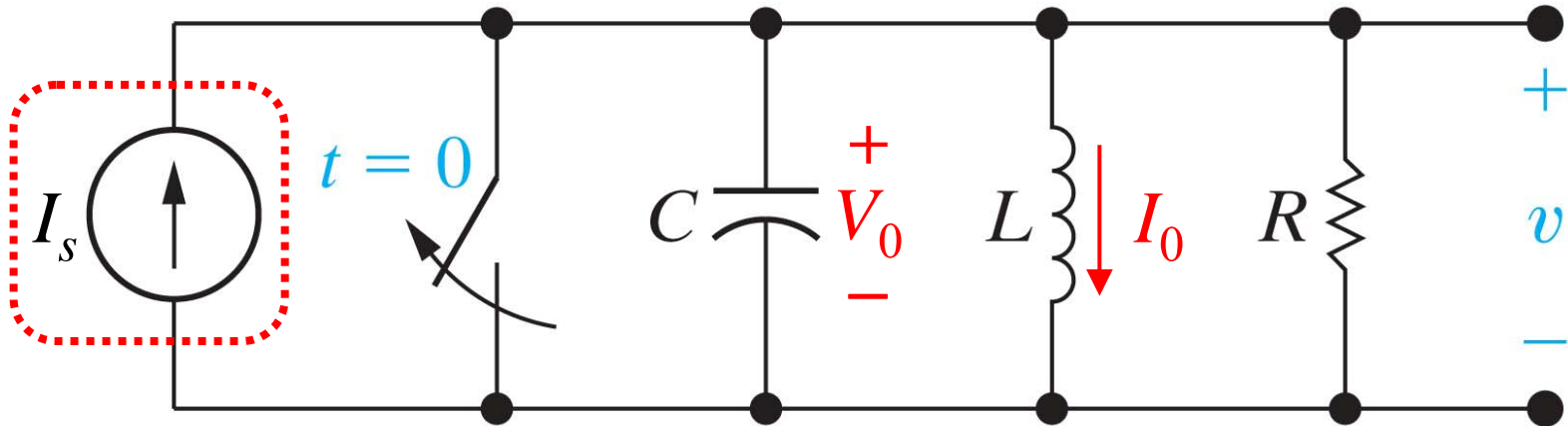

- By KCL:  $C \frac{dv}{dt} + \left[ I_0 + \frac{1}{L} \int_0^t v(t') dt' \right] + \frac{v}{R} = I_s.$
- Perform time derivative, we got a homogeneous ODE of  $v(t)$  independent of the source current  $I_s$ :

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0.$$


## The inhomogeneous ODE

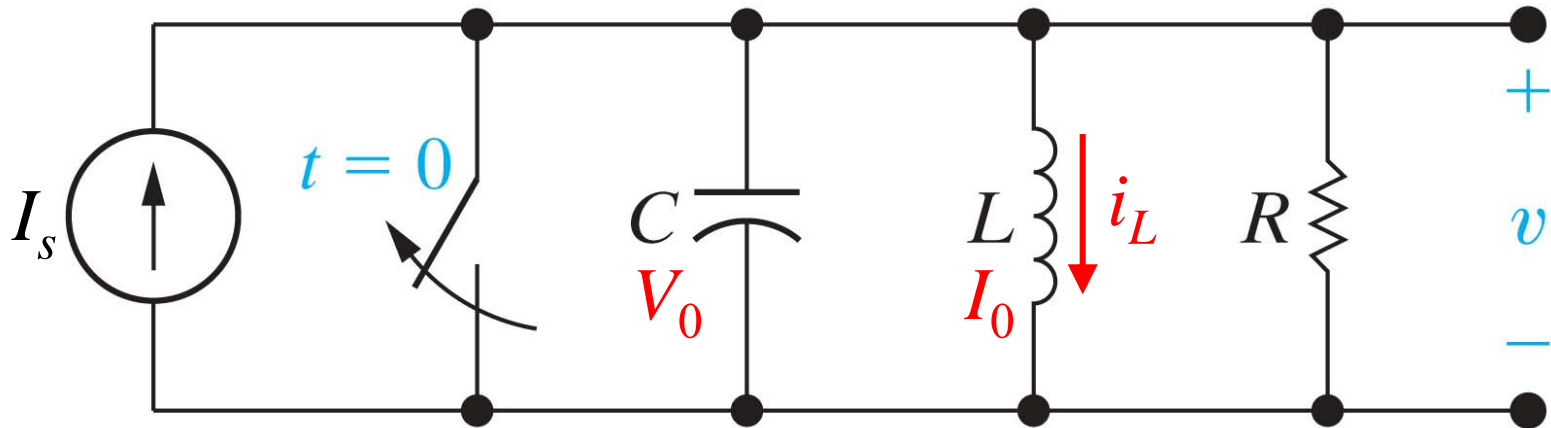

- Change the unknown to the inductor current  $i_L(t)$ :

$$\begin{cases} C \frac{dv}{dt} + i_L + \frac{v}{R} = I_s, \\ v = L \frac{di_L}{dt}, \end{cases} \Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I_s}{LC}$$

## The two initial conditions (ICs)

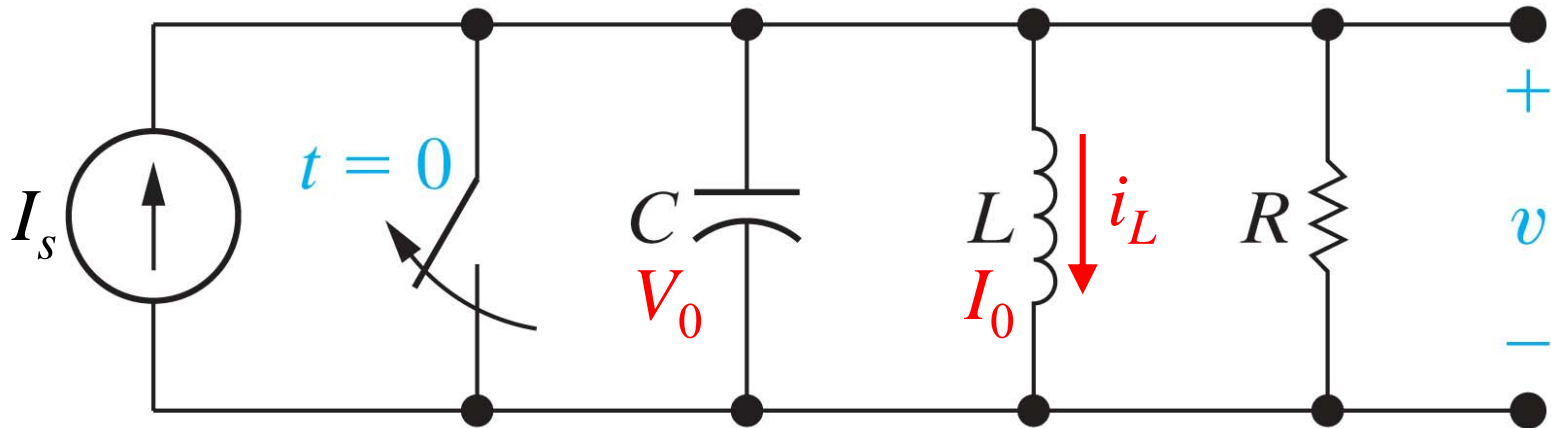

- The inductor current cannot change abruptly,  
 $\Rightarrow i_L(0^+) = I_0 \dots (1)$
- The capacitor voltage cannot change abruptly,  
 $\Rightarrow v_C(0^+) = V_0 = v_L(0^+),$   
 $\because v_L(0^+) = L \frac{di_L}{dt} \Big|_{t=0^+}, \Rightarrow i'_L(0^+) = \frac{V_0}{L} \dots (2)$

## General solution

- The solution is the sum of final current  $I_f = I_s$  and the nature response  $i_{L,nature}(t)$ :

$$i_L(t) = I_f + i_{L,nature}(t),$$


where the three types of nature responses were elucidated in Section 8.2:

$$i_L(t) = \begin{cases} I_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}, & \text{if } \alpha > \omega_0, \\ I_f + e^{-\alpha t} (B'_1 \cos \omega_d t + B'_2 \sin \omega_d t), & \text{if } \alpha < \omega_0, \\ I_f + e^{-\alpha t} (D'_1 t + D'_2), & \text{if } \alpha = \omega_0. \end{cases}$$



## Example 8.7: Charging a parallel RLC circuit (1)

■ Q:  $i_L(t) = ?$

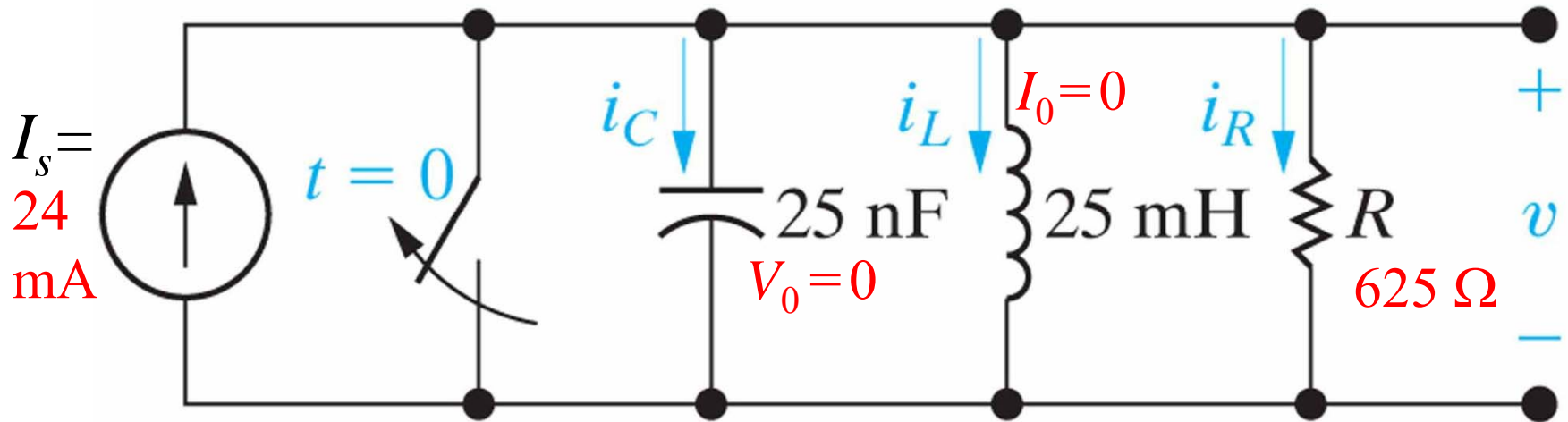

$$\begin{cases} \alpha = \frac{1}{2RC} = \frac{1}{2(625)(2.5 \times 10^{-8})} = 32 \text{ kHz}, \\ \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2.5 \times 10^{-2})(2.5 \times 10^{-8})}} = 40 \text{ kHz}. \end{cases} \Rightarrow \alpha < \omega_0, \text{ under-damped}$$

## Example 8.7: Solving the parameters (2)

- The complete solution is of the form:

$$i_L(t) = I_s + e^{-\alpha t} (B'_1 \cos \omega_d t + B'_2 \sin \omega_d t),$$



$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{40^2 - 32^2} = 24 \text{ kHz.}$$

- The 2 expansion coefficients are:

$$\begin{cases} \textcircled{I_s} + B'_1 = I_0 = 0 \cdots (1) \\ -\alpha B'_1 + \omega_d B'_2 = \frac{V_0}{L} = 0 \cdots (2) \end{cases} \Rightarrow \begin{cases} B'_1 = -24 \text{ mA}, \\ B'_2 \approx -32 \text{ mA} \end{cases}$$

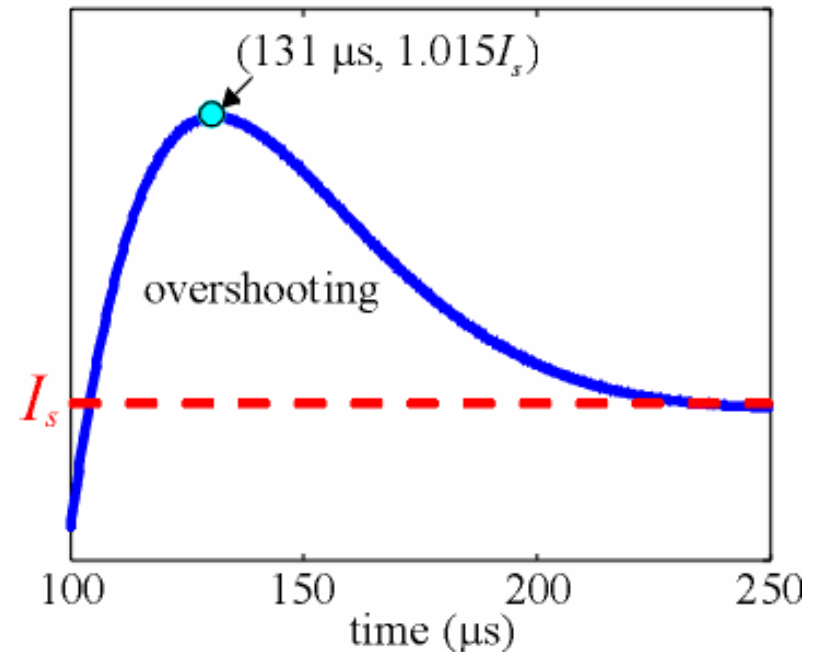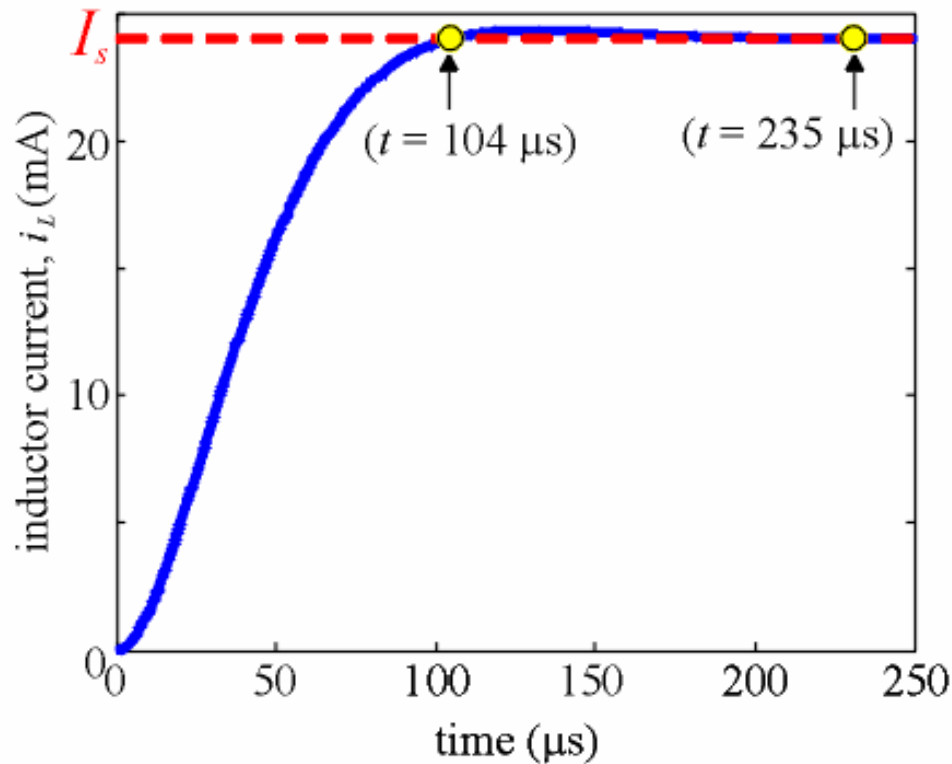
## Example 8.7: Inductor current evolution (3)

$$i_L(t) = \left[ 24 - 24e^{-32,000t} \cos(24,000t) - 32e^{-32,000t} \sin(24,000t) \right] \text{ mA.}$$


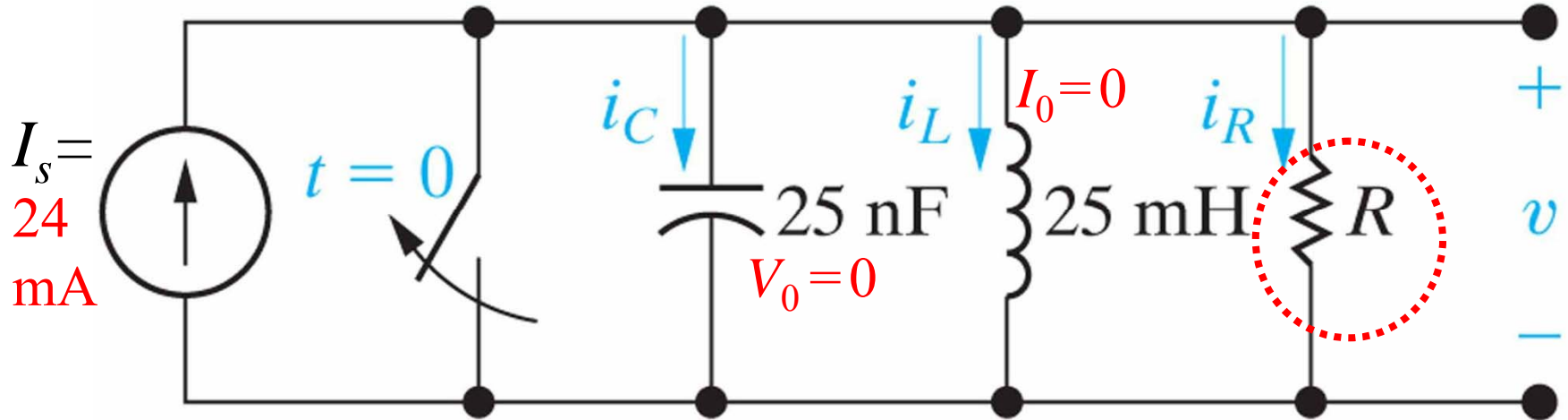
## Example 8.9: Charging of parallel RLC circuits (1)


- Q: Compare  $i_L(t)$  when the resistance  $R = 625\ \Omega$  (under-damp),  $500\ \Omega$  (critical damp),  $400\ \Omega$  (over-damp), respectively.




- Initial & final conditions remain:  $i_L(0^+) = 0$ ,  $i'_L(0^+) = 0$ ,  $I_f = 24\text{ mA}$ . Different  $R$ 's give different functional forms and expansion constants.
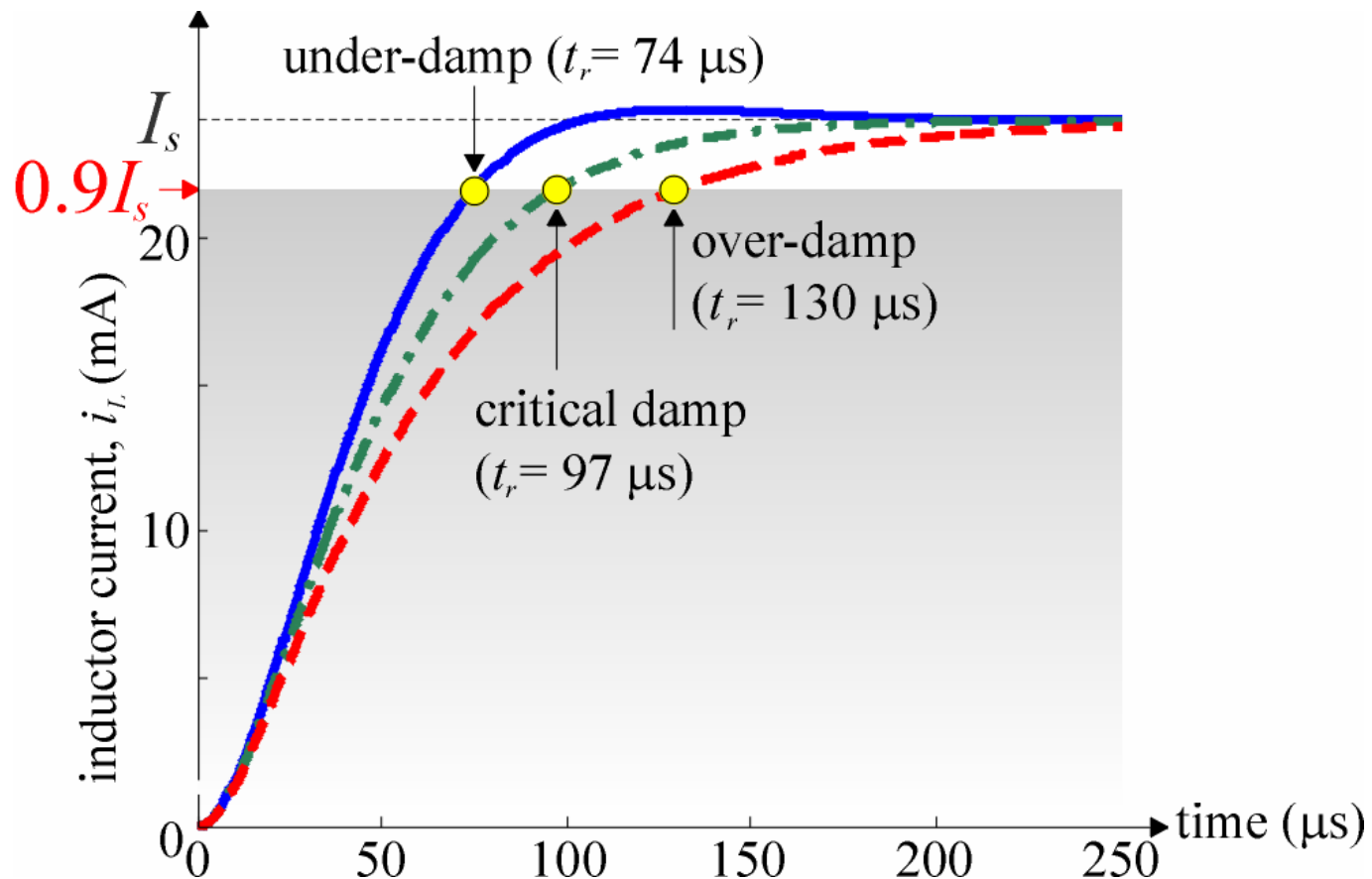
## Example 8.9: Comparison of rise times (2)

- The current of an under-damped circuit rises faster than that of its over-damped counterpart.



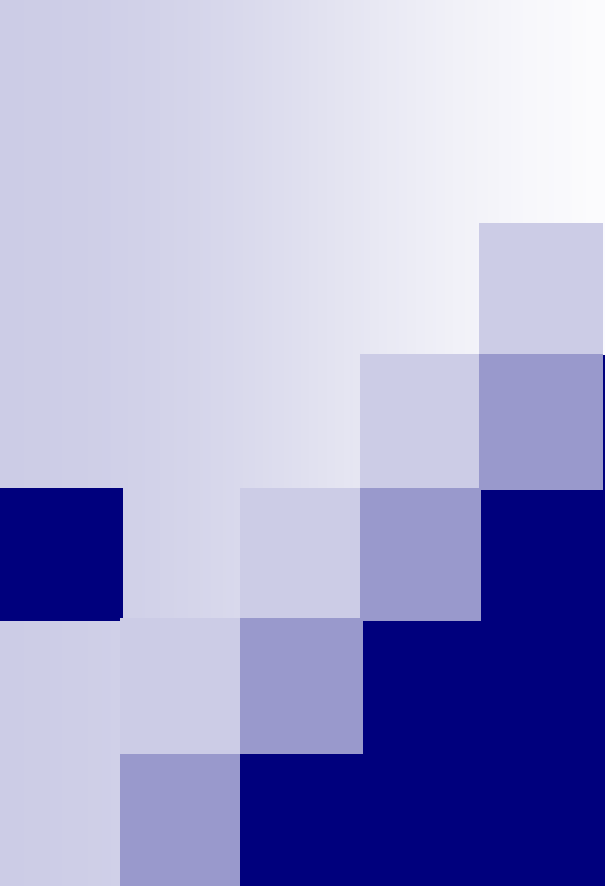


## Section 8.4

# The Natural and Step Response of a Series *RLC* Circuit

1. Modifications of time constant, neper frequency

## ODE of nature response

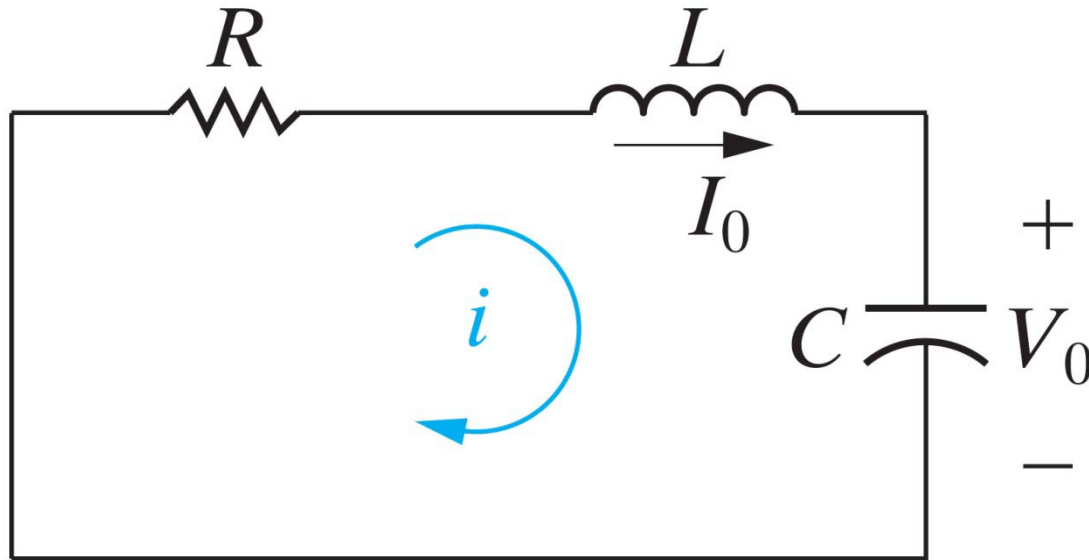


$V_0, I_0, i(t)$  must satisfy the **passive sign convention**.

- By KVL:  $Ri + L \frac{di}{dt} + \left[ V_0 + \frac{1}{C} \int_0^t i(t') dt' \right] = 0.$

- By derivative:  $\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0.$

$\frac{1}{RC}$  in parallel RLC

## The two initial conditions (ICs)

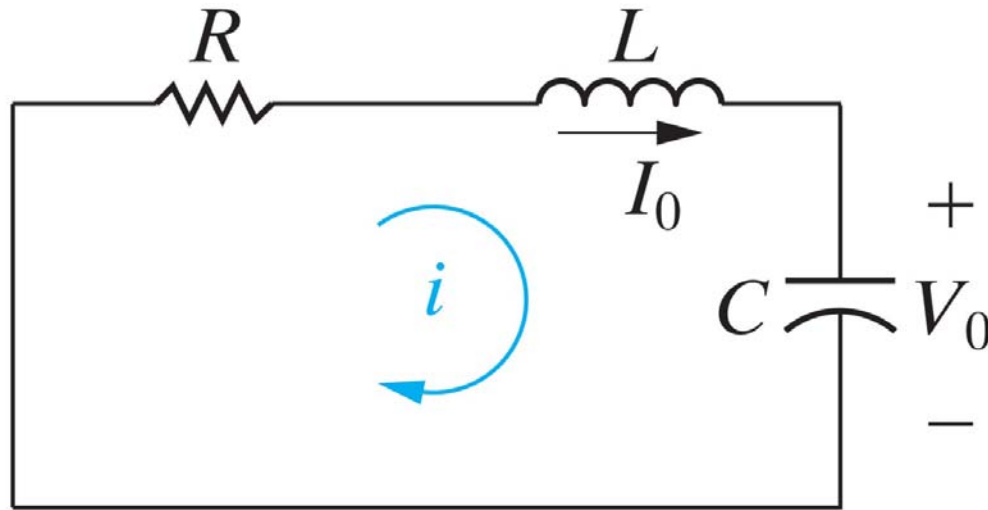

- The inductor cannot change abruptly,

$$\Rightarrow i(0^+) = I_0 \cdots (1)$$

- The capacitor voltage cannot change abruptly,

$$\Rightarrow v_C(0^+) = V_0, \quad v_L(0^+) = -v_C(0^+) - v_R(0^+) = -V_0 - I_0 R,$$

$$\because v_L(0^+) = L \left. \frac{di_L}{dt} \right|_{t=0^+}, \quad \Rightarrow i'_L(0^+) = i'(0^+) = -\frac{V_0 + I_0 R}{L} \cdots (2)$$



## General solution

- Substitute  $i(t) = Ae^{st}$  into the ODE, we got a different characteristic equation of  $s$ :

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0. \Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$

- The form of  $s_{1,2}$  determines the form of general solution:


$$i(t) = \begin{cases} A_1 e^{s_1 t} + A_2 e^{s_2 t}, & \text{if } \alpha > \omega_0 \\ e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t), & \text{if } \alpha < \omega_0 \\ e^{-\alpha t} (D_1 t + D_2), & \text{if } \alpha = \omega_0 \end{cases}$$

where  $\alpha = \frac{R}{2L}$ ,  $\omega_0 = \frac{1}{\sqrt{LC}}$ ,  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ .

$(2RC)^{-1}$  in parallel RLC

## Example 8.11: Discharging a series RLC circuit (1)

■ Q:  $i(t)$ ,  $v_C(t) = ?$

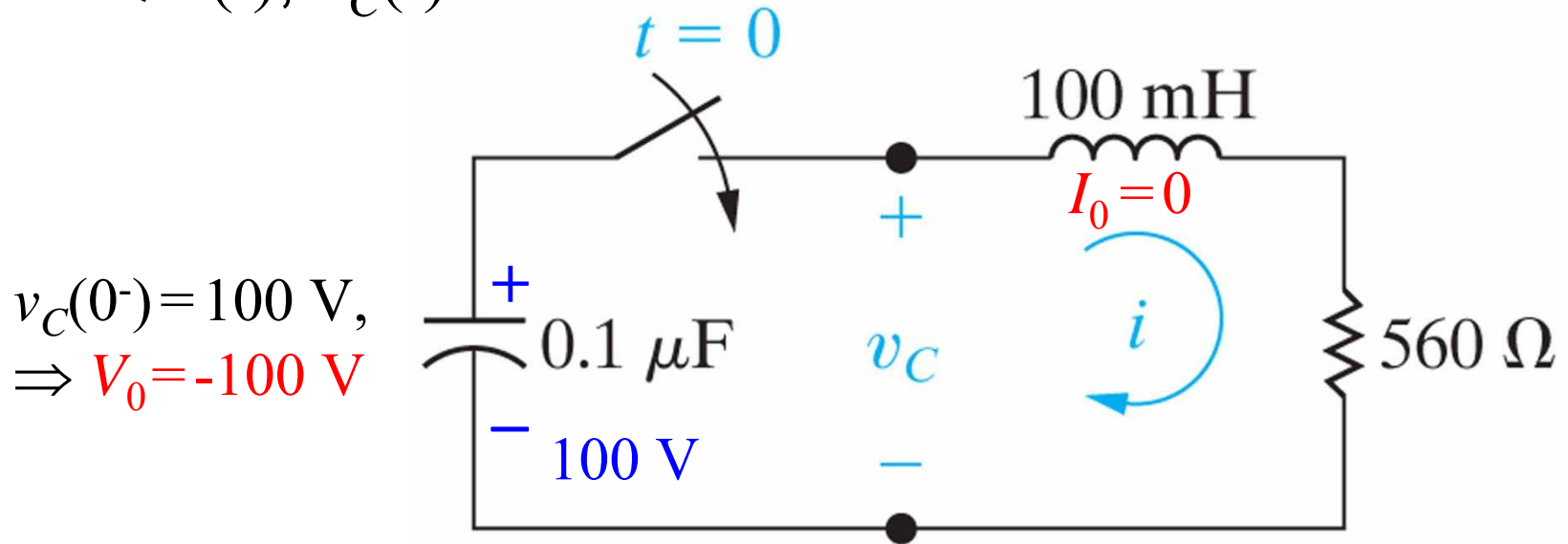

$$\begin{cases} \alpha = \frac{R}{2L} = \frac{560}{2(0.1)} = 2.8 \text{ kHz}, \\ \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.1)(1 \times 10^{-7})}} = 10 \text{ kHz}. \end{cases} \quad \Rightarrow \alpha < \omega_0, \text{ under-damped}$$

## Example 8.11: Solving the parameters (2)

- The damped frequency is:


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^2 - 2.8^2} = 9.6 \text{ kHz.}$$

- The 2 expansion coefficients are:

$$\begin{cases} B_1 = I_0 = 0 \dots (1) \\ -\cancel{\alpha B_1} + \underset{\substack{9.6 \\ \text{kHz}}}{\omega_d} B_2 = -\frac{\overset{-100 \text{ V}}{V_0} + \cancel{I_0 R}}{\underset{100 \text{ mH}}{L}} \dots (2) \end{cases} \Rightarrow \begin{cases} B_1 = 0, \\ B_2 \approx 104.2 \text{ mA} \end{cases}$$

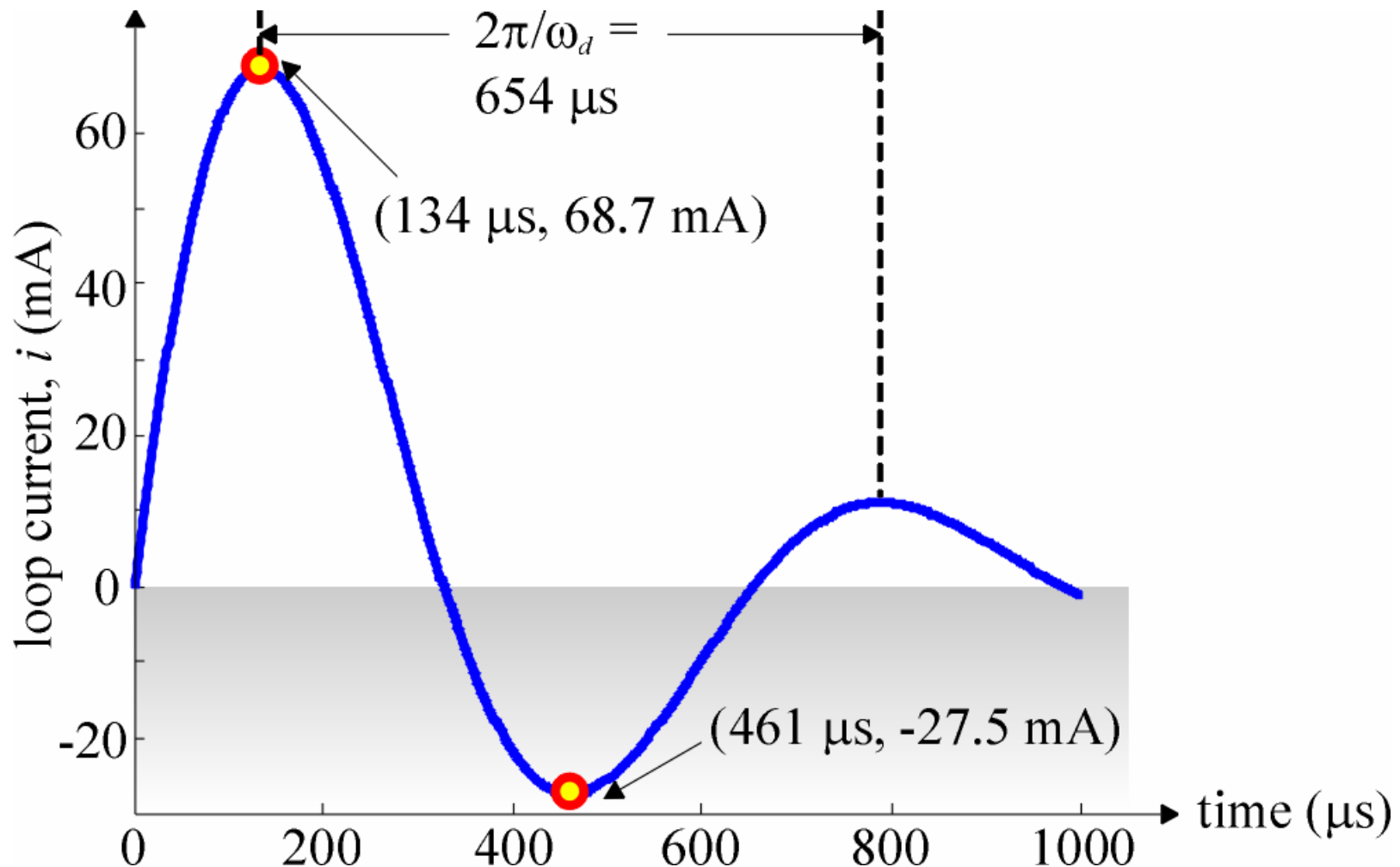
## Example 8.11: Loop current evolution (3)

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) = (104.2 e^{-2,800t} \sin 9,600t) \text{ mA}.$$



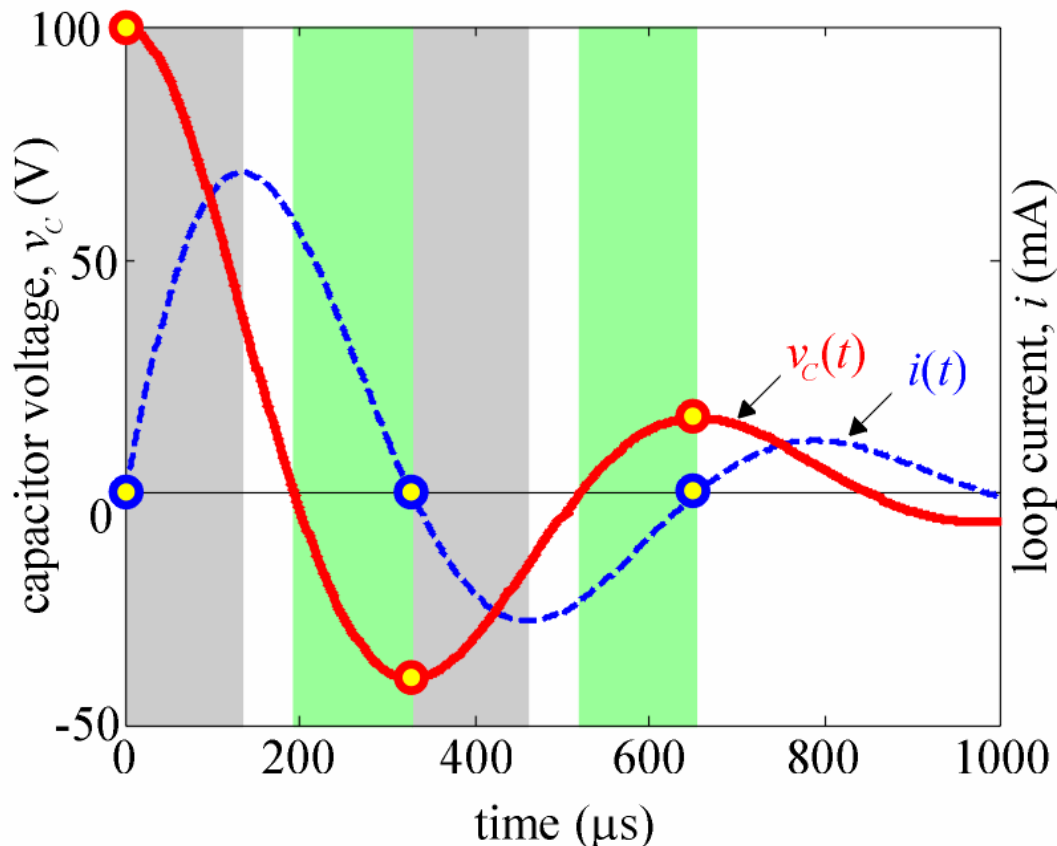
## Example 8.11: Capacitor voltage evolution (4)

$$v_c(t) = Ri(t) + Li'(t) = e^{-2,800t} (100 \cos 9,600t + 29.17 \sin 9,600t) \text{ V.}$$



- When the capacitor energy starts to decrease, the inductor energy starts to increase.
- Inductor energy starts to decrease before capacitor energy decays to 0.


## ODEs of step response

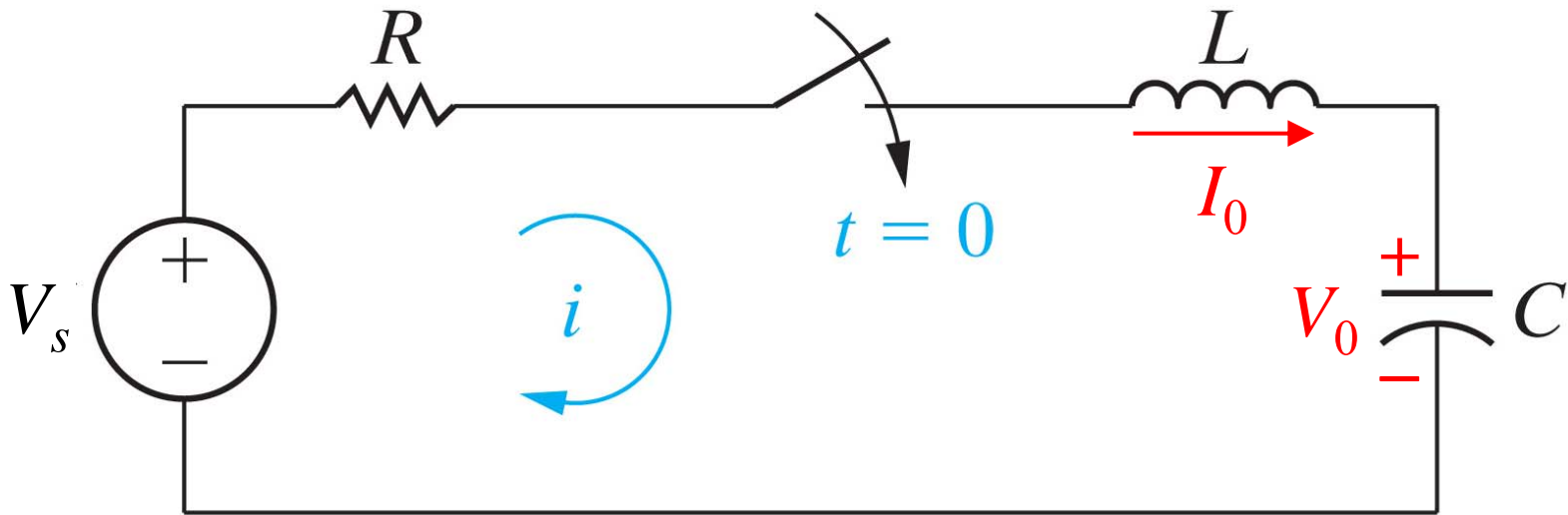

- By KVL:  $Ri + L \frac{di}{dt} + \left[ V_0 + \frac{1}{C} \int_0^t i(t') dt' \right] = V_s.$
- The homogeneous and inhomogeneous ODEs of  $i(t)$  and  $v_C(t)$  are:

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0, \text{ and } \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V_s}{LC}.$$

## The two initial conditions (ICs)

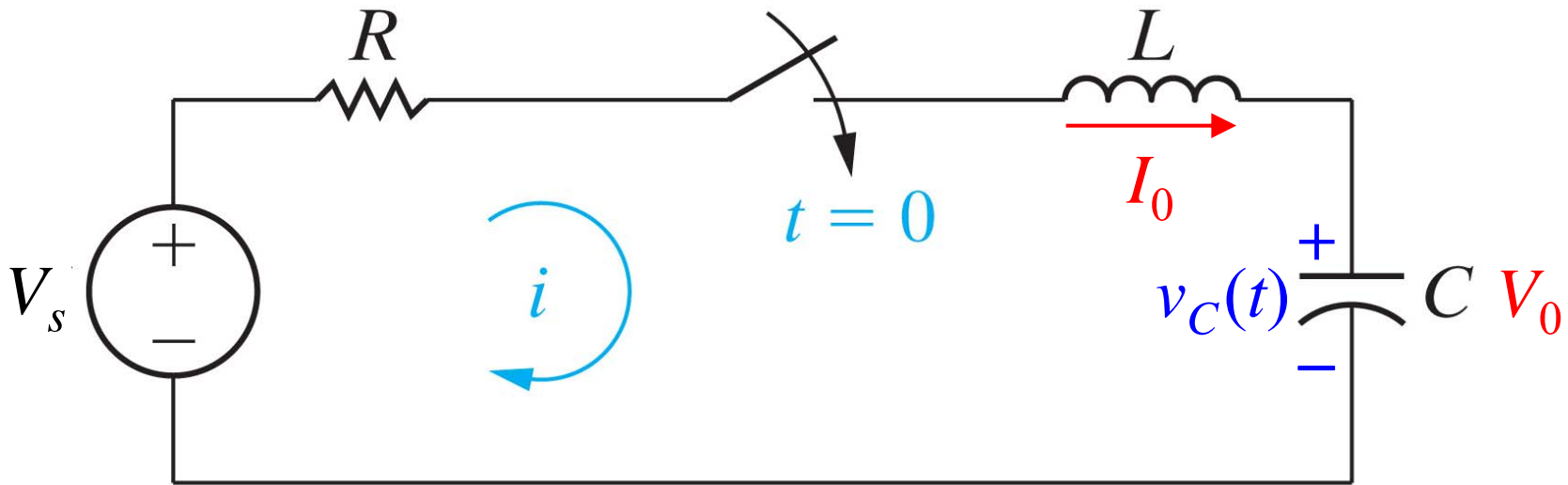

- The capacitor voltage cannot change abruptly,

$$\Rightarrow v_C(0^+) = V_0 \cdots (1)$$

- The inductor current cannot change abruptly,

$$\Rightarrow i_L(0^+) = I_0 = i_C(0^+),$$

$$\because i_C(0^+) = C \frac{dv_C}{dt} \Big|_{t=0^+}, \Rightarrow v'_C(0^+) = \frac{I_0}{C} \cdots (2)$$

## General solution

- The solution is the sum of final voltage  $V_f = V_s$  and the nature response  $v_{C,nature}(t)$ :

$$v_C(t) = V_f + v_{C,nature}(t),$$

where the three types of nature responses were elucidated in Section 8.4.

$$v_C(t) = \begin{cases} V_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}, & \text{if } \alpha > \omega_0, \\ V_f + e^{-\alpha t} (B'_1 \cos \omega_d t + B'_2 \sin \omega_d t), & \text{if } \alpha < \omega_0, \\ V_f + e^{-\alpha t} (D'_1 t + D'_2), & \text{if } \alpha = \omega_0. \end{cases}$$



## Key points

- What do the **response curves** of over-, under-, and critically-damped circuits look like? How to choose  $R$ ,  $L$ ,  $C$  values to achieve fast switching or to prevent overshooting damage?
- What are the **initial conditions** in an RLC circuit? How to use them to determine the expansion coefficients of the complete solution?
- Comparisons between: (1) natural & step responses, (2) parallel, series, or **general RLC**.