Chapter 14 Introduction to Frequency Selective Circuits

- 14.1 Some preliminaries
- 14.2 Low-pass filters
- 14.3 High-pass filters
- 14.4 Bandpass filters
- 14.5 Bandreject filters

Overview

- We have seen that the response of a circuit depends on the types of elements, the way the elements are connected, and the impedance of the elements that varies with frequency.
- In this chapter, we analyze the effect of varying source frequency on circuit voltages and currents. In particular, the circuits made of passive elements (*R*, *L*, *C*) that pass only a finite range of input frequencies.

Section 14.1 Some Preliminaries

- 1. Frequency response
- 2. Four types of filters

Frequency response plot

- The steady-state response due to a sinusoidal input Acos ωt is determined by sampling the transfer function H(s) along the imaginary axis, i.e. H(jω).
- Since H(jω)∈C, a frequency response plot consists of two parts: (1) magnitude plot |H(jω)|,
 (2) phase angle plot θ(jω).

Four types of ideal filters

 $\theta(j\omega_{c2})$



 $\theta(j\omega_{c1})$

Section 14.3 High-pass Filters (HPFs)

- 1. Frequency response of HPF
- 2. Effects of load

Series RC circuit

$$\blacksquare Z_c = 1/(j\omega C).$$

■ $Z_c \rightarrow \infty$ as $\omega \rightarrow 0$, $\Rightarrow v_o \rightarrow 0$ (no current flows through *R*).

■
$$Z_c \rightarrow 0$$
 as $\omega \rightarrow \infty$, $\Rightarrow v_o \rightarrow v_i$
(short circuit).

The input voltage can pass through the circuit if the source frequency is high enough.







Frequency response plot of a series RC circuit

By the equivalent circuit in the s-domain:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R}{R + (sC)^{-1}} = \frac{s}{s + \omega_c}, \text{ where } \omega_c = \frac{1}{RC}.$$
$$\Rightarrow H(j\omega) = \frac{j\omega}{j\omega + \omega_c}, \qquad |H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \omega_c^2}} = \frac{\omega}{\sqrt{\omega^2 + \omega^2}} = \frac{\omega}{\sqrt{\omega^2$$

Example: Superposition of sinusoids

• Let
$$x(t) = x_1(t) + x_2(t) = \cos(\frac{\omega_1}{0.1\omega_c}t) + \sin(\frac{\omega_2}{3\omega_c}t)$$
.
 $H(j\omega) = \frac{j(\omega/\omega_c)}{j(\omega/\omega_c) + 1}, \Rightarrow \begin{cases} H(j\omega_1) \approx 0.10 \angle 84^\circ \\ H(j\omega_2) \approx 0.95 \angle 18^\circ \end{cases}$
 $Y_1 \approx 1 \angle 0^\circ \times 0.10 \angle 84^\circ, \Rightarrow y_1(t) \approx 0.1\cos(0.1\omega_c t + 84^\circ);$
 $Y_2 \approx 1 \angle -90^\circ \times 0.95 \angle 18^\circ, \Rightarrow y_2(t) \approx 0.95\cos(3\omega_c t - 72^\circ);$
 $\int_{0}^{0} \frac{f(\omega/\omega_c)}{f(\omega/\omega_c) + 1} = \int_{0}^{0} \frac{f(\omega/\omega_c)}{f(\omega/\omega_c) + 1} =$

9

Example: Filtering in the spatial-frequency domain

An image is a function of (x,y), which can be decomposed into many "spatial-frequency" components (f_x, f_y). HPF enhances the contrast.



(wikipedia.org)

Example 14.4: RL circuit with load (1)

- An RL circuit can be an HPF if $v_o \equiv v_L$. (E.g. 14.3)
- When a load resistor R_L is in parallel with the output inductor *L*:



Example 14.4: RL circuit with load (2)

• The effects of R_1 are: (1) reducing the passband magnitude by a factor of K, (2) lowering the cutoff frequency by the same factor of K.



Problem: the response varies with the load. Solution: use active filters (Ch15).

Section 14.4 Bandpass Filters (BPFs)

- 1. Frequency response of BPF
- 2. Relation with the poles, zeros

Series RLC circuit

$$Z_{c}=1/(j\omega C), Z_{L}=j\omega L.$$

$$Z_{c}\rightarrow\infty \text{ as } \omega\rightarrow0, \Rightarrow v_{o}\rightarrow0.$$

$$Z_{L}\rightarrow\infty \text{ as } \omega\rightarrow\infty, \Rightarrow v_{o}\rightarrow0.$$

$$At \text{ some frequency } \omega_{0}\in(0,\infty), Z_{c}+Z_{L}=0, v_{o}=v_{i}.$$

 The input voltage can pass through the circuit if the source frequency is near ω₀.







 $(\rightarrow 0)$

Frequency response plot of a series RLC circuit

By the equivalent circuit in the s-domain:

$$\frac{H(s)}{sL + (sC)^{-1} + R} = \frac{\beta s}{s^2 + \beta s + \omega_0^2}, \text{ where } \beta = \frac{R}{L}, \ \omega_0 = \frac{1}{\sqrt{LC}}.$$

$$\Rightarrow \begin{cases} \left| H(j\omega) \right| = \frac{\beta\omega}{\sqrt{\left(\omega^2 - \omega_0^2\right)^2 + (\beta\omega)^2}} & |H(j\omega)| \\ \frac{1.0}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \theta(j\omega) = 90^\circ - \tan^{-1} \left(\frac{\beta\omega}{\omega_0^2 - \omega^2} \right) & \theta(j\omega) \\ \frac{90^\circ}{90^\circ} & 0 \\ -90^\circ & 0 \\ -90^\circ & 0 \\ \end{array}$$

Calculations of parameters

Center (resonance) frequency is derived by:

$$j\omega L + \frac{1}{j\omega C} = 0, \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Cutoff frequencies are derived by:

$$|H(j\omega)| = \frac{1}{\sqrt{2}}, \implies \omega_{c1,c2} = \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2 \mp \frac{\beta}{2}}.$$

$$\Rightarrow \text{Bandwidth } \omega_{c2} - \omega_{c1} = \beta = \frac{R}{L}; \quad \omega_0 = \sqrt{\omega_{c1}\omega_{c2}} \neq \frac{\omega_{c1} + \omega_{c2}}{2}.$$

Quality factor (~ inversed relative bandwidth) is:

$$Q \equiv \frac{\omega_0}{\beta} = \frac{\sqrt{L/C}}{R}$$

Example: White-noise rejection

If a signal of specific frequency f₁ is buried in strong "white" noise, a BPF centered at f₁ can be used to extract the signal.



(www.chem.vt.edu)

Frequency response visualized by poles, zeros

The poles and zeros of HPF and BPF are:

$$H_{HPF}(s) = \frac{s}{s + \omega_c}, \implies p = -\omega_c, z = 0.$$

$$H_{BPF}(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}, \implies p = \frac{-\beta \pm \sqrt{\beta^2 - 4\omega_0^2}}{2}, z = 0.$$



Practical Perspective Pushbutton Telephone Circuits

Application of BPFs

Q: How to tell which button was pushed? How to tell the difference between the button tones and the normal vocal sounds (both are within 300-3000 Hz) or ringing bell tones (20 Hz)?



(jouielovesyou.wordpress.com)



(wikipedia.org)

Dual-tone-multiple-frequency (DTMF)

Each bottom is encoded with a "Low Group" frequencies [Hz] unique pair of sinusoidal tones (f_I , f_H), where the relative timing and amplitudes must be close enough.

"High Group" frequencies [Hz]



(sohilp.blogspot.com)

BPFs: (1) identify whether both freq. groups are present, (2) select among possible tones.

BPF design for the low-frequency group

The transmission spectrum of a series RLC is:



For the low-freq. group, \$\omega_{c1} = 2\pi(697) = 4379\$ rad/s, \$\omega_{c2} = 2\pi(941) = 5912\$ rad/s, \$\Rightarrow \beta = \omega_{c2} - \omega_{c1} = 1533\$ rad/s.
\$\beta = R/L\$, \$\Rightarrow L = R/\beta = (600 \Omega)/1533 = 0.39\$ H. \$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = 1/\sqrt{LC}\$, \$\Rightarrow C = 1/(L\omega_{c1}\omega_{c2}) = 100\$ nF.

BPF performance (1)

The transmission of the 4 frequencies in the lowfrequency group are imperfect (<1):</p>

$$|H_{697Hz}| = |H_{941Hz}| = \frac{1}{\sqrt{2}} = 0.707,$$

$$|H_{770Hz}| = |H_{852Hz}| = \frac{\beta\omega}{\sqrt{(\omega^2 - \omega_0^2)^2 + (\beta\omega)^2}} = 0.948.$$

$$1.0 - \frac{1}{\sqrt{2}} = 0.948.$$

BPF performance (2)

The transmission of the high-frequency group tones and the 20 Hz ringing tone are imperfect (>0): |H(f)|(1209 Hz, 0.344) 0.5 (1633 Hz, 0.194) (20 Hz,

0.74%)

BPF design for the high-frequency group

The transmission spectrum of a series RLC is:

$$|H(j\omega)| = \frac{\beta\omega}{\sqrt{(\omega^2 - \omega_0^2)^2 + (\beta\omega)^2}}, \quad \beta = \frac{R}{L}, \ \omega_0 = \frac{1}{\sqrt{LC}}.$$

- For the high-freq. group, $\omega_{c1} = 2\pi(1209) = 7596$ rad/s, $\omega_{c2} = 2\pi(1633) = 10260$ rad/s, $\Rightarrow \beta = \omega_{c2} - \omega_{c1} = 2664$ rad/s.
- Both L and C values are smaller:

$$\beta = R/L, \Rightarrow L = R/\beta = (600 \,\Omega)/2664 = 0.26 \,\mathrm{H}.$$
$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = 1/\sqrt{LC}, \Rightarrow C = 1/(L\omega_{c1}\omega_{c2}) = 57 \,\mathrm{nF}.$$

BPF performance

The transmission of the low-frequency group tones and the 20 Hz ringing tone are imperfect (>0): |H(f)|(941 Hz, 0.344)0.5 Ιz. 0.194 (20 Hz, 0.43%)