

Homework 2

(Due date: 2014/3/12)

This assignment covers Ch3 and Ch4.1-4.9 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 3.8 of the textbook (p100), while the right resistor is changed from $6\ \Omega$ to $9\ \Omega$.
- 2) (10 points) Problem 3.60 of the textbook (p107), while the voltage source is changed from 500 V to 900 V and the right resistor is changed from $27\ \Omega$ to $17\ \Omega$.
- 3) (15 points) Problem 3.71 of the textbook (p109).
- 4) (15 points) Problem 4.27 of the textbook (p155), while the voltage source is changed from 24 V to 18 V and the voltage-controlled voltage source is changed from $5v_{\Delta}$ to $3v_{\Delta}$. Also calculate v_o when the $33\text{-}\Omega$ resistor is eliminated.
- 5) (20 points) Problem 4.38 of the textbook (p156), while the voltage source is changed from 135 V to 225 V. Also find the power extracted or dissipated by the current controlled voltage source.
- 6) (10 points) Problem 4.45 of the textbook (p157), while the current source is changed from 20 A to 160 A and the current-controlled voltage source is changed from $6.5i_{\Delta}$ to

$$8i_{\Delta}.$$

- 7) (10 points) Problem 4.58 of the textbook (p158), while the top current source is changed from 4 A to 10 A.
- 8) (10 points) Problem 4.59 of the textbook (p159), while the right current source is changed from 0.6 mA to 1.2 mA.