

Homework2 solutions

(Due date: 2014/3/12)

This assignment covers Ch3 and Ch4.1-4.9 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 3.8 of the textbook (p100), while the right resistor is changed from $6\ \Omega$ to $9\ \Omega$.

Ans:

1a)

$$p_{4\Omega} = i_s^2 4 = \left(\frac{120}{11.2}\right)^2 4 \cong 459.1837\ \Omega \quad p_{18\Omega} = i_1^2 18 = \left(\frac{120}{11.2} \times \frac{2}{5}\right)^2 18 \cong 330.6122\ \Omega$$

$$p_{3\Omega} = i_2^2 3 = \left(\frac{120}{11.2} \times \frac{3}{5}\right)^2 3 \cong 123.9796\ \Omega \quad p_{9\Omega} = i_2^2 9 = \left(\frac{120}{11.2} \times \frac{3}{5}\right)^2 9 \cong 371.9388\ \Omega$$

1b)

$$p_{120V}(\text{delivered}) = 120i_s = 120 \times \frac{120}{11.2} \cong 1285.714\ \text{W}$$


1c)

$$p_{\text{diss}} = 459.1837 + 330.6122 + 123.9796 + 371.9388 \cong 1285.714\ \text{W}$$

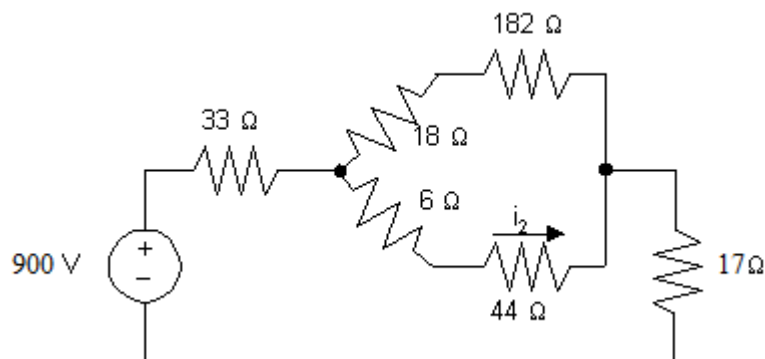
- 2) (10 points) Problem 3.60 of the textbook (p107), while the voltage source is changed from 500 V to 900 V and the right resistor is changed from $27\ \Omega$ to $17\ \Omega$.

Ans:

Replace the 30—60—10 Ω delta with a wye equivalent to get



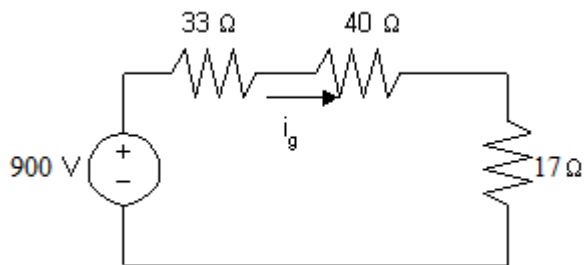
Using series/parallel reductions the circuit reduces to



$$i_g = \frac{900}{90} = 10 \text{ A}$$

$$i_2 = \frac{200}{250} (10) = 8 \text{ A}$$

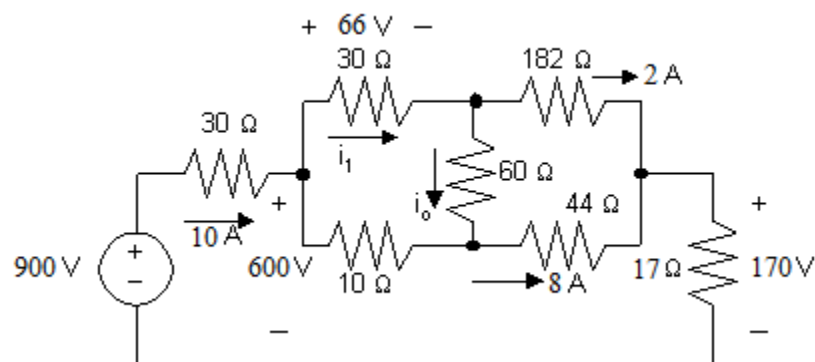Returning to the original circuit we have



$$i_1 = \frac{66}{30} = 2.2 \text{ A}$$

$$i_o = 2.2 - 2 = 0.2 \text{ A}$$

$$v = 60i_o = 12 \text{ V}$$

$$P_{\text{supplied}} = 900 \times 10 = 9000 \text{ W}$$

3) (15 points) Problem 3.71 of the textbook (p109).

Ans:

From Eq 3.69

$$\frac{i_1}{i_3} = \frac{R_2 R_3}{D}$$

But $D = (R_1 + 2R_a)(R_2 + 2R_b) + 2R_b R_2$

Where $R_a = \sigma R_1$; $R_2 = (1 + 2\sigma)^2 R_1$ and $R_b = \frac{(1+2\sigma)^2 \sigma R_1}{4(1+\sigma)^2}$

Therefore D can be written as

$$\begin{aligned} D &= (R_1 + 2\sigma R_1) \left[(1 + 2\sigma)^2 R_1 + \frac{2(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} \right] + 2(1 + 2\sigma)^2 R_1 \left[\frac{(1 + 2\sigma)^2 \sigma R_1}{4(1 + \sigma)^2} \right] \\ &= (1 + 2\sigma)^3 R_1^2 \left[1 + \frac{\sigma}{2(1 + \sigma)^2} + \frac{(1 + 2\sigma)\sigma}{2(1 + \sigma)^2} \right] \\ &= \frac{(1 + 2\sigma)^3 R_1^2}{2(1 + \sigma)^2} \{ 2(1 + \sigma)^2 + \sigma + (1 + 2\sigma)\sigma \} \\ &= \frac{(1 + 2\sigma)^3 R_1^2}{2(1 + \sigma)^2} \{ 1 + 3\sigma + 2\sigma^2 \} \\ D &= \frac{(1 + 2\sigma)^4 R_1^2}{1 + \sigma} \\ \therefore \frac{i_1}{i_3} &= \frac{R_2 R_3 (1 + \sigma)}{(1 + 2\sigma)^4 R_1^2} = \frac{(1 + 2\sigma)^2 R_1 R_3 (1 + \sigma)}{(1 + 2\sigma)^4 R_1^2} = \frac{(1 + \sigma) R_3}{(1 + 2\sigma)^2 R_1} \end{aligned}$$

When this result is substituted into Eq 3.69 we get

$$R_3 = \frac{(1 + \sigma)^2 R_3^2 R_1}{(1 + 2\sigma)^4 R_1^2}$$

Solving for R_3 gives

$$R_3 = \frac{(1 + 2\sigma)^4 R_1}{(1 + \sigma)^2}$$

4) (15 points) Problem 4.27 of the textbook (p155), while the voltage source is changed

from 24 V to 18 V and the voltage-controlled voltage source is changed from $5v_\Delta$ to $3v_\Delta$. Also calculate v_o when the $33\text{-}\Omega$ resistor is eliminated.

Ans:

Place $5v_\Delta$ inside a supernode and use the lower node as a reference. Then

$$\frac{v_\Delta - 18}{10} + \frac{v_\Delta}{2} + \frac{v_\Delta - 3v_\Delta}{20} + \frac{v_\Delta - 3v_\Delta}{40} = 0$$

$$18v_\Delta = 72; \quad v_\Delta = 4 \text{ V}$$

$$v_o = v_\Delta - 3v_\Delta = -8 \text{ V}$$

When the $33\text{-}\Omega$ resistor is eliminated,


$$\frac{v_\Delta - 18}{10} + \frac{v_\Delta}{2} + i_{5v_\Delta} = 0$$

$$\frac{-2v_\Delta}{20} + \frac{-2v_\Delta}{40} = i_{5v_\Delta}$$

$$v_o = -8 \text{ V}$$

- 5) (20 points) Problem 4.38 of the textbook (p156), while the voltage source is changed from 135 V to 225 V. Also find the power extracted or dissipated by the current controlled voltage source.

Ans:

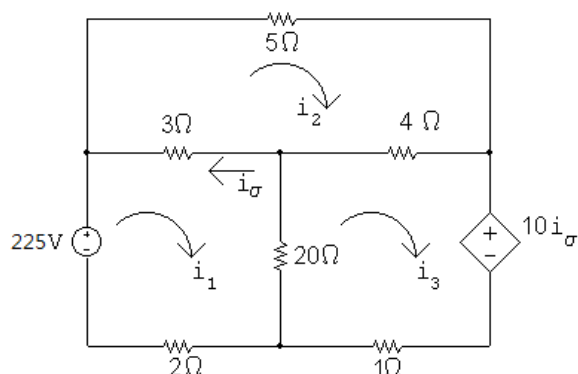

$$25i_1 - 3i_2 - 20i_3 + 0i_\sigma = 225$$

$$-3i_1 + 12i_2 - 4i_3 + 0i_\sigma = 0$$

$$-20i_1 - 4i_2 + 25i_3 + 10i_\sigma = 0$$

$$1i_1 - 1i_2 + 0i_3 + 1i_\sigma = 0$$


Solving, $i_1 = 108 \text{ A}$, $i_2 = 65 \text{ A}$, $i_3 = 114 \text{ A}$, $i_\sigma = -43 \text{ A}$

$$P_{20\Omega} = (114 - 108)^2(20) = 720 \text{ W}$$

$$P_{10i_\sigma} = 10i_\sigma i_3 = -49.02 \text{ kW, extracted.}$$

- 6) (10 points) Problem 4.45 of the textbook (p157), while the current source is changed from 20 A to 160 A and the current-controlled voltage source is changed from $6.5 i_\Delta$ to $8 i_\Delta$.

Ans:

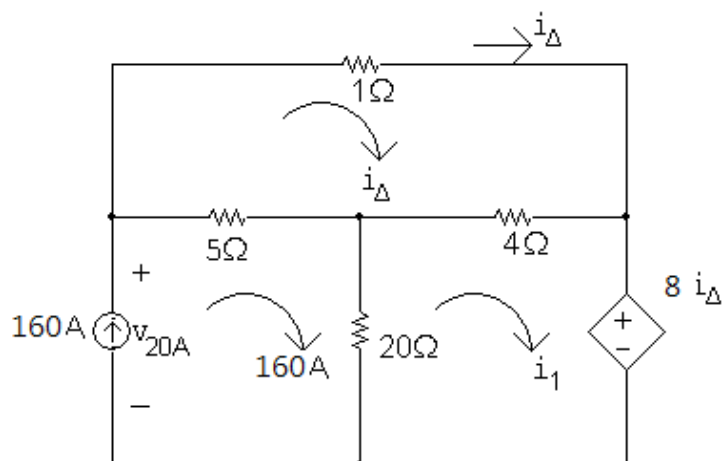

$$10i_\Delta - 4i_1 = 800$$

$$-4i_\Delta + 24i_1 + 8i_\Delta = 3200$$

Solving, $i_1 = 112.5 \text{ A}$, $i_\Delta = 125 \text{ A}$

$$v_{20\Omega} = 1i_\Delta + 8i_\Delta = 9(125) = 1125 \text{ V}$$

$$p_{20\Omega} = -160v_{20\Omega} = -160(1125) = -180 \text{ kW}$$

$$p_{8i_\Delta} = 8i_\Delta i_1 = (8)(125)(112.5) = 112.5 \text{ kW}$$

Therefore, the independent source is developing 180 kW, all other elements are absorbing

power, and the total power developed is thus **180 kW**.

CHECK:

$$p_{1\Omega} = (125)^2(1) = 15.625 \text{ kW}$$

$$p_{5\Omega} = (160 - 125)^2(5) = 6.125 \text{ kW}$$

$$p_{4\Omega} = (125 - 112.5)^2(4) = 0.625 \text{ kW}$$


$$p_{20\Omega} = (160 - 112.5)^2(20) = 45.125 \text{ kW}$$

$$\sum p_{abs} = 112.5 + 15.625 + 6.125 + 0.625 + 45.125 = 180 \text{ kW}$$

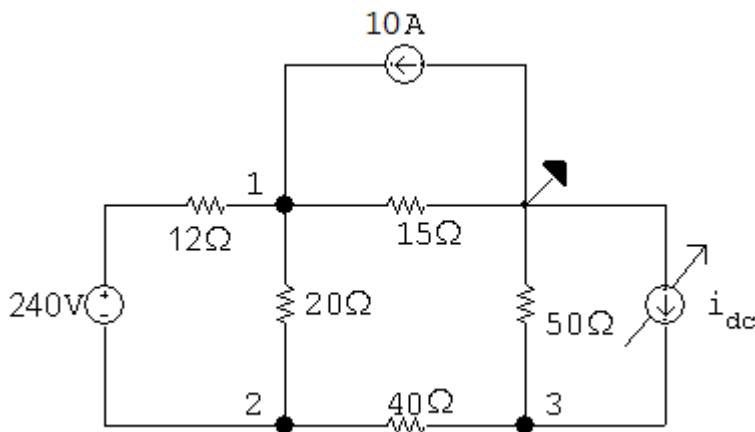- 7) (10 points) Problem 4.58 of the textbook (p158), while the top current source is changed from 4 A to 10 A.

Ans:

Choose the reference node so that a node voltage is identical to the voltage across the 10 A source; thus:



Since the 10 A source is developing 0 W, v_1 must be 0 V.

Since v_1 is known, we can sum the currents away from node 1 to find v_2 ; thus:

$$\frac{0 - (240 + v_2)}{12} + \frac{0 - v_2}{20} + \frac{0}{15} - 10 = 0$$

$$\therefore v_2 = -225\text{V}$$

Now that we know v_2 , we sum the currents away from node 2 to find v_3 ; thus:

$$\frac{v_2 + 240 - 0}{12} + \frac{v_2 - 0}{20} + \frac{v_2 - v_3}{40} = 0$$

$$\therefore v_3 = -625 \text{ V}$$

Now that we know v_3 , we sum the currents away from node 3 to find i_{dc} ; thus:


$$\frac{v_3}{50} + \frac{v_3 - v_2}{40} = i_{dc}$$

$$\therefore i_{dc} = -22.5 \text{ A}$$

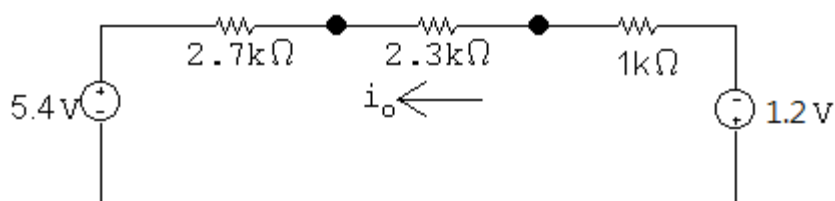- 8) (10 points) Problem 4.59 of the textbook (p159), while the right current source is changed from 0.6 mA to 1.2 mA.


Ans:

8a) Apply source transformations to both current sources to get



$$i_o = \frac{-(5.4 + 1.2)}{2700 + 2300 + 1000} = -1.1 \text{ mA}$$

8b)

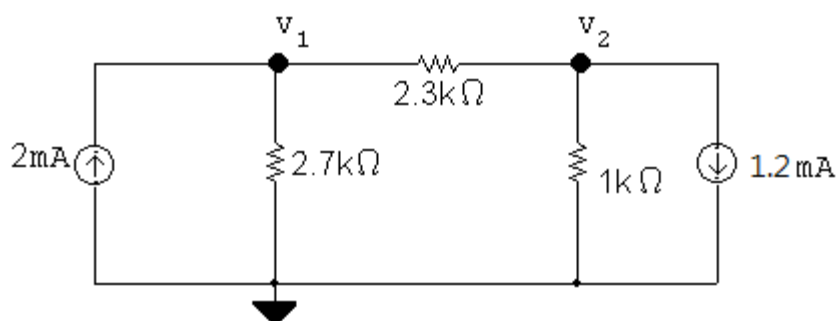

The node voltage equation:

$$-2 \times 10^{-3} + \frac{v_1}{2700} + \frac{v_1 - v_2}{2300} = 0$$

$$\frac{v_2}{1000} + \frac{v_2 - v_1}{2300} + 1.2 \times 10^{-3} = 0$$

Solving, $v_1 = 2.43 \text{ V}$, $v_2 = -0.1 \text{ V}$

$$\therefore i_o = \frac{v_2 - v_1}{2300} = \frac{-2.53}{2300} = -1.1 \text{ mA}$$