

## Homework 4

(Due date: 2014/4/16)

This assignment covers Ch9 and Ch10 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 9.14 of the textbook (p371), while the maximum amplitude of the steady-state current in the inductor is changed from 25 A to 20 A.
- 2) (10 points) Problem 9.35 of the textbook (p374), while the impedance of the left inductor is changed from  $j5\ \Omega$  to  $j2\ \Omega$ .
- 3) (20 points) Problem 9.45 of the textbook (p375), while the impedance of capacitor is changed from  $-j48\ \Omega$  to  $-j36\ \Omega$  and the resistor  $R_0$  is changed from  $36\ \Omega$  to  $24\ \Omega$ .
- 4) (10 points) Problem 9.59 of the textbook (p377), while the current source is changed from  $10+j10$  to  $10+j20$ .
- 5) (10 points) Problem 9.78 of the textbook (p379), while the left resistor is changed from  $5\ \Omega$  to  $10\ \Omega$ .
- 6) (10 points) Problem 10.5 of the textbook (p409), while the current source is changed from  $4 \cos 5000t$  mA to  $4 \cos 2000t$  mA.
- 7) (10 points) Problem 10.27 of the textbook (p412), while the voltage drop is changed

from 250 V to 200 V (rms).

- 8) (20 points) Problem 10.56 of the textbook (p416).