

Homework 7

(Due date: 2014/6/11)

This assignment covers Ch14 and Ch18 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 14.8 of the textbook (p574), while the inductor in (e) is changed from 10 mH to 5 mH.
- 2) (10 points) Problem 14.15 of the textbook (p575), while the resistor is changed from 150 Ω to 200 Ω .
- 3) (10 points) Problem 14.30 of the textbook (p576), while the center frequency ω_0 is changed from 50 krad/s to 100 krad/s and the capacitor is changed from 20 nF to 10 nF.
- 4) (20 points) Problem 14.31 of the textbook (p577).
- 5) (10 points) Problem 18.18 of the textbook (p722), while the resistor is changed from 4 Ω to 10 Ω and the goal is changed from expressions for the a parameters to those of the g parameters.
- 6) (10 points) Problem 18.19 of the textbook (p722).
- 7) (15 points) Problem 18.29 of the textbook (p722), while the right resistor is changed

from $100\ \Omega$ to $60\ \Omega$.

- 8) (15 points) Problem 18.34 of the textbook (p723), while the value of V_1 in Measurement 2 is changed from 20 mV to 25 mV.