

Homework 1

(Due date: 2014/3/3)

This assignment covers Ch1 and Ch2 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (15 points) Problem 1.13 of the textbook (p41), while the current is changed from 9 mA to 12 mA.
- 2) (15 points) Problem 2.7 of the textbook (p71), while the left and middle independent voltage sources are changed from 50 V and 80 V to 100 V and 200 V, respectively.
- 3) (20 points) Problem 2.17 of the textbook (p73), while the resistor in (c) is changed from 400 Ω to 100 Ω .
- 4) (10 points) Problem 2.20 of the textbook (p73), while the current i_a is changed from 2 mA to 5 mA.
- 5) (15 points) Problem 2.25 of the textbook (p74), while the voltage source is changed from 240 V to 300 V and the 45- Ω to 180- Ω resistances are changed to 50 Ω and 170 Ω , respectively.
- 6) (15 points) Problem 2.30 of the textbook (p75), while the left voltage source is changed from 100 V to 125 V.

- 7) (10 points) Problem 2.34 of the textbook (p76), while the resistance of the trunk is changed from $50\ \Omega$ to $150\ \Omega$.