


## Homework3 solutions

(Due date: 2014/3/19)

This assignment covers Ch4 and Ch6.1-6.3 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 4.66 of the textbook (p160), while the current source is changed from 4 A to 6 A.

Ans:

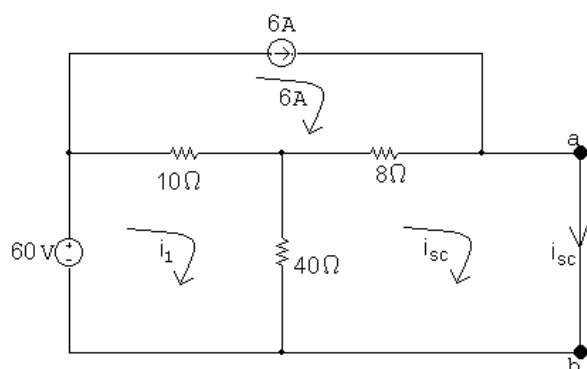


$$50i_1 - 40i_{sc} = 60 + 60$$

$$-40i_1 + 48i_{sc} = 48$$

Solving,  $i_{sc} = 9 \text{ A}$

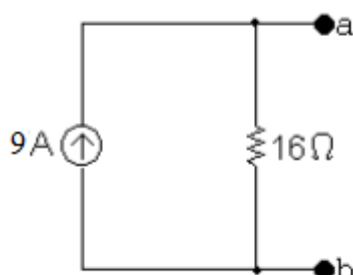
$$R_{Th} = 8 + \frac{(10)(40)}{50} = 16 \Omega$$



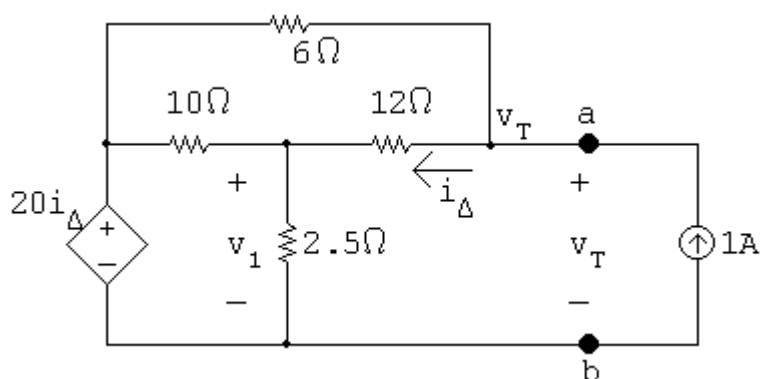- 2) (10 points) Problem 4.77 of the textbook (p161), while the current-controlled voltage source is changed from  $10 i_{\Delta}$  to  $20 i_{\Delta}$ .

Ans:

$V_{Th} = 0$ , since circuit contains no independent sources.



$$\frac{v_1 - 20i_{\Delta}}{10} + \frac{v_1}{2.5} + \frac{v_1 - v_T}{12} = 0$$

$$\frac{v_T - v_1}{12} + \frac{v_T - 20i_{\Delta}}{6} - 1 = 0$$

$$i_{\Delta} = \frac{v_T - v_1}{12}$$

In standard form:

$$v_1 \left( \frac{1}{10} + \frac{1}{2.5} + \frac{1}{12} \right) + v_T \left( -\frac{1}{12} \right) + i_{\Delta}(-2) = 0$$


$$v_1 \left( -\frac{1}{12} \right) + v_T \left( \frac{1}{12} + \frac{1}{6} \right) + i_{\Delta} \left( \frac{-20}{6} \right) = 1$$

$$v_1(1) + v_T(-1) + i_{\Delta}(12) = 0$$

Solving,

$$v_1 = 9 \text{ V}; \quad v_T = 27 \text{ V}; \quad i_{\Delta} = 1.5 \text{ A}$$

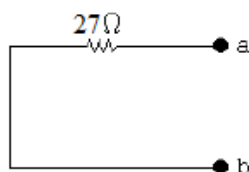
$$\therefore R_{Th} = \frac{v_T}{1 \text{ A}} = 27 \Omega$$



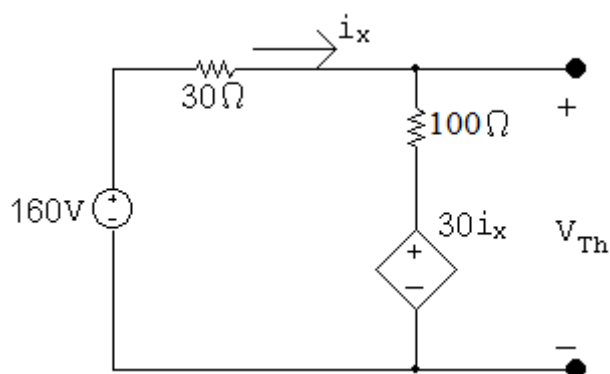- 3) (20 points) Problem 4.83 of the textbook (p162), while the right resistor is changed from  $20\ \Omega$  to  $100\ \Omega$  and the power dissipated in the resistor  $R_0$  is changed from  $250\ \text{W}$  to  $225\ \text{W}$ .

Ans:


We begin by finding the Thévenin equivalent with respect to  $R_0$ . After making a couple of source transformations the circuit simplifies to



$$i_x = \frac{160 - 30i_x}{130}; \quad i_x = 1\ \text{A}$$

$$V_{\text{Th}} = 100i_x + 30i_x = 130i_x = 130\ \text{V}$$

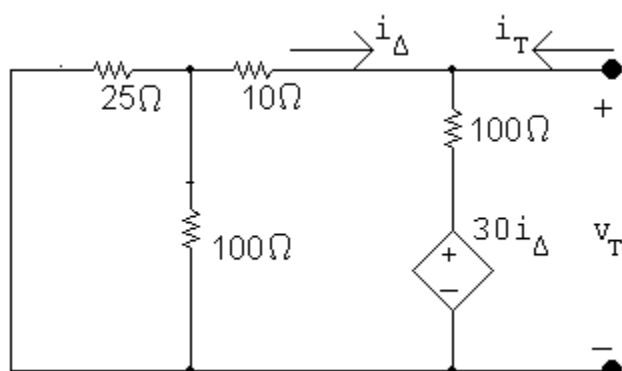Using the test-source method to find the Thévenin resistance gives




$$i_T = \frac{v_T}{30} + \frac{v_T - 30(-\frac{v_T}{30})}{100}$$

$$\frac{i_T}{v_T} = \frac{1}{30} + \frac{1}{50} = \frac{8}{150} = \frac{4}{75}$$

$$R_{Th} = \frac{v_T}{i_T} = \frac{75}{4} = 18.75 \Omega$$

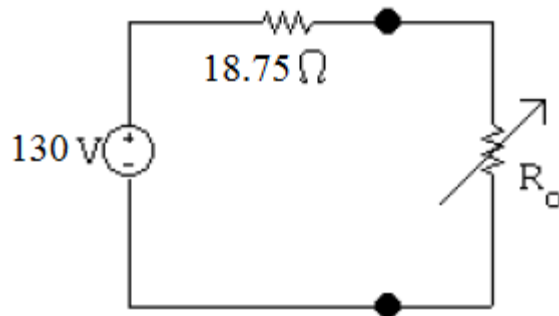Thus our problem is reduced to analyzing the circuit shown below.



$$p = \left( \frac{130}{18.75 + R_o} \right)^2 R_o = 225$$

$$\frac{(130)^2}{R_o^2 + 37.5R_o + 18.75^2} R_o = 225$$

$$\frac{(130)^2}{225} R_o = R_o^2 + 37.5R_o + 18.75^2$$

$$R_o^2 + \left( 37.5 - \frac{(130)^2}{225} \right) R_o + 18.75^2 = 0$$

Solving,


$$R_o = 20.25 \Omega \text{ \& } 17.36 \Omega$$

- 4) (10 points) Problem 4.95 of the textbook (p163), while the top current source is changed from 5 mA to 10 mA.

Ans:

4a)

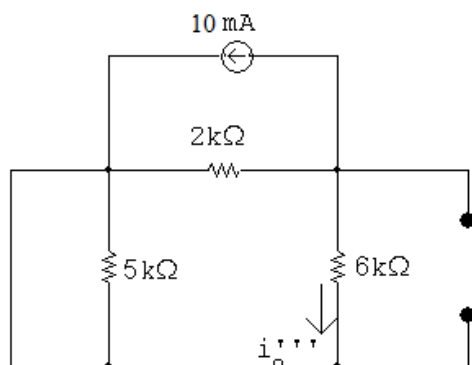By hypothesis  $i_o' + i_o'' = 3.5 \text{ mA}$



$$i_o''' = -10 \frac{2}{8} = -2.5; \quad i_o = 3.5 - 2.5 = 1 \text{ mA}$$

4b)

With all three sources in the circuit write a single node voltage equation.

$$\frac{v_b}{6} + \frac{v_b - 8}{2} + 10 - 10 = 0$$


$$\therefore v_b = 6 \text{ V}$$

$$i_o = \frac{v_b}{6} = 1 \text{ mA}$$

- 5) (10 points) Problem 4.102 of the textbook (p165), while the resistor is changed from 20  $\Omega$  to 30  $\Omega$ .

**Ans:**

5a)

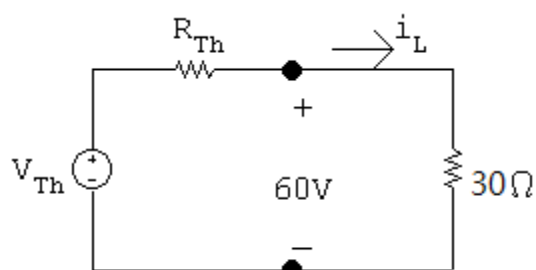

$$v_{oc} = V_{Th} = 75 \text{ V}; \quad i_L = 60/30 = 2 \text{ A};$$

$$i_L = 75 - 60/R_{Th} = 15/R_{Th}; \quad R_{Th} = 7.5 \Omega$$

5b)

$$i_L = \frac{v_o}{R_L} = \frac{V_{Th} - v_o}{R_{Th}}$$

$$R_{Th} = \frac{V_{Th} - v_o}{v_o/R_L} = \left( \frac{V_{Th}}{v_o} - 1 \right) R_L$$

- 6) (10 points) Problem 6.15 of the textbook (p228), while the initial voltage on the capacitor is changed from -60.6 V to -100 V.

**Ans:**

6a)

$$v = 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 100$$

$$= 500 \times 10^3 \left. \frac{e^{-1000t}}{-1000} \right|_0^{250 \times 10^{-6}} - 100$$

$$= 500(1 - e^{-0.25}) - 100 = 10.6 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2)(10^{-6})(10.6)^2 = 11.236 \text{ } \mu\text{J}$$


6b)

$$v = 500 - 100 = 400 \text{ V}$$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (400)^2 = 16 \text{ mJ} = 16000 \text{ } \mu\text{J}$$

- 7) (20 points) Problem 6.31 of the textbook (p230), while the resulting current  $i(t)$  is changed from  $800e^{-25t}$  to  $960e^{-30t}$ .

**Ans:**

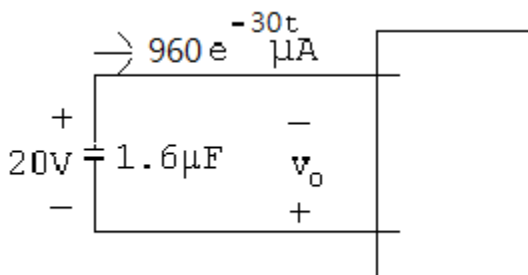

7a)

$$v_o = \frac{10^6}{1.6} \int_0^t 960 \times 10^{-6} e^{-30x} dx - 20$$

$$= 600 \frac{e^{-30x}}{-30} \Big|_0^t = -20e^{-30t} \text{ V}, \quad t \geq 0$$

7b)

$$v_1 = \frac{10^6}{2} (960 \times 10^{-6}) \frac{e^{-30x}}{-30} \Big|_0^t + 5 = -16e^{-30t} + 21 \text{ V}, \quad t \geq 0$$

7c)

$$v_2 = \frac{10^6}{8} (960 \times 10^{-6}) \frac{e^{-30x}}{-30} \Big|_0^t - 25 = -4e^{-30t} - 21 \text{ V}, \quad t \geq 0$$

7d)

$$p = -vi = -(-20e^{-30t})(960 \times 10^{-6})e^{-30t} = 19.2 \times 10^{-3} e^{-60t}$$

$$w = \int_0^\infty 19.2 \times 10^{-3} e^{-60t} dt = 19.2 \times 10^{-3} \frac{e^{-60x}}{-60} \Big|_0^\infty = 320 \mu\text{J}$$

7e)

$$w = \frac{1}{2} (2 \times 10^{-6})(5)^2 + \frac{1}{2} (8 \times 10^{-6})(25)^2 = 2525 \mu\text{J}$$

7f)

$$w_{\text{trapped}} = w_{\text{initial}} - w_{\text{delivered}} = 2525 - 320 = 2205 \mu\text{J}$$

7g)

$$w_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(21)^2 + \frac{1}{2}(8 \times 10^{-6})(-21)^2 = 2205 \mu\text{J}$$

8) (10 points) Problem 6.34 of the textbook (p230).**Ans:**

$$\begin{aligned} v_2(t) &= L \frac{di_o}{dt} \\ &= 20 \times 10^{-3} \times 50 \times (-8000e^{-8000t}) \times (\cos 6000t + \sin 6000t) \times 10^{-3} \\ &\quad + 20 \times 10^{-3} \times 50 \times e^{-8000t} \times (6000 \times (-\sin 6000t) + 12000 \cos 6000t) \times 10^{-3} \\ &= e^{-8000t}(4 \cos 6000t - 22 \sin 6000t) \end{aligned}$$

$$v_2(0^+) = 4 \text{ V}$$

$$V_{320\Omega}(0^+) = 320 \times i_o(0^+) = 320 \times 50 \times 10^{-3} = 16 \text{ V}$$

$$\therefore v_1(0^+) = 16 + 4 = 20 \text{ V}$$