

Homework4 solutions

(Due date: 2014/4/16)

This assignment covers Ch9 and Ch10 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 9.14 of the textbook (p371), while the maximum amplitude of the steady-state current in the inductor is changed from 25 A to 20 A.

Ans:

1a)

$$400 \text{ Hz}$$

1b)

$$\theta_v = 0^\circ$$

$$\mathbf{I} = \frac{100 \angle 0^\circ}{j\omega L} = \frac{100}{\omega L} \angle -90^\circ, \quad \theta_i = -90^\circ$$

1c)

$$\frac{100}{\omega L} = 20, \quad \omega L = 5 \, \Omega$$

1d)

$$L = \frac{5}{800\pi} \approx 2 \text{ mH}$$

1e)

$$Z_L = j\omega L = j5 \, \Omega$$

- 2) (10 points) Problem 9.35 of the textbook (p374), while the impedance of the left inductor is changed from $j5\ \Omega$ to $j2\ \Omega$.

Ans:

V_2 is the voltage across the $-j10\Omega$ impedance.

$$\frac{V_1 - V_g}{20} + \frac{V_1}{j2} + \frac{V_1 - V_2}{Z} = 0$$

$$\frac{(40 + j30) - (100 - j50)}{20} + \frac{40 + j30}{j2} + \frac{(40 + j30) - V_2}{Z} = 0$$

$$\therefore V_2 = 40 + j30 + (12 - j16)Z$$

$$\frac{V_2 - V_1}{Z} + \frac{V_2}{-j10} - (20 + j30) + \frac{V_2 - (100 - j50)}{3 + j1} = 0$$

$$\frac{V_2 - (40 + j30)}{Z} + \frac{V_2}{-j10} - (20 + j30) + \frac{V_2 - (100 - j50)}{3 + j1} = 0$$

Substituting the expression for V_2 found at the start and simplifying yields:

$$Z = 0.5 + j4\ \Omega$$

- 3) (20 points) Problem 9.45 of the textbook (p375), while the impedance of capacitor is changed from $-j48\ \Omega$ to $-j36\ \Omega$ and the resistor R_0 is changed from $36\ \Omega$ to $24\ \Omega$.

Ans:

Step 1 to Step 2:


$$\frac{240\angle 0^\circ}{j24} = -j10 = 10\angle -90^\circ\text{ A}$$

Step 2 to Step 3:

$$j24 \parallel 24 = 12 + j12\ \Omega$$

Step 3 to Step 4:
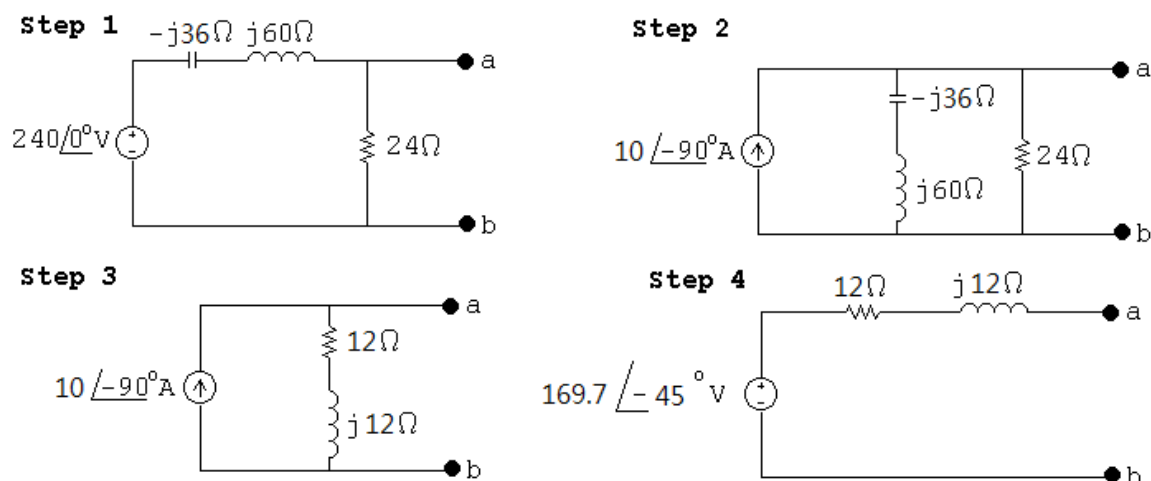
$$(10\angle -90^\circ)(12 + j12) = 120 - j120 = 169.7\angle -45^\circ\text{ V}$$



- 4) (10 points) Problem 9.59 of the textbook (p377), while the current source is changed from $10+j10$ to $10+j20$.

Ans:

$$\frac{V_o}{-j8} + \frac{V_o - 2.4I_\Delta}{j4} + \frac{V_o}{5} - (10 + j20) = 0$$

The constant equation is:

$$I_\Delta = \frac{V_o}{-j8}, \text{ Solving that, } V_o = -40 + j120 = 126.5\angle 108.43^\circ \text{V}$$

- 5) (10 points) Problem 9.78 of the textbook (p379), while the left resistor is changed from 5Ω to 10Ω .


Ans:

Remove the voltage source to find the equivalent impedance:

$$Z_{Th} = 45 + j125 + \left(\frac{20}{|10 + j5|} \right)^2 (10 - j5) = 77 + j109\Omega$$

Using voltage division:

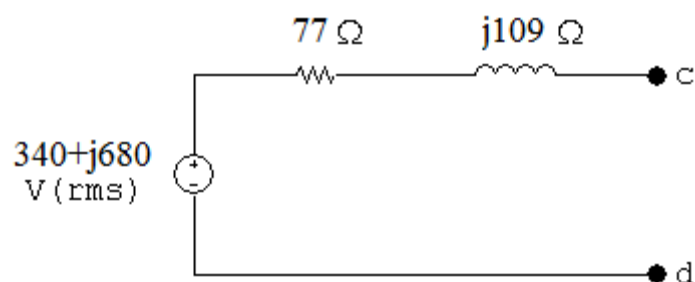
$$V_{Th} = V_{cd} = j20I_1 = j20 \left(\frac{425}{10 + j5} \right) = 340 + j680 \text{ V}$$



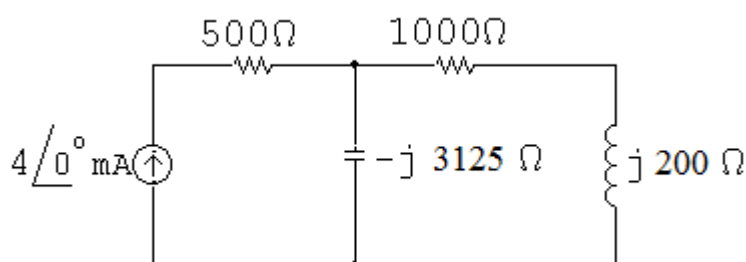- 6) (10 points) Problem 10.5 of the textbook (p409), while the current source is changed from $4 \cos 5000t$ mA to $4 \cos 2000t$ mA.

Ans:

$$I_g = 4 \angle 0^\circ \text{ mA}; \quad \frac{1}{j\omega C} = -j3125 \Omega; \quad j\omega L = j200 \Omega$$



$$Z_{eq} = 500 + [-j3125 \parallel (1000 + j200)] = 1522 - j135.72 \Omega$$

$$P_g = -\frac{1}{2} |I|^2 \text{Re}\{Z_{eq}\} = -\frac{1}{2} (0.004)^2 (1522) = -0.0122 = -12.2 \text{ mW}$$

The source delivers 12.2 mW of power to the circuit.

- 7) (10 points) Problem 10.27 of the textbook (p412), while the voltage drop is changed from 250 V to 200 V (rms).

Ans:

7a)

$$S_1 = 16 + j28 \text{ kVA}; \quad S_2 = 6 - j8 \text{ kVA}; \quad S_3 = 8 + j0 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 30 + j20 \text{ kVA}$$

$$200\mathbf{I}^* = (30 + j20) \times 10^3; \quad \therefore \mathbf{I} = 150 - j100 \text{ A}$$

$$Z = \frac{200}{150 - j100} = 0.9234 + j0.6154 \Omega = 1.1094 \angle 33.69^\circ$$

7b)

$$\text{pf} = \cos(33.69^\circ) = 0.8321$$

8) (20 points) Problem 10.56 of the textbook (p416).

Ans:

8a)

$$V_{Th} = \frac{760 \angle 0^\circ}{28 + j96} (j50) = 380 \angle 16.26^\circ \text{ V}$$


$$Z_{Th} = 31 + j100 + \left(\frac{50}{100}\right)^2 (28 - j96) = 38 + j76 \Omega$$

$$\therefore Z_L = 38 - j76 \Omega$$

$$\mathbf{I}_L = \frac{380 \angle 16.26^\circ}{76} = 4.8 + j1.4 = 5 \angle 16.26^\circ \text{ A(rms)}$$

$$P_L = |\mathbf{I}_L|^2 (38) = 950 \text{ W}$$

8b)

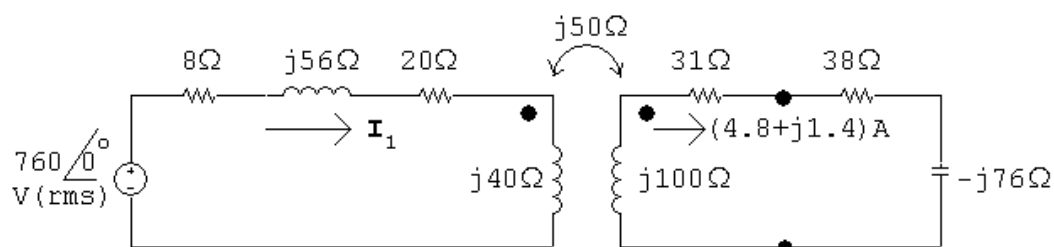

$$760 \angle 0^\circ = \mathbf{I}_1 (28 + j96) - j50 (4.8 + j1.4)$$

$$\therefore \mathbf{I}_1 = \frac{690 + j240}{100 \angle 73.74^\circ} = 7.31 \angle -54.56^\circ = 4.24 - j5.95 \text{ A}$$

$$S_g(\text{delivered}) = 760(4.24 + j5.95) = 3219.36 + j4523.52 \text{ VA}$$

$$P_{\text{loss}} = |\mathbf{I}_1|^2(8) = 426.96 \text{ W}$$

$$P_{\text{in}}(\text{transformer}) = 3219.36 - 426.96 = 2792.4 \text{ W}$$

$$\% \text{ delivered to } Z_L = \frac{950}{2792.4} \times 100\% = 34.02\%$$