

Homework 5


(Due date: 2014/4/30)

This assignment covers Ch7 and Ch8 of the textbook. The full credit is 100 points. For each question, detailed derivation processes and accurate numbers are required to get full credit.

- 1) (10 points) Problem 7.17 of the textbook (p271), while the dependent source current is changed from $4v_o$ to $2.5v_o$.


Ans:

$t < 0$

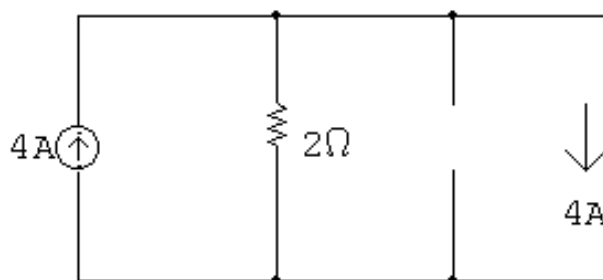


$$i_L(0^-) = i_L(0^+) = 4 \text{ A}$$

$t > 0$

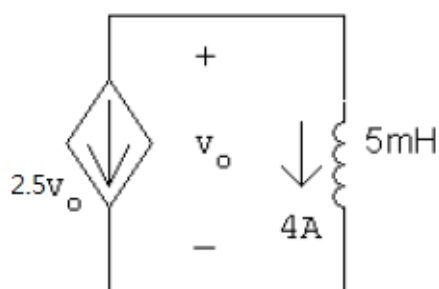


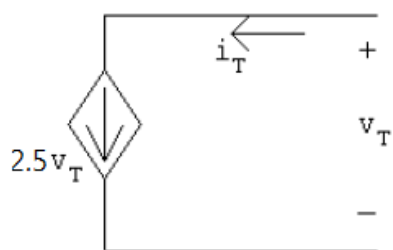Find Thévenin resistance seen by inductor :



$$i_T = 2.5v_T; \quad \frac{v_T}{i_T} = R_{Th} = \frac{1}{2.5} = 0.4 \, \Omega$$
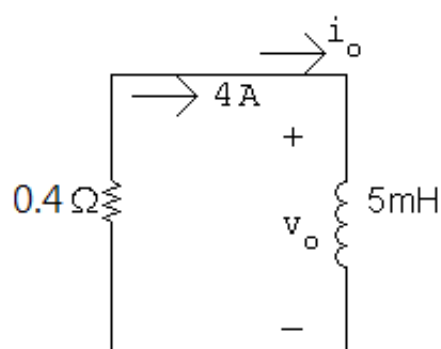
$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{0.4} = 12.5 \, \text{ms}, \quad \frac{1}{\tau} = 80$$



$$i_o = 4e^{-80t} \, \text{A}, \quad t \geq 0$$


$$v_o = L \frac{di_o}{dt} = (5 \times 10^{-3})(-320e^{-80t}) = -1.6e^{-80t} \, \text{V}, \quad t \geq 0^+$$

- 2) (20 points) Problem 7.52 of the textbook (p276), while the middle resistor is changed from 12.5 k Ω to 2.5 k Ω .

Ans:

2a)
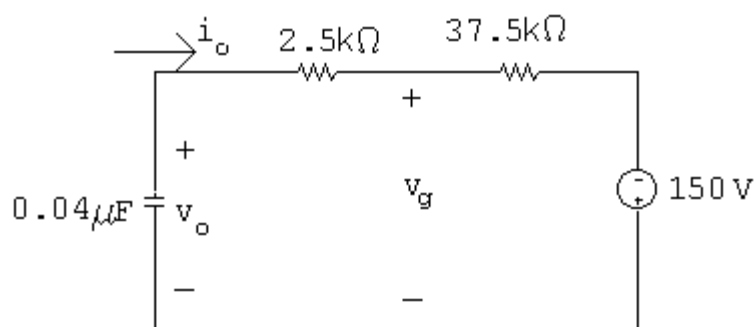
$$v_o(0^-) = v_o(0^+) = 120 \, \text{V}$$



$$v_o(\infty) = -150 \text{ V}; \quad \tau = 1.6 \text{ ms}; \quad \frac{1}{\tau} = 625$$

$$v_o = -150 + (120 - (-150))e^{-625t}$$

$$v_o = -150 + 270e^{-625t} \text{ V}, t \geq 0$$

2b)

$$i_o = -0.04 \times 10^{-6}(-625)[270e^{-625t}] = 6.75e^{-625t} \text{ mA}, t \geq 0^+$$

2c)

$$v_g = v_o - 2.5 \times 10^3 i_o = -150 + 253.125e^{-625t} \text{ V}$$


2d)

$$v_g(0^+) = -150 + 253.125 = 103.125 \text{ V}$$

- 3) (10 points) Problem 7.84 of the textbook (p280), while the dependent source voltage is changed from $12 \times 10^4 i_\Delta$ to $13 \times 10^4 i_\Delta$.

Ans:

$t > 0$:

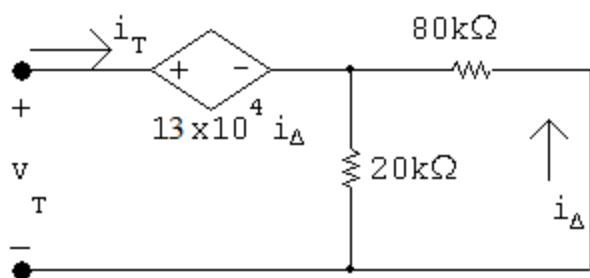

$$v_T = 13 \times 10^4 i_A + 16 \times 10^3 i_T$$

$$i_A = -\frac{20}{100} i_T = -0.2 i_T$$

$$\therefore v_T = -26 \times 10^3 i_T + 16 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = -10 \text{ k}\Omega$$

$$\tau = RC = (-10 \times 10^3)(2.5 \times 10^{-6}) = -0.025, \quad \frac{1}{\tau} = -40$$

$$v_c = 20e^{40t} \text{ V}; \quad 20e^{40t} = 20000$$

$$40t = \ln(1000), \quad \therefore t = 172.7 \text{ ms}$$

- 4) (20 points) Problem 8.16 of the textbook (p321), while the voltage source is changed from -15 V to -10 V.

Ans:

4a)

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(2.5)(100)} = 4 \times 10^6$$

$$\omega_o = 2000 \text{ rad/s}$$

$$\frac{1}{2RC} = 2000; \quad R = \frac{1}{4000C} = 2500 \Omega$$

4b)

$$v(t) = D_1 t e^{-2000t} + D_2 e^{-2000t}$$

$$v(0) = -10 \text{ V} = D_2$$

$$i_C(0) = 6 + \frac{10}{2.5} = 10 \text{ mA}$$

$$\frac{dv}{dt}(0) = \frac{i_C(0)}{C} = \frac{10 \times 10^{-3}}{100 \times 10^{-9}} = 1 \times 10^5$$

$$D_1 - 2000(-10) = 1 \times 10^5 \quad \text{so } D_1 = 80000 \frac{\text{V}}{\text{s}}$$

$$\therefore v(t) = (80000t - 10)e^{-2000t} \text{ V, } t \geq 0$$

4c)

$$i_C(t) = 0 \quad \text{when } \frac{dv}{dt}(t) = 0$$

$$\frac{dv}{dt} = (100,000 - 160 \times 10^6 t)e^{-2000t}$$

$$\frac{dv}{dt} = 0 \quad \text{when } 160 \times 10^6 t_1 = 100000; \quad \therefore t_1 = 625 \mu\text{s}$$

$$v(625 \mu\text{s}) = (50 - 10)e^{-1.25} = 11.4602 \text{ V}$$

4d)

$$w(0) = \frac{1}{2}(100 \times 10^{-9})(10)^2 + \frac{1}{2}(2.5)(0.006)^2 = 50 \mu\text{J}$$

$$w(625 \mu\text{s}) = \frac{1}{2}(100 \times 10^{-9})(11.46)^2 + \frac{1}{2}(2.5)\left(\frac{11.46}{2500}\right)^2 = 32.83 \mu\text{J}$$

$$\% \text{ remaining} = \frac{32.83}{50}(100\%) = 65.66\%$$

5) (10 points) Problem 8.29 of the textbook (p322), while the resistor is changed from 150 Ω to 100 Ω .

Ans:

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8; \quad \omega_o = 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(100)(0.2 \times 10^{-6})} = 25000 \text{ rad/s} \quad \therefore \text{overdamped}$$

$$s_{1,2} = -25000 \pm \sqrt{(-25000)^2 - 10^8} = -25000 \pm 22912.9 \text{ rad/s}$$

$$s_1 = -2087.1 \text{ rad/s}; \quad s_2 = -47912.9 \text{ rad/s};$$

$$I_f = 60 \text{ mA}$$

$$i_L = 60 \times 10^{-3} + A'_1 e^{-2087.1t} + A'_2 e^{-47912.9t}$$

$$\therefore -45 \times 10^{-3} = 60 \times 10^{-3} + A'_1 + A'_2; \quad A'_1 + A'_2 = -105 \times 10^{-3}$$

$$\frac{di_L}{dt} = -2087.1A'_1 - 47912.9A'_2 = \frac{15}{0.05} = 300$$

$$\text{Solving, } A'_1 = -0.10324 \quad A'_2 = -0.00176$$

$$i_L = 60 \times 10^{-3} - 0.10324e^{-2087.1t} - 0.00176A'_2e^{-47912.9t} \text{ (A)}$$

- 6) (10 points) Problem 8.44 of the textbook (p323), while the initial capacitor voltage is changed from 15 V to 10 V.

Ans:

6a)

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(125)(0.32)} = 25 \times 10^6$$

$$\alpha = \frac{R}{2L} = \omega_o = 5000 \text{ rad/s}$$

$$\therefore R = (5000)(2)L = 1250 \Omega$$

6b)

$$i(0) = i_L(0) = 4 \text{ mA}$$

$$v_L(0) = 10 - (0.004)(1250) = 5 \text{ V}$$

$$\frac{di}{dt}(0) = \frac{5}{0.125} = 40 \text{ A/s}$$

6c)

$$v_C = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v_C(0) = D_2 = 10 \text{ V}$$

$$\frac{dv_C}{dt}(0) = D_1 - 5000D_2 = \frac{i_C(0)}{C} = \frac{-i_L(0)}{C} = -12500$$

$$\therefore D_1 = 37500 \text{ V/s}$$

$$v_C = 37500te^{-5000t} + 10e^{-5000t} \text{ V, } t \geq 0$$

7) (10 points) Problem 8.50 of the textbook (p324), while the voltage source is changed from 60 V to 30 V.

Ans:

$$\alpha = \frac{R}{2L} = 2000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(6.25 \times 10^{-6})} = 256 \times 10^4$$

$$s_{1,2} = -2000 \pm \sqrt{4 \times 10^6 - 256 \times 10^4} = -2000 \pm 1200 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-800t} + A'_2 e^{-3200t}$$

$$v_o(0) = 0 = V_f + A'_1 + A'_2$$

$$v_o(\infty) = 30 \text{ V; } \therefore A'_1 + A'_2 = -30$$

$$\frac{dv_o(0)}{dt} = 0 = -800A'_1 - 3200A'_2$$

$$\therefore A'_1 = -40 \text{ V; } A'_2 = 10 \text{ V}$$

$$v_o = 30 - 40e^{-800t} + 10e^{-3200t} \text{ V, } t \geq 0$$

8) (10 points) Problem 8.57 (a) of the textbook (p325).

Ans:

$$v_c = V_f + [B'_1 \cos w_d t + B'_2 \sin w_d t]e^{-\alpha t}$$

$$\frac{dv_c}{dt} = [(w_d B'_2 - \alpha B'_1) \cos w_d t - (\alpha B'_2 + w_d B'_1) \sin w_d t]e^{-\alpha t}$$

Since the initial stored energy is zero,

$$v_c(0^+) = 0 \quad \text{and} \quad \frac{dv_c(0^+)}{dt} = 0$$

It follows that $B'_1 = -V_f$ and $B'_2 = \alpha B'_1 / w_d$

When these values are substituted into the expression for $[dv_c/dt]$, we get

$$\frac{dv_c}{dt} = \left(\frac{\alpha^2}{w_d} + w_d \right) V_f e^{-\alpha t} \sin w_d t$$

$$\text{But } V_f = V \quad \text{and} \quad \frac{\alpha^2}{w_d} + w_d = \frac{\alpha^2 + w_d^2}{w_d} = \frac{w_o^2}{w_d}$$

$$\text{Therefore} \quad \frac{dv_c}{dt} = \left(\frac{w_o^2}{w_d} \right) V e^{-\alpha t} \sin w_d t$$