# Homework 7

### (Due date: 2014/6/11)

This assignment covers <u>Ch14 and Ch18</u> of the textbook. The full credit is <u>100 points</u>. For each question, <u>detailed derivation processes</u> and <u>accurate numbers</u> are required to get full credit.

 (10 points) <u>Problem 14.8</u> of the textbook (p574), while the inductor in (e) is changed from 10 mH to 5 mH.

Ans:

1a)

- $Z_L = j\omega L = j0L = 0$  so it is a short circuit.
- At  $\omega = 0$ ,  $V_o = V_i$

#### 1b)

 $Z_L = j\omega L = j\infty L = \infty$  so it is a open circuit. At  $\omega = \infty$ ,  $V_o = 0$ 

#### 1c)

This is a low pass filter, with a gain of 1 at low frequencies and a gain of 0 at high frequencies.

1d)

$$H(s) = \frac{V_o}{V_i} = \frac{R}{R+sL} = \frac{\frac{R}{L}}{\frac{R}{s+\frac{R}{L}}}$$

**Electric Circuits** 

1e)  
$$\omega_c = \frac{R}{L} = \frac{330}{0.005} = \frac{66 \text{ krad/s}}{66 \text{ krad/s}}$$

2) (10 points) <u>Problem 14.15</u> of the textbook (p575), while the resistor is changed from  $150 \Omega$  to  $200 \Omega$ .

Ans:

2a)

For  $\omega = 0$ , the inductor behaves as a short circuit, so  $V_o = 0$ .

For  $\omega = \infty$ , the inductor behaves as an open circuit, so  $V_o = V_i$ .

2b)

$$H(s) = \frac{sL}{R+sL} = \frac{s}{s+R/L} = \frac{s}{s+20000}$$

$$\omega_c = \frac{R}{L} = \frac{20000 \text{ rad/s}}{10000 \text{ rad/s}}$$

2d)

$$|H(jR/L)| = \left|\frac{jR/L}{\frac{jR}{L} + R/L}\right| = \left|\frac{j}{j+1}\right| = \frac{1}{\sqrt{2}}$$

3) (10 points) <u>Problem 14.30</u> of the textbook (p576), while the center frequency  $\omega_0$  is changed from 50 krad/s to 100 krad/s and the capacitor is changed from 20 nF to 10 nF.

Ans:



$$L = \frac{1}{\omega_o^2 C} = \frac{1}{(100 \times 10^3)^2 (10 \times 10^{-9})} = 10 \text{ mH}$$
$$R = \frac{\omega_o L}{Q} = \frac{(100 \times 10^3)(10 \times 10^{-3})}{6.25} = 160 \Omega$$

$$R_e = 160||480 = 120 \Omega$$

$$R_e + R_i = 120 + 80 = 200 \Omega$$

$$Q_{\text{system}} = \frac{\omega_o L}{R_e + R_i} = \frac{(100 \times 10^3)(10 \times 10^{-3})}{200} = 5$$

$$\beta_{\text{system}} = \frac{\omega_o}{Q_{\text{system}}} = \frac{100 \times 10^3}{5} 20 \text{ krad/s}$$
$$\beta_{\text{system}}(\text{Hz}) = \frac{20000}{2\pi} = \frac{3183.1 \text{ Hz}}{3183.1 \text{ Hz}}$$

## 4) (20 points) <u>Problem 14.31</u> of the textbook (p577).

Ans:

4a)

**Electric Circuits** 

$$\frac{V_o}{V_i} = \frac{Z}{Z+R} \text{ where } Z = \frac{1}{Y}$$
And  $Y = sC + \frac{1}{sL} + \frac{1}{R_L} = \frac{LCR_L s^2 + sL + R_L}{R_L Ls}$ 

$$H(s) = \frac{R_L Ls}{RLCR_L s^2 + (R+R_L)Ls + RR_L} = \frac{\left(\frac{1}{RC}\right)s}{s^2 + \left[\left(\frac{R+R_L}{R_L}\right)\left(\frac{1}{RC}\right)\right]s + \frac{1}{LC}}$$

$$= \frac{\left(\frac{R_L}{R+R_L}\right)\left(\frac{R+R_L}{R_L}\right)\left(\frac{1}{RC}\right)s}{s^2 + \left[\left(\frac{R+R_L}{R_L}\right)\left(\frac{1}{RC}\right)\right]s + \frac{1}{LC}} = \frac{K\beta s}{s^2 + \beta s + \omega_o^{2'}}$$

$$K = \frac{R_L}{R+R_L}, \qquad \beta = \frac{1}{(R|R_L)C}$$

 $\beta = \left(\frac{R+R_L}{R_L}\right) \left(\frac{1}{RC}\right)$ 

$$\beta_U = \frac{1}{RC}$$
  
$$\therefore \beta_L = \left(\frac{R + R_L}{R_L}\right) \beta_U = \left(1 + \frac{R}{R_L}\right) \beta_U$$

4d)

$$Q = \frac{\omega_o}{\beta} = \frac{\omega_o RC}{\left(\frac{R+R_L}{R_L}\right)}$$

4e)

$$Q_U = \omega_o RC$$
  
$$\therefore Q_L = \left(\frac{R + R_L}{R_L}\right) Q_U = \frac{1}{\left(1 + \frac{R}{R_L}\right)} Q_U$$

4f)

$$H(j\omega) = \frac{Kj\omega\beta}{\omega_o^2 - \omega^2 + j\omega\beta}$$
$$H(j\omega_o) = K$$

Let  $\omega_c$  represent a corner frequency. Then

$$|H(j\omega_c)| = \frac{K}{\sqrt{2}} = \frac{K\omega_c\beta}{\sqrt{(\omega_o^2 - \omega_c^2)^2 + \omega_c^2\beta^2}}$$
$$\therefore \frac{1}{\sqrt{2}} = \frac{\omega_c\beta}{\sqrt{(\omega_o^2 - \omega_c^2)^2 + \omega_c^2\beta^2}}$$

Squaring both sides leads to

 $(\omega_o^2 - \omega_c^2)^2 = \omega_c^2 \beta^2 \text{ or } \omega_o^2 - \omega_c^2 = \pm \omega_c \beta$  $\therefore \omega_c^2 \pm \omega_c \beta - \omega_o^2 = 0$ 

$$\omega_c = \mp \frac{\beta}{2} \pm \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$

The two positive roots are

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\frac{\beta^2}{4} + \omega_o^2}$$
 and  $\omega_{c2} = \frac{\beta}{2} - \sqrt{\frac{\beta^2}{4} + \omega_o^2}$ 

Where

$$\beta = \left(1 + \frac{R}{R_L}\right) \frac{1}{RC}$$
 and  $\omega_o^2 = \frac{1}{LC}$ 

5) (10 points) Problem 18.18 of the textbook (p722), while the resistor is changed from 4
 Ω to 10 Ω and the goal is changed from expressions for the *a* parameters to those of the *g* parameters.

Ans:

For  $I_2=0$ :



$$V_2 = \frac{V_1}{10 + \frac{1}{s}} \times 10 = \frac{10sV_1}{10s + 1}, \qquad g_{21} = \frac{V_2}{V_1}\Big|_{I_2 = 0} = \frac{10s}{10s + 1}$$

$$I_1 = \frac{V_1}{10 + \frac{1}{s}} = \frac{sV_1}{10s + 1}, \qquad g_{11} = \frac{I_1}{V_1}\Big|_{I_2 = 0} = \frac{s}{\frac{10s + 1}{10s + 1}}$$

For  $V_1=0$ :



$$I_{1} = \frac{-I_{2} \times 10}{10 + \frac{1}{s}}, \qquad g_{12} = \frac{I_{1}}{I_{2}}\Big|_{V_{1}=0} = \frac{-10s}{10s + 1}$$
$$V_{2} = \frac{(10s^{2} + s + 10)I_{2}}{1 + 10s}, \qquad g_{22} = \frac{V_{2}}{I_{2}}\Big|_{V_{1}=0} = \frac{(10s^{2} + s + 10)}{1 + 10s}$$

6) (10 points) <u>Problem 18.19</u> of the textbook (p722).

Ans:

$$z_{11} = \frac{V_1}{I_1}\Big|_{I_{2=0}} = \frac{(1+1/s)(1)}{2+1/s} + s = \frac{s+1}{2s+1} + s = \frac{2s^2+2s+1}{2s+1}$$
  

$$z_{22} = z_{11} \quad \text{(the circuit is reciprocal and symmetrical)}$$
  

$$z_{21} = \frac{V_2}{I_1}\Big|_{I_{2=0}}$$

$$V_{2} = I_{1} \frac{1}{2 + \frac{1}{s}} (1) + sI_{1}; \quad \frac{V_{2}}{I_{1}} = \frac{s}{2s + 1} + s = \frac{2s^{2} + 2s}{2s + 1}$$
$$z_{21} = \frac{2s^{2} + 2s}{2s + 1} = \frac{2s(s + 1)}{2s + 1}$$



(the circuit is reciprocal and symmetrical)

7) (15 points) <u>Problem 18.29</u> of the textbook (p722), while the right resistor is changed from 100  $\Omega$  to 60  $\Omega$ .

$$\frac{V_2}{V_g} = \frac{\Delta b Z_L}{b_{12} + b_{11} Z_g + b_{22} Z_L + b_{21} Z_g Z_L}$$

$$\Delta b = b_{11} b_{22} - b_{12} b_{21} = (25)(-40) - (1000)(-1.25) = 250$$

$$\therefore \frac{V_2}{V_g} = \frac{250(60)}{1000 + 25(20) - 40(60) - 1.25(1200)} = -6.25$$

$$V_2 = -6.25(120 \angle 0^\circ) = 750 \angle 180^\circ \text{ V(rms)}$$

$$I_2 = \frac{-V_2}{60} = \frac{-750 \angle 180^\circ}{60} = 12.5 \text{ A(rms)}$$

$$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21} Z_L} = \frac{-250}{25 - 1.25(60)} = 5$$

$$\therefore I_1 = \frac{I_2}{5} = \frac{12.5}{5} = 2.5 \text{ A(rms)}$$

$$\therefore P_g = (120)(2.5) = 300 \text{ W}; \quad P_o = 12.5^2(60) = 9375 \text{ W}$$

$$\therefore \frac{P_0}{P_g} = \frac{9375}{300} = \frac{31.25}{25}$$

8) (15 points) <u>Problem 18.34</u> of the textbook (p723), while the value of  $V_1$  in Measurement 2 is changed from 20 mV to 25 mV.

Ans:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

From the first measurement:

$$h_{11} = \frac{V_1}{I_1} = \frac{4}{5 \times 10^{-3}} = 800 \ \Omega$$
$$h_{21} = \frac{I_2}{I_1} = \frac{-200}{5} = -40$$

From the second measurement:

$$h_{22}V_2 = 40I_1, \qquad h_{22} = 40 \times \frac{20 \times 10^{-6}}{40} = 20 \ \mu\text{S}$$
  
 $25 \times 10^{-3} = 800(20 \times 10^{-6}) + 40h_{12}, \qquad h_{12} = 2.25 \times 10^{-4}$ 

Summary:

$$h_{11} = 800 \ \Omega; \ h_{12} = 2.25 \times 10^{-4}; \ h_{21} = -40; \ h_{22} = 20 \ \mu\text{S}$$

From the circuit,

$$Z_g = 250 \ \Omega; \ V_g = 5.25 \ \text{mV}$$

$$Z_{\text{Th}} = \frac{Z_g + h_{11}}{h_{22}Z_g + \Delta h}; \ \Delta h = 800(20 \times 10^{-6}) + 40(2.25 \times 10^{-4}) = 0.025$$

$$Z_{\text{Th}} = \frac{250 + 800}{20 \times 10^{-6}(250) + 0.025} = 35 \ \text{k}\Omega$$

$$V_{\text{Th}} = \frac{-h_{21}V_g}{h_{22}Z_g + \Delta h} = \frac{40(5.25 \times 10^{-3})}{20 \times 10^{-6}(250) + 0.025} = 7 \ \text{V}$$

$$i = \frac{7}{70000} = 1 \times 10^{-4} \ \text{A}$$

 $P_{\text{max}} = (1 \times 10^{-4})^2 \times 35000 = 0.00035 = 350 \,\mu\text{W}$