 


國立清華大學電機系

EE-6250
超大型積體電路測試
VLSI Testing



Chapter 3
Fault Simulation

Outline

- ➔ • Fault Simulation for Comb. Ckt
 - Basic of Logic Simulation
 - Parallel Fault Simulation
 - Deductive Fault Simulation
 - Concurrent Fault Simulation
- Approximation Approach
- Techniques for Sequential Circuits


Note: Comb. Ckt: Combinational Circuits

Why Fault Simulation ?

- To evaluate the quality of a test set
 - I.e., to compute its fault coverage
- Part of an ATPG program
 - A vector usually detects multiple faults
 - Fault simulation is used to compute the faults **accidentally** detected by a particular vector
- To construct fault-dictionary
 - For post-testing diagnosis
- To Evaluate the fault coverage of a functional patterns

Ch3-3

Conceptual Fault Simulation

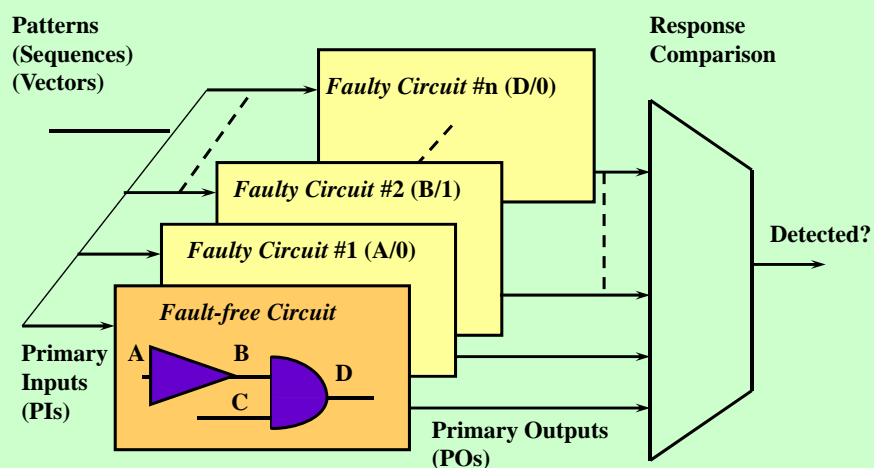

Logic simulation on both good (fault-free) and faulty circuits


Ch3-4

Some Basics for Logic Simulation

- For fault simulation purpose,
 - mostly the **gate delay is assumed to be zero** unless the delay faults are considered. Our main concern is the **functional faults**
- The logic values
 - can be either two (0, 1) or **three values (0, 1, X)**
- Two simulation mechanisms:
 - Oblivious **compiled-code**:
 - circuit is translated into a program and **all** gates are executed for each pattern. (may have **redundant computation**)
 - Interpretive **event-driven**:
 - Simulating a vector is viewed as a sequence of **value-change events** propagating from the PI's to the PO's
 - Only those logic gates affected by the events are **re-evaluated**

Ch3-5


Compiled-Code Simulation

 


- Compiled code
 - LOAD *A* /* load accumulator with value of *A* */
 - AND *B* /* calculate *A and B* */
 - AND *C* /* calculate *E = AB and C* */
 - OR *D* /* calculate *Z = E or D* */
 - STORE *Z* /* store result of *Z* */

Ch3-6

Event-Driven Simulation

 

Complexity of Fault Simulation

 


- Complexity $\sim F \cdot P \cdot G \sim O(G^3)$, where G is the no. of gates
- The complexity is higher than logic simulation by a factor of F , while usually is much lower than ATPG
- The complexity can be greatly reduced using
 - **Fault dropping** and other advanced techniques

Ch3-8

Characteristics of Fault Simulation

- Fault activity with respect to fault-free circuit
 - is often **sparse** both in **time** and in **space**.
- For example
 - F1 is not activated by the given pattern, while F2 affects only the lower part of this circuit.

 

Ch3-9

Fault Simulation Techniques

- Serial Fault Simulation
 - trivial single-fault single-pattern
- Parallel Fault Simulation
- Deductive Fault Simulation
- Concurrent Fault Simulation

Ch3-10

- Simulate multiple circuits at a time:

- The inherent parallel operation of **computer words** to simulate faulty circuits in parallel with fault-free circuit
- **The number of faulty circuits**, or faults, can be processed simultaneously is limited by the word length, e.g., **32** circuits for a 32-bit computer


- Extra Cost:

- An **event**, a value-change of a single fault or fault-free circuit leads to the computation of the entire word
- The **fault-free logic simulation** is repeated for each pass

Ch3-11

- Consider three faults:
(J s-a-0, B s-a-1, and F s-a-0)
- Bit-space: (FF denotes fault-free)

fault-free

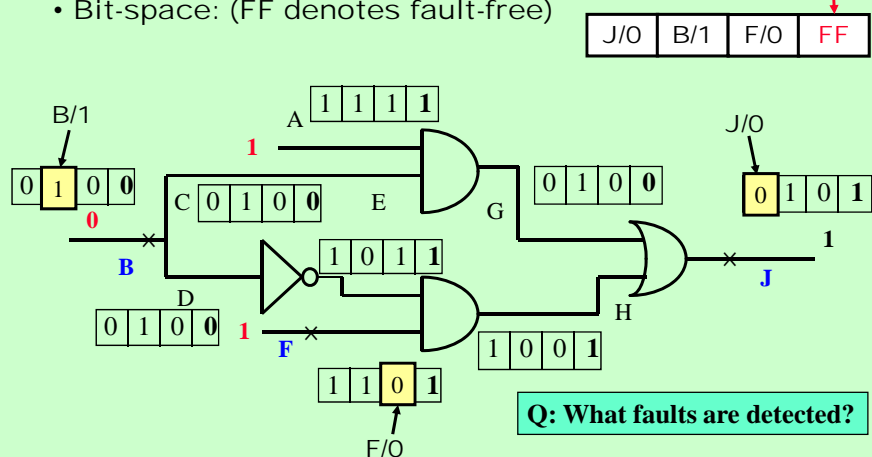

Q: What faults are detected?


Ch3-12

Example: Parallel-Pattern Simulation

- Consider one fault F/0 and four patterns: P3,P2,P1,P0

Bit-Space:


P3	P2	P1	P0
----	----	----	----

 


Ch3-13

Parallel-Pattern v.s. Parallel-Fault

Parallel-pattern

 

Parallel-fault

 

- P1, P2, P3 are patterns events
- F1, F2, F3 are faults
- Complexity**
 - Is proportional to the **events** that need to be processed
 - The **value-change events** (upper figure) seems to be fewer than the **fault-events** (lower figure)
 - Hence, **parallel-pattern** seems to be more efficient than **parallel-fault** methods


Ch3-14

Deductive Fault Simulation

- Simulate all faulty circuits in one pass
 - For each pattern, sweep the circuit from PI's to PO's.
 - During the process, a list of faults is associated with each line
 - The list contains faults that would produce a **fault effect** on this line
 - The **union fault list at every PO** contains the detected faults by the simulated input vector
- Major operation: fault list propagation
 - Related to the gate types and values
 - The size of the list may grow dynamically, leading to a potential **memory explosion problem**

Ch3-15

Controlling Value of a Logic Gate

 

Whenever there is a '0' in the inputs, Z will be '0'
→ Controlling value for NAND gate is '0'
→ Non-Controlling value is '1'


Gate Type	Controlling Value	Non-Controlling Value
AND	'0'	'1'
OR	'1'	'0'
NAND	'0'	'1'
NOR	'1'	'0'

Ch3-16

 Example: Fault List Propagation

Fault-free simulation results: {A=0, B=0, C=0}
Q: What is the detected fault list at line C?

- (Reasoning) To create a fault effect at line C, we need {A=1, B=1}
 → which means that we need a fault effect at A as well as B
 → It can be achieved in faulty circuits $LA \cdot LB$
 → Also C/1 is a new fault to be included in the fault list of C



LA, LB, LC are fault list propagated to their respective lines


\overline{LA} is the set of all faults not in LA

Ch3-17

Example: Fault List Propagation

LA, LB, LC are detected fault list at their respective lines

Consider a two-input AND-gate:

 

Non-controlling case: **Case 1:** A=1, B=1, C=1 at fault-free,
 $LC = LA + LB + \{C/0\}$

Controlling cases: **Case 2:** A=1, B=0, C=0 at fault-free,
 $LC = \overline{LA} \cdot LB + \{C/1\}$


Case 3: A=0, B=0, C=0 at fault-free,
 $LC = LA \cdot LB + \{C/1\}$

\overline{LA} is the set of all faults not in LA

Ch3-18

Example: Deductive Simulation (1)

- Consider 3 faults: B/1, F/0, and J/0

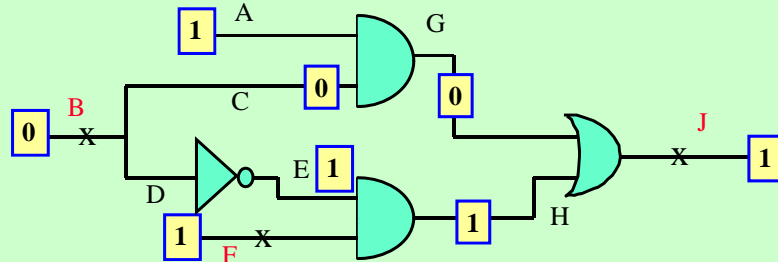


Fault List at PI's:

$$\mathbf{LB = \{B/1\}, \quad LF = \{F/0\}, \quad LA = \phi, \quad LC=LD = \{B/1\}}$$

Ch3-19

Example: Deductive Simulation (2)

- Consider 3 faults: B/1, F/0, and J/0

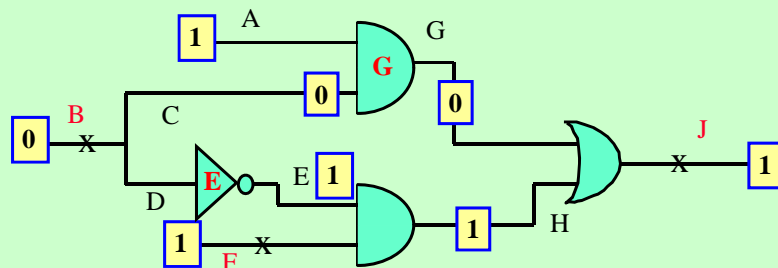

Fault Lists at G and E:

$$\mathbf{LB = \{B/1\}, \quad LF = \{F/0\}, \quad LA = \phi, \quad LC=LD = \{B/1\},}$$


$$\mathbf{LG = (\overline{LA} * LC) = \{B/1\}}$$

$$\mathbf{LE = (LD) = \{B/1\}}$$

Ch3-20

Example: Deductive Simulation (3)

- Consider 3 faults: B/1, F/0, and J/0

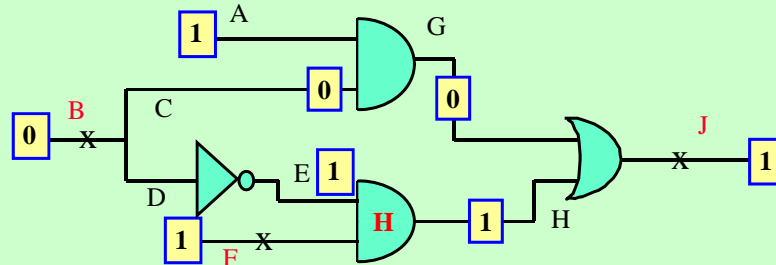


Computed Fault List at H:

$$\begin{aligned} \mathbf{LB} &= \{\mathbf{B/1}\}, \quad \mathbf{LF} = \{\mathbf{F/0}\}, \quad \mathbf{LC=LD} = \{\mathbf{B/1}\}, \\ \mathbf{LG} &= \{\mathbf{B/1}\}, \quad \mathbf{LE} = \{\mathbf{B/1}\} \\ \mathbf{LH} &= (\mathbf{LE} + \mathbf{LF}) = \{\mathbf{B/1, F/0}\} \end{aligned}$$

Ch3-21

Example: Deductive Simulation (4)

- Consider 3 faults: B/1, F/0, and J/0

 


Final Fault List at the output J:

$$\begin{aligned} \mathbf{LB} &= \{\mathbf{B/1}\}, \quad \mathbf{LF} = \{\mathbf{F/0}\}, \quad \mathbf{LC=LD} = \{\mathbf{B/1}\}, \\ \mathbf{LG} &= \{\mathbf{B/1}\}, \quad \mathbf{LE} = \{\mathbf{B/1}\} \\ \mathbf{LH} &= \{\mathbf{B/1, F/0}\}, \\ \mathbf{LJ} &= (\overline{\mathbf{LG}} \cdot \mathbf{LH}) \{\mathbf{F/0, J/0}\} \end{aligned}$$

Ch3-22

Example: Even-Driven Deductive Fault Simulation

- When A changes from 1 to 0

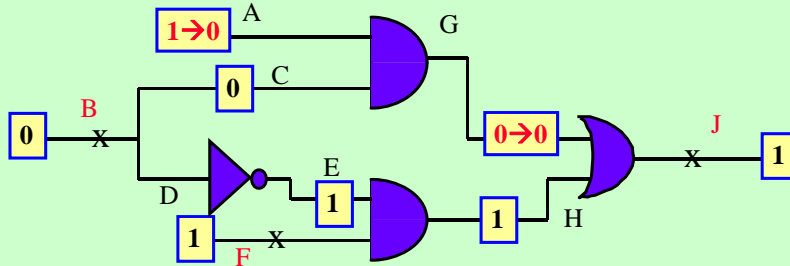

Event-driven operation:

$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \phi$

$LC=LD = \{B/1\}$, $LG = \phi$,

$LE = \{B/1\}$, $LH = \{B/1, F/0\}$, $LJ = \{B/1, F/0, J/0\}$


Ch3-23

Concurrent Fault Simulation

- Simulate all faulty circuits in one pass:
 - Each gate retains a list of fault copies, each of which stores the status of a fault exhibiting difference from fault-free values
- Simulation mechanism
 - is similar to the conceptual fault simulation except that only the dynamical difference w.r.t. fault-free circuit is retained.
- Theoretically,
 - all faults in a circuit can be processed in one pass
- Practically,
 - memory explosion problem may restrict the number of faults that can be processed in each pass

Ch3-24


Concurrent Fault Simulation

 

Ch3-25

Example: Concurrent Simulation (1)

- Consider 3 faults: B/1, F/0, and J/0

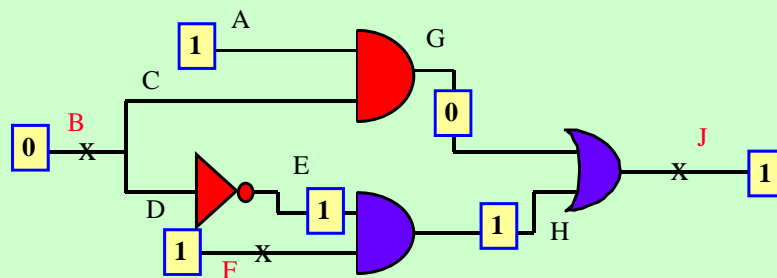


$LG = \{10_0, B/1:11_1\}$ $LE = \{0_1, B/1:1_0\}$

Fault Free A fault B/1

Ch3-26

Example: Concurrent Simulation (2)

- Consider 3 faults: B/1, F/0, and J/0

 


LG = {10_0, B/1:11_1} LE = {0_1, B/1:1_0}
 LH = {11_1, B/1:01_0, F/0:10_0}

Ch3-27

Example: Concurrent Simulation (3)

- Consider 3 faults: B/1, F/0, and J/0

 


LG = {10_0, B/1:11_1} LE = {0_1, B/1:1_0}
 LH = {11_1, B/1:01_0, F/0:10_0}
 LJ = {01_1, B/1:10_1, F/0:00_0, J/0:01_0}

dropped

Ch3-28

Example: Concurrent Simulation (4)


- When A changes from 1 to 0

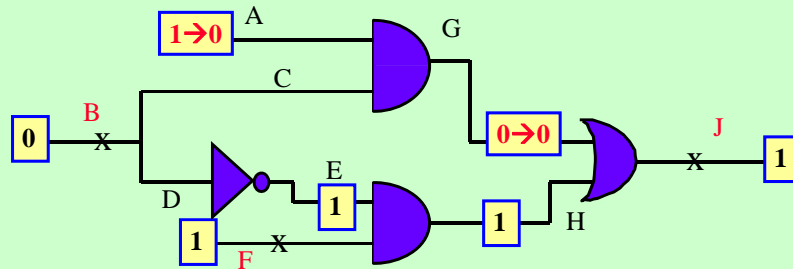

$LG = \{00_0, B/1:01_0\}$ $LE = \{0_1, B/1:1_0\}$
 $LH = \{11_1, B/1:01_0, F/0:10_0\}$
 $LJ = \{01_1, B/1:00_0, F/0:00_0, J/0:01_0\}$


Ch3-29

Fault List Including New Borns

 

Ch3-30

Fault List Propagation

 


Ch3-31

Outline

- Fault Simulation for Comb. Circuits
- ➔ • Approximation Approach
 - Critical Path Tracing
 - Probabilistic Approach
- Techniques for Sequential Circuits

Ch3-32


Sensitive Input and Critical Path

 

- Sensitive Input of a gate:
 - A gate input i is *sensitive* if complementing the value of i changes the value of the gate output
- Critical line
 - Assume that the fault-free value of w is v in response to t
 - A line w is *critical* w.r.t. a pattern t iff t detects the fault w stuck-at \bar{v}
- Critical paths
 - Paths consisting of critical lines only

Ch3-33

Basics of Critical Path Tracing

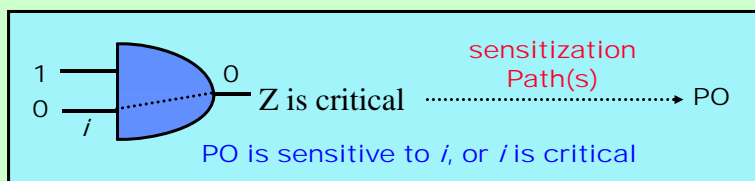

- A gate input i is critical w.r.t. a pattern t if
 - (1) the gate *output is critical* and
 - (2) i is a *sensitive input* to t
 - Use recursion to prove that i is also critical
- In a fanout-free circuit
 - the criticality of a line can be determined by *backward traversal* to the sensitive gate's inputs from PO's, *in linear time*


Ch3-34

Analysis of Critical Path Tracing

- Three-step Procedure:
 - Step 1: Fault-free simulation
 - Step 2: Mark the **sensitive inputs** of each gate
 - Step 3: Identification of the **critical lines** by backward critical path tracing)
- Complexity is $O(G)$
 - Where G is the gate count
 - for fanout-free circuits --- very rare in practice
- Application
 - Applied to **fanout-free regions**, while stem faults are still simulated by parallel-pattern fault simulator.

Ch3-35

Example of Critical Path Tracing

 

Detected faults in the fanout-free region:


{J/0, H/0, F/0, E/0, D/1}

Question: is B stuck-at-1 detected ?

Ch3-36

Anomaly of Critical Path Tracing

 
- **Stem criticality** is hard to infer from branches.
E.g. is B/1 detectable by the given pattern?



- It turns out that **B/1 is not detectable** even though both C and D are critical, because their effects cancel out each other at gate J, (i.e., **fault masking problem**)
- There is also a so-called **multiple path sensitization problem**.

Ch3-37

Multiple Path Sensitization

 

Both C and D are not critical, yet **B is critical** and B/0 can be **detected at J by multiple path sensitization**.

Ch3-38

Parallel and Distributed Simulation

- To share the fault simulation effort
 - by a number of processors either **tightly** connected as in parallel computation or **loosely** connected as in distributed computation.
- The speed-up
 - with respect to the processor number depends on the **degree of duplicated computation**, and the **communication overhead** among processors.
- The distributed simulation
 - on a cluster of **networked workstations** is especially appealing.

Ch3-39


Distributed Simulation Techniques

- Fault Partition
 - **Distributes faults** among many processors.
 - Works relatively well for both combinational and sequential circuits.
- Pattern Partition
 - **Distributes patterns** among processors.
 - no duplicated logic simulation
 - Works well for combinational circuits.
- Circuit Partition
 - Difficult to achieve synchronization without incurring excessive communication overhead.

Ch3-40

Distributed Fault Simulation

 - Typical Speed-up versus No. of Processors



- Diminished increase of speed-up ratio with more processors

Ch3-41

Fault Grading

- Approximate fault coverage
 - Can be obtained in much shorter computational time than regular fault simulation.
 - Not suitable for high fault-coverage requirement.
- Typical fault grading methods:
 - Toggle test, e.g. DATAS
 - Detection probability computation, e.g. STAFAN
 - Fault sampling
 - estimate from a selected subset of total faults
 - Test set sampling
 - estimate from a subset of complete test sequence

Ch3-42


STAFAN

- Compute fault detection probability from logic simulation.
 - d_l = detection probability of s-a-0 on l = $C1(l)O(l)$
 - d_l = detection probability of s-a-1 on l = $C0(l)O(l)$

$$C0(l) = \frac{0\text{-count}}{n}, \quad C1(l) = \frac{1\text{-count}}{n}$$

$$S(l) = \frac{\text{sensitization-count}}{n}$$

$$O(l) = S(l)O(m)$$

 

- **m** is the immediate successor of **l**
- **observability** can be computed backwards from POs

Ch3-43

STAFAN (cont.)

$$d_f^n = 1 - (1 - d_f)^n \quad n \text{ is the no. of vectors}$$

$$\text{Statistical Fault Coverage} = \frac{\sum_{\Phi} d_f^n}{|\Phi|}$$

the summation of each fault's detection probability

Φ is the set of faults of interest

- More sophisticated than toggle test with same computation complexity

Ch3-44

Outline

- Fault Simulation for Comb. Circuits
- Approximation Approach
 - Toggle Counting
 - Critical Path Tracing
 - Probabilistic Approach
- ➔ • Techniques for Sequential Circuits

Ch3-45

Fault Grading for Functional Input Sequence

Inputs:

- (1) A test application program
- (2) A sequential design



Output: The fault coverage

Application: High-Performance CPU Designs

Major challenge: often too time-consuming

Sequential Design Model


Sequential Circuits

  

Ch3-47

Time-Frame-Expansion Model

 Ex: Input Sequence ('0', '0', '0')
State Sequence ($S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3$)



Notations: PPI: pseudo primary inputs (i.e., outputs of flip-flops)
PPO: pseudo primary outputs (i.e., inputs of flip-flops)

A single fault becomes multiple faults in the time-frame-expansion model

Ch3-48

Hypertrophic Faults

- A hypertrophic fault
 - Is a fault that diverges from the fault-free circuit with a large number of Xs, which usually is a stuck-at fault occurring at a control line and thus prevents the circuit initialization
- A small number of hypertrophic faults
 - account for a large percentage of fault events and CPU time
- These faults are sometimes dropped
 - as potentially detected faults to reduce simulation time. However, the resultant fault coverage then becomes approximate


A potentially detected fault is a fault detected only when the circuit is powered on in certain states, not every state.

Ch3-49

Fault Emulation


We can utilize FPGA to speed up the sequential fault grading

FPGA-Based Emulation Process

 

Ch3-51

Serial Fault Emulation by FPGA's

 

Ch3-52

Fault Injection Should Be Efficient !

- Fault Injection

- Is to convert a **fault-free FPGA** implementation to a **faulty one**
- If not efficient, could become the new **bottleneck**

- (1) Static Fault Injection


- Directly changes the **configuration** of the fault-free implementation to a faulty one

- (2) Dynamic Fault Injection

- Do not change the configuration directly
- Fault inject is injected through the **control of some hardware** originally built-in to the netlist

Ch3-53


Static Fault Injection

 

Ch3-54


Example: FPGA-implementation

Two faults are being considered:
A stuck-at 1
G stuck-at-0

 

Ch3-55

Dynamic Fault Injection (I)

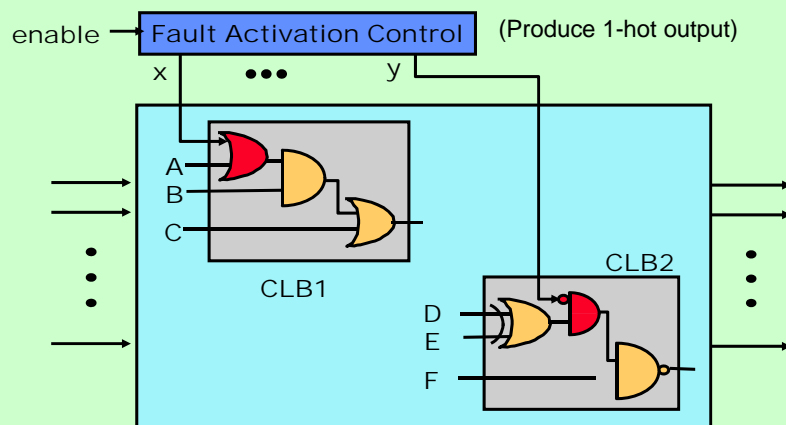


($x=1, y=0$) → The above netlist behaves like A s-a-1 faulty circuit
($x=0, y=1$) → The above netlist behaves like G s-a-0 faulty circuit

Ch3-56

Dynamic Fault Injection (II)

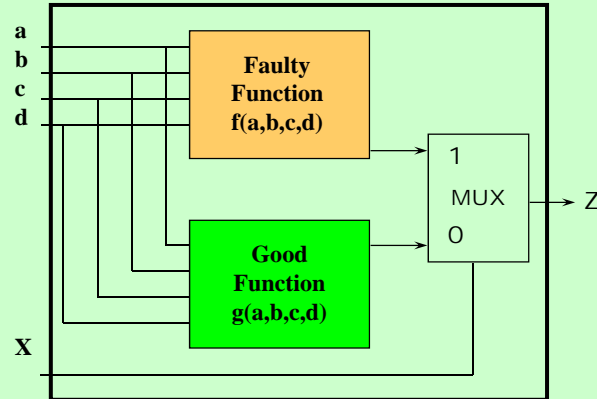- (1) Conservatively map only 4-input function to a CLB, which is originally assumed to be capable of realizing 5-input function.
- (2) Extra input, i.e., x , is reserved for the control of dynamic fault injection.




A Configurable Logic Block (CLB)
with a dynamic fault injected (activated with $x=1$)

Ch3-57

Overview of Dynamic Fault Injection (II)

In the following configuration:
5 faults are injected (one for each column), but only 1 is activated

 

Ch3-58