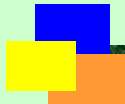


國立清華大學電機系

EE-6250
超大型積體電路測試
VLSI Testing



Chapter 5
Design For Testability
& Scan Test

Outline

- 
- Introduction
 - Why DFT?
 - What is DFT?
 - Ad-Hoc Approaches
 - Full Scan
 - Partial Scan

Why DFT ?

- Direct Testing is Way Too Difficult !
 - Large number of FFs
 - Embedded memory blocks
 - Embedded analog blocks
- Design For Testability is inevitable
 - Like death and tax

ch5-3

Design For Testability

- Definition
 - Design For Testability (DFT) refers to those **design techniques** that make test generation and testing cost-effective
- DFT Methods
 - **Ad-hoc methods**
 - **Scan**, full and partial
 - **Built-In Self-Test** (BIST)
 - **Boundary scan**
- Cost of DFT
 - **Pin count, area, performance, design-time, test-time**

ch5-4

Why DFT Isn't Universally Used Previously?

- Short-sighted **view** of management
- **Time-to-market** pressure
- Life-cycle **cost ignored** by development management/contractors/buyers
- **Area/functionality/performance** myths
- Lack of **knowledge** by design engineers
- Testing is **someone else's problem**
- **Lack of tools** to support DFT until recently

We don't have to worry about this management barrier any more
→ **Most design teams now have DfT people**

ch5-5

Important Factors

- **Controllability**
 - Measure the ease of controlling a line
- **Observability**
 - Measure the ease of observing a line at PO
- **Predictability**
 - Measure the ease of predicting output values
- **DFT deals with ways of improving**
 - Controllability
 - Observability
 - Predictability

ch5-6

Outline

- Introduction
- ➡ • Ad-Hoc Approaches
 - Test Points
 - Design Rules
- Full Scan
- Partial Scan

ch5-7


Ad-Hoc Design For Testability

- Design Guidelines
 - Avoid redundancy
 - Avoid asynchronous logic
 - Avoid clock gating (e.g., ripple counter)
 - Avoid large fan-in
 - Consider tester requirements (tri-stating, etc.)
- Disadvantages
 - High fault coverage not guaranteed
 - Manual test generation
 - Design iterations required

ch5-8

Some Ad-Hoc DFT Techniques

- Test Points
- Initialization
- Monostable multivibrators
 - One-shot circuit
- Oscillators and clocks
- Counters / Shift-Registers
 - Add control points to long counters
- Partition large circuits
- Logical redundancy
- Break global feedback paths

 

ch5-9

On-Line Self-Test & Fault Tolerance By Redundancy


- Information Redundancy
 - Outputs = (information-bits) + (check-bits)
 - Information bits are the original normal outputs
 - Check bits always maintains a specific pre-defined logical or mathematical relationship with the corresponding information bits
 - Any time, if the information-bits and check-bits violate the pre-defined relationship, then it indicates an error
- Hardware Redundancy
 - Use extra hardware (e.g., duplicate or triplicate the system) so that the fault within one module will be masked (I.e., the faulty effect never observed at the final output)

ch5-10

Module Level Redundancy

- Triple Module Redundancy (TMR)

- majority voting on three identical modules' outputs help mask out faults that occur in a single module

 

ch5-11

Test Point Insertion

- Employ test points to enhance


- Controllability
- Observability

- CP: Control Points

- Primary inputs used to enhance controllability

- OP: Observability Points

- Primary outputs used to enhance observability

 

ch5-12

0/1 Injection Circuitry

- Normal operation


When CP_enable = 0

- Inject 0

– Set CP_enable = 1 and CP = 0

- Inject 1

– Set CP_enable = 1 and CP = 1

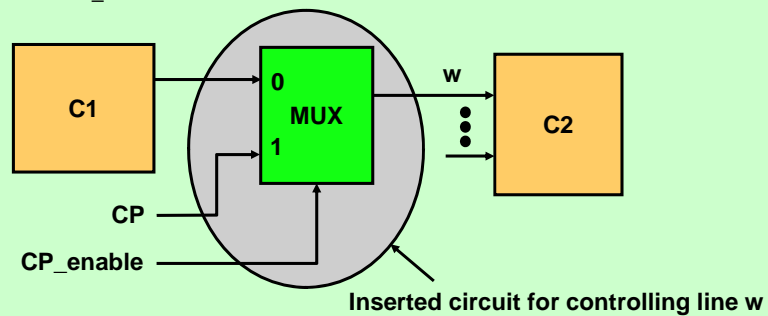


ch5-13

Single I/O Port for Multiple Test Points

- Constraints of using test points


- A large demand on I/O pins
- This constraint can be somewhat relieved by using MUX & DEMUX at the cost of increasing the test time

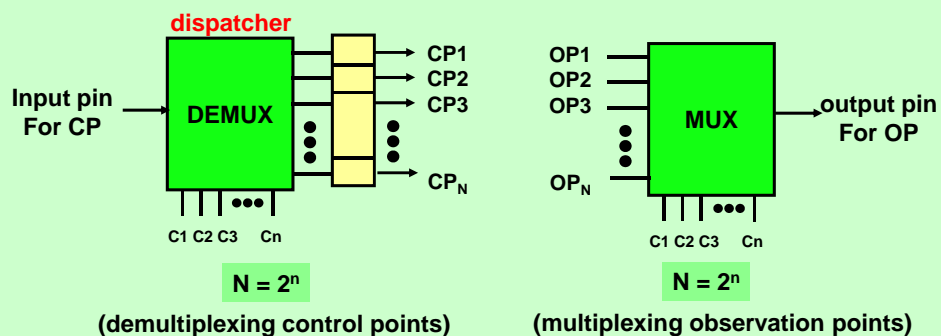

ch5-14

Sharing Between Test Points & Normal I/O

- Advantage: Even fewer I/O pins for Test Points
- Overhead: Extra MUX delay for normal I/O

 

ch5-15

Control Point Selection

- Impact
 - The **controllability** of the fanout-cone of the added point is improved
- Common selections
 - Control, address, and data buses
 - Enable / Hold inputs
 - Enable and read/write inputs to memory
 - **Clock** and **set/clear** signals of flip-flops
 - Data select inputs to multiplexers and demultiplexers

ch5-16


Example: Use CP to Fix DFT Rule Violation

- DFT rule violations

- The **set/clear** signal of a flip-flop is generated by other logic, instead of directly controlled by an input pin
- **Gated clock** signals

- Violation Fix

 - Add a control point to the **set/clear signal** or clock signals




Example: Fixing Gated Clock

- Gated Clocks

- **Advantage**: power dissipation of a logic design can thus be reduced
- **Drawback**: the design's testability is also reduced

- Testability Fix

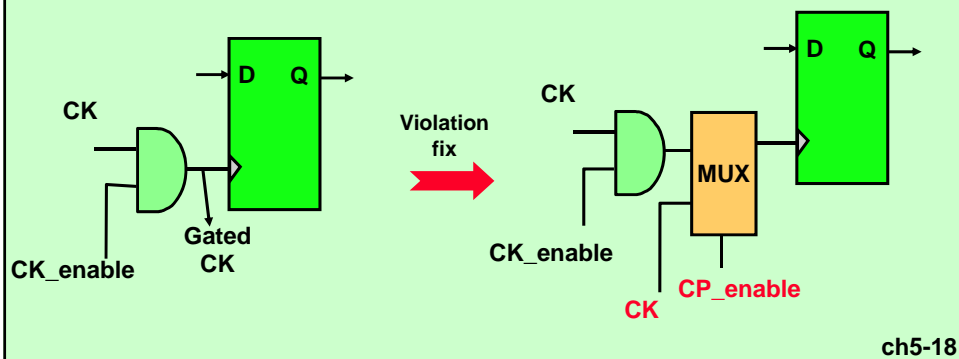

Example: Fixing Tri-State Bus Contention


- **Bus Contention**

- A stuck-at-fault at the **tri-state enable line** may cause bus contention – **multiple active drivers** are connected to the bus simultaneously

- **Fix**

- Add CPs to **turn off tri-state devices** during testing

(A Bus Contention Scenario in the presence of a fault)

 


ch5-19

Example: Partitioning Counters

- **Consider a 16-bit ripple-counter**

- Could take up to $2^{16} = 65536$ cycles to test
- After being partitioned into **two 8-bit counters** below, it can be tested with just $2 \times 2^8 = 512$ cycles

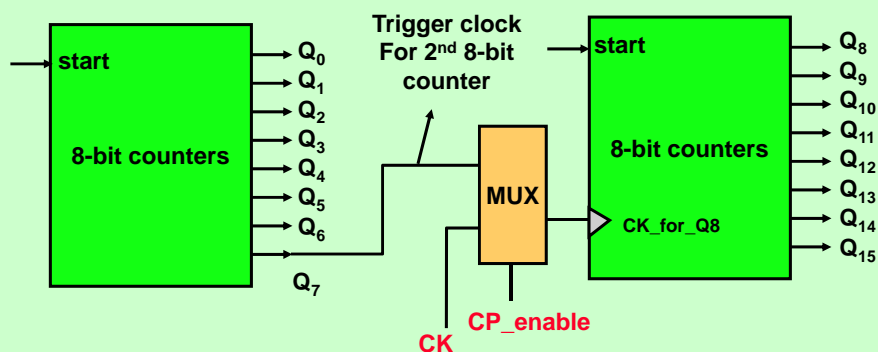

ch5-20

Observation Point Selection

- Impact

- The **observability** of the fanin-cone (or transitive fanins) of the added OP is improved

- Common choice

- Stem lines having a **large number of fanouts**
- Global feedback paths
- Redundant signal lines
- Output of logic devices having many inputs
 - MUX, XOR trees
- **Output from state devices**
- Address, control and data buses
(常為電路區塊間之介面訊號)


ch5-21

Problems of CP & OP

- Large number of I/O pins

- Add MUXes to reduce the number of I/O pins
- Serially shift CP values by shift-registers

- Larger test time

 

ch5-22

Outline

- Introduction
- Ad-Hoc Approaches
- ➡ • Full Scan
 - The Concept
 - Scan Cell Design
 - Random Access Scan
- Partial Scan


ch5-23

What Is Scan ?

- Objective
 - To provide controllability and observability at **internal state variables** for testing
- Method
 - Add **test mode** control signal(s) to circuit
 - Connect **flip-flops to form shift registers** in test mode
 - Make inputs/outputs of the flip-flops in the shift register controllable and observable
- Types
 - Internal scan
 - **Full scan, Partial scan, Random access**
 - Boundary scan


ch5-24

The Scan Concept

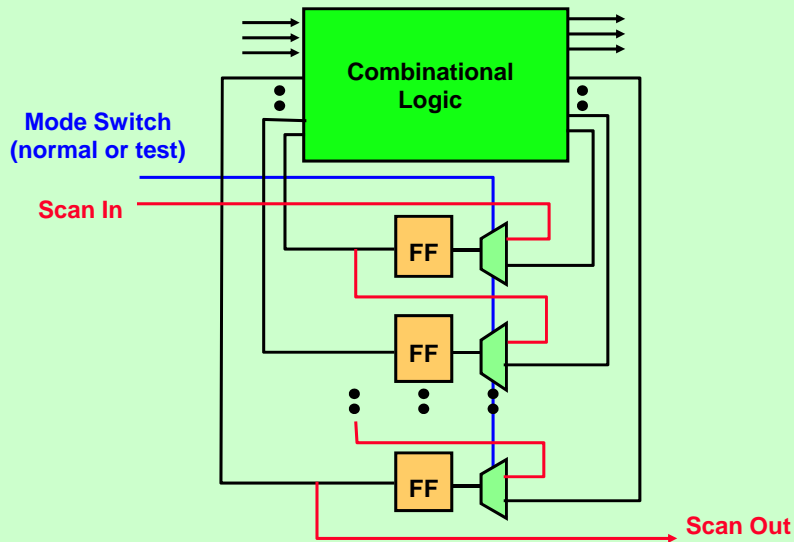

ch5-25


A Logic Design Before Scan Insertion

 

Sequential ATPG is extremely difficult:
due to the lack of controllability and observability at flip-flops.

ch5-26


Example: A 3-stage Counter

 

It takes 8 clock cycles to set the flip-flops to be (1, 1, 1),
for detecting the g stuck-at-0 fault
(2^{20} clock cycles for a 20-stage counter !)

ch5-27

A Logic Design After Scan Insertion

 

Scan Chain provides an **easy access** to flip-flops
→ Pattern Generation is much easier !!


Note: Scan Enable (SE), not shown here, controls every MUX.

ch5-28

Procedure of Applying Test Patterns

• Notation

 - Test vectors $\mathbf{T} = \langle t_i^I, t_i^F \rangle i=1, 2, \dots$
- Output Response $\mathbf{R} = \langle r_i^O, r_i^F \rangle i=1, 2, \dots$



• Test Application

- (1) $i = 1$;
- (2) Scan-in t_1^F /* scan-in the **first state vector** for PPI's */
- (3) Apply t_i^I /* apply **current input vector** at PI's */
- (4) Observe r_i^O /* observe **current output response** at PO's */
- (5) **Capture PPOs to FFs as r_i^F** /* capture the response at PPO's to FFs */
 - (Set to '**Normal Mode**' by raising SE to '1' for one clock cycle)
- (6) Scan-out r_i^F while scanning-in t_{i+1}^F /* **overlap scan-in and scan-out** */
- (7) $i = i+1$; Goto step (3)

ch5-29

Testing Scan Chain ?

• Common practice

- Scan chain is often **first tested** before testing the core logic by a so-called **flush test** - which pumps random vectors in and out of the scan chain


• Procedure (flush test of scan chain)

- (1) $i = 0$;
- (2) Scan-in 1st random vector to flip-flops
- (3) Scan-out (i)th random vector while scanning-in (i+1)th vector for flip-flops.
 - The (i)th **scan-out vector** should be identical to (i)th **vector scanned in** earlier, otherwise scan-chain is **mal-functioning**
- (4) If necessary $i = i+1$, goto step (3)

ch5-30

MUX-Scan Flip-Flop


- Only **D-type master-slave flip-flops** are used
- All flip-flop clocks controlled from primary inputs
 - No **gated clock** allowed
- Clocks must not feed data inputs of flip-flops
- Most popularly supported in standard cell libraries

 

ch5-31

Two-Port Dual-Clock Scan FF

- **Separate normal clock from the clock used for scanning**
 - **D**: normal input data
 - **CK1**: normal clock
 - **SI**: scan input
 - **CK2**: scan clock

 


ch5-32

Race-Free Scan FF

- Use two-phase clocking

- CK1 and CK2 are **two-phase non-overlapping** clocks which insure race-free operation

 

ch5-33


LSSD flip-flop (1977 IBM)

- LSSD: Level Sensitive Scan Design

- Less performance degradation than MUX-scan FF


- Clocking

- Normal operation: non-overlapping CK1=1 → CK3=1
- Scan operation: non-overlapping CK2=1 → CK3=1

 



ch5-34

Symbol of LSSD FF

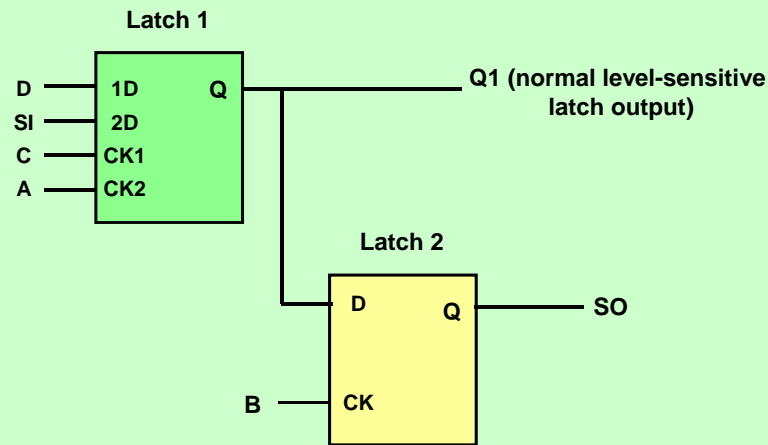

ch5-35

Scan Rule Violation Example

  

All FFs are triggered by the same clock edge
Set and reset signals are not controlled by any internal signals

ch5-36

Some Problems With Full Scan

Major Commercial Test Tool Companies

Synopsys
Mentor-Graphics
SynTest (華騰科技)
Cadence

- Problems
 - Area overhead
 - Possible performance degradation
 - High test application time
 - Power dissipation
- Features of Commercial Tools
 - Scan-rule violation check (e.g., DFT rule check)
 - Scan insertion (convert a FF to its scan version)
 - ATPG (both combinational and sequential)
 - Scan chain reordering after layout

ch5-37


Performance Overhead

- The increase of delay along the normal data paths include:
 - Extra gate delay due to the multiplexer
 - Extra delay due to the capacitive loading of the scan-wiring at each flip-flop's output
- Timing-driven partial scan
 - Try to avoid scan flip-flops that belong to the timing critical paths
 - The flip-flop selection algorithm for partial scan can take this into consideration to reduce the timing impact of scan to the design

ch5-38

Scan-Chain Reordering

 - Scan-chain order is often decided at gate-level **without knowing the physical locations of the cells**
- Scan-chain consumes a lot of **routing resources**, and could be minimized by **re-ordering the flip-flops** in the chain after layout is known



Overhead of Scan Design

- Number of CMOS gates = 2000
- Fraction of flip-flops = 0.478


Scan implementation	Predicted overhead	Actual area overhead	Normalized operating frequency
None	0	0	1.0
Hierarchical	14.05%	16.93%	0.87
Optimized	14.05%	11.9%	0.91

ch5-40

Random Access Scan

- Comparison with Scan-Chain

- More **flexible** – any FF can be accessed in constant time
- **Test time** could be reduced
- **More hardware and routing overhead**

 

ch5-41

Outline

- Introduction
- Ad-Hoc Approaches
- Full Scan
- ➡ • Partial Scan

ch5-42

Partial Scan

- Basic idea

- Select a subset of flip-flops for scan
- Lower overhead (area and speed)
- Relaxed design rules

- Cycle-breaking technique


- Cheng & Agrawal, IEEE Trans. On Computers, April 1990
- Select scan flip-flops to simplify sequential ATPG
- Overhead is about 25% off than full scan

- Timing-driven partial scan

- Jou & Cheng, ICCAD, Nov. 1991
- Allow optimization of area, timing, and testability simultaneously

ch5-43


Full Scan vs. Partial Scan

 

test time	longer	shorter
hardware overhead	more	less
fault coverage	~100%	unpredictable
ease-of-use	easier	harder


ch5-44

A Partial-Scan DfT Flow

 

ch5-45

Directed Graph Of A Synchronous Sequential Circuit

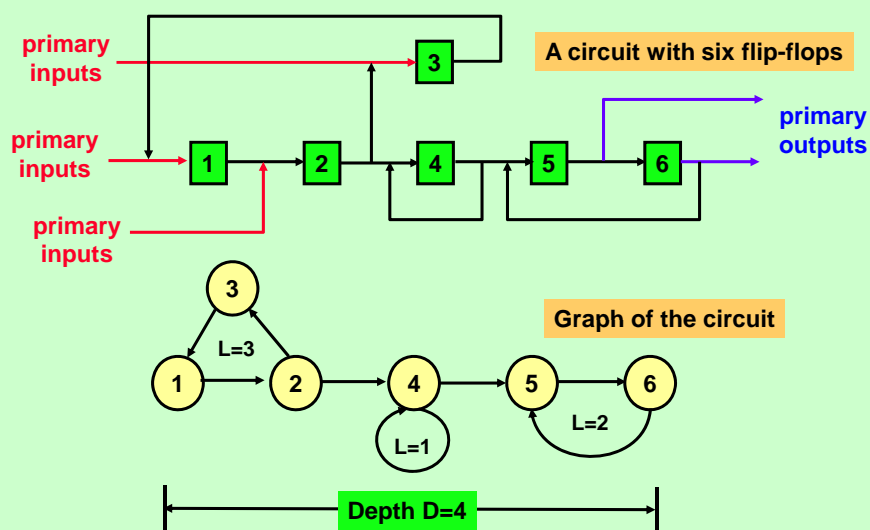

ch5-46

Partial Scan For Cycle-Free Structure

- Select minimal set of flip-flops
 - To eliminate some or **all cycles**
- Self-loops of unit length
 - **Are not broken** to reduce scan overhead
 - The number of self-loops in real design can be quite large
- Limit the length of
 - **Consecutive self-loop paths**
 - Long consecutive self-loop paths in large circuits may pose problems to sequential ATPG


ch5-47

Test Generation for Partial Scan Circuits

- Separate scan clock is used
- Scan flip-flops are removed
 - And their input and output signals are added to the PO/PI lists
- A sequential circuit test generator
 - is used for test generation
- The vector sequences
 - Are then converted into **scan sequences**
 - Each vector is preceded by a **scan-in sequence** to set the states of scanned flip-flops
 - A **scan-out sequence** is added at the end of applying each vector


ch5-48

Partial Scan Design

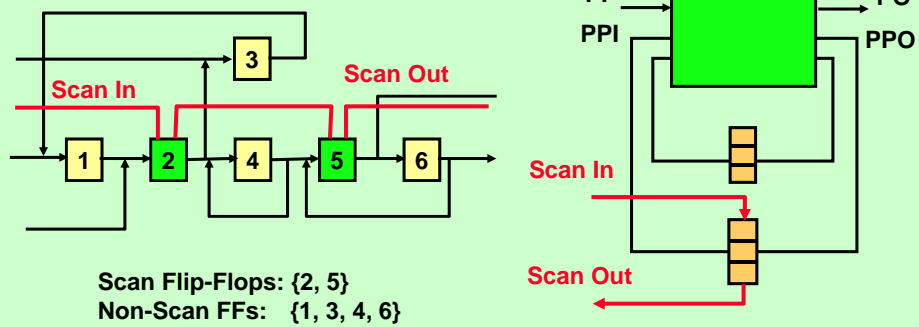

ch5-49

Trade-Off of Area Overhead v.s. Test Generation Effort

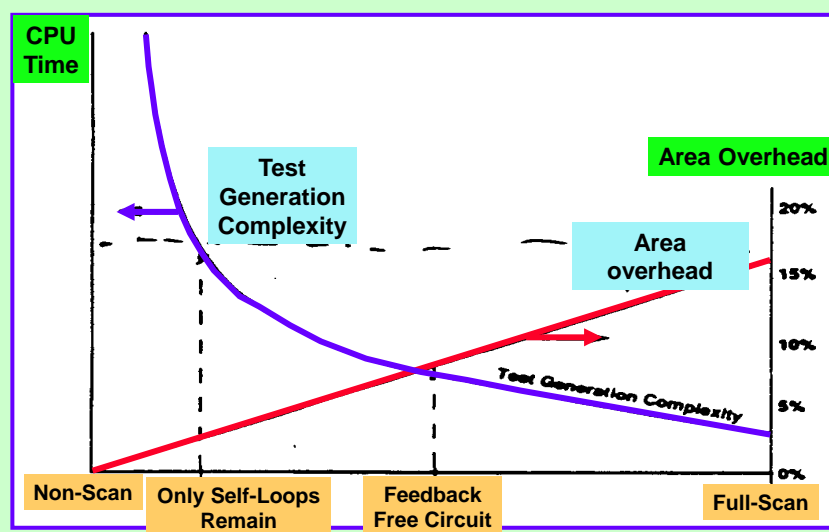

ch5-50

Summary of Partial-Scan

- Partial Scan
 - Allows the trade-off between test generation effort and hardware overhead to be automatically explored
- Breaking Cycles
 - Dramatically simplifies the sequential ATPG
- Limiting the Length of Self-Loop Paths
 - Is crucial in reducing test generation effort for large circuits
- Performance Degradation
 - Can be minimized by using timing analysis data for flip-flop selection

ch5-51