

Chapter 6

Delay Testing

Acknowledgements:
Mainly based on the lecture notes of
“VLSI Test Principles and Architectures”

ch6-1

Introduction of Delay Testing


- ❑ **Delay Faulty:**
 - Fault that cause delay across a circuit to violate certain timing constraint
- ❑ **Delay Fault Models:**
 - **Path delay fault**
 - Too much delay along a path
 - **Transition fault** (or Gate delay fault)
 - Too much delay across a particular gate

ch6-2

Basic Delay Testing

□ Delay Test Pattern:

 - A **two-pattern test**: $\langle v1, v2 \rangle$
- $v1$ is an initialization vector
- $v2$ causes the fault to be detected



Challenge: The **launch time** and **capture time** are just away by a high-speed clock cycle time

ch6-3

Applications of Delay Tests

□ Launch-off shifting (LOS)

- Aka (also known as) **skewed-load**
- $v1$ is arbitrary, $v2$ is derived by a 1-bit shift of $v1$

□ Launch-off capture (LOC)

- Aka **broadside** or **double-capture**
- $v1$ is arbitrary, $v2$ is derived from $v1$ through the circuit function


ch6-4

Timing Sequence of Launch-off-Shifting

PROS: Easier Test Generation to achieve a Higher Fault Coverage

CONS: Hard to produce the Scan-Enable signal 'SE'

(Note: 'SE' has to go LOW between S1 and C1)

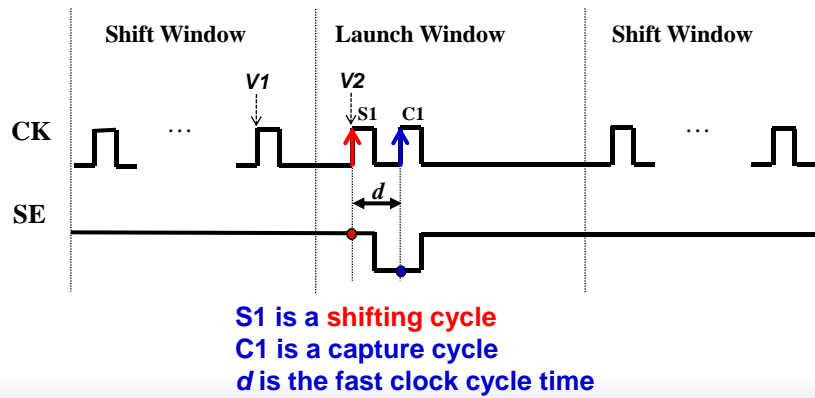

ch6-5


Example of LOS

Question:

v1 is {y1='0', y2='0', y3='1'}

What is vector v2 if using LOS?

Assuming scan chain order y3→y2→y1

 


ch6-6

Timing Sequence of Launch-off-Capture

PROS: Scan-Enable signal 'SE' to easy to produce

CONS: Fault Coverage is Lower than LOS

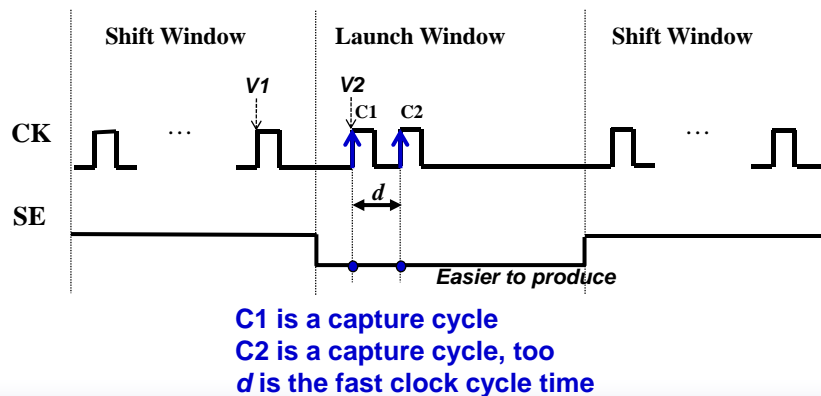

ch6-7

Transition Fault Model

- **Assumption:**
 - a large/gross delay is present at a circuit node
- **Path independence:**
 - Irrespective of which path the effect is propagated, the gross delay defect will **be arriving late at an observable point**
- **De-facto standard in Industry**
 - Simple and the number of faults is linear to circuit size
 - Also needs 2 vectors to test a fault
- **Formulation of transition-fault test generation:**
 - Node **x slow-to-rise (x-STR)** can be modeled simply as **two stuck-at faults**
 - (1) First time-frame: x/1 needs to be excited
 - (2) Second time-frame: x/0 needs to be excited and propagated

ch6-8


Ex: LOS Pattern Generation

- Target fault:
- A slow-to-rise



Test Requirement:

1st time frame: initialize a1 to '0'

2nd time frame: detect a2 s-a-0 fault

 

1st Time Frame

  

2nd Time Frame

Final 1st Pattern: (y1, y2, y3, SE) = (0, 1, 1, 0) → Shifted to become 2nd Pattern

ch6-9


Ex: LOC Pattern Generation

- Target fault:
- A slow-to-rise



Test Requirement:

1st time frame: initialize a1 to '0'

2nd time frame: detect a2 s-a-0 fault

 

1st Time Frame

  

2nd Time Frame

ch6-10

Summary

- ❑ More and more ICs require **delay testing** (or called timing testing, performance testing), to ensure that an IC can perform up to its target speed.
- ❑ Better understand what **LOS, LOC** means, since It's industrial practice.
- ❑ Some IC, e.g., CPU, needs to go through **speed binning process**, to determine the “quality bin” of each IC and its sell price.
- ❑ Delay test is still a tough issue and still evolving. Rigorous delay testing also aims to detect “**small defects**” so as to **reduce the test escape of latent defects** that might hurt an IC's reliability in its field.

ch6-11